



Very Large Scale Integration II - VLSI II

Adder Topologies

Gürer Özbek

ITU VLSI Laboratories
Istanbul Technical University



Outline

- Single Bit Addition
- Carry Propagate Adders
- PGK Representation & PG Diagram
- Tree Adders (Parallel Prefix Adders)





Adder Topologies

- Single Bit Addition
 - Half Adder
 - Full Adder
- Carry Propagate Adders
 - Carry Ripple (normal & inverse)
 - Carry Skip
 - Carry Select
 - Carry Lookahead
- Tree Adders (parallel prefix adders)
 - Brent Kung
 - Sklansky
 - Kogge-Stone
 - Ladner-Fischer
 - Knowles
 - Han-Carlson
 - Sparse Tree




Single Bit Addition

  - What's the deal?
 - All we want to do is add up a couple numbers...



A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


- $A \oplus B$ etc.



Half Adder

 
- 2 bit input, 2 bit output
- Used to build a Full Adder



$$S = A \oplus B$$

$$C_{out} = A \cdot B$$


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 




Full Adder

 - Main element of n-bit adders
- Consists of 2 HAs



$$S = A \oplus B \oplus C_i$$

$$C_{out} = MAJ(A, B, C_i)$$

 


A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



Carry Propagate Adders

 - N-bit adder called as CPA
 - Each sum bit consists inf. of all previous carries
 - It's the main problem to calculate them all quickly




$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{0}000\textcircled{0} \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{1}111\textcircled{1} \\ 1111 \\ +0000 \\ \hline 0000 \end{array} \quad \begin{array}{l} \text{carries} \\ A_{4...1} \\ B_{4...1} \\ S_{4...1} \end{array}$$



Carry Ripple Adder


 
- Simplest Design: Cascaded FAs
 - Second area efficient of all 😊
 - Slowest of all ☹️
 - Default topology to be synthesized





Carry Ripple Adder Delay

 
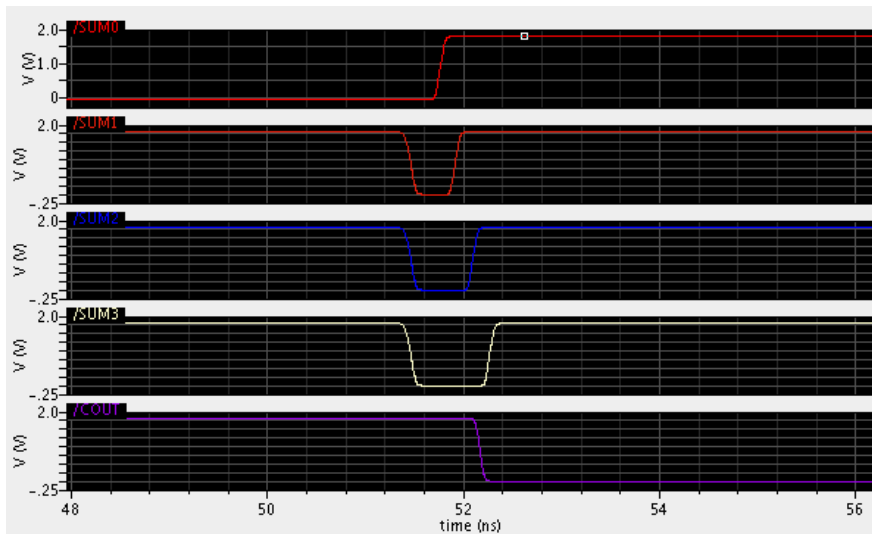
- Delay grows with $O(N)$
- Every FA waits for previous' output





Inverse Carry Ripple Adder

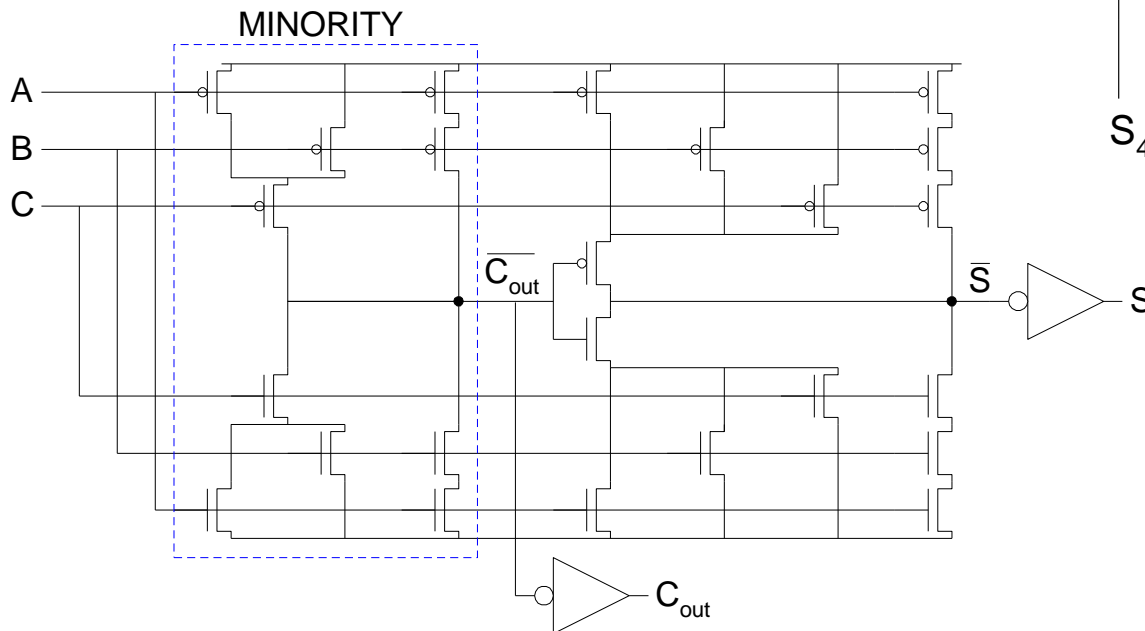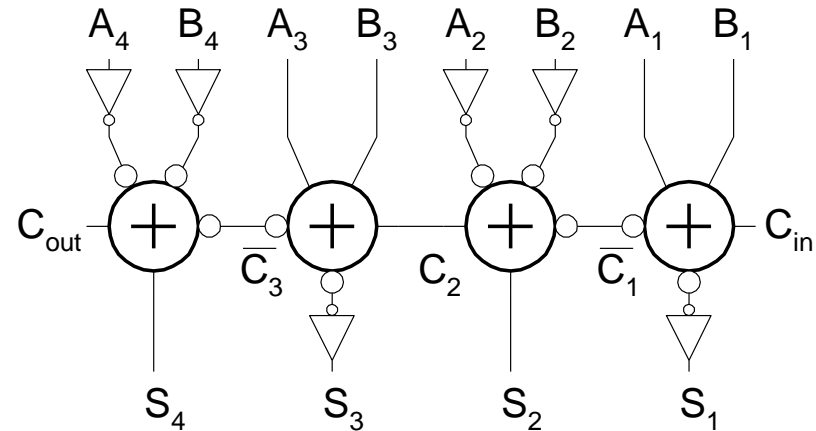- Uses inverting FAs
 - Most area efficient of all 😊
 - Second Slowest of all





Propagate, Generate and Kill the Carry

- Three operation can be defined to describe status of carry
 - Propagate: Previous carry is propagated to next bit
 - Generate: Generate a carry bit
 - Kill: Kill the previous carry

$$G_{i:i} \equiv G_i = A_i \cdot B_i$$

$$P_{i:i} \equiv P_i = A_i \oplus B_i$$

$$K_{i:i} \equiv K_i = \overline{A_i + B_i}$$

A	B	P	G	K
0	0	0	0	1
0	1	1	0	0
1	0	1	0	0
1	1	0	1	0



Propagate and Generate the Carry

- Kill is not used mostly
- Carry Merge Tree (CM)
- Initial values

$$G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$$

$$P_{i:j} = P_{i:k} \cdot P_{k-1:j}$$

$$G_{0:0} \equiv G_0 = C_{in}$$


$$P_{0:0} \equiv P_0 = 0$$

- Final Sum

$$S_i = P_i \oplus G_{i-1:0}$$




PG Diagram

 



Carry Ripple in PG Diagram 1

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

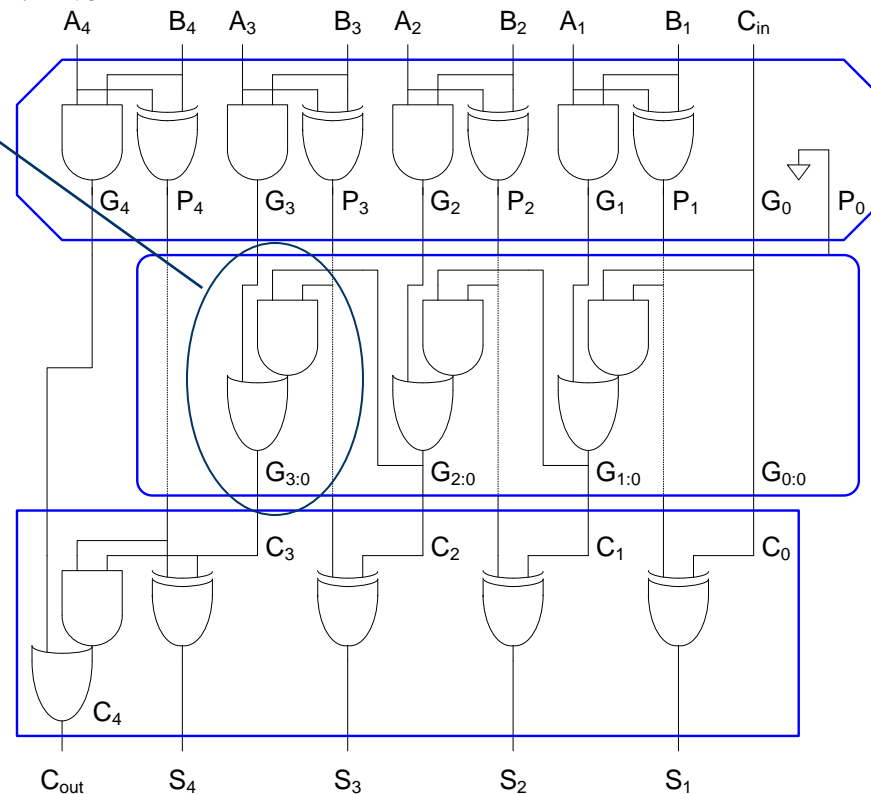



Carry Ripple in PG Diagram 2


$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{xor}$$

1-bit prop/gen cell

delay of And/OR in grey cell

Final SUM bit xor


- Delay grows as $O(N)$

 




PG Diagram Notation



Black cell

 


Gray cell

 


Buffer

  

Both Gen/Prop

 

Generate only

 


Different load





Carry Skip in PG Diagram

 - For k n-bit groups ($N = nk$)
- Delay grows as $O(\sqrt{N})$



skip thru muxes


First & last group ripple

$$t_{\text{skip}} = t_{pg} + \left[2(n-1) + (k-1) \right] t_{AO} + t_{xor}$$



Carry Select Adder

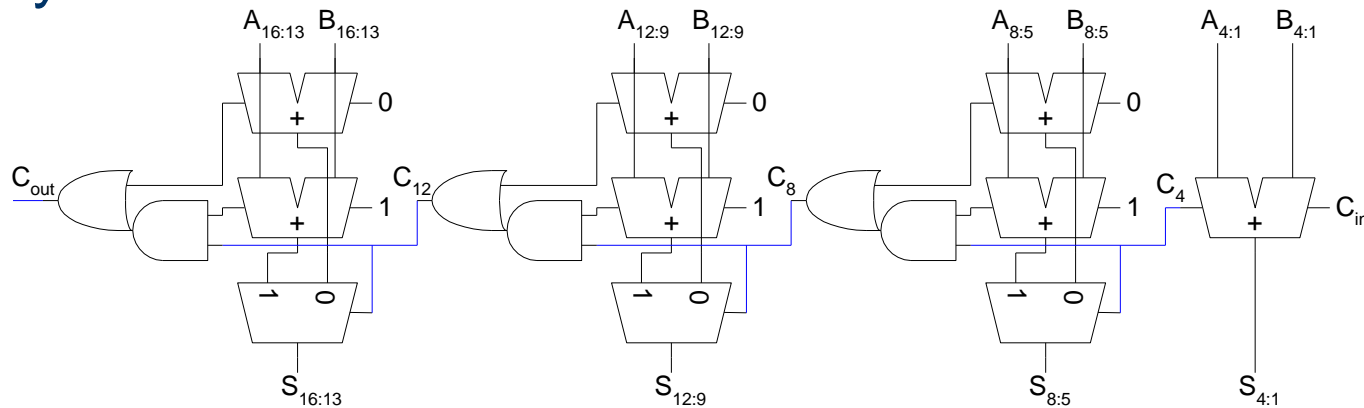- Precomputes sum of n-bit groups for both carry conditions
- Final Mux selects the correct sum value when correct carry value arrives




$$t_{\text{select}} = t_{pg} + [n + (k - 2)]t_{AO} + t_{mux}$$



Carry Select in PG Diagram

 - Precomputes sum of n-bit groups for both carry conditions




$$t_{\text{select}} = t_{pg} + \left[(n - 1) + (k - 1) \right] t_{AO} + t_{xor}$$



Carry Lookahead Adder

 
- Computes Generate bits in parallel
- Higher-valency cells are used





Carry Lookahead in PG Diagram

 
Collecting Generate/Propagate over many cells





Higher Valency Cells in CLA

- Difficult to design with static CMOS

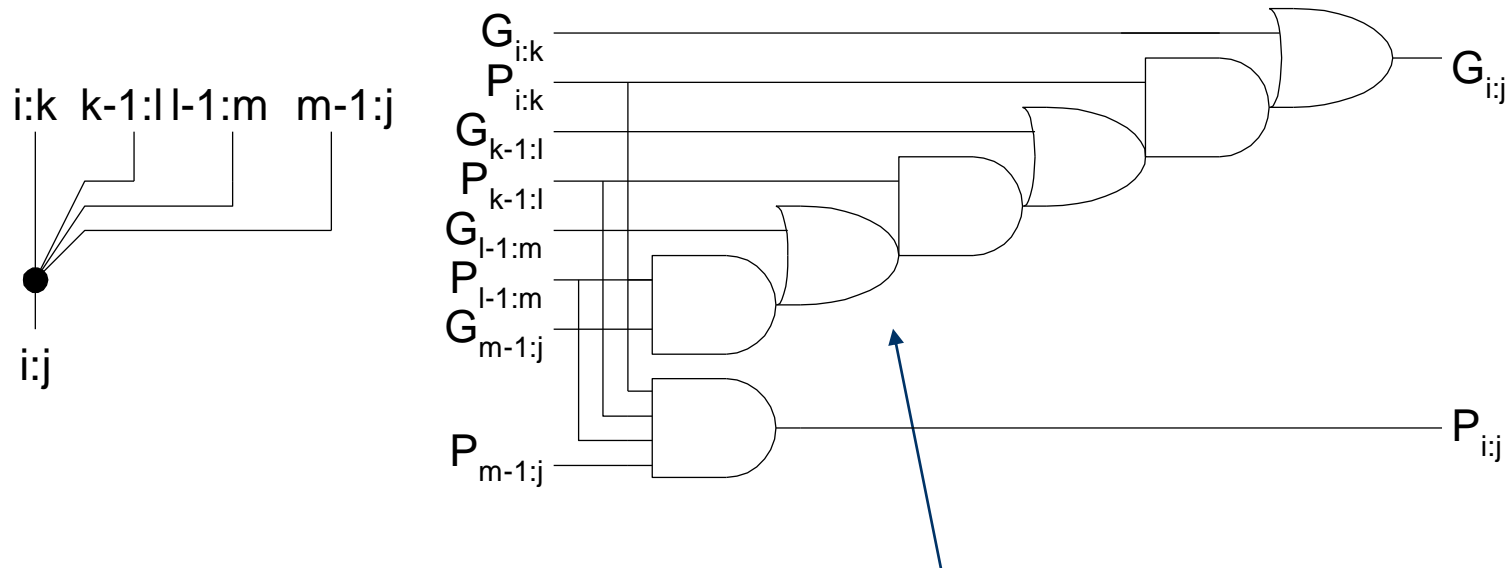




Tree Adders

- Parallel PG calculation without linear propagation
- $O(\log N)$ delay
- Suitable for large-bit adders



Brent-Kung


- Very First and Bad one

 



Sklansky


- Least Logic Levels
- Highest Fanout

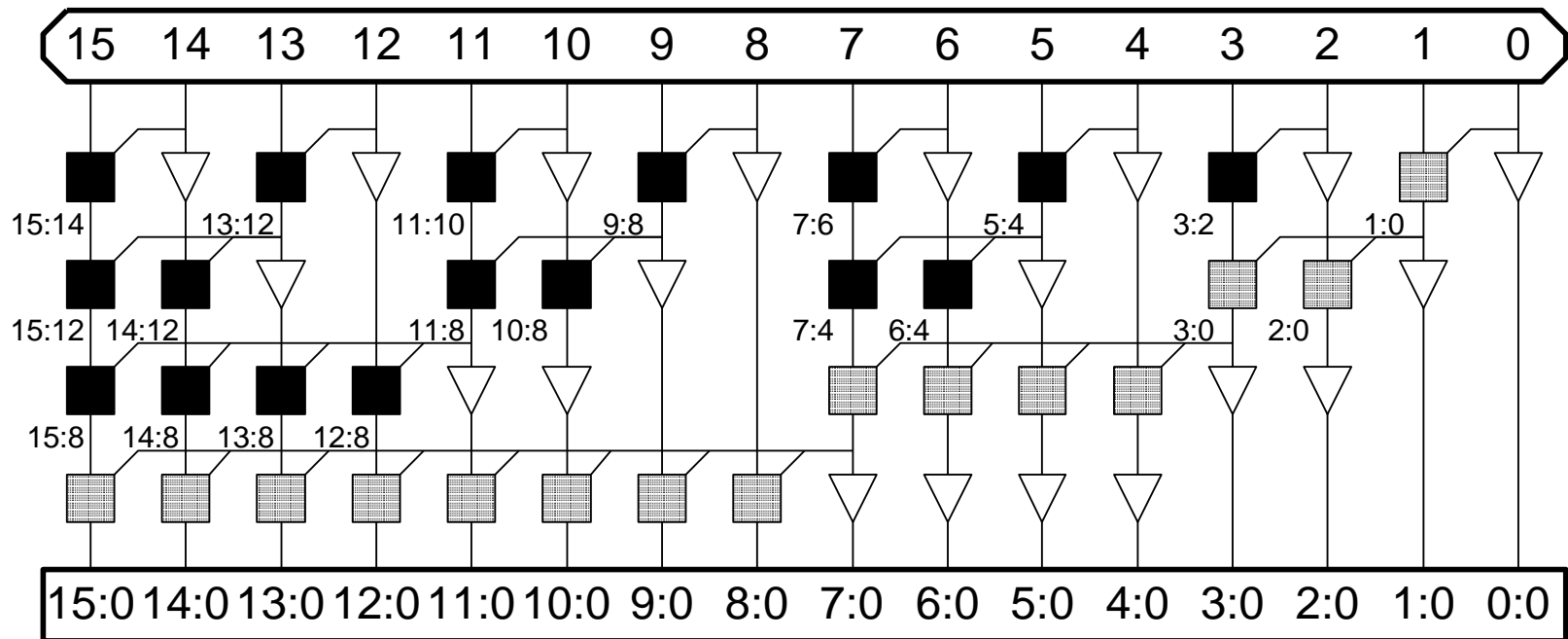



Kogge-Stone

- Least Logic Levels
- Hard to P&R

 




Tree Adder Taxonomy

- Ideal N-bit tree adder would have
 - $L = \log N$ logic levels
 - Fanout of 2
 - No more than one wiring track between levels
- Describe adder with 3-D taxonomy (l, f, t)
 - Logic levels: $L + l$
 - Fanout: $2^f + 1$
 - Wiring tracks: 2^t
- Known tree adders sit on plane defined by
$$l + f + t = L - 1$$




Tree Adder Taxonomy 2

 



Ladner-Fischer


- A bit more logic levels
- High Fanout

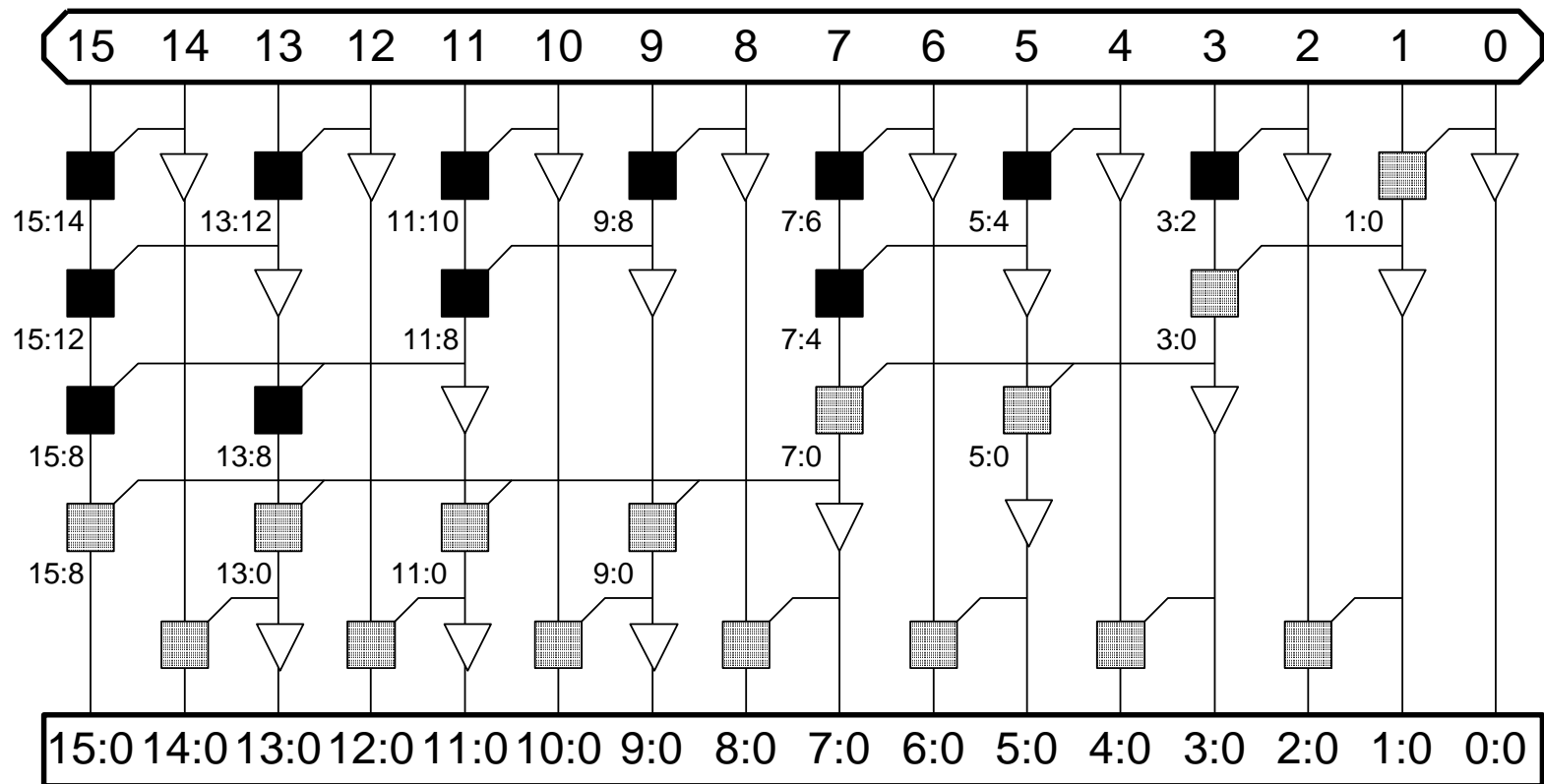



Knowles [2, 1, 1, 1]


- So many cells and wires
- Some Fanout

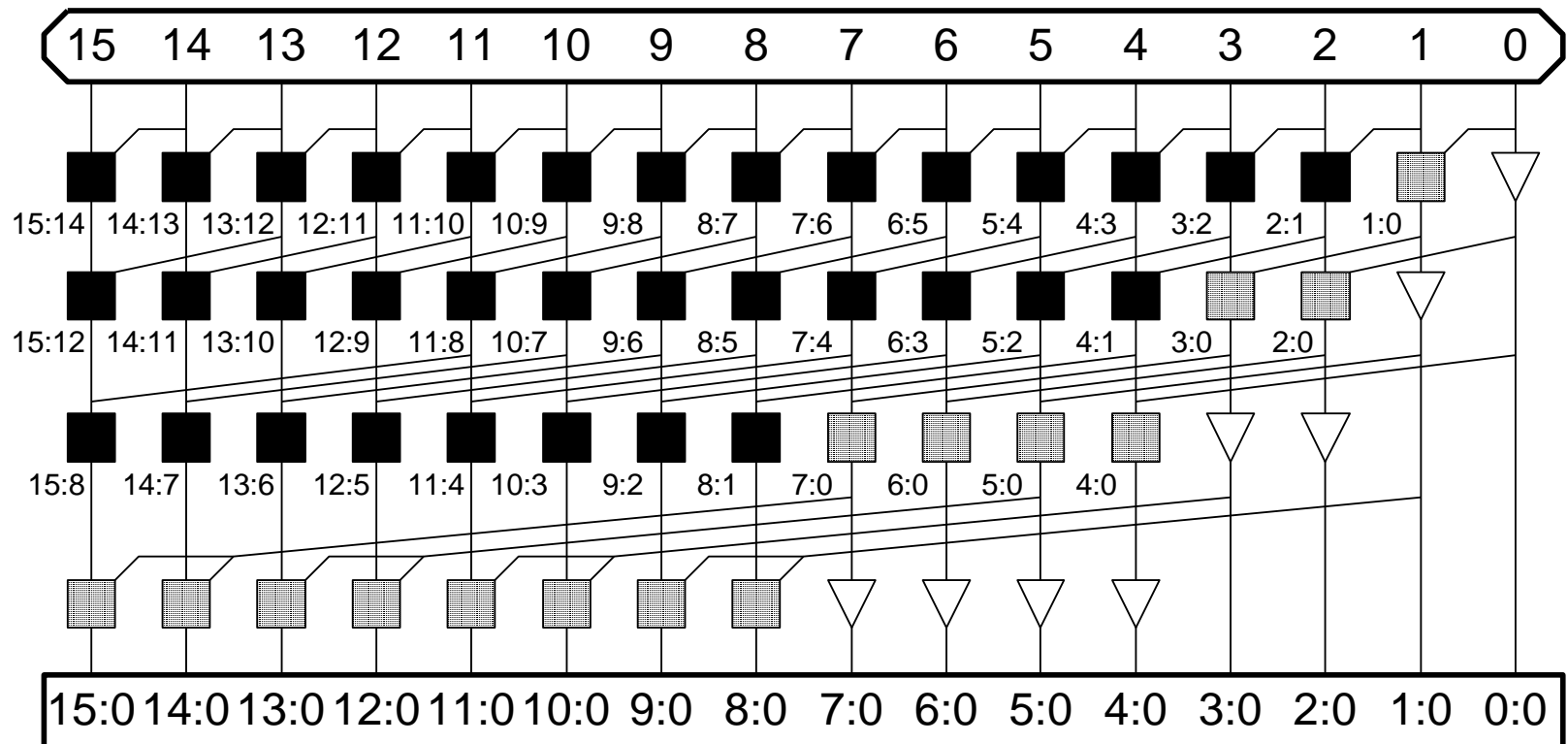



Han-Carlson

- A bit more logic levels
- Less cells

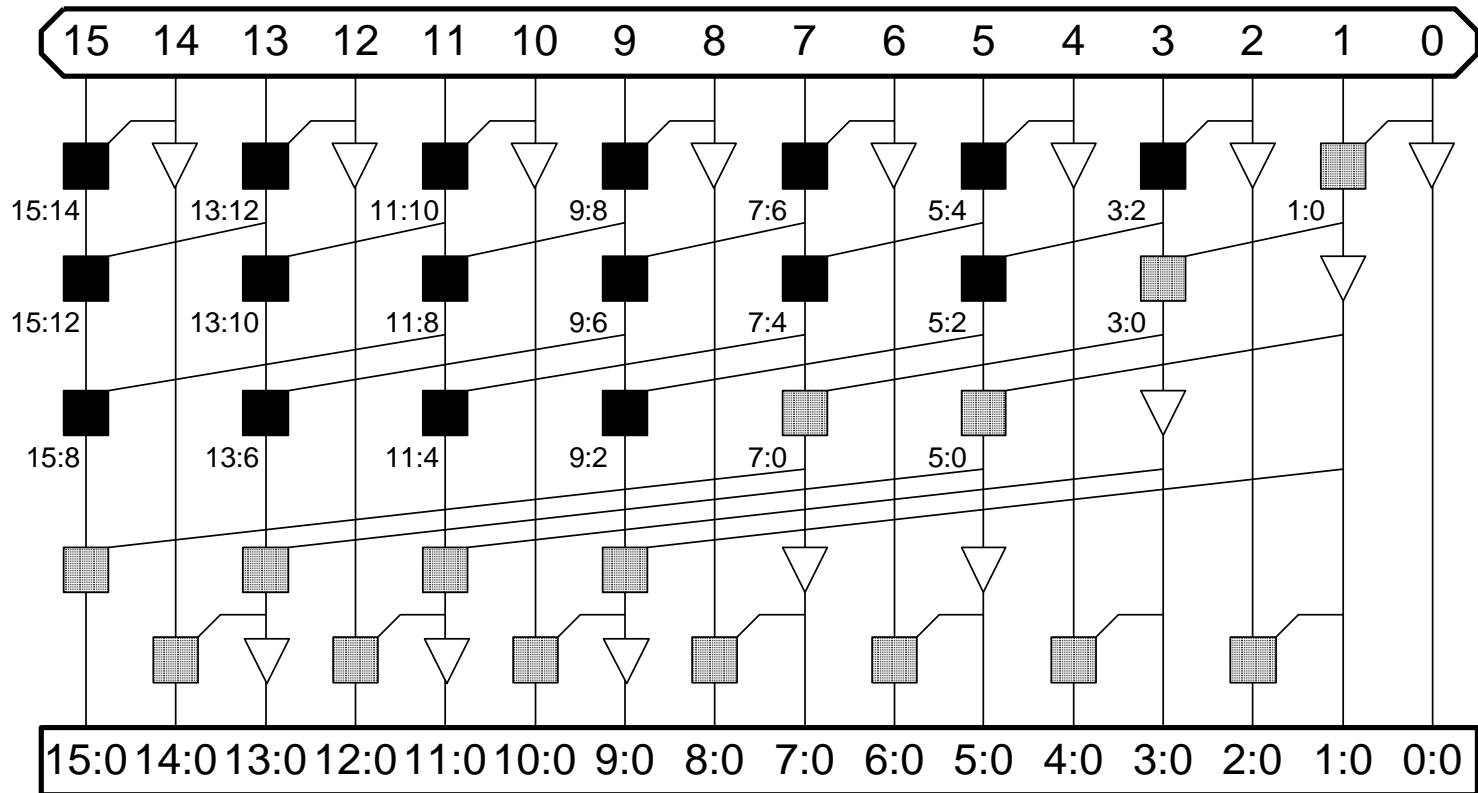




HOMEWORK

- 32-bit Sparse Tree Adder
 - Literature Search
 - What, When, Who, Where, Why, How
 - PG Diagram
 - Black cells, grey cells, buffers, muxes etc.
 - Gate Level Schematic
 - One per group
 - Delay Model wrt gate delays
 - $t_{\text{sparse}} = \dots$
 - 1 week





Tree Adder Taxonomy 3


(f) Ladner-Fischer

 

(e) Knowles [2,1,1,1]

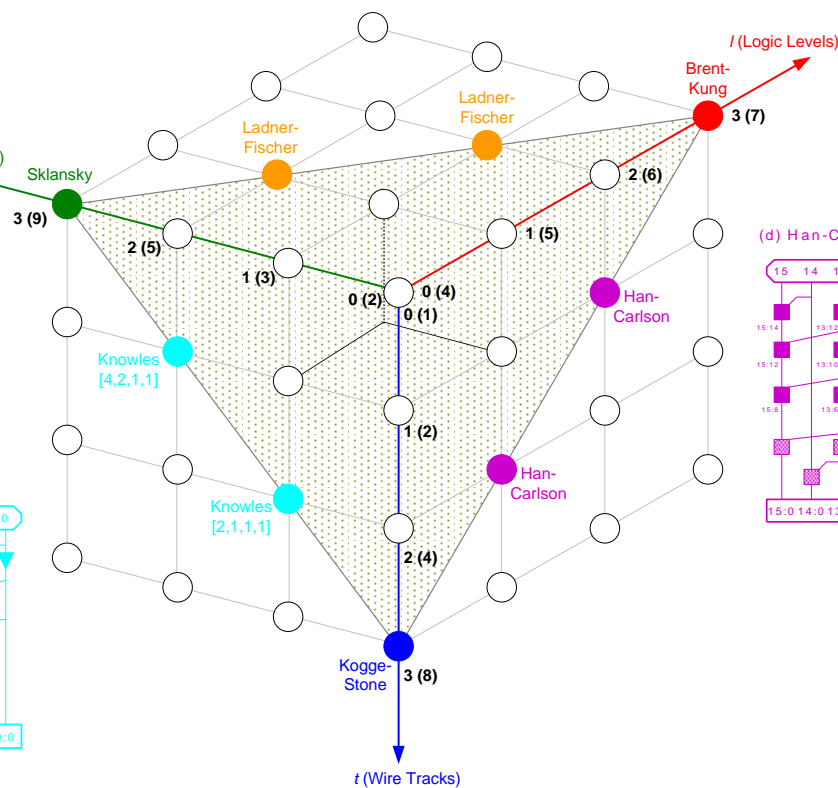 

(d) Han-Carlson

 



Summary

- Adders with Area-Power-Delay Tradeoffs

Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		$N-1$	1	1	N
Carry-Skip $n=4$		$N/4 + 5$	2	1	$1.25N$
Carry-Sel. $n=4$		$N/4 + 2$	4	1	$2N$
Brent-Kung	$(L-1, 0, 0)$	$2\log_2 N - 1$	2	1	$2N$
Sklansky	$(0, L-1, 0)$	$\log_2 N$	$N/2 + 1$	1	$0.5 N \log_2 N$
Kogge-Stone	$(0, 0, L-1)$	$\log_2 N$	2	$N/2$	$N \log_2 N$



References

- <http://bwrc.eecs.berkeley.edu/icbook/Slides/chapter11.ppt>
- <http://www.cmosvlsi.com/lect11.pdf>
- <http://www.eng.utah.edu/~cs5830/Slides/addersx2.pdf>
- Knowles, S. (1999) A Family of Adders