




SERDEN SAIT ERANIL

040170025

EHB 335E HW#5

1)

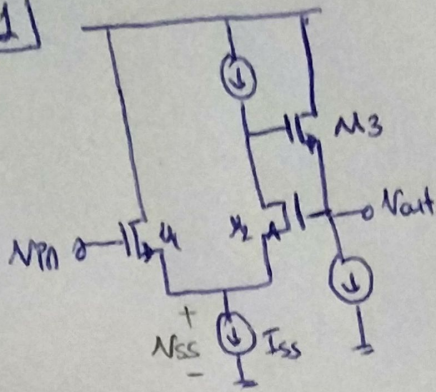

- Assume $V_{in} \uparrow$, Since $I_{d,u2}$ and hence $I_{d,u1}$ cannot change. To accommodate the increase in V_{in} , V_{ss} should increase.

- Ass $V_{ss} \uparrow$, $V_{out} \uparrow$ ($V_{gs,2} = V_{out} - V_{ss}$), $I_{d,u2}$ is fixed.

- As $V_{out} \uparrow$, $V_{o3} \uparrow$ ($V_{gs,3} = V_{o3} - V_{out}$), $I_{d,u3}$ is fixed.

- As $V_{o3} \uparrow$, drain-to-source voltage of $M2$ increases and $I_{d,u2}$ tends to increase but since $I_{d,u2}$ cannot increase $V_{gs,2}$ has to decrease to hold $I_{d,u2}$ constant. Therefore V_{out} has to decrease. Therefore this circuit employs negative feedback.


In Summary,

$$V_{in} \uparrow \rightarrow V_{ss} \uparrow \rightarrow V_{out} \uparrow \rightarrow V_{o3} \uparrow \rightarrow V_{out} \downarrow$$

negative feedback

Second Method

$$V_{in} = 0$$

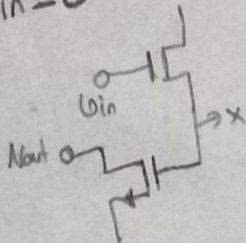

$$A_V = \frac{V_{out}}{V_{in}} = \frac{V_x}{V_{in}} \cdot \frac{V_{out}}{V_x}$$

CS stage (<0)

SF stage (>0)

$$(<0) \times (>0) = (<0) \Rightarrow \text{Negative Feedback.}$$


Sensed: current
Returned: current

\Rightarrow Current-Current Amplifier (Shunt-Series)

How to Break the loop \Rightarrow
Open-loop Gain Calculation

$$I_1 = \frac{R_F + R_L}{\frac{1}{g_{m1}} + R_F + R_L} I_{in} \quad (\text{Current Divider})$$

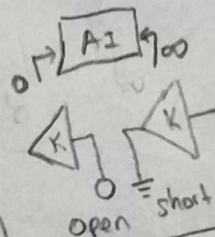
$$V_x = R_O I_1 = \frac{R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L} I_{in}$$




$$R_{in} = \frac{1}{g_{m1}} \parallel (R_F + R_L)$$

$$R_{out} = R_F \parallel R_L$$

2)

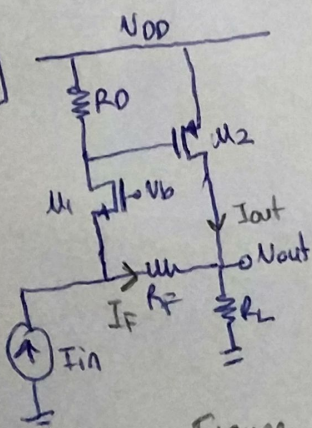

New Figure

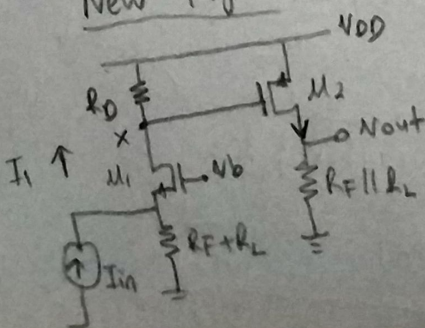


$$V_{out} = -g_{m2} (R_F \parallel R_L) V_x$$

$$I_{out} = \frac{V_{out}}{I_{out}} = -g_{m2} V_x = -\frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L} I_{in}$$

$$A_I = \frac{I_{out}}{I_{in}} = -\frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L}$$

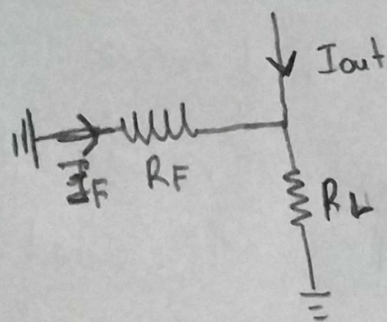(1)

Now, let us determine the Feedback Factor (K)



By Current Division

$$I_F = - \frac{R_L}{R_F + R_L} I_{out}$$


$$\Rightarrow K = \frac{I_{out}}{I_F} = - \frac{R_L}{R_F + R_L}$$

$$\Rightarrow A_{I,CL} = \frac{A_I}{1 + K A_I} = \frac{- \frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L}}{1 + \left(- \frac{R_L}{R_F + R_L} \right) \left(- \frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L} \right)}$$

$$\Rightarrow A_{I,CL} = - \frac{g_{m2} R_O (R_F + R_L)}{\left(\frac{1}{g_{m1}} + R_F + R_L \right) (1 + g_{m2} R_O R_L)}$$

$$R_{out,CL} = R_{out} (1 + K A_I) = (R_F || R_L) \left[1 + \frac{g_{m2} R_O R_L}{\frac{1}{g_{m1}} + R_F + R_L} \right]$$


$$R_{in,CL} = \frac{R_{in}}{1 + K A_I} = \frac{\frac{1}{g_{m1}} || (R_F + R_L)}{1 + \frac{g_{m2} R_O R_L}{\frac{1}{g_{m1}} + R_F + R_L}}$$

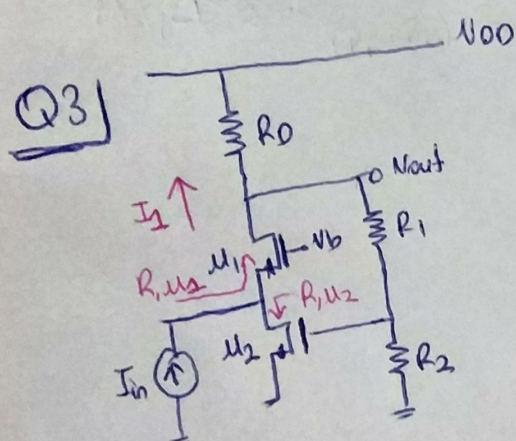

We sense voltage and return current.

\Rightarrow voltage current amplifier (shunt-shunt)

First determine open-loop gain R_O

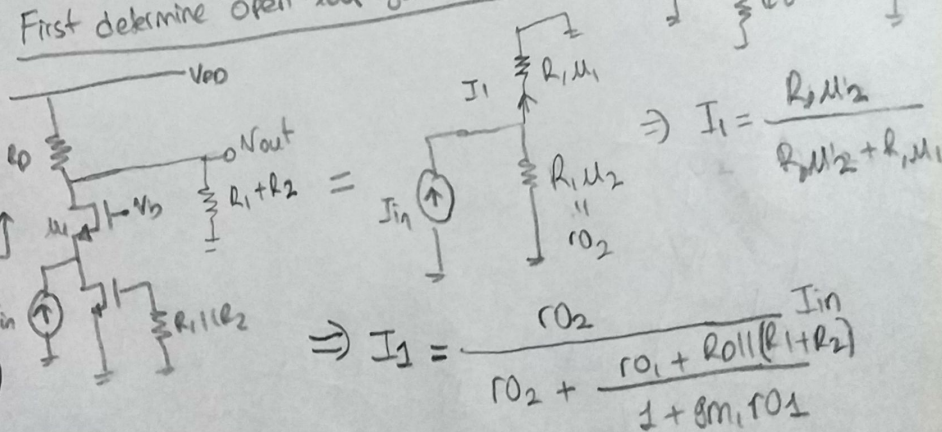

$$\Rightarrow I_1 = \frac{R_O g_{m1} V_x}{R_O g_{m1} V_x + R_1 + R_2}$$

$$\Rightarrow I_1 = \frac{R_O}{R_O + \frac{R_1 + R_2}{1 + g_{m1} R_O1}} I_{in}$$


$$V_{out} = (R_O || (R_1 + R_2)) I_1$$

$$V_{out} = \frac{(R_O || (R_1 + R_2)) R_O}{R_O + \frac{R_1 + R_2}{1 + g_{m1} R_O1}} I_{in}$$

open-loop gain of the circuit

$$\Rightarrow R_O = \frac{V_{out}}{I_{in}} = \frac{(R_O || (R_1 + R_2)) R_O}{R_O + \frac{R_1 + R_2}{1 + g_{m1} R_O1}}$$

In order to find R_{in}

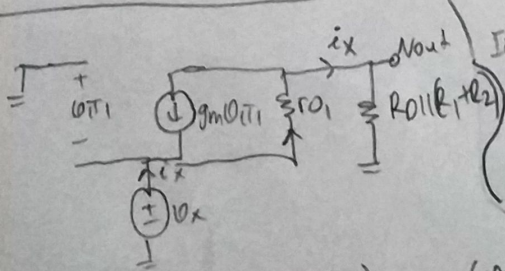


$$V_{out} = V_x - (I_x + g_{m1} V_x) R_O1 ; (V_{in} = -V_x)$$

$$I_x (R_O1 || (R_1 + R_2)) = V_x - I_x R_O1 + g_{m1} R_O1 V_x$$

$$\frac{V_x}{I_x} = R_{in} = \frac{R_O1 + R_O1 || (R_1 + R_2)}{1 + g_{m1} R_O1}$$


we draw

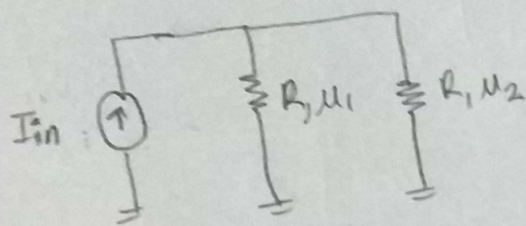

$$\Rightarrow R_{in} = R_1 || R_2$$


$$R_{in} = \left[\frac{r_{o2} + (R_0 || (R_1 + R_2))}{1 + g_{m1} r_{o1}} \right] || r_{o2}$$

and R_{out} can be calculated as

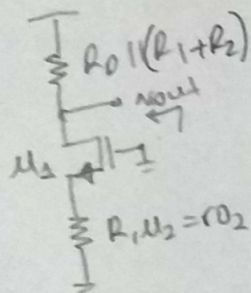

$$R_{out} = R_0 || (R_1 + R_2) || \left[(1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \right]$$

Let's calculate the feedback factor K

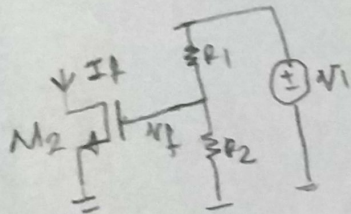

$$\Rightarrow K = \frac{I_f}{V_i} = \frac{V_f}{V_i} \cdot \frac{I_f}{V_f} = \frac{R_2}{R_1 + R_2} \cdot g_{m2}$$

Now, we can calculate the closed-loop parameters

$$R_{o,CL} = \frac{R_0}{1 + K R_0} = \frac{\frac{(R_0 || (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_0 || (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}{1 + \frac{g_{m2} R_2}{R_1 + R_2} \cdot \frac{(R_0 || (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_0 || (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}$$

\Rightarrow closed-loop gain of transimpedance amplifier


$$R_{in,CL} = \frac{R_{in}}{1 + K R_0} = \frac{\left[\frac{r_{o1} + (R_0 || (R_1 + R_2))}{1 + g_{m1} r_{o1}} \right] || r_{o2}}{1 + \frac{g_{m2} R_2}{R_1 + R_2} \cdot \frac{(R_0 || (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_0 || (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}$$

\Rightarrow closed-loop input impedance of transimpedance amplifier

$$R_{out,CL} = \frac{R_{out}}{1 + K R_0} = \frac{R_0 || (R_1 + R_2) || \left[(1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \right]}{1 + \frac{g_{m2} R_2}{R_1 + R_2} \cdot \frac{(R_0 || (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_0 || (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}$$

\Rightarrow closed-loop output impedance of transimpedance amplifier

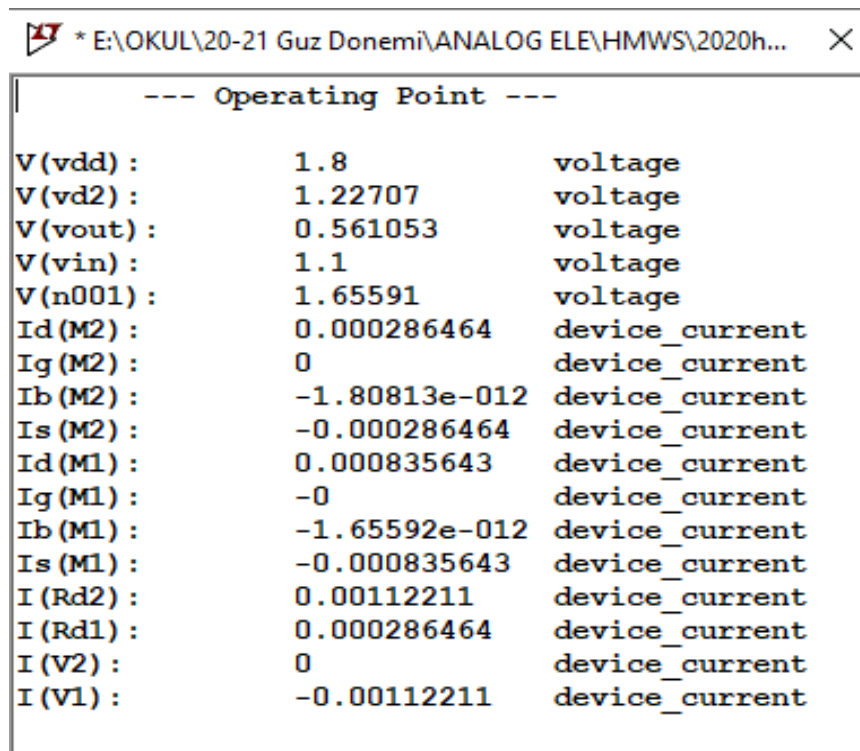
\Rightarrow Negative feedback makes the amplifier close to the ideal by reducing R_{out} and R_{in} at the cost of reducing the gain.




b-) Now, we are asked to find the closed loop gain, input and output impedances.

We add 1V AC to easily find the closed loop gain in the AC analysis.

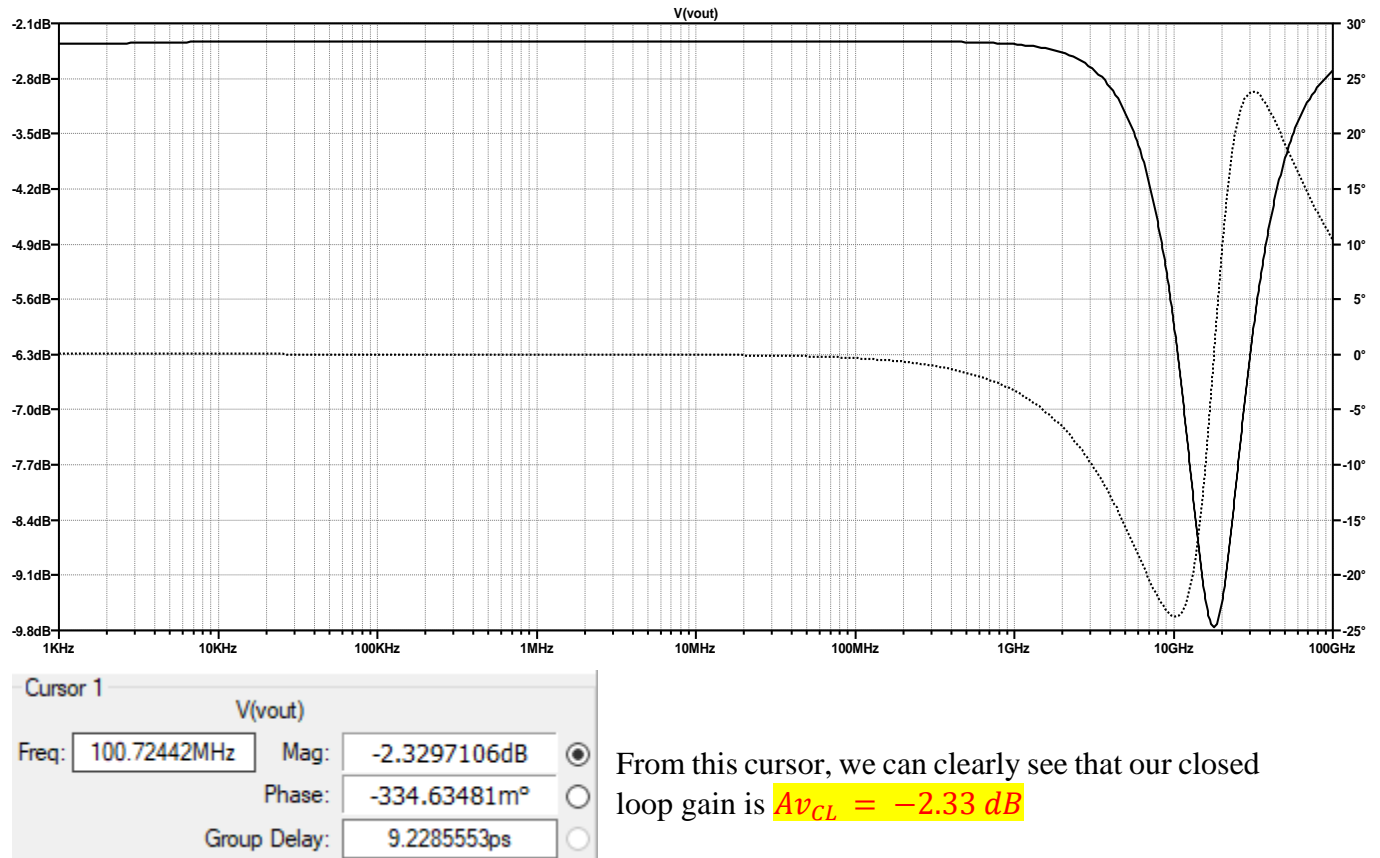
By using the command `.ac dec 100k 1k 100giga`. We can see the gain over a range of frequencies



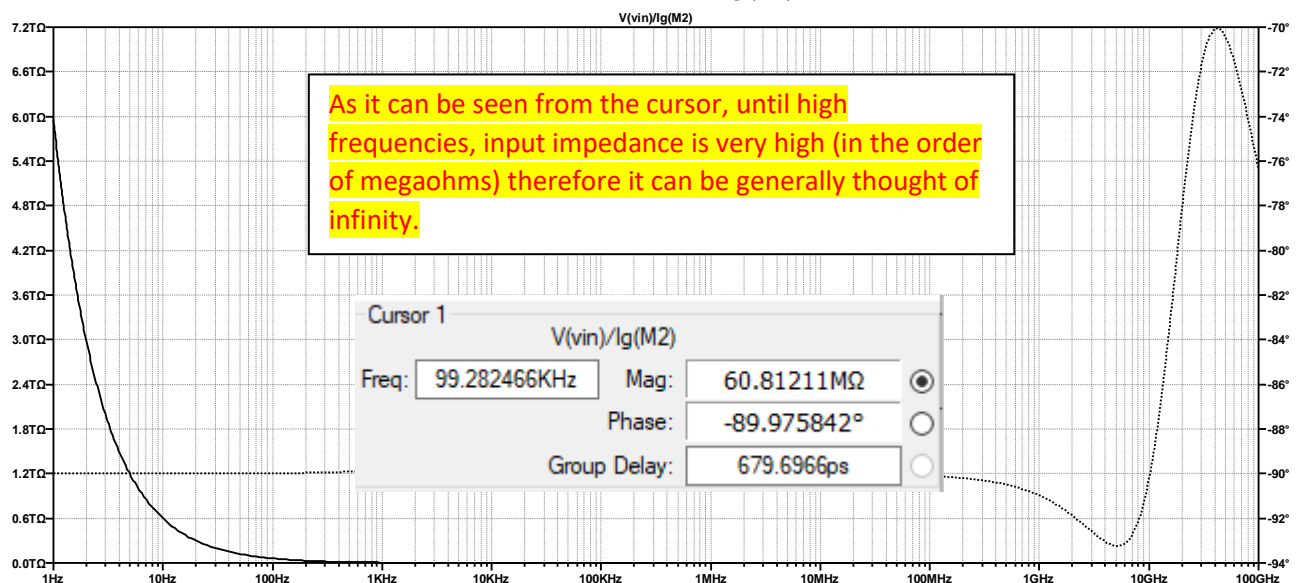To calculate closed loop input impedance, we take the ratio $\frac{V_{in}}{I_g(M2)}$




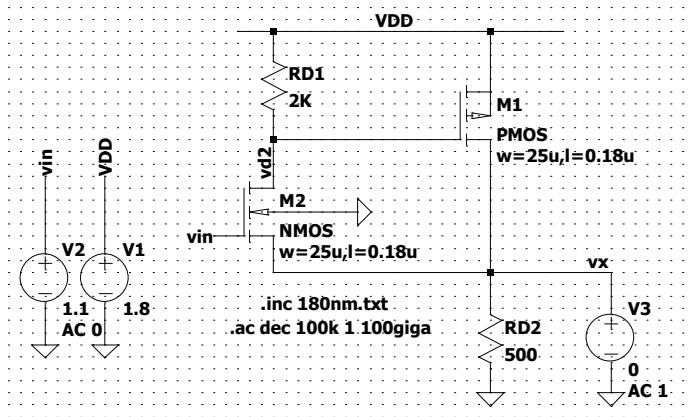
In order to calculate closed loop output impedance, we configure the circuit as follows (set the AC input voltage to zero, and tie a voltage source to the output).



After configuration of the circuit, we can calculate the closed loop output impedance by taking the ratio

$$Rout_{CL} = \frac{V_x}{I_x}$$

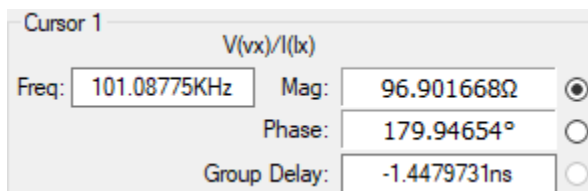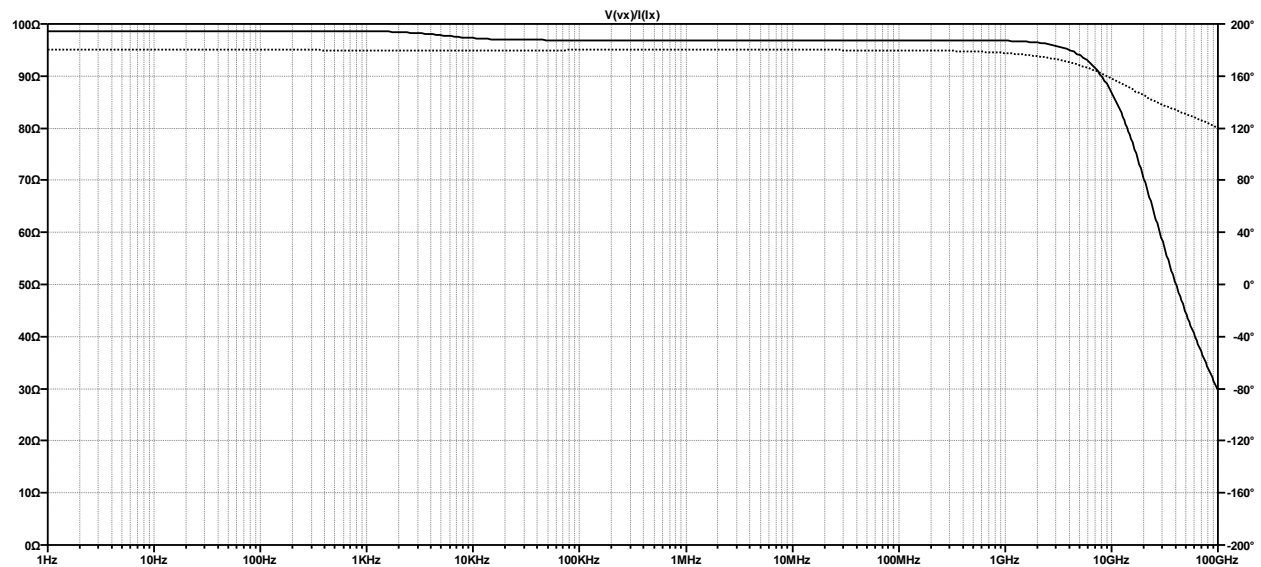And this ratio can be seen for a range of frequencies as follows



From the circuit it can be seen that, until high frequency dominates the closed loop output impedance is approximately $Rout_{CL} = 100 \Omega$