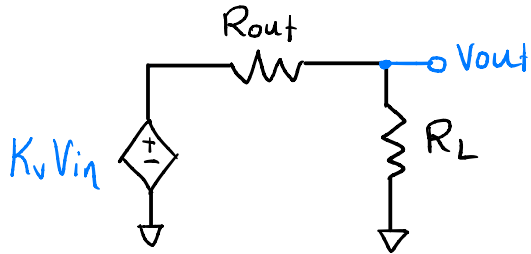


Homework-1 Solutions

(50p)


1) a)  $\frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s}$ . Let's start with  $\frac{V_{out}}{V_{in}}$



Using resistive divider:

$$V_{out} = K_v V_{in} \frac{R_L}{R_L + R_{out}} \Rightarrow \frac{V_{out}}{V_{in}} = K_v \frac{R_L}{R_L + R_{out}}$$

Let's find  $\frac{V_{in}}{V_s}$  now:

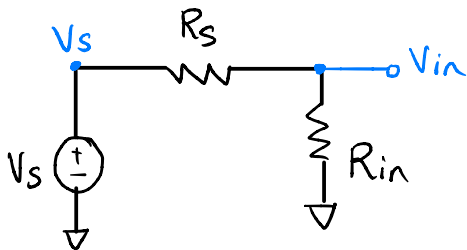

Using resistive divider again:

$$V_{in} = V_s \cdot \frac{R_{in}}{R_{in} + R_s} \Rightarrow \frac{V_{in}}{V_s} = \frac{R_{in}}{R_{in} + R_s}$$

Finally, gain equation is  $\frac{V_{out}}{V_s} = \frac{R_{in}}{R_{in} + R_s} \times K_v \times \frac{R_L}{R_L + R_{out}}$

b)  $\frac{V_{out}}{V_s} = \frac{1k}{1k + 10k} \times 100 \times \frac{100}{100 + 100k} \approx 0.009 \frac{V}{V}$

As you can see, we actually do not amplify the signal, we attenuate it. This is because  $R_{in}$  is too small and  $R_{out}$  is too large with respect to  $R_s$  and  $R_L$ , respectively. In order to get high gain,  $R_{in}$  must be large (ideally infinite) and  $R_{out}$  must be small (ideally zero). Through this course, we will see that some amplifier topologies have this characteristics.

(50p)

$$2) \quad g_m = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_{v_{BE}=V_{BE,Q}} = I_S \cdot e^{\frac{v_{BE}}{V_T}} \cdot \frac{1}{V_T} \bigg|_{v_{BE}=V_{BE,Q}} = \underbrace{I_S e^{\frac{V_{BE,Q}}{V_T}}}_{I_{C,Q}} \cdot \frac{1}{V_T}$$

$g_m = \frac{I_{C,Q}}{V_T} \rightarrow$

- i) If we move to the left,  $I_{C,Q}$  decreases and slope is less steep.
- ii) If we move to the right, slope is more steep.

So, the derived equation agrees with characteristics.