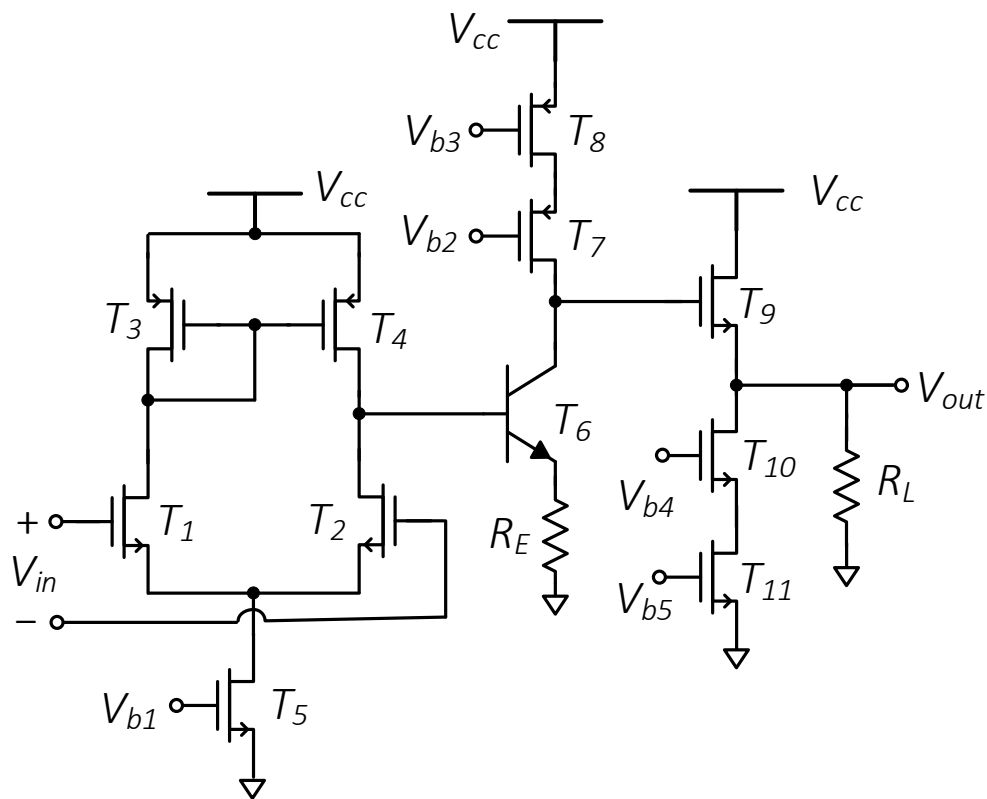


Group 1 (Student last number: 0,1,2,3)

(G2 and G3 problems are in the next pages)

For the amplifier below, $g_{m,npn} = 10 \text{ mS}$, $g_{m,nmos} = 5 \text{ mS}$, $g_{m,pmos} = 1 \text{ mS}$, $R_E = 100 \Omega$, $R_L = 1 \text{ k}\Omega$, $r_{o,npn} = 50 \text{ k}\Omega$, $r_{o,nmos} = 5 \text{ k}\Omega$, $r_{o,pmos} = 10 \text{ k}\Omega$, and $\beta = 100$ are given. Assume that MOSFETs operate in the saturation region and the BJT is in the forward-active region, where V_{B1} through V_{B5} are DC biasing voltages.


- Find the mid-band voltage gain expression $A_V = V_{out}/V_{in}$ of the amplifier, and calculate it in dB.
- How would you improve the CMRR of this amplifier? Suggest a modification in the circuit topology, and calculate (approximately) the factor of improvement of your proposal.



Group 2 (Student last number: 4,5,6) (G3 problem is in the next page)

For the amplifier below, $g_{m,npn} = 20 \text{ mS}$, $g_{m,nmos} = 10 \text{ mS}$, $g_{m,pmos} = 2 \text{ mS}$, $R_E = 100 \Omega$, $R_L = 2 \text{ k}\Omega$, $r_{o,npn} = 60 \text{ k}\Omega$, $r_{o,nmos} = 8 \text{ k}\Omega$, $r_{o,pmos} = 12 \text{ k}\Omega$, and $\beta = 100$ are given. Assume that MOSFETs operate in the saturation region and the BJT is in the forward-active region, where V_{B1} through V_{B5} are DC biasing voltages.

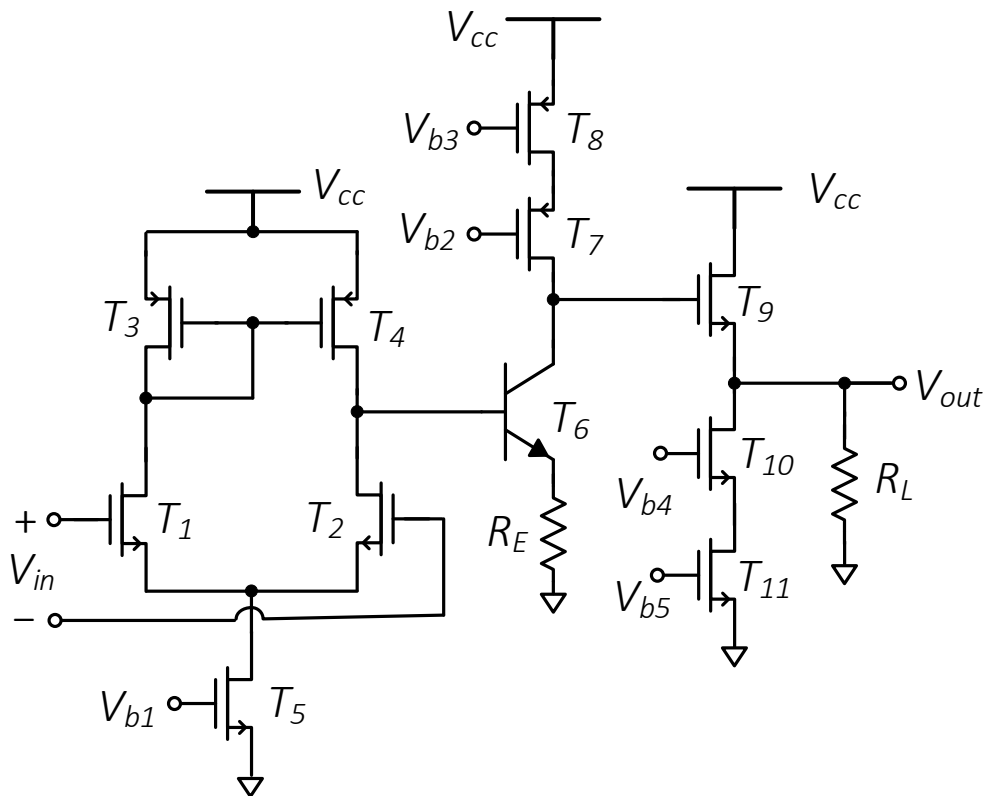- Find the mid-band voltage gain expression $A_V = V_{out}/V_{in}$ of the amplifier, and calculate it in dB.
- How would you improve the CMRR of this amplifier? Suggest a modification in the circuit topology, and calculate (approximately) the factor of improvement of your proposal.



Group 3 (Student last number: 7,8,9)

For the amplifier below, $g_{m,npn} = 15 \text{ mS}$, $g_{m,nmos} = 8 \text{ mS}$, $g_{m,pmos} = 1.5 \text{ mS}$, $R_E = 100 \Omega$, $R_L = 2 \text{ k}\Omega$, $r_{o,npn} = 55 \text{ k}\Omega$, $r_{o,nmos} = 6 \text{ k}\Omega$, $r_{o,pmos} = 11 \text{ k}\Omega$, and $\beta = 100$ are given. Assume that MOSFETs operate in the saturation region and the BJT is in the forward-active region, where V_{B1} through V_{B5} are DC biasing voltages.

- Find the mid-band voltage gain expression $A_V = V_{out}/V_{in}$ of the amplifier, and calculate it in dB.
- How would you improve the CMRR of this amplifier? Suggest a modification in the circuit topology, and calculate (approximately) the factor of improvement of your proposal.

