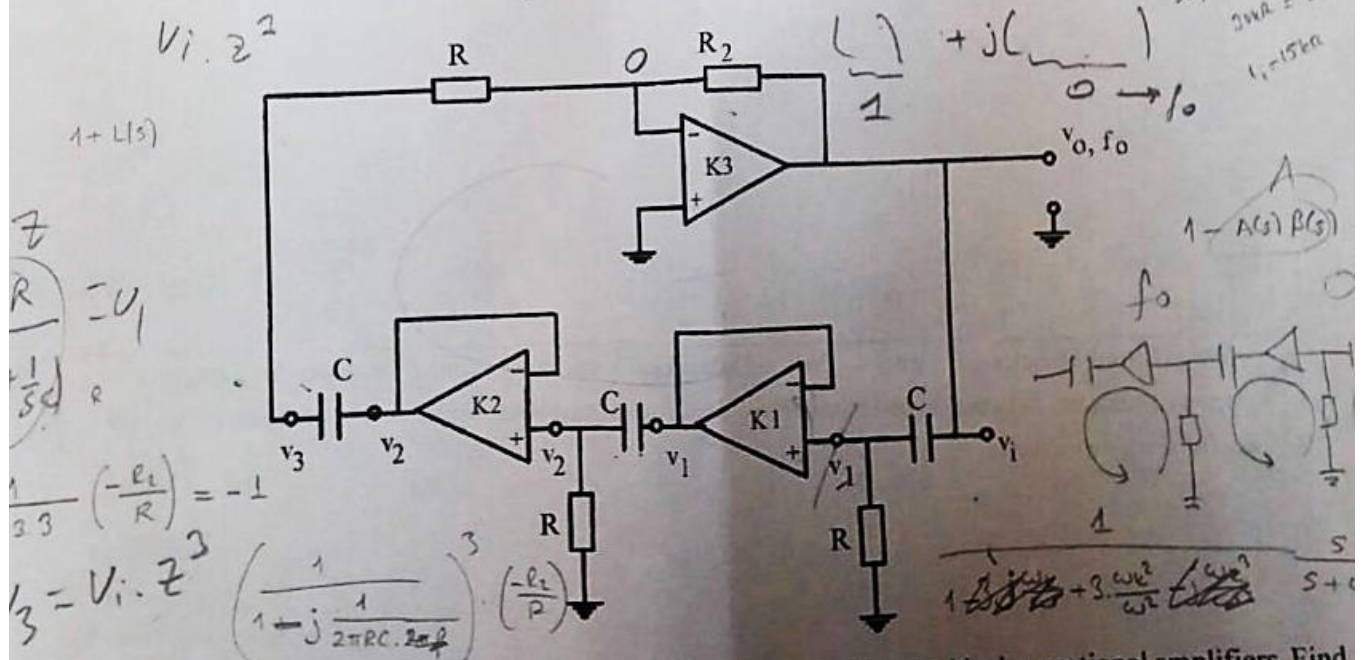


- 1)- The unloaded voltage gain of a given inverting amplifier is 100, and the amplifier is driven with a voltage source with an internal impedance of R_g . The small signal model is given above:
 - a)- At midband, the gain is measured as $v_o/v_i = -100$ for the unloaded circuit ($R_L = \infty$); when $R_g = 10k\Omega$ and $R_L = 10k\Omega$, we measure $v_o/v_g = -48$ & $v_o/v_i = -80$. Find the input and output resistances of the circuit (i.e., r_i and r_o)
 - b)- The amplifier is connected to the source and load over coupling capacitors C_1 and C_2 , respectively. Find the C_1/C_2 ratio so that their associated low frequency poles coincide. Find C_1 & C_2 for a low frequency cutoff (-3dB) of $f_L = 70\text{Hz}$.
 - c)- When the input is a pulse, find the maximum pulse width so that the output tilt stays less than 2%.
 - d)- When the input pulse has a negligible rise time, the risetime measured using a scope at the output is 726ns ($R_g = 10k\Omega$). When $R_g = 0\Omega$ (t_{rg} still negligible), the output risetime drops down to 10ns. If output capacitance $C_o = 2\text{pF}$, find C_i (amplifier input capacitance) & C_f (feedback capacitance).

Note: Miller theorem: input: $(1-K)C_f$, output $(1-1/K)C_f$; $t_r = \frac{0.35}{f_H}$, $t_r = \sqrt{t_1^2 + t_2^2 + \dots}$




- 2)- The above circuit is a sinusoidal RC phase shift oscillator. K1-2-3 are ideal operational amplifiers. Find the oscillation frequency f_o as a function of RC , and also find the necessary R_2 in terms of R .

CONTINUED ON THE BACK- TURN OVER

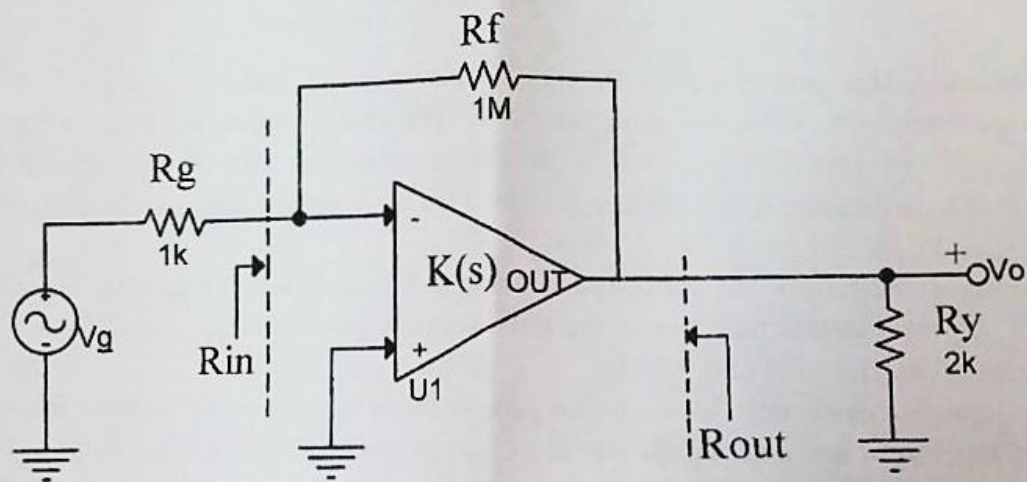3)- The amplifier in the circuit below has the transfer function:

$$K(s) = \frac{V_o}{V_i} = \frac{2\pi 10^7}{(s + 2\pi 10^3)}, \quad r_{id} = 100k\Omega, \quad r_o = 1k\Omega$$

- What is the **amplifier** gain at the low and midband frequencies.
- What is the feedback topology? Find the input (R_{in}) and output (R_{out}) resistances of the **circuit** (with feedback).
- Find the bandwidth of the **circuit** (with feedback).
- Find the gain of the **circuit** (V_o/V_g) (with feedback).



Points: 38 + 28 + 34 = 100

Time 120".

Notes: Closed books & notes. No cellphones. You may make reasonable engineering approximations. All your approximations, roundings, and assumptions should be clearly visible. Be careful with your units.