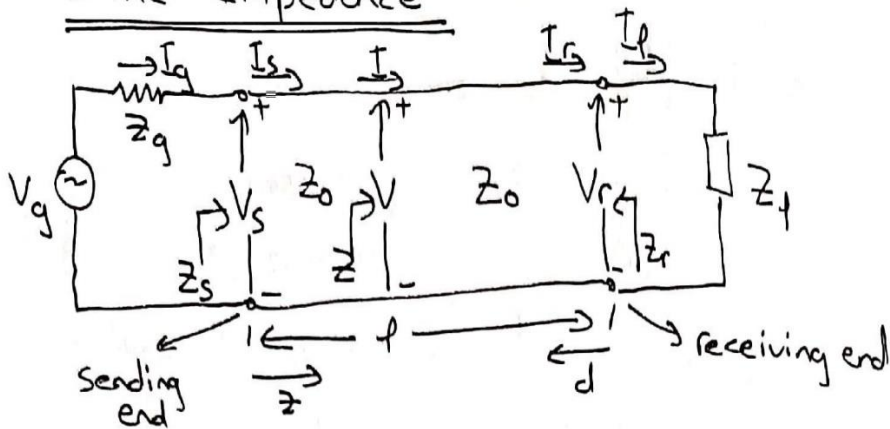


Line Impedance



The line impedance of a transmission line is the ratio of the voltage to the current at any z point:

$$Z \equiv \frac{V(z)}{I(z)}$$

where, $V = V_{inc} + V_{ref} = V_+ e^{-\gamma z} + V_- e^{\gamma z}$

and $I = I_{inc} + I_{ref} = (V_+ e^{-\gamma z} - V_- e^{\gamma z}) Y_0$

Impedance Computed from the Sending End (or input port)

At the sending end, $z=0$,

$$V_s = I_s Z_s \quad \text{and} \quad I_s = I_s$$

$$\text{and } V(z=0) = V_s = V_+ + V_- = I_s Z_s, \quad I(z=0) \cdot Z_0 = V_+ - V_- = I_s Z_0$$

Solving these two equations for V_+ and V_- , we have

$$V_+ = \frac{I_s}{2} (Z_s + Z_0) \quad \text{and} \quad V_- = \frac{I_s}{2} (Z_s - Z_0)$$

Substituting V_+ and V_- into $V(z)$ and $I(z)$ yields,

$$V = \frac{I_s}{2} [(Z_s + Z_0)e^{-\gamma z} + (Z_s - Z_0)e^{\gamma z}]$$

$$\text{and } I = \frac{I_s}{2Z_0} [(Z_s + Z_0)e^{-\gamma z} - (Z_s - Z_0)e^{\gamma z}]$$

Then, the line impedance at a point z (from the sending end) is

$$Z = Z_0 \frac{(Z_s + Z_0)e^{-\gamma z} + (Z_s - Z_0)e^{\gamma z}}{(Z_s + Z_0)e^{-\gamma z} - (Z_s - Z_0)e^{\gamma z}}$$

For $z=l$, we express the line impedance at the receiving end Z_r in terms of Z_s and Z_0 .

If $Z_s = Z_0$ (Z_s matches Z_0), Z_r will equal to Z_0 and the line impedance Z at any z point will also equal to Z_0 .

We can find the line impedance at any point from the source voltage V_g , current I_g , and impedance Z_g by using these relations,

$$I_s = I_g \quad \text{and} \quad \frac{V_g}{I_g} = Z_g + Z_s, \quad \underline{Z_s = \frac{V_g}{I_g} - Z_g}$$

Impedance Computed from the Receiving End (or Output port)

At the receiving end, $z=l$ and $V_r = I_l Z_l$. We can express the line impedance in terms of Z_l and Z_0 :

$$I_l Z_l = V_+ e^{-\gamma l} + V_- e^{\gamma l} \quad \text{and} \quad I_l Z_0 = V_+ e^{-\gamma l} - V_- e^{\gamma l}$$

We can obtain V_+ and V_- by solving the equations above:

$$V_+ = \frac{I_l}{2} (Z_l + Z_0) e^{\gamma l} \quad \text{and} \quad V_- = \frac{I_l}{2} (Z_l - Z_0) e^{-\gamma l}$$

Then, substituting these results into $V(z)$ and $I(z)$ and letting $l-z=d$, we have

$$V = \frac{I_l}{2} [(Z_l + Z_0) e^{\gamma d} + (Z_l - Z_0) e^{-\gamma d}] \quad \text{and} \quad I = \frac{I_l}{2Z_0} [(Z_l + Z_0) e^{\gamma d} - (Z_l - Z_0) e^{-\gamma d}]$$

Next, we find the line impedance at any point from the receiving end in terms of Z_l and Z_0 :

$$Z = Z_0 \frac{(Z_l + Z_0) e^{\gamma d} + (Z_l - Z_0) e^{-\gamma d}}{(Z_l + Z_0) e^{\gamma d} - (Z_l - Z_0) e^{-\gamma d}}$$

We get the line impedance at the sending end ^(Z_s) by setting $d=l$ into this equation.

If $Z_l = Z_0$ (Z_l matches Z_0), Z_s will equal to Z_0 .

Transfer Impedance

Transfer impedance, Z_{tr} , is defined as the ratio of V_s/I_r . We get Z_{tr} by using V and I definitions (which are given in terms of Z_l, Z_0 and d):

$$Z_{tr} = \frac{V_s}{I_r} = \frac{1}{2} [(Z_l + Z_0) e^{\gamma l} + (Z_l - Z_0) e^{-\gamma l}]$$

This eq. is useful for finding the V_s from the known quantities at the receiving end.

Impedance in Terms of Hyperbolic or Circular Functions:

The hyperbolic functions are $e^{\pm \gamma z} = \cosh(\gamma z) \pm \sinh(\gamma z)$. Substituting these functions into the $Z(z_s)$ eq. yields the line impedance at any point from the sending end in terms of the hyperbolic functions:

$$Z = Z_0 \frac{Z_s \cosh(\gamma z) - Z_0 \sinh(\gamma z)}{Z_0 \cosh(\gamma z) - Z_s \sinh(\gamma z)} = Z_0 \frac{Z_s - Z_0 \tanh(\gamma z)}{Z_0 - Z_s \tanh(\gamma z)}$$

Similarly, for $Z(z_r)$ eq., we obtain Z from the receiving end;

$$Z = Z_0 \frac{Z_r \cosh(\gamma d) + Z_0 \sinh(\gamma d)}{Z_0 \cosh(\gamma d) + Z_r \sinh(\gamma d)} = Z_0 \frac{Z_r + Z_0 \tanh(\gamma d)}{Z_0 + Z_r \tanh(\gamma d)}$$

For a lossless line, $\gamma = j\beta$ ($Z_0 = R_0$) and using the following relationships, $\sinh(j\beta z) = j\sin(\beta z)$ and $\cosh(j\beta z) = \cos(\beta z)$, we can express the Z impedance in terms of the circular functions,

$$Z = R_0 \frac{Z_s - jR_0 \tan(\beta z)}{R_0 - jZ_s \tan(\beta z)} \quad (\text{from the sending end})$$

$$\text{or } Z = R_0 \frac{Z_r + jR_0 \tan(\beta d)}{R_0 + jZ_r \tan(\beta d)}$$

(from the receiving end)

For a lossless line, the line impedance or admittance repeats at intervals of $\lambda/2$

Two special cases are,

- Short circuit: if $Z_p = 0$, the input impedance becomes,

$$Z_{in} = jR_0 \tan(\beta d) \quad (\text{inductor})$$

- Open circuit: if the load is open, that is, $Z_p = \infty$,

$$Z_{in} = -jR_0 \cot(\beta d) \quad (\text{capacitor})$$

For the general lossy case and for the $Z_p = 0$ we obtain the sending-end impedance as, ($d = l$)

$$Z_{sc} = Z_0 \tanh(\gamma l)$$

For the $Z_p = \infty$, we obtain, ($d = l$) ^{letting}

$$Z_{oc} = Z_0 \coth(\gamma l) = Z_0 / \tanh(\gamma l)$$

Now, we can calculate the characteristic impedance from

$$Z_0 = \sqrt{Z_{oc} Z_{sc}}$$

and the propagation constant from

$$\gamma l = \alpha l + j\beta l = \tanh^{-1} \sqrt{Z_{sc} / Z_{oc}}$$

- If we let $d = n\lambda/2$ in eq. $Z(Z_p)$ for lossless case, $n = 1, 2, 3, \dots$ - then $Z_s = Z_p$

- If we let $d = \lambda/4$, then $Z_s = Z_0^2 / Z_p$ or $Z_s \cdot Z_p = Z_0^2$


If we define normalized impedances $Z_s = \frac{Z_s}{Z_0}$ and $Z_p = \frac{Z_p}{Z_0}$ then the ^{above} relationship becomes $z_s = 1/z_p$

The line which has the length of $\lambda/4$, is referred to as quarter-wave transformer. If a given resistive load $Z_p \neq Z_0$, a quarter-wave transformer can be used to convert Z_p to Z_0 of the main transmission line. To obtain this result, the characteristic impedance of the transformer will be,

$$Z_{0q} = \sqrt{Z_p Z_0} \quad \Omega \quad (\text{Note that } Z_{0q}, Z_p \text{ or } Z_0 \text{ are pure resistances})$$

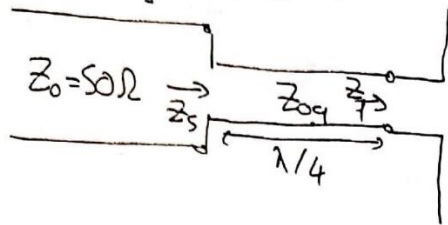Example:

A half-wave, centered antenna has a driving-point impedance of 73Ω . But the transmission line connected to the antenna has $Z_0 = 50 \Omega$. Determine the characteristic impedance of a quarter wavelength line to be used for matching the dipole antenna to the line.



For a proper match, $Z_0 = Z_S = 50 \Omega$
then, $Z_{0q} = \sqrt{Z_L \cdot Z_S} = \sqrt{73 \cdot 50} = 60 \Omega$.

Example: A certain open-wire telephone line has the following parameters at a frequency of 2 kHz :

$R = 6.75 \Omega/\text{mi}$, $L = 0.00340 \text{ H}/\text{mi}$, $G = 0.400 \mu\text{S}/\text{mi}$, $C = 0.00862 \mu\text{F}/\text{mi}$
 $D = 100 \text{ mi}$ and $Z_L = 200 - j200 \Omega$

Calculate the a) Z_0 , b) γ of the line and c) line impedance Z_{line} at a distance D from the receiving load Z_L .

a) $Z = R + j\omega L = 6.75 + j42.7$, $Y = G + j\omega C = (0.4 + j108.26) \cdot 10^{-6}$

$$Z_0 = \sqrt{Z/Y} = 632 \angle -4.4^\circ = 630 - j48.3 \Omega$$

b) The propagation constant is $\gamma = \sqrt{ZY} = 0.085 \angle 85.6^\circ = 0.00545 + j0.08$
 $\alpha = 0.00545 \text{ Np}/\text{mi}$ and $\beta = 0.0680 \text{ rad}/\text{mi}$

c) $Z_{\text{line}} = Z_0 \frac{Z_L \cosh(\gamma D) + Z_0 \sinh(\gamma D)}{Z_0 \cosh(\gamma D) + Z_L \sinh(\gamma D)}$

$$\cosh(\gamma D) = \cosh(\alpha + j\beta)D = \cosh(\alpha D) \cos(\beta D) + j \sinh(\alpha D) \sin(\beta D) \\ = 0.990 + j0.296$$

$$\sinh(\gamma D) = \sinh(\alpha + j\beta)D = \sinh(\alpha D) \cos(\beta D) + j \cosh(\alpha D) \sin(\beta D) \\ = 0.1494 + j0.593 \quad \text{then } Z_{\text{line}} = 460.1 \angle 46^\circ = 488.6 + j368 \Omega$$