

10 December 2020

3) For the class AB output stage below, $V_{CEmin,Q1} = |V_{CEmin,Q2}| = 0.8\text{ V}$, $V_{CEmin,Q3} = |V_{CEmin,Q4}| = 0.5\text{ V}$, $V_{BE,Q1} = |V_{BE,Q2}| = 0.5\text{ V}$, $V_{BE,Q5} = 0.8\text{ V}$, $R_L = 8\ \Omega$, $\beta_n = \beta_p = 50$.

- Calculate the proper V_{CC} value considering the peak value of the load voltage for $P_{L,ave} = 49\text{ W}$.
- Find the maximum efficiency of this output stage. You can use the expressions we derived in our lectures.
- Calculate the value of R_2 in order to avoid crossover distortion.
- If the breakdown voltages of Q_1 and Q_2 are equal, i.e., $V_{CEmax,Q1} = |V_{CEmax,Q2}|$, what should be the minimum value?

