

For transistors in the circuit
 $\beta_F=100$, $|V_{BE}|=0.6V$ $V_T=25mV$
 $F_{T1}=100MHz$ $C_{be1}=130pF$
 $F_{T2}=50MHz$ $C_{be2}=650pF$
 are given.


In DC case;
 $V_i=0V$ $I_{C1}\approx 2.3mA$ $I_{C2}\approx 5.7mA$

The load at the output : $R_L=10k$ $C_L=0.5nF$
 (The load does not affect DC values in the circuit)

Investigate v_o/v_i for peak behaviour.

F_T is the transition frequency of a transistor.
 At this frequency, current gain is 1.

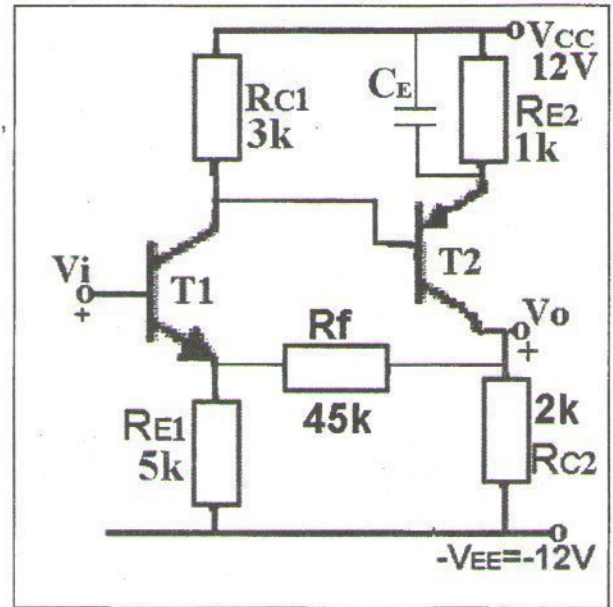
F_T is given approximately; $F_T=gm/2\pi(C_{be}+C_{cb})$



input voltage, output voltage

$$\beta = - \frac{v_o}{v_i} \rightarrow \beta = - \frac{1}{10}$$

$A=v_o/v_t$

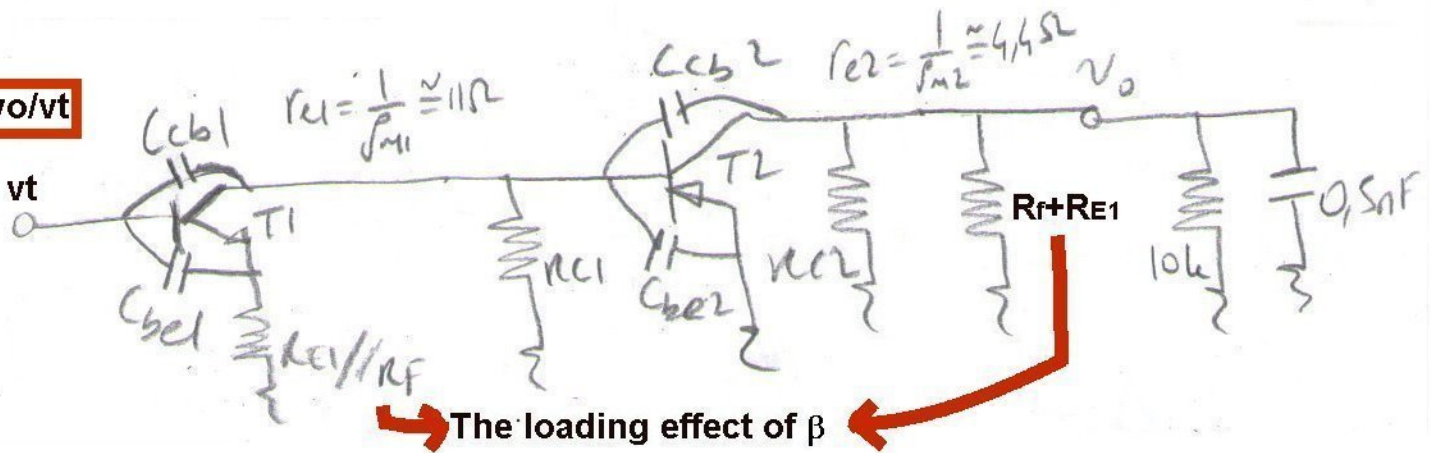

The loading effect of β


$$C_{cb1} = \frac{1}{2\pi f_{c1} F_{T1}} - C_{be1}$$

$$\approx 15pF$$

Miller

$$C_{cb2} = \frac{1}{2\pi f_{c2} F_{T2}} - C_{be2}$$

$$\approx 73pF$$

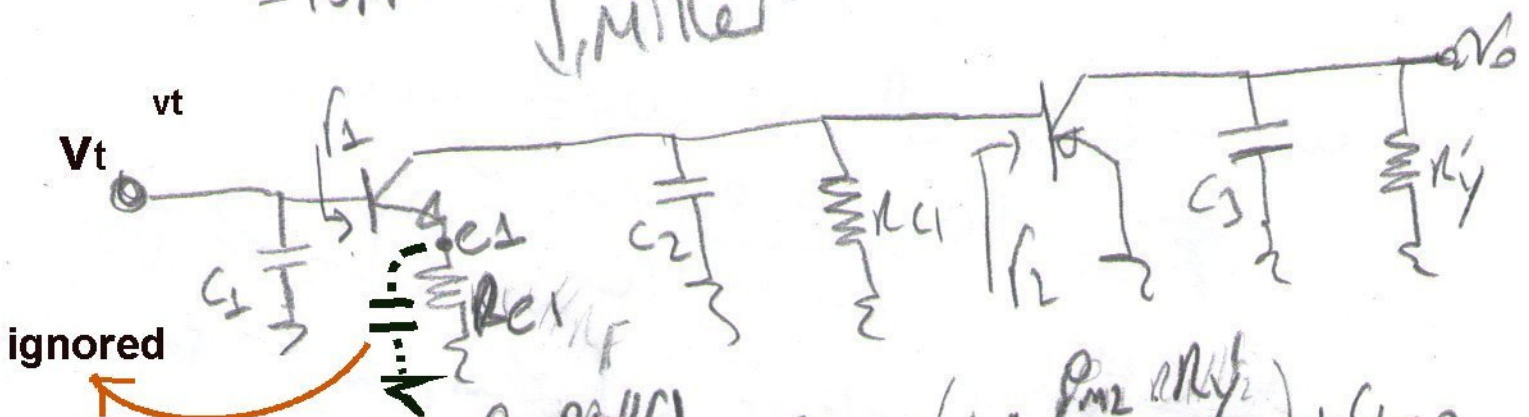

ignored

$$C_2 = C_{cb1} \left(1 + \frac{\rho_{m1} R_{eff1}}{1 + \rho_{m1} R_{eff1}} \right) + C_{cb2} \left(1 + \frac{\rho_{m2} R_{eff2}}{1 + \rho_{m2} R_{eff2}} \right) + C_{be2}$$

$$C_3 = C_{cb2} \left(1 + \frac{1}{\rho_{m2} R_{eff2}} \right) + 0.5nF$$

$$r_2 = \beta F r_{e2} = 440 \Omega \rightarrow R_{c1} // r_2 \approx 380 \Omega$$

$$R_{e1} = R_{e1} // R_F = 4,5 k$$

$$C_2 = 28,4 nF \quad C_3 \approx 0,57 nF //$$

(C1 is not effective for v_o/v_i)

$$R_2 = R_{c1} // r_2 \quad R_3 = R_4 \rightarrow \omega_{H2}$$

$$\omega_{H1} \leftarrow \omega_{H1} = \frac{1}{R_2 C_2} = 92,7 k$$

$$\omega_{H2} = \frac{1}{R_3 C_3} = 1,06 M$$

$$A_o \leftarrow K_o = - \frac{g_{m1} R_{c1} // r_2}{1 + g_{m1} R_{e1}} \times -g_{m2} R_4 \approx 32$$

(v_o/v_t)

$$A = K_o \cdot \frac{\omega_{H1}}{s + \omega_{H1}} \cdot \frac{\omega_{H2}}{s + \omega_{H2}} \quad B = -\frac{1}{10}$$

(v_o/v_i)

$$A_F(s) \approx \frac{32 \times 92,7 k \times 1,06 M}{s^2 + 1,15 M s + 4,12 \cdot 10^{11}}$$

$$\omega_o^2 = 4,12 \cdot 10^{11} \rightarrow \omega_o = 642 k$$

$$\xi = \frac{1,06 M + 92,7 k}{2 \times 642 k} \approx 0,9 \geq \frac{1}{\sqrt{2}}$$

There is no peak on the gain function v_o/v_i

Alternative investigation

$$1 - \beta_o A_o \leq \frac{(f_{c1} + f_{c2})^2}{2 f_{c1} f_{c2}} \rightarrow 4,2 \leq 6,73$$

no peak