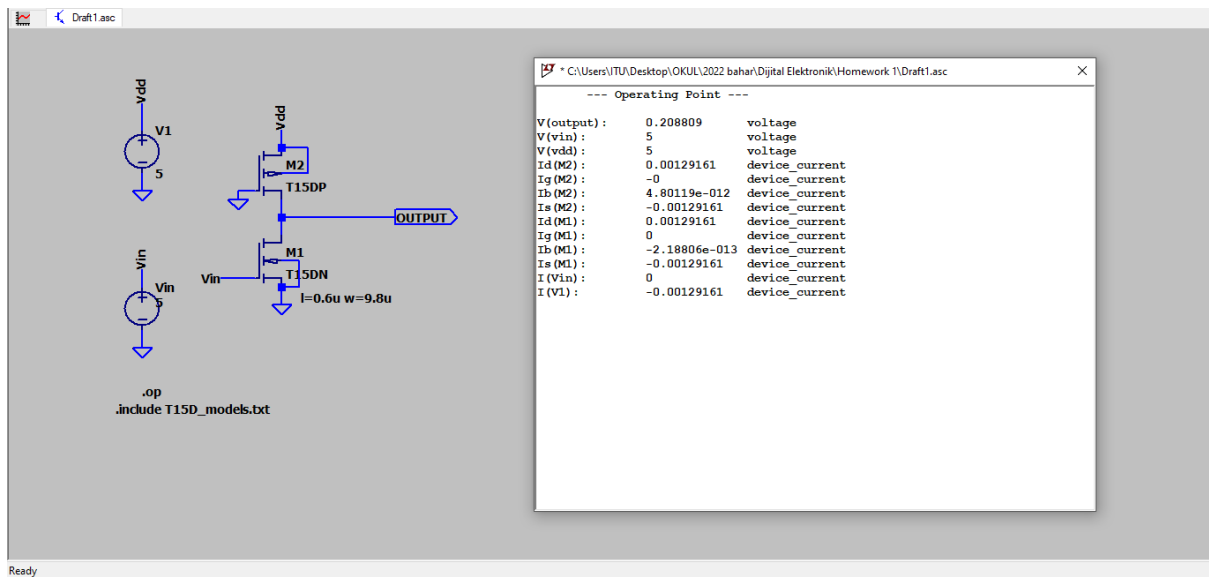



2-)

a-) Value of W_n 9.8u




b-)

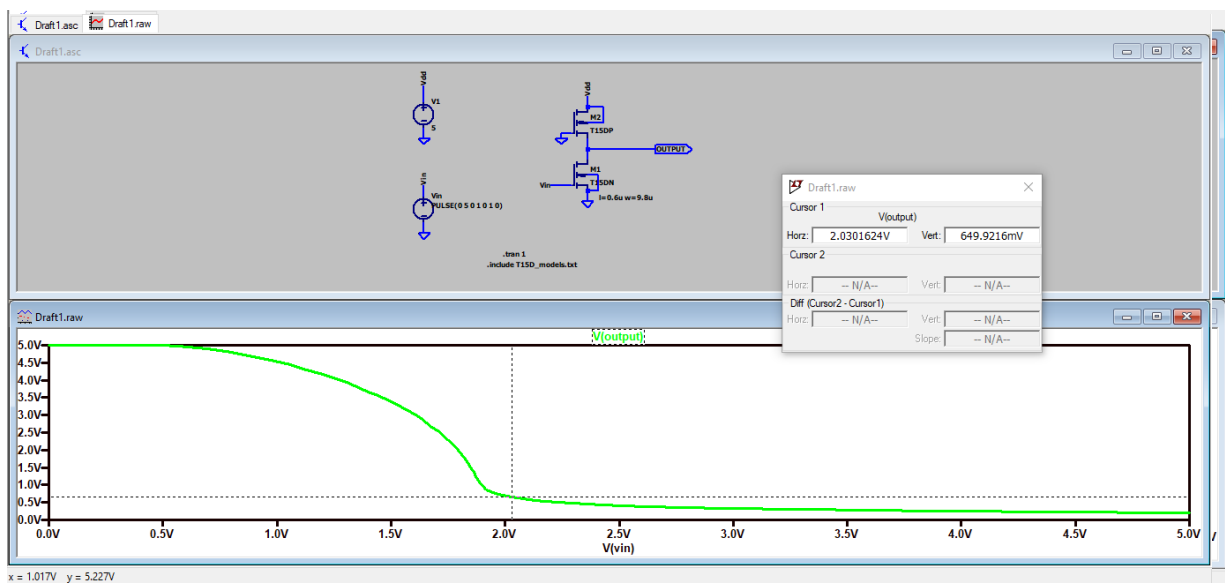
Slope of the curve is -1 when V_{in} equals 765.66mV. So NML is approximately 0.766 V



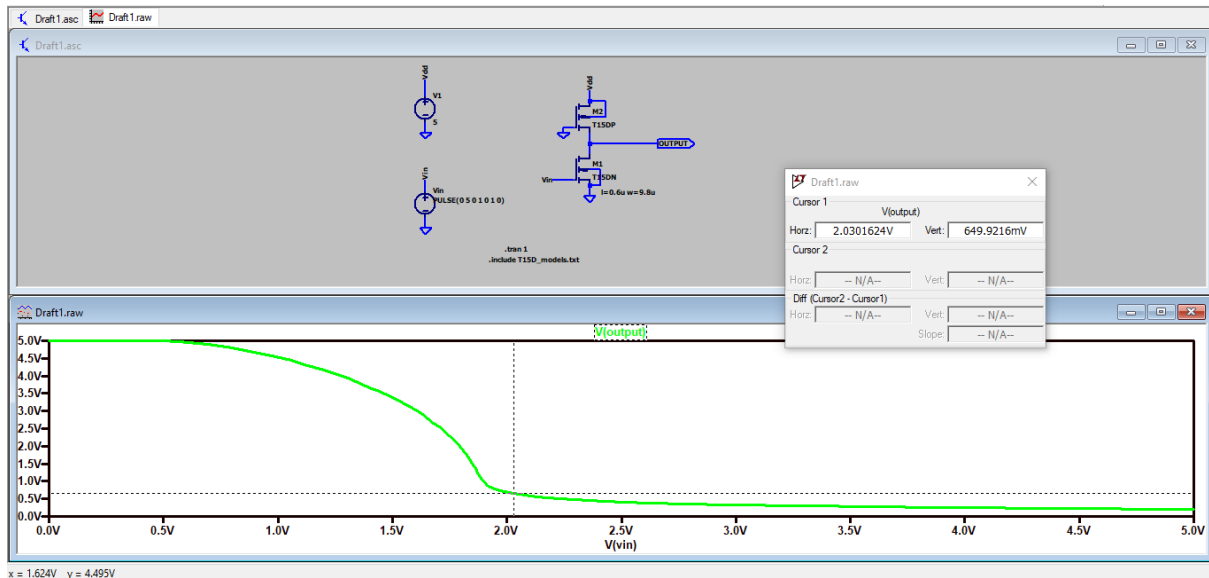Slope of the graph is -1 when V_{in} equals to 2.03 V. So NMH is approximately 2.97 V. ($V_{dd} - 2.03$)




Switch voltage is approximately 1.81 V.

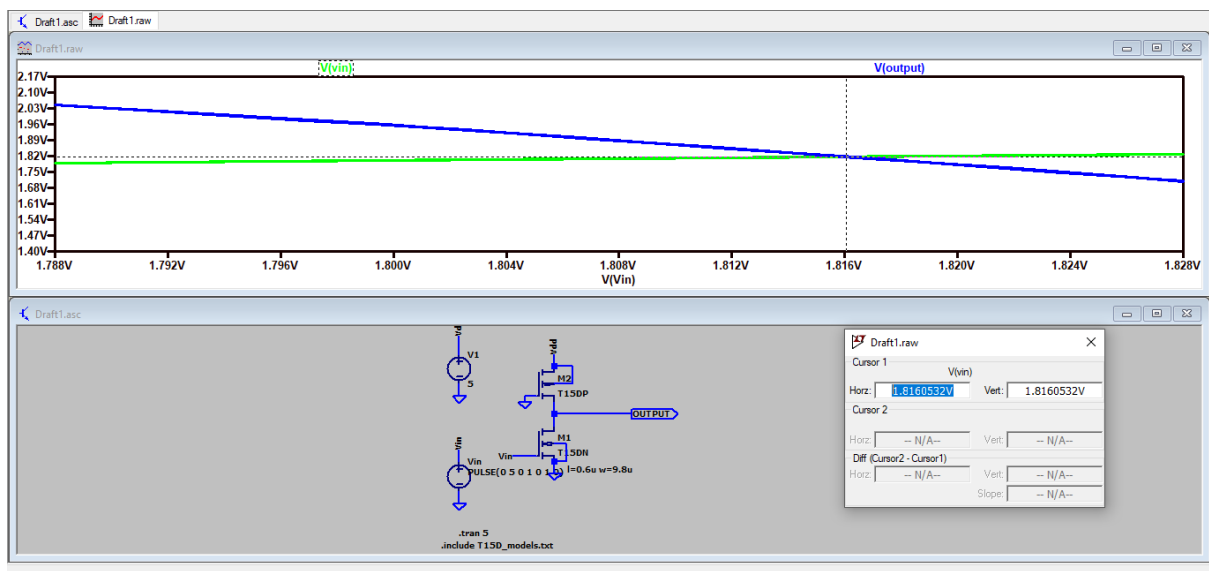

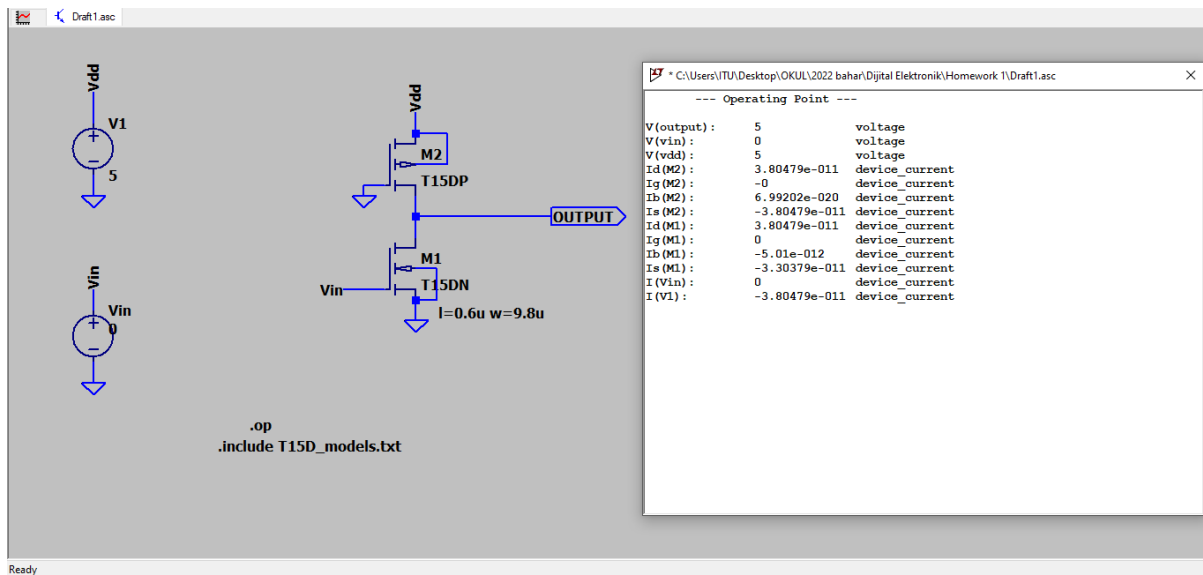
c) Static power consumption for $V_{in}=0 \rightarrow P=V \cdot I$

$$5 \cdot 3.8 \cdot 10^{-11} = 19 \cdot 10^{-11} \text{ W.}$$




Static power consumption for $V_{in}=5 \rightarrow P=V \cdot I$
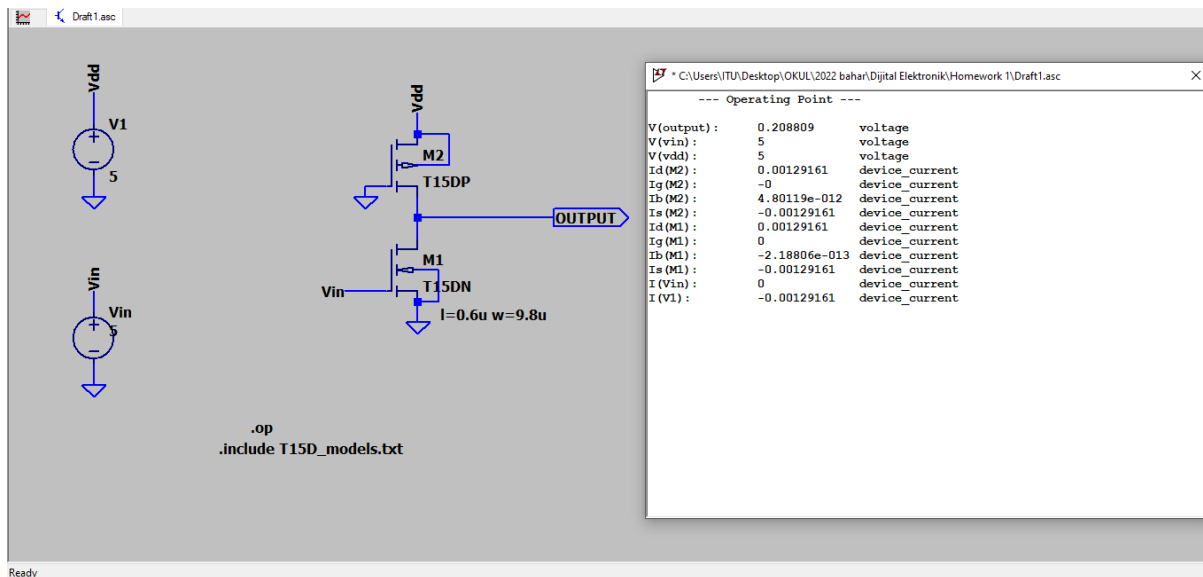
$$5 \cdot 12.9 \cdot 10^{-3} = 64.5 \cdot 10^{-3} \text{ W.}$$



d) $t_{PLH}=9.8 \text{ ns}$

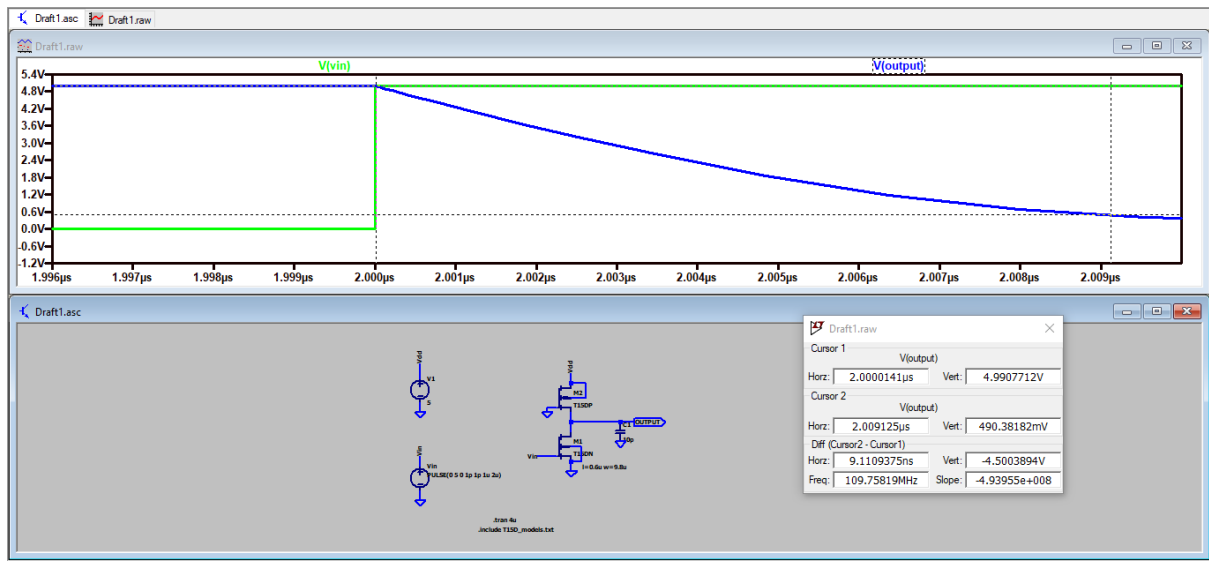

e-)

i) calculation = $9.61 \mu\text{m}$ simulation = $10 \mu\text{m}$

ii) calculation = 1.955 V simulation = 1.816 V

iii) calculation $\rightarrow 0 \text{ W}$ for $V_{in} = 0$, 10.5 mW for $V_{in} = 5\text{V}$ and 5.25 mW Avg Power

iv) $\rightarrow 0$ for $V_{in} = 0$, 6.45 mW for $V_{in}=5\text{V}$ and 3.225 mW Avg Power

iv) calculation = 8.44ns simulation 9.11 ns