

Transmission Line Matching Techniques

Smith Chart and Impedance Matching:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma_L| e^{j\theta_L} = \Gamma_r + j\Gamma_i$$

Since $|\Gamma_L| \leq 1$, the value of Γ_L must lie on or within the unit circle.

Define the normalized impedance as,

$$z = \frac{Z}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{R + jX}{Z_0} = r + jx$$

then $\Gamma = \frac{z-1}{z+1} = \Gamma_r + j\Gamma_i$ and thus,



$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad \text{and} \quad x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


we can rearrange the above eq.s as;

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

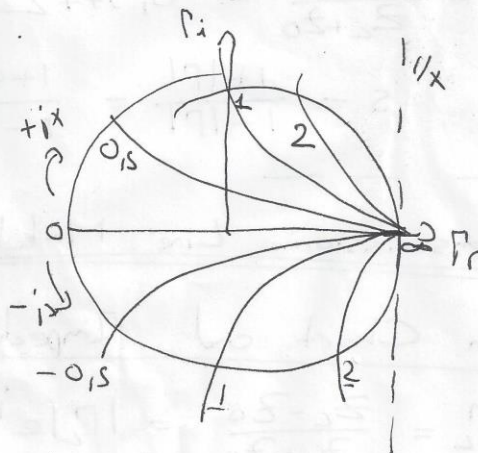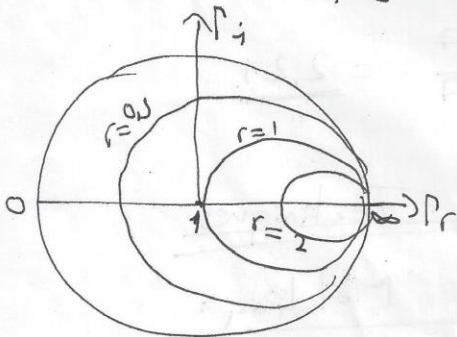These eq.s represents a family of circles, for the first eq., radius is $1/(1+r)$ and center is $\Gamma_r = r/(1+r)$, $\Gamma_i = 0$, for the second eq., $\Gamma_r = 1$ and $\Gamma_i = 1/x$ are the center coordinates and the radius is $1/x$.



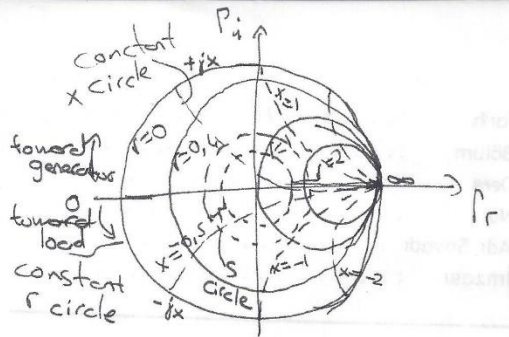

The Smith chart also contains relative distance scales (in wavelength) along the circumference and a phase scale specifying the angle of the reflection coefficient.

When you locate a normalized z impedance on the chart, you can then find the normalized impedance of any other location along the line by using the relation:

$$z = \frac{1 + \Gamma e^{-2\gamma d}}{1 - \Gamma e^{-2\gamma d}} \quad \text{where } \Gamma e^{-2\gamma d} = |\Gamma| e^{-2\alpha d} e^{j(\theta - 2\beta d)}$$

You can also use the Smith chart to determine normalized admittance. Since $Y_0 = 1/Z_0 = G + jB_0$ and $Y = 1/Z = G + jB$, the normalized admittance is

$$y = \frac{Y}{Y_0} = \frac{Z_0}{Z} = \frac{1}{z} = g + jb$$

Note that Γ is the radial coordinate and that the circles concentric with the center of the unit circle are circles of constant reflection coefficient. Since SWR is determined only by the magnitude of the Γ , these circles are also contours of constant standing-wave ratio. Since the SWR is never less than one, the scale for the SWR varies from 1 to ∞ on the real axis. Note also that the distances are given in wavelengths toward both the generator and the load, so that we can easily determine in which direction to advance as position on the line changes.

We can summarize the Smith chart properties as follows:

1. The constant r and x loci form two orthogonal circles families on the chart.
2. The constant r and x circles all pass through the point $(r=1, x=0)$.
3. The upper half of the diagram represents $+jx$
4. The lower " " " " " " $-jx$
5. For admittance, r circles become g circles, and x circles become b circles.
6. The distance around the Smith chart once is $\lambda/2$.
7. At a point of $z_{min} = 1/s$, there is a V_{min} on the line.
8. " " " " $z_{max} = s$, " " " V_{max} " " "
9. The horizontal radius to the right of the chart's center corresponds to $V_{max}, I_{max}, z_{max}$ and s
10. " " " " " left " " " " " $V_{min}, I_{min}, z_{min}$ and $1/s$
11. The corresponding quantities in the admittance chart are 180° out of phase with those in the impedance chart.
12. The normalized impedance (or admittance) is repeated for every one-half wavelength of distance.

You can use the standing-wave pattern (or SWR) on the chart to calculate $|P|$, reflected and transmitted power and the load impedance. Typical values are shown at the bottom of the complete Smith chart.

The Complete Smith Chart

Black Magic Design


Dalgaboyu
cetvelleri

Sanal yay
değerleri

Yansıma
katsayısı açısı


Reel çember
değerleri

Kaynak
yönü

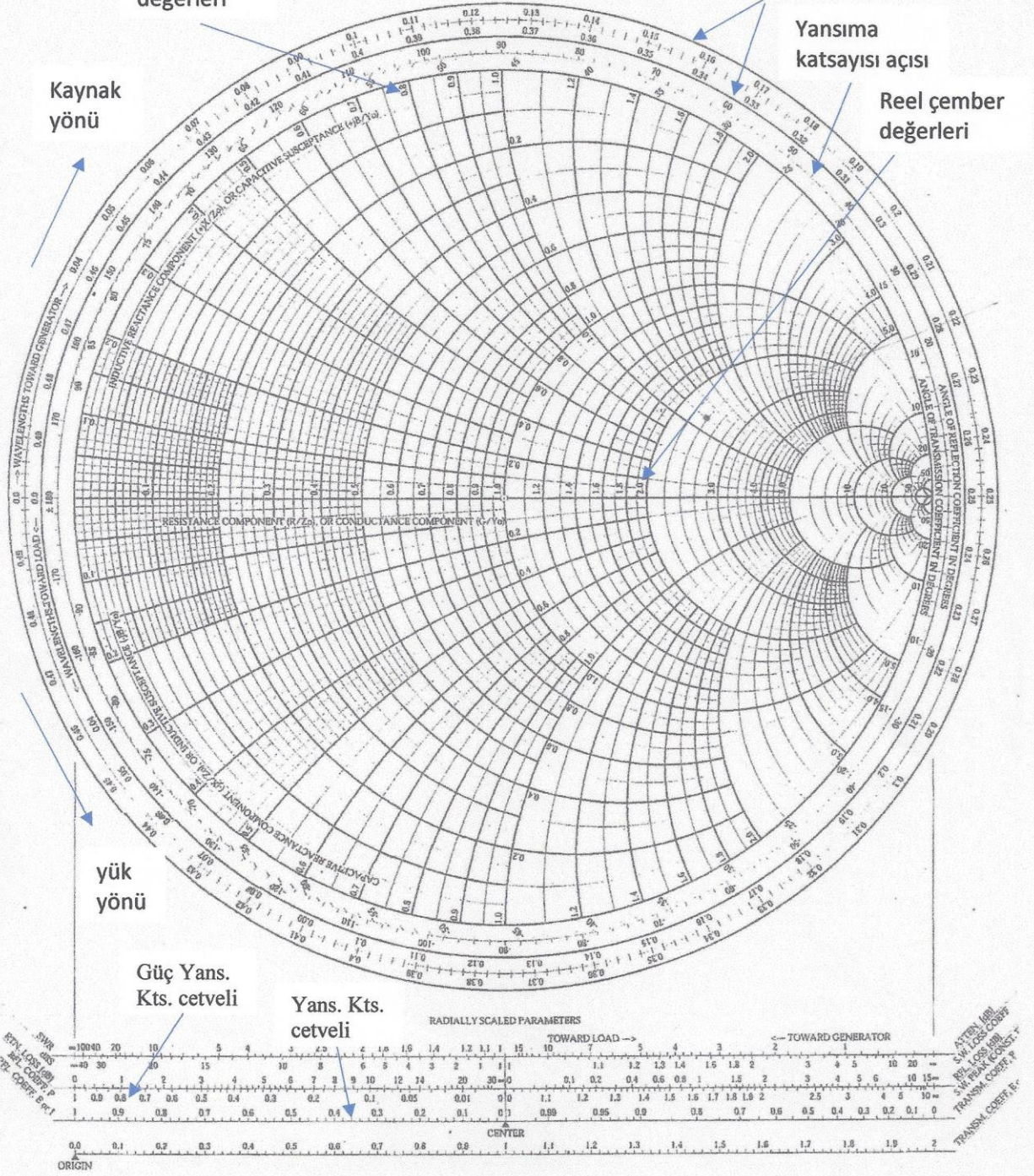


① Örnek: ✓

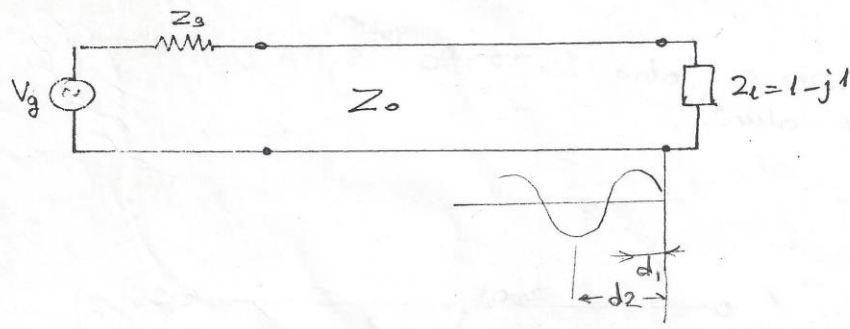Normalize yük emp. $z_L = 1 - j1$, çalışma dalga boyu $\lambda = 5 \text{ cm}$
 1) a) V_{\max} ^{ilk} ⁱⁿ ^{itt} ^{ne} ^{kasar} ^{olusacağını} ^{bul} ^{yükten} ^{uzaktaki} ^{ilk} ^{değerler} b) V_{\min} c) $s = ?$



a) z_L abakta işaretlenir.

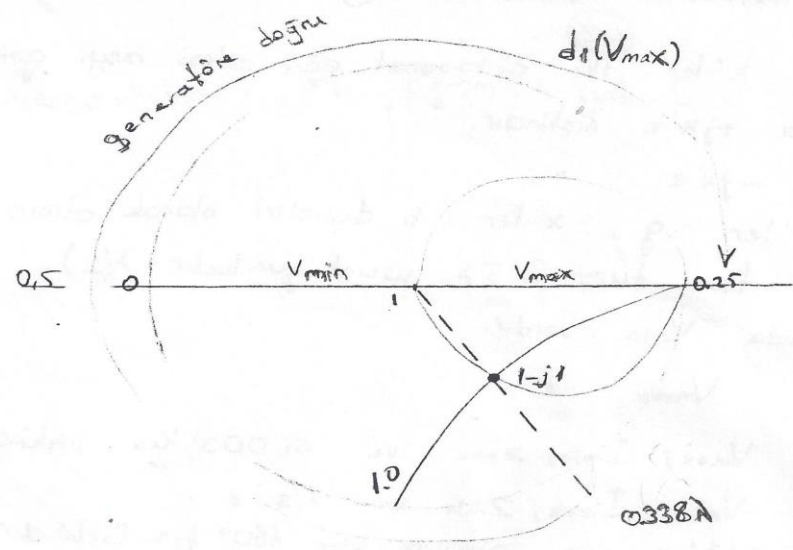

2. merkez ile yük birleştirilirse 0.338λ okunur.
3. 0.338λ 'den kaynağa doğru ger. max. a kadar dönülür.

$$d_1(V_{\max}) = (0.25 + 0.162)\lambda = 2.06 \text{ cm.}$$

- b) 0.338λ 'den ger. min. a kadar dönülür.

$$d_2(V_{\min}) = (0.5 - 0.338)\lambda = 0.81 \text{ cm.}$$



- c) DDO 'yu bulmak için merkezi (1.0) olan ve yükten geçen daire çizilir. DDO dairesi ile reel eksenin sağ tarafını kesen noktadan $DDO = s = 2.6$ okunur.

Örnek:

$Z_0 = 50 \Omega$ $Z_L = 100 \Omega$ olan bir hatta ^{yükten} 3.15λ ve 4.75λ uzaklıkta emp. ne olur?

$$Z_L = \frac{Z_L}{Z_0} = 2$$

isaretleştir. DDO
göresi çizilir

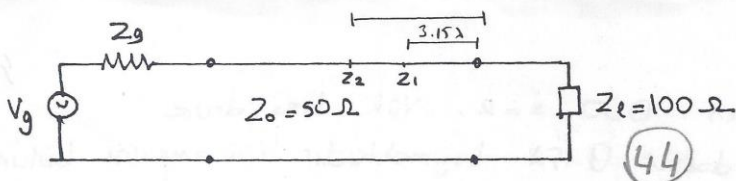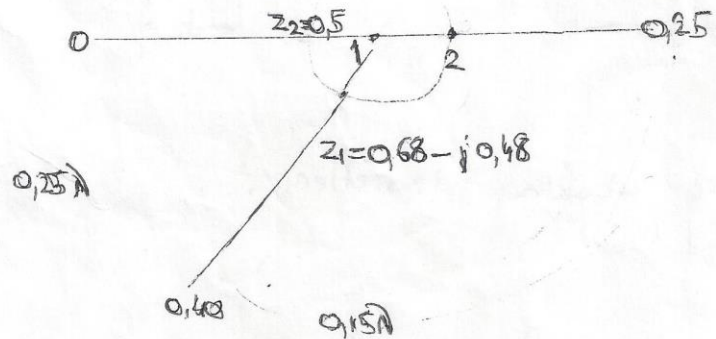

3.15λ ve 4.75λ sırasıyla 0.15λ ve 0.25λ 'ya karşı gelir. 0.15λ koy. dağılım dönülürse 0.40 'a gelir.

$$Z_1 = 0.68 - j0.48j$$

0.25λ ise 0.50 'ye karşı gelir.

$$Z_2 = 0.5 \text{ (min direnç)}$$

$$Z_1 = 50 \cdot 2 = 34 - j24 \Omega$$

$$Z_2 = 50 \cdot 0.5 = 25 \Omega$$


Geyrek dalgı transformatör bağlantısından

$$Z_0 = \sqrt{Z_2 \cdot Z_1} \rightarrow Z_2 = \frac{Z_0^2}{Z_1} = \frac{2500}{100} = 25 \Omega$$


Örnek:

$$Z_0 = 100 \Omega \quad Y_L = 0.0025 - j0.0025 \text{ S}$$

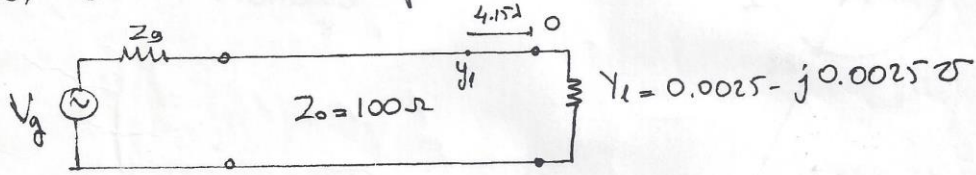- a) Yükten 4.15λ uzakta DDO $s=?$?
 b) Bu noktadaki emp. nedir?



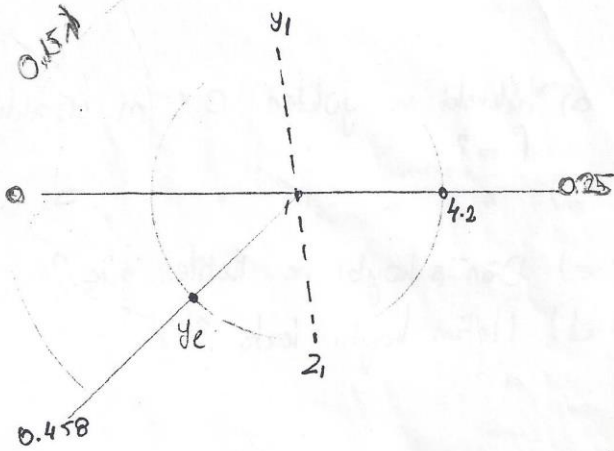a) $y_1 = \frac{Y_L}{Y_0} = Y_L Z_0 = 0.25 - j0.25$
 $\rightarrow 10.108$



Abakta işaretlenir.

DDO dairesi işaretlenir.

$s = 4.2$ okunur.

- b) 0.458 'deki y_e 'den 4.15λ kay.a doğru ilerlenir.
 0.108 'de durulur.

$$y_1 = 0.38 + j0.74 \text{ bulunur.}$$

180° dönmüş hali z_1 'dir

$$Z_1 = 0.55 - j1.1$$

$$Z_1 = Z_0 \cdot Z_1 = 550 - j110 \Omega$$