

Lecture 8

Parallel Communication

1


Topics

- Input/Output Interface
- I/O Transfer Synchronization
- Parallel Communication

2

Input/Output Interfaces

 - **Peripheral Devices** are I/O devices that exchange data with a CPU.
 - Examples : Switch, push-button, light-emitting diode (LED), monitor, LCD screen, printer, mouse, keyboard, disk drive, sensor, motor, audio, etc.
- **Interface Chips** are used to resolve the differences between CPU and I/O devices.



3

I/O Interfacing

- An interface chip resolves the differences between the CPU and a peripheral device.
- Data codes and formats in peripherals may be different.
- A synchronization mechanism is needed.
Data transfer rate of peripherals are usually slower than CPU.
- Communication between CPU and Interface Chip:
Always parallel.
- Communication between Interface Chip and I/O Device:
Can be either parallel or serial.

4

I/O Interfacing Methods

■ Isolated I/O Method

- Separate memory and I/O address spaces are used.
- There are distinct input and output instructions.
Example assembly language instructions : **IN , OUT**

■ Memory Mapped I/O Method


- Memory and I/O addresses share common address space.
- There are no specific input/output instructions.
- Usual memory load/store instructions are used.
Example assembly language instructions : **LDA , STA**
- Flexibility in handling I/O operations.

5

Isolated I/O Interfacing

Separate Buses are used for Input-Output Interfaces and Memory.

 - Memory Bus : Address & Data & Control
- Input-Output Bus : Address & Data & Control




6

Isolated I/O Interfacing

MEM / $\overline{\text{IO}}$ control signal is used as Memory chip selection and Input-Output Interface chip selection.

 
- MEM / $\text{IO}' = 1$ means Memory chip is selected
- MEM / $\text{IO}' = 0$ means Input-Output chip is selected



7

Memory Mapped I/O Interfacing

 
A Common Bus is used for I/O Interfaces and Memory.



8

Example: Memory Mapped I/O Interfacing

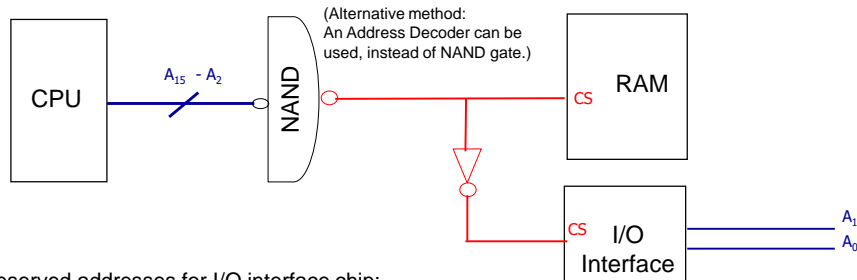- Example: 4 memory addresses are reserved (dedicated) for Input-Output register addresses.
- Suppose the memory addresses from \$0000 to \$0003 are reserved for I/O registers.
- The NAND gate can be used on address lines $A_{15} - A_2$ for **chip selections (RAM or I/O)**.
- For I/O register selections within the I/O interface chip, A_0 and A_1 lines can be used.



Reserved addresses for I/O interface chip:

Address (Hex)	A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	A_9	A_8	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
\$0000	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
\$0001	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
\$0002	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
\$0003	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1

Address Map	Used by which chip
\$0000 - \$0003	I/O
\$0004 - \$FFFF	RAM

9


Topics

- Input/Output Interface
- I/O Transfer Synchronization
- Parallel Communication

10

I/O Transfer Synchronization

 - The tasks of the interface chip are :
 - Synchronizing data transfer between CPU and Interface chip (Control signals).
 - Also between Interface chip and I/O device (Handshaking signals).



11

CPU and I/O Interfaces

- **Programmed I/O (Polling method)**
 - CPU checks device status in a loop
 - CPU waits for I/O module to complete operation
 - Wastes CPU time
- **Interrupt Driven I/O**
 - Overcomes CPU unnecessary waiting
 - No repeated CPU checking of device
 - I/O module interrupts when ready
- **Direct Memory Access (DMA)**
 - Requires additional hardware module on bus
 - DMA controller takes over from CPU, for I/O operations

12

Programmed I/O (Polling method)

- **Input Operations :**

Microprocessor checks a status bit of the interface chip, to find out whether the interface **has received** new data from input device.

- **Output Operations :**

Microprocessor checks a status bit of the interface chip, to find out whether it **can send** new data to interface chip.

13

Interrupt Driven I/O

- **Input Operations :**

Interface chip interrupts the microprocessor, whenever it **has received** new data from input device.

- **Output Operations :**

Interface chip interrupts the microprocessor, whenever it **can accept** new data from microprocessor.

14


Topics

- Input/Output Interface
- I/O Transfer Synchronization
- Parallel Communication

15

Parallel Communication

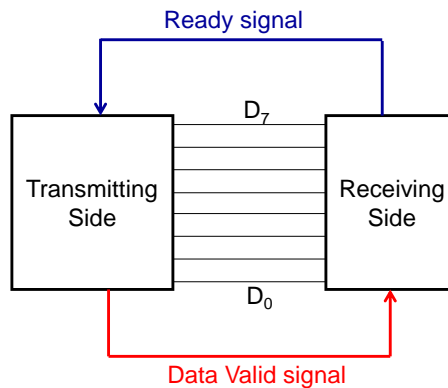
- In parallel communication, all bits are transferred at the same time.
- Each bit is transferred along its own line.
- In addition to eight parallel data lines, other lines are used to read status information and send control signals.



16

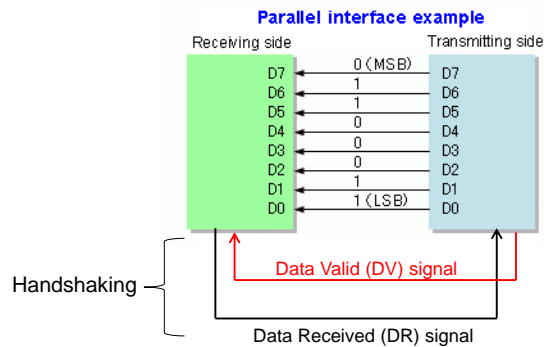Example: Synchronization of two parallel connected computers


- **Transmitter** and **receiver** interfaces use handshaking protocol.
- **Transmitter** initiates 2-wire handshaking
 - DV low indicates new data is available.
 - DR low indicates that receiver has read the data.



17

Basic Parallel Input Interface

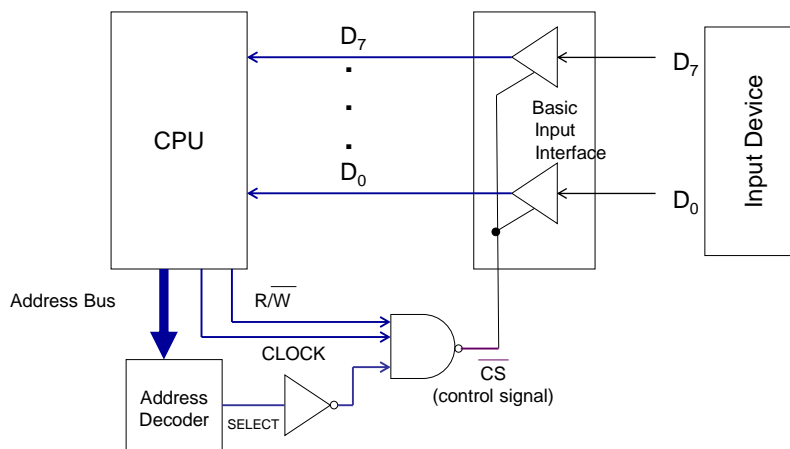- **Tri-state buffers** are used inside the interface chip. (Example chip: 74LS244)
- Output pins of **interface** are connected to **Data Bus** of CPU (as input of CPU).
- Input pins of **interface** are connected to an input device.



18

Input Interface Timing Diagram

- 1) Address placed on address bus at the falling edge of clock



- 2) Address decoded, in order to form the Select signal




- 3) NAND {CLK, $\overline{\text{SELECT}}$, $\overline{\text{R/W}}$ } applied, in order to form CS signal



19

Basic Parallel Output Interface

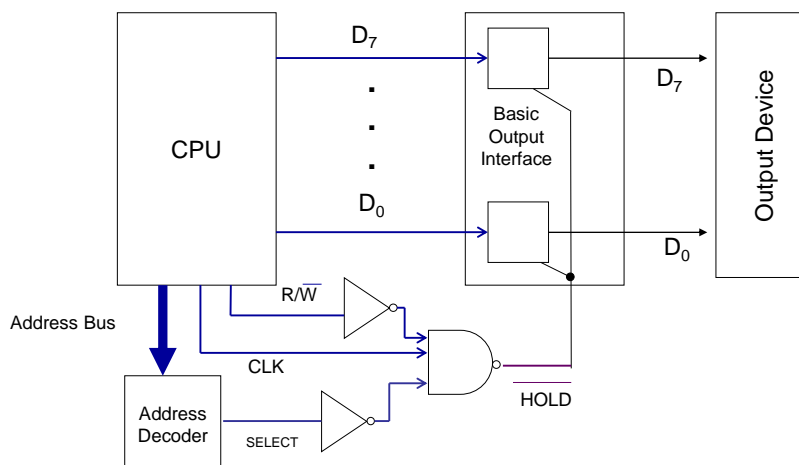- **D Latches** are used in interface (Example chip: 74LS374 D Latch).
- Inputs of **interface** are connected to the **Data Bus** of CPU.
- Outputs of **interface** are connected to an output device.



20

Output Interface Timing Diagram

- 1) Address placed on address bus at the falling edge of clock



- 2) Data is placed on the data bus



- 3) Address decoded, in order to form the Select signal
- 4) NAND {CLK, SELECT, R/W} applied, in order to form HOLD




21

Peripheral Interface Adapter (PIA)

- PIA is a **parallel interface chip** that can be programmed to handle both input or output data.
- PIA contains the following 3 registers:
 - **Port Register(s):** Connects the PIA to peripheral devices. Each pin (bit) of the port can be conditioned (configured) as *transmit (TX)* or *receive (RX)*
 - **Data Direction Register:** Conditions the port pins as TX or RX.
 - 1 : Pin is Transmitter
 - 0 : Pin is Receiver
 - **Status / Control Register:**
 - Status bits: Indicates the status of the handshaking bits
 - Control bits: Used to control handshaking signals and interrupt conditions


22

PIA and CPU Connections

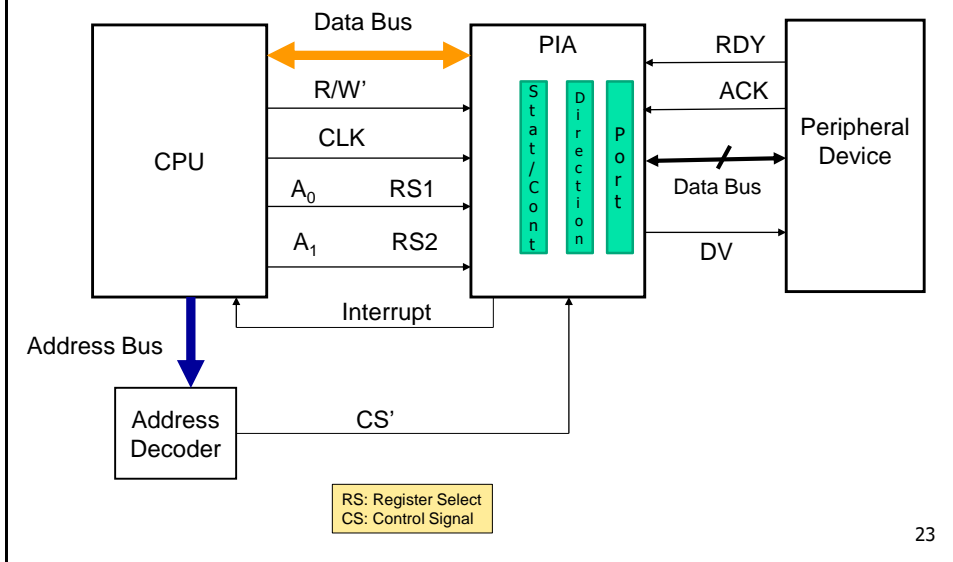

23


PIA Registers

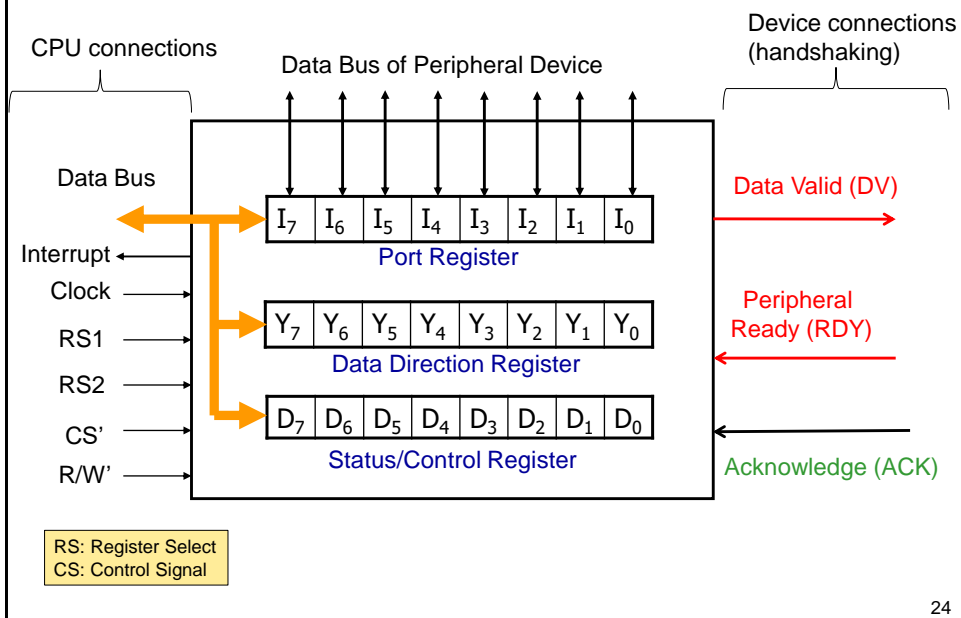

24

EDU-PIA port connections to I/O peripherals

 - The Educational PIA chip has two port registers connected to two peripheral devices permanently.
 - Port A is used for inputs from DIP switches (ON / OFF).
 - Port B is used for outputs to LEDs (Light Emitted Diodes).



25

Port names and addresses in EDU-PIA

- EDU-PIA contains 6 registers.

Register Type	Predefined Symbolic Name	Predefined Address
Port Registers	İSKELE.A (PORT.A)	\$8080
	İSKELE.B (PORT.B)	\$8083
Data Direction Registers	YÖNLEN.A (DIRECT.A)	\$8081
	YÖNLEN.B (DIRECT.B)	\$8084
Status/Control Registers	DURDEN.A (STATCON.A)	\$8082
	DURDEN.B (STATCON.B)	\$8085

26

Example1: Input /Output with PIA

- The following program runs in an endless loop.
 - Reads **switches** from PORT.A port into accumulator A.
 - Writes content of accumulator A into PORT.B port (**LEDs**).

Example : User changes some switches to ON, then the respective LEDs are turned ON.



```


START
* Conditioning of PIA ports
  STA $00, <YÖNLEN.A> ; All bits of Port-A are input
  STA $FF, <YÖNLEN.B> ; All bits of Port-B are output

LOOP
  LDA  A, <İSKELE.A>   ; Read from Port-A
  STA  A, <İSKELE.B>   ; Write to Port-B
  BRA  LOOP            ; Endless loop
    
```

27

 Example2: Walking LED

- The following program displays a rotating LED from **right-to-left**.



```

Main
program
START  STA $FF, YÖNLEN.B ;Port-B conditioned as output
      LDA A, %00000001 ;Rightmost bit is 1 initially (Rightmost LED)

DEVAM  STA A, İSKELE.B   ;Display the LEDs
      BSR WAIT           ;Call subroutine WAIT

      MOV B, A           ;Copy A to B
      LSL B              ;Shift Left B, so leftmost bit goes to Carry flag
      ROL A              ;Rotate left A, so Carry flag goes to rightmost bit
      BRA DEVAM          ; Endless loop
    
```

```

Wait
Subroutine
WAIT  LDA SK, 30000 ;Wait loop limit
AZALT DEC SK        ;Decrement loop counter
      BNE AZALT     ;If not equal to zero, goto loop
      RTS           ;Return from subroutine
    
```

28

Alternative1: Using STA and BSR instructions 8 times

```
START    STA $FF, YÖNLEN.B

DEVAM
  STA %00000001, İSKELE.B
  BSR WAIT

  STA %00000010, İSKELE.B
  BSR WAIT

  STA %00000100, İSKELE.B
  BSR WAIT

  STA %00001000, İSKELE.B
  BSR WAIT

  STA %00010000, İSKELE.B
  BSR WAIT

  STA %00100000, İSKELE.B
  BSR WAIT

  STA %01000000, İSKELE.B
  BSR WAIT

  STA %10000000, İSKELE.B
  BSR WAIT

  BRA DEVAM      ;Endless loop
```

29

Alternative2: Using an array and inner loop

```
ARRAY RMB 8
ORG ARRAY
DAT %00000001, %00000010, %00000100, %00001000, %00010000, %00100000, %01000000, %10000000

START
  STA $FF, YÖNLEN.B
  LDA CD, ARRAY      ;Get address of array

DEVAM
  LDA A, <CD>         ;Inner loop
                     ;Get data from array
  STAA, İSKELE.B      ;Write to LEDS
  BSR WAIT

  INC D               ;Increment inner loop counter
  CMP D, 8             ;Compare with limit
  BLT DEVAM           ;Goto inner loop

  BRA START           ;Goto endless loop
```


30

Example3 : Using 1 Button, 4 Switches, 4 LEDs

- PIA is connected to an 8-bit microprocessor with 16-line address bus.
 - Beginning address of PIA registers is \$A0A0.
 - **First four pins (0-3)** of PIA are connected to **4 switches**.
 - **Last four bits (4-7)** of PIA are connected to **4 LEDs**.
(Type of LEDs is common voltage, which lights when port pin is 0).
- Design a system that will illuminate the LEDs depending on the closed switches.
- The LEDs will illuminate after the user arranges the switches and then presses a **button**.
- As long as the button is kept pressed, the LEDs will continuously illuminate.
- Program should check the Status/Control register of PIA for button pressing.

31

Example 3 (continued)

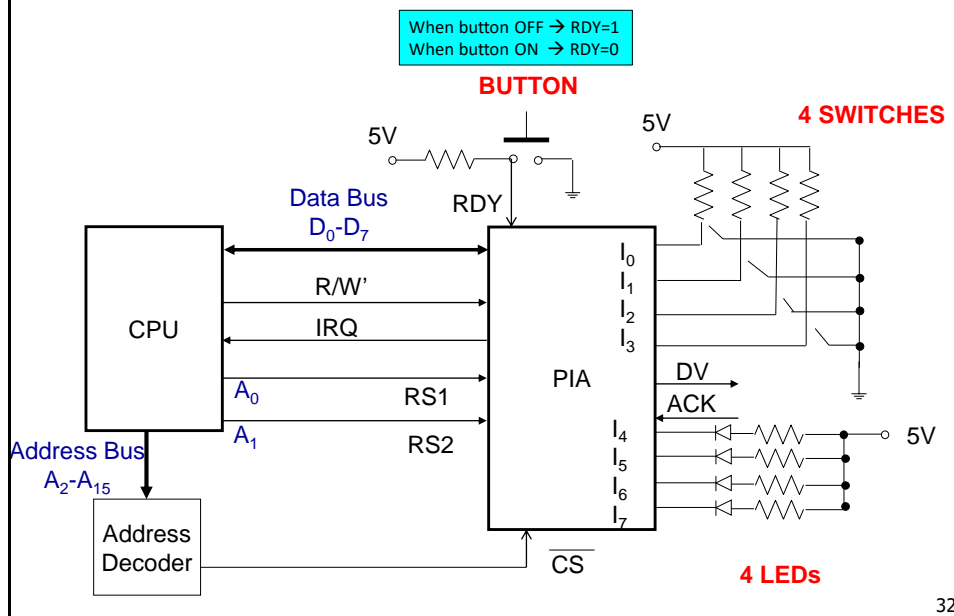

32


Example 3 (continued)

Note: Button hardware is not implemented in Mikbil.

```
PORT      EQU    $A0A0
DIRECT    EQU    $A0A1
STATCON   EQU    $A0A2
```

```
START  LDA    A, $F0 ;Half input, half output
      STA    A, DIRECT ;Conditioning
      LDA    A, $00
      STA    A, STATCON ;Reset
DEVAM  LDA    A, <STATCON>
      BIT    A, $80 ;Check RDY (button)
      BEQ    DEVAM ;Button not pressed
      LDA    A, <PORT> ;Read switches
```

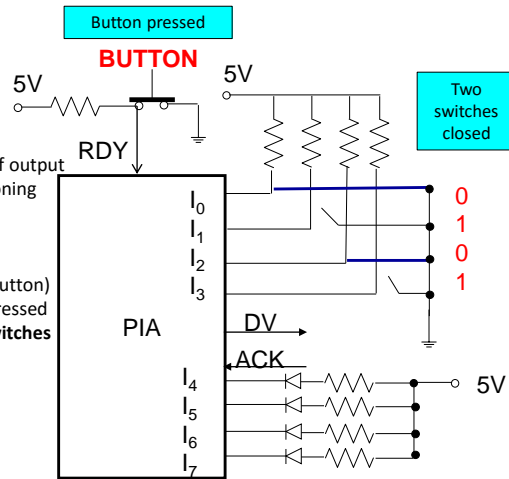PIA Status/Control Register :
\$80 = %1000 0000
 Leftmost (D7) status bit = 1
 indicates
 RDY = 1 (button OFF)




33

Example 3 (continued)

```
PORT      EQU    $A0A0
DIRECT    EQU    $A0A1
STATCON   EQU    $A0A2
```

```
START  LDA    A, $F0
      STA    A, DIRECT
      LDA    A, $00
      STA    A, STATCON
DEVAM  LDA    A, <STATCON>
      BIT    A, $80
      BEQ    DEVAM
      LDA    A, <PORT>
      LSL    A ;I3 goes to I4
```

1st Logical shift left

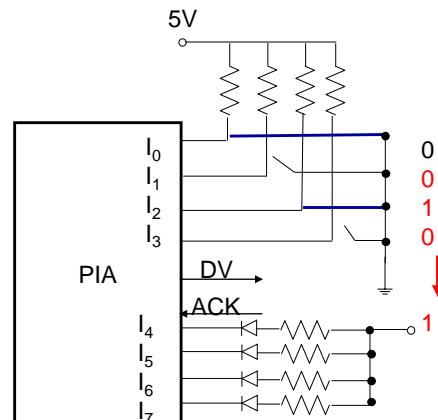


34

Example 3 (continued)

```
PORT      EQU    $A0A0
DIRECT    EQU    $A0A1
STATCON   EQU    $A0A2
```

```
START  LDA    A, $F0
        STA    A, DIRECT
        LDA    A, $00
        STA    A, STATCON
DEVAM   LDA    A, <STATCON>
        BIT    A, $80
        BEQ    DEVAM
        LDA    A, <PORT>
        LSL    A
        LSL    A
```

2nd Logical shift left

 


Example 3 (continued)

```
PORT      EQU    $A0A0
DIRECT    EQU    $A0A1
STATCON   EQU    $A0A2
```

```
START  LDA    A, $F0
        STA    A, DIRECT
        LDA    A, $00
        STA    A, STATCON
DEVAM   LDA    A, <STATCON>
        BIT    A, $80
        BEQ    DEVAM
        LDA    A, <PORT>
        LSL    A
        LSL    A
        LSL    A
```

3rd Logical shift left

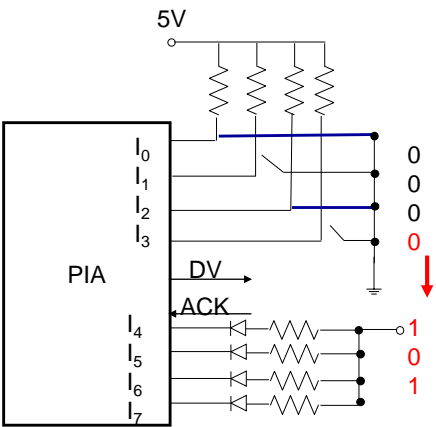

Example 3 (continued)

```

PORT      EQU    $A0A0
DIRECT    EQU    $A0A1
STATCON   EQU    $A0A2


```

```

START  LDA    A, $F0
       STA    A, DIRECT
       LDA    A, $00
       STA    A, STATCON
DEVAM  LDA    A, <STATCON>
       BIT    A, $80
       BEQ    DEVAM
       LDA    A, <PORT>
       LSL    A
       LSL    A
       LSL    A
       LSL    A

```

4th Logical shift left

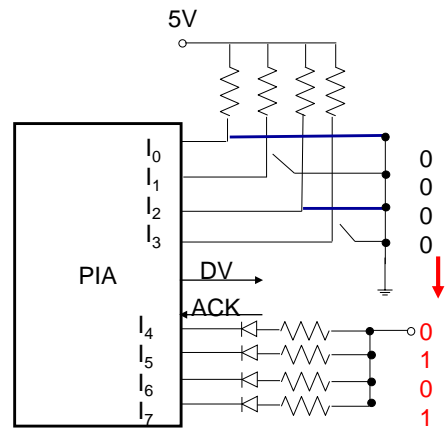

37

Example 3 (end)

```


PORT      EQU    $A0A0
DIRECT    EQU    $A0A1
STATCON   EQU    $A0A2

```

```

START  LDA    A, $F0
       STA    A, DIRECT
       LDA    A, $00
       STA    A, STATCON
DEVAM  LDA    A, <STATCON>
       BIT    A, $80
       BEQ    DEVAM
       LDA    A, <PORT>
       LSL    A
       LSL    A
       LSL    A
       LSL    A
       STA    A, <PORT>;Display LEDS
       BRA    DEVAM ;Goto loop

```

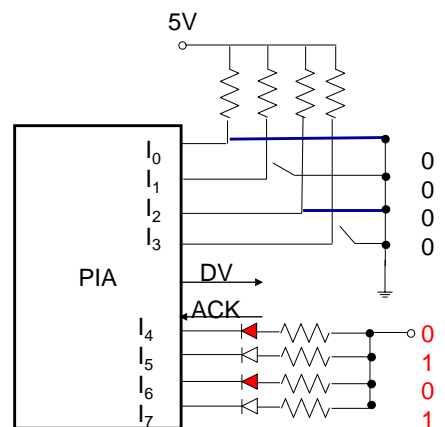

Two LEDS
illuminated

38