
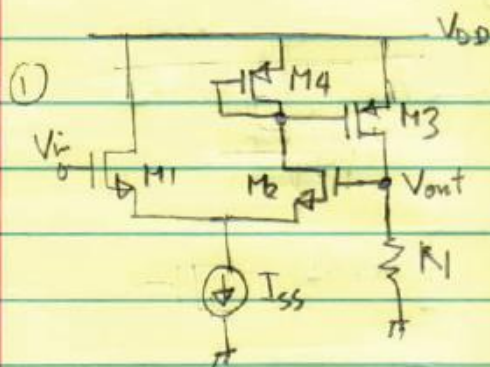



# EEB 335E HW #3 Solutions

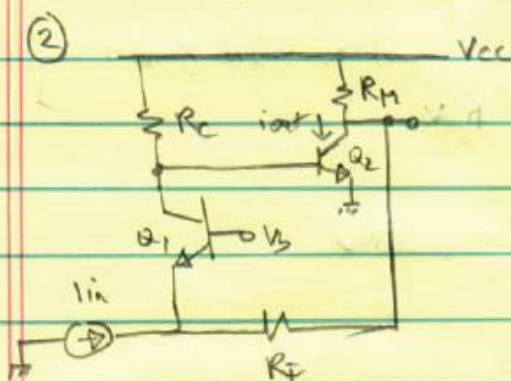

As  $V_{in} \uparrow$   $I_{s1} \uparrow$   $I_{s2} \downarrow$   
 $V_{g,M3} \downarrow$   $I_{d,M3} \downarrow$   $V_{out} \downarrow$   $I_{s2} \downarrow$   
 As can be seen, this is a positive feedback



With loading effects taken into account:

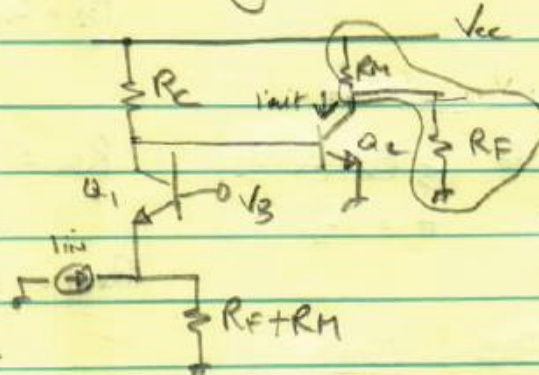

Since  $I_{out}$  is chosen, all these are considered external


current-current amplifier  
 shunt-series feedback

$$A_o = \frac{(R_F + R_L) R_C g_{m2}}{\frac{1}{g_{m1}} + (R_F + R_L)}$$

$$R_{in} = \frac{1}{g_{m1}} \parallel (R_L + R_F) \approx \frac{1}{g_{m1}}$$

$$A_o \approx g_{m2} R_C$$

$$R_{out} = R_M \parallel R_F$$

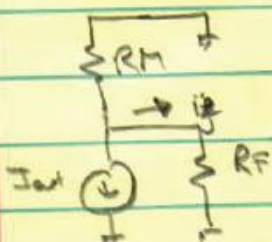

$$f = \frac{I_{out} R_L}{R_F + R_L} \Rightarrow \frac{I}{I_{out}} = \frac{R_L}{R_F + R_L} \approx \frac{R_L}{R_F} = K$$

Closed loop gain:  $\frac{A_o}{1 + K A_o}$



Closed loop  
 input resistance

$$R_{in} = \frac{R_{in}}{1 + K A_o}$$

Closed loop output resistance:  $R_{out} = R_{out} (1 + K A_o)$




(3)

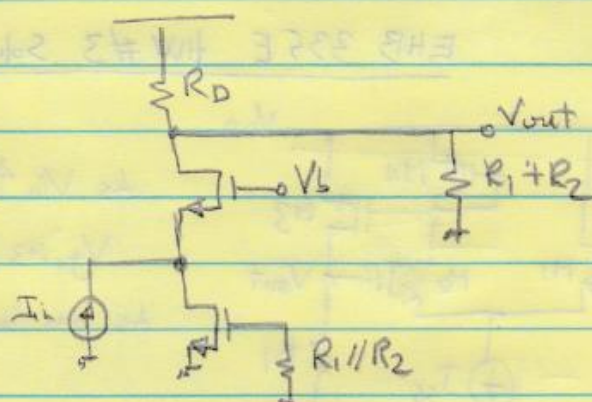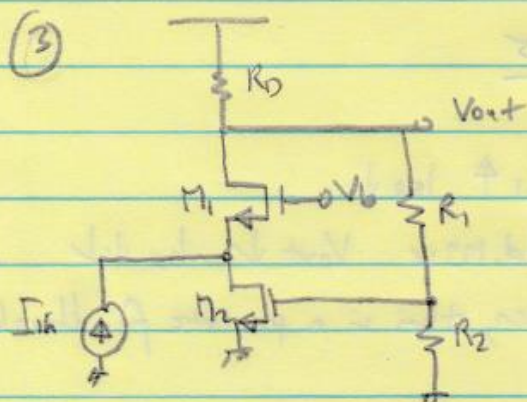

Current-voltage amplifier  
shunt-shunt feedback

$$R_o = \left( \frac{r_{o2}}{r_{o2} + R_V} \right) \left[ R_D \parallel (R_1 + R_2) \right]$$

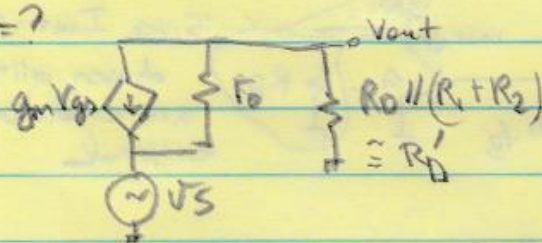 $R_V = ?$ 


$$R_{in} = r_{o2} \parallel R_V$$

$$R_{out} = R_D \parallel (R_1 + R_2) \parallel g_{m1} r_{o1} r_{o2}$$

$$g_m V_s + \frac{V_s - V_{out}}{r_o} = \frac{V_{out}}{R_D'}$$

$$V_s \left( g_m + \frac{1}{r_o} \right) = V_{out} \left( \frac{1}{R_D'} + \frac{1}{r_o} \right)$$

$$V_{out} = V_s \frac{\left( g_m + \frac{1}{r_o} \right)}{\frac{1}{R_D'} + \frac{1}{r_o}}$$

$$K = \frac{R_2}{R_1 + R_2} g_{m2}$$

$$CL R_o = \frac{R_o}{1 + K R_o}$$

$$CL R_{in} = \frac{R_{in}}{1 + K R_{in}}$$

$$CL R_{out} = \frac{R_{out}}{1 + K R_{out}}$$


$$i_s = g_m V_s + \frac{V_s + V_{out}}{r_o}$$

$$i_s = V_s \left[ g_m + \frac{1}{r_o} \frac{\frac{1}{R_D'} - g_m}{\frac{1}{R_D'} + \frac{1}{r_o}} \right]$$


$$i_s = V_s \left[ g_m \left( \frac{r_o}{R_D'} + 1 \right) + \frac{1}{R_D'} - g_m \right] / \left( 1 + \frac{r_o}{R_D'} \right)$$

$$\frac{V_s}{i_s} = R_V = \frac{R_D' \left( 1 + \frac{r_o}{R_D'} \right)}{(g_m r_o + 1)}$$

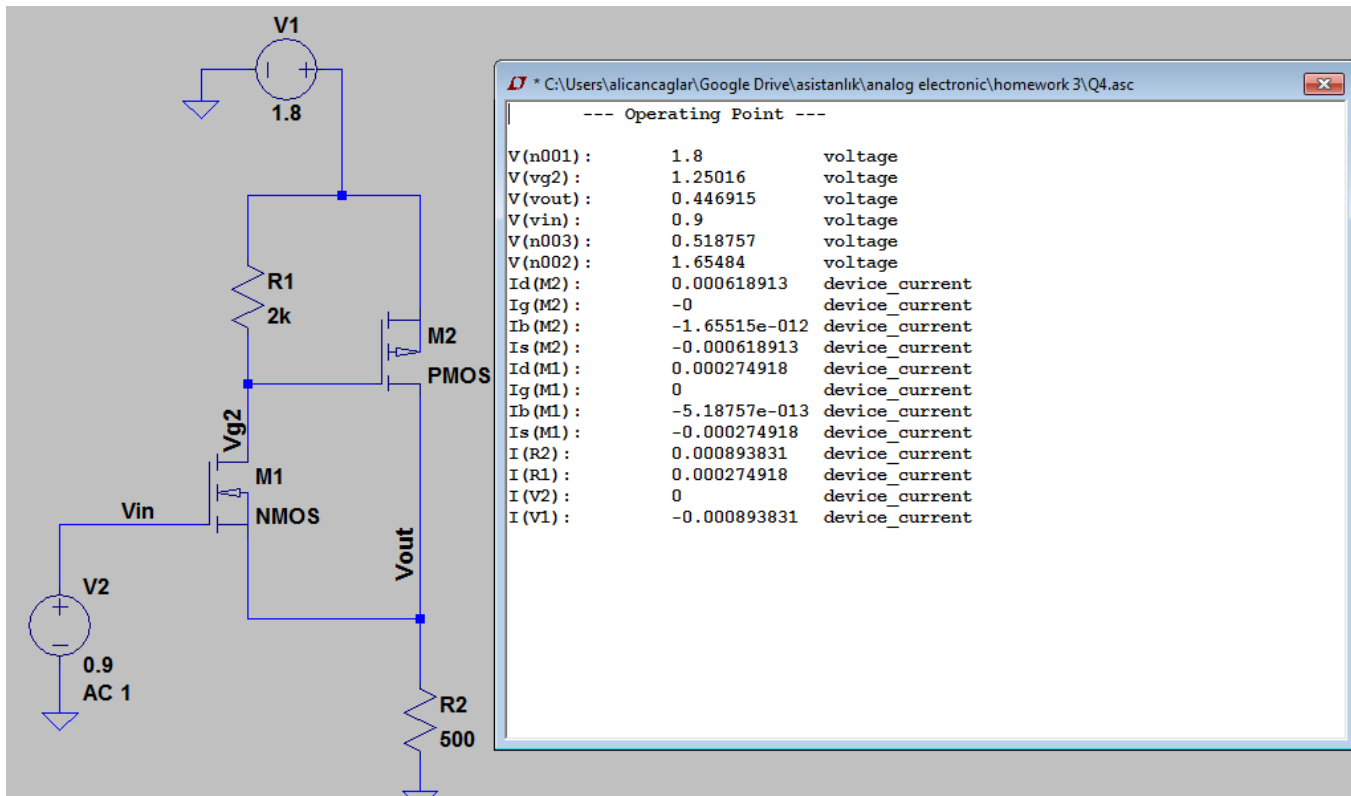
4.a) Operating points of the circuit, when input voltage is 0.9 V.



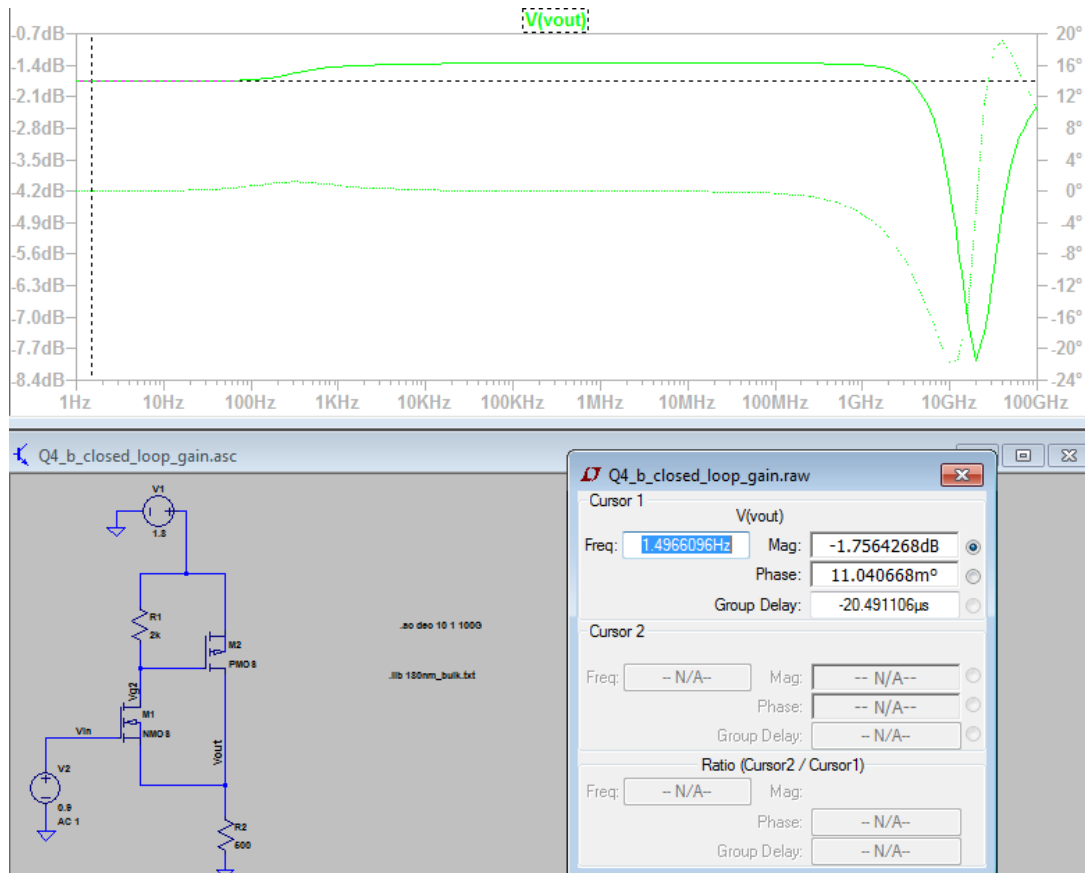4.b) Closed loop gain is about -1.75 dB at low frequency.



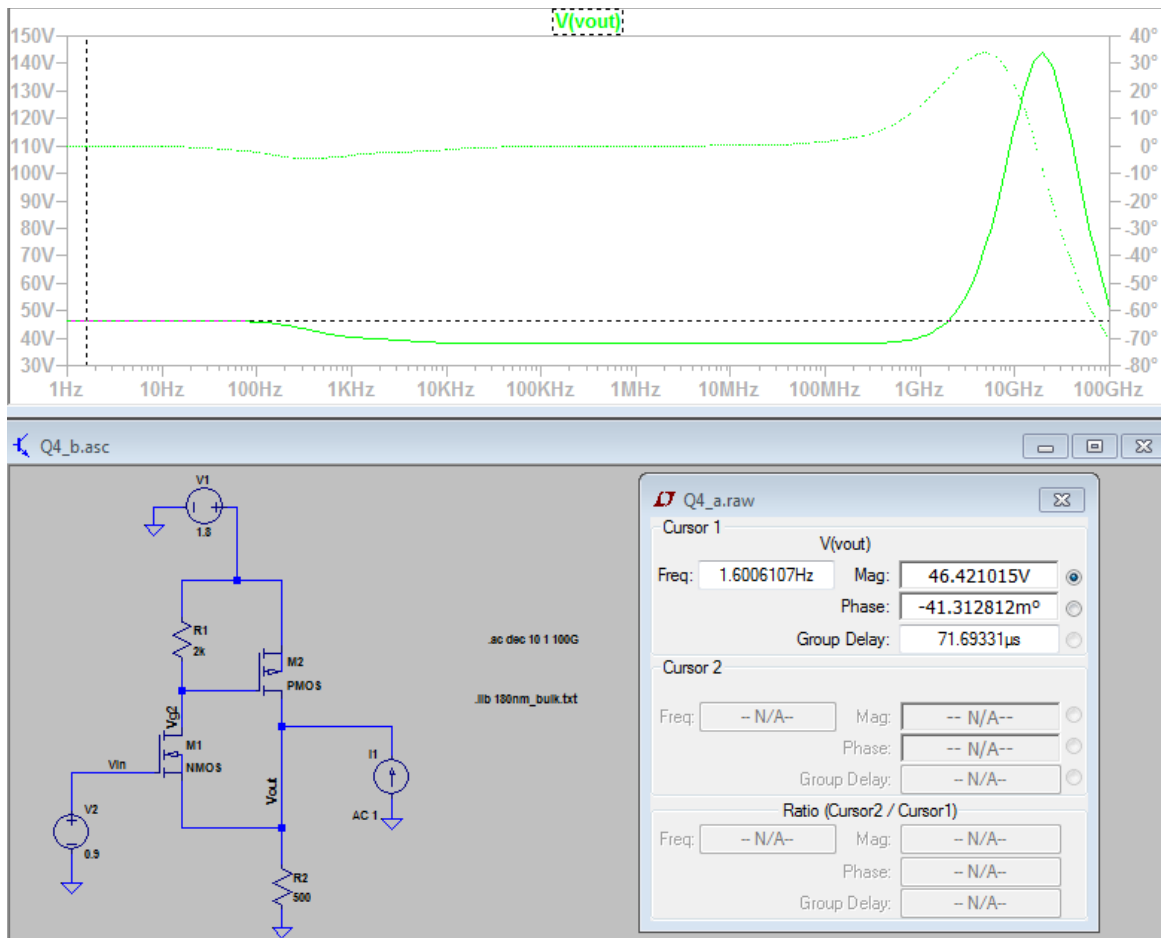Output impedance at low frequency is approximately 46.4 ohm.



Input impedance is infinite.