

EXAMPLE 2.3 Transfer function of an op-amp circuit

The operational amplifier (op-amp) belongs to an important class of analog integrated circuits commonly used as building blocks in the implementation of control systems and in many other important applications. Op-amps are active elements (that is, they have external power sources) with a high gain when operating in their linear regions. A model of an ideal op-amp is shown in Figure 2.14.

The operating conditions for the ideal op-amp are (i) $i_1 = 0$ and $i_2 = 0$, thus implying that the input impedance is infinite, and (ii) $v_2 - v_1 = 0$ (or $v_1 = v_2$). The input-output relationship for an ideal op-amp is

$$v_0 = K(v_2 - v_1) = -K(v_1 - v_2),$$

where the gain K approaches infinity. In our analysis, we will assume that the linear op-amps are operating with high gain and under idealized conditions.


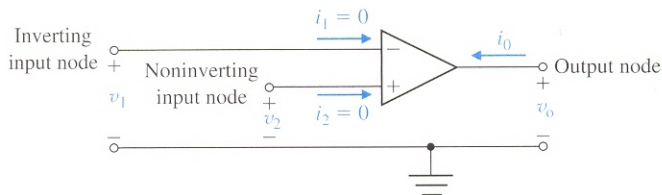


FIGURE 2.14
The ideal op-amp.

FIGURE 2.15

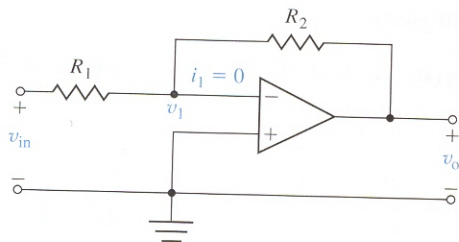An inverting amplifier operating with ideal conditions.



Consider the inverting amplifier shown in Figure 2.15. Under ideal conditions, we have that $i_1 = 0$, so that writing the node equation at v_1 yields

$$\frac{v_1 - v_{\text{in}}}{R_1} + \frac{v_1 - v_o}{R_2} = 0.$$

Since $v_2 = v_1$ (under ideal conditions) and $v_2 = 0$ (see Figure 2.15 and compare it with Figure 2.14), it follows that $v_1 = 0$. Therefore,

$$-\frac{v_{\text{in}}}{R_1} - \frac{v_o}{R_2} = 0,$$

and rearranging terms, we obtain

$$\frac{v_o}{v_{\text{in}}} = -\frac{R_2}{R_1}.$$

We see that when $R_2 = R_1$, the ideal op-amp circuit inverts the sign of the input, that is, $v_o = -v_{\text{in}}$ when $R_2 = R_1$. ■