

2020 – 2021 Spring, CSA CRN:25203
Homework 4

Rules:

- 1) Your homework should be hand-written on A4 paper.
- 2) Have at least 2,0 cm margin from the edges.
- 3) Each page of the solution has to be numbered and should have name, last name, student ID number and signature on top right corner.
- 4) If you do not comply with the format rules your grade will be reduced by 10 (over 100) points.
- 5) Assignments in PDF format are required to be uploaded to the Ninova system before the deadline. There won't be extra time for uploading the assignments.
- 6) The students are expected to work on the solutions on their own. The points of identical or very similar looking assignments will be divided to the number of such assignments.

- a) Find the Thevenin equivalent of the 2-terminal a – b in sinusoidal steady state. (Fig.1)
 $e(t)=2\sin(2t)$, $C=1F$, $L=1H$, $R=\frac{1}{2}\Omega$ (50 points)
- b) A load impedance $Z_L=2+j2$ is connected to this 2-terminal. Find the active, reactive and apparent power of Z_L . (15 points)
- c) Find the element types and their values for the matching circuit in Fig.2 (50 points) and find the active, reactive and apparent power of Z_L in this case (15 points).



