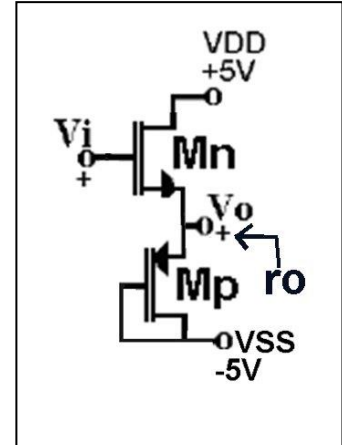


P1 MOS transistors in the circuit are complementary ($\beta_N = \beta_P$, $|V_{THP}| = V_{THN}$). $I_{DN} = I_{DP} = 1\text{mA}$ is given for $V_i = 0\text{V}$.

- Find $\beta_N (= \beta_P)$. (20P)
- Find the ac gain (v_o/v_i). (20P)
- Find r_o . (20P)



P2 $\beta_F = 200$, $|V_{BE}| = 0.6\text{V}$, $V_T = 25\text{mV}$, $V_A = \infty$ are given for transistors in the figure. $g_{m4} = 4g_{m1}$ for $V_i = 0$ (bias point). ac gain of the circuit (v_o/v_i) is measured as -50. Find R_2 and R_1 . (40P)

