

# EHB322E Digital Electronic Circuits

## Quiz 1

*Duration: 30 Minutes*


*Grading: 1) 20%, 2) 80%,*

*Quiz is in closed-notes and closed-books format*

*For your answers please use the space provided in the exam sheet*

**GOOD LUCK!**

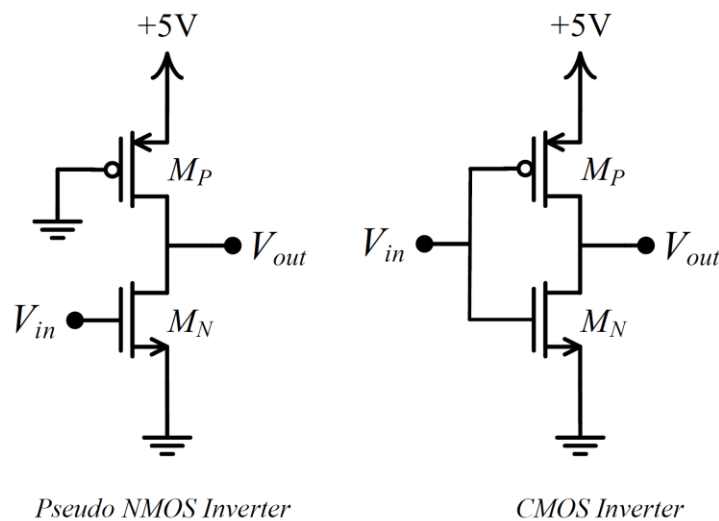- 1) Please circle TRUE if you think that the statement is true; FALSE otherwise.



- a. Consider the pseudo NMOS inverter shown above.

**Statement:** Increasing  $W$  value of  $M_N$  makes the value of  $V_{OH}$  increase.

TRUE / FALSE

- b. Consider the pseudo NMOS inverter shown above.

**Statement:** Increasing  $W$  value of  $M_N$  makes the value of  $t_{PLH}$  decrease.

TRUE / FALSE

- c. Consider the CMOS inverter shown above.

**Statement:** If  $(W/L)$  ratios and absolute threshold voltage values of PMOS/NMOS transistors are same then the switching threshold value of  $V_M$  is  $5/2V$ .


TRUE / FALSE

- d. Consider the CMOS inverter shown above.

**Statement:** The output (load) capacitor is a sum of  $C_{GS}$  and  $C_{GD}$  capacitors of the transistors.

TRUE / FALSE

 - 2) Consider the buffer of two CMOS inverters shown below. A capacitor of 10fF is connected to the output. A signal switching from low to high is applied to the input.  
*Transistor parameters:*  $c_{ox}=1 \text{ fF}/\mu\text{m}^2$ ,  $\tau_n = \tau_p=1\text{ps}$ ,  $W_{P1}=2\mu$ ,  $W_{N1}=1\mu$ ,  $W_{P2}=4\mu$ ,  $W_{N2}=2\mu$ ,  $L_{N1}=L_{P1}=L_{N2}=L_{P2}=1\mu$ .



*A buffer of two CMOS inverters.*

Propagation delays of an inverter is formulized as follows.  $C_L$  represents the load capacitor of the inverter.

$$t_{PHL} = (C_L/C_N) \tau_n \quad C_N = c_{ox} W_N L_N$$

$$t_{PLH} = (C_L/C_P) \tau_p \quad C_P = c_{ox} W_P L_P$$

Determine **the total propagation delay** at the output. Neglect  $C_{GD}$  capacitors.

$$C_{GS-N}=C_N, \quad C_{GS-P}=C_P$$