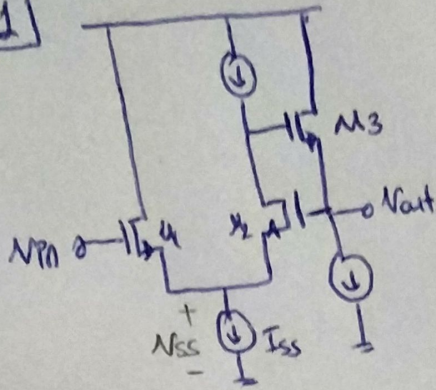


EHB 335E HW#5

1)



- Assume $V_{in} \uparrow$, Since $I_{d,u2}$ and hence $I_{d,u1}$ cannot change. To accommodate the increase in V_{in} , V_{ss} should increase.

Ass $V_{ss} \uparrow$, $V_{out} \uparrow$ ($V_{gs,2} = V_{out} - V_{ss}$), $I_{d,u2}$ is fixed.

As $V_{out} \uparrow$, $V_{o3} \uparrow$ ($V_{gs,3} = V_{o3} - V_{out}$), $I_{d,u3}$ is fixed.

- As $V_{o3} \uparrow$, drain-to-source voltage of $M2$ increases and $I_{d,u2}$ tends to increase but since $I_{d,u2}$ cannot increase $V_{gs,2}$ has to decrease to hold $I_{d,u2}$ constant. Therefore V_{out} has to decrease. Therefore this circuit employs negative feedback.


In Summary,

$$V_{in} \uparrow \rightarrow V_{ss} \uparrow \rightarrow V_{out} \uparrow \rightarrow V_{o3} \uparrow \rightarrow V_{out} \downarrow$$

negative feedback

Second Method

$V_{in} = 0$

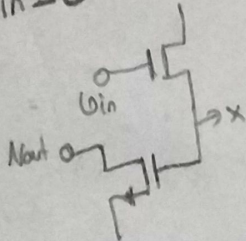

$$A_v = \frac{V_{out}}{v_{in}} = \frac{V_x}{v_{in}} \cdot \frac{V_{out}}{V_x}$$

CS stage (<0)

SF stage (>0)

$$(<0) \times (>0) = (<0) \Rightarrow \text{Negative Feedback.}$$


Sensed: current
Returned: current

\Rightarrow Current-Current Amplifier (Shunt-Series)

How to Break the loop \Rightarrow
Open-loop Gain Calculation

$$I_1 = \frac{R_F + R_L}{\frac{1}{g_{m1}} + R_F + R_L} I_{in} \quad (\text{Current Divider})$$
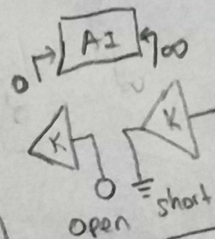
$$V_x = R_O I_1 = \frac{R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L} I_{in}$$



$$R_{in} = \frac{1}{g_{m1}} \parallel (R_F + R_L)$$

$$R_{out} = R_F \parallel R_L$$


$$V_{out} = -g_{m2} (R_F \parallel R_L) V_x$$

$$I_{out} = \frac{V_{out}}{I_{out}} = -g_{m2} V_x = -\frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L} I_{in}$$


$$A_I = \frac{I_{out}}{I_{in}} = -\frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L}$$

(1)


2)

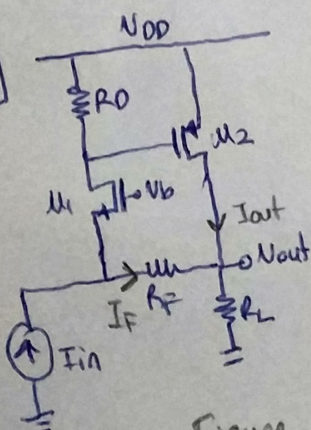

New Figure

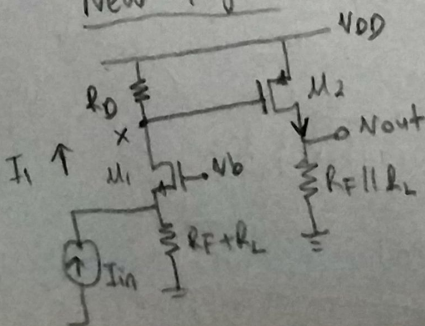

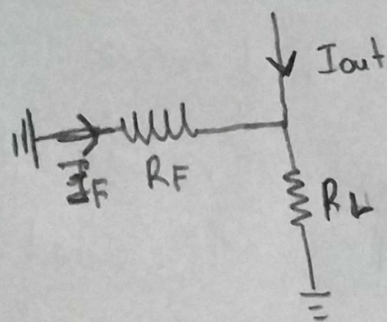Now, let us determine the Feedback Factor (K)



By Current Division

$$I_F = - \frac{R_L}{R_F + R_L} I_{out}$$


$$\Rightarrow K = \frac{I_{out}}{I_F} = - \frac{R_L}{R_F + R_L}$$

$$\Rightarrow A_{I,CL} = \frac{A_I}{1 + K A_I} = \frac{- \frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L}}{1 + \left(- \frac{R_L}{R_F + R_L} \right) \left(- \frac{g_{m2} R_O (R_F + R_L)}{\frac{1}{g_{m1}} + R_F + R_L} \right)}$$

$$\Rightarrow A_{I,CL} = - \frac{g_{m2} R_O (R_F + R_L)}{\left(\frac{1}{g_{m1}} + R_F + R_L \right) (1 + g_{m2} R_O R_L)}$$

$$R_{out,CL} = R_{out} (1 + K A_I) = (R_F || R_L) \left[1 + \frac{g_{m2} R_O R_L}{\frac{1}{g_{m1}} + R_F + R_L} \right]$$


$$R_{in,CL} = \frac{R_{in}}{1 + K A_I} = \frac{\frac{1}{g_{m1}} || (R_F + R_L)}{1 + \frac{g_{m2} R_O R_L}{\frac{1}{g_{m1}} + R_F + R_L}}$$

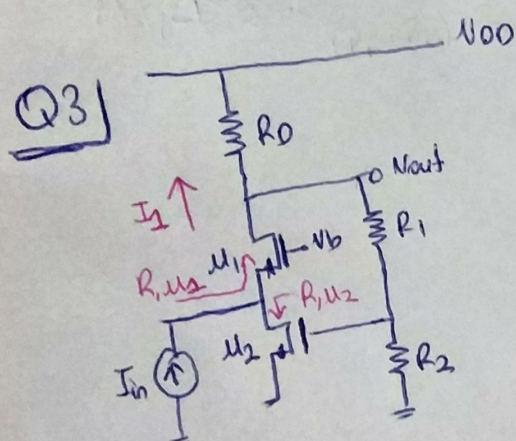

We sense voltage and return current.

\Rightarrow voltage current amplifier (shunt-shunt)

First determine open-loop gain R_O

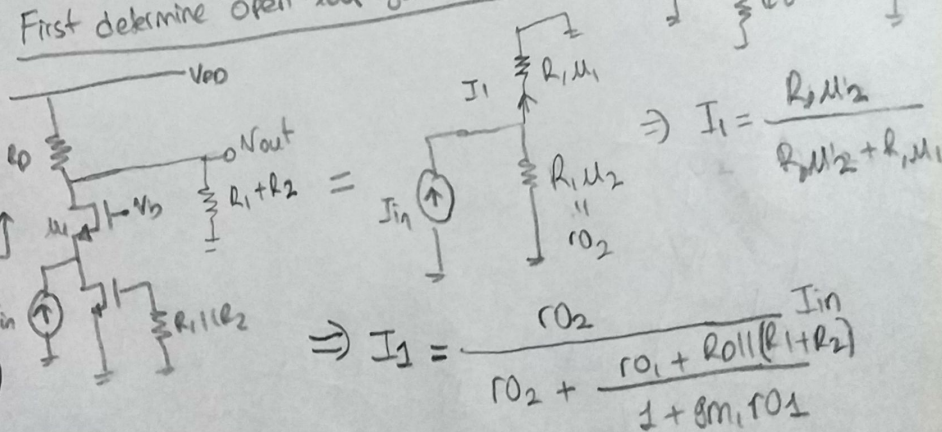

$$\Rightarrow I_1 = \frac{R_O g_{m1} V_x}{R_O g_{m1} V_x + R_1 + R_2}$$


$$\Rightarrow I_1 = \frac{R_O}{R_O + \frac{R_1 + R_2}{1 + g_{m1} R_O1}} I_{in}$$

$$V_{out} = (R_O || (R_1 + R_2)) I_1$$

$$V_{out} = \frac{(R_O || (R_1 + R_2)) R_O}{R_O + \frac{R_1 + R_2}{1 + g_{m1} R_O1}} I_{in}$$

open-loop gain of the circuit

In order to find R_{in}

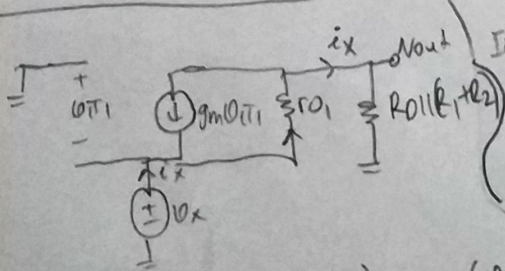


$$V_{out} = V_x - (i_x + g_{m1} V_x) R_O1 ; (V_{in} = -V_x)$$

$$i_x (R_O || (R_1 + R_2)) = V_x - i_x R_O1 + g_{m1} R_O1 V_x$$

$$\frac{V_x}{i_x} = R_{in} = \frac{R_O1 + R_O || (R_1 + R_2)}{1 + g_{m1} R_O1}$$

$$\Rightarrow R_O = \frac{V_{out}}{I_{in}} = \frac{(R_O || (R_1 + R_2)) R_O}{R_O + \frac{R_1 + R_2}{1 + g_{m1} R_O1}}$$


we draw

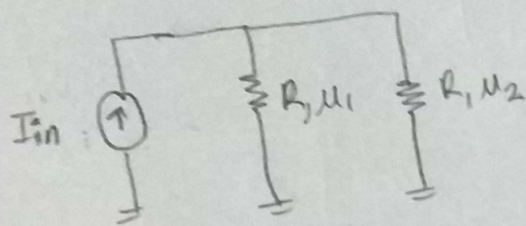

$$\Rightarrow R_{in} = R_{1, u_1} \parallel R_{1, u_2}$$


$$R_{in} = \left[\frac{r_{o2} + (R_{o1} \parallel (R_1 + R_2))}{1 + g_{m1} r_{o1}} \right] \parallel r_{o2}$$

and R_{out} can be calculated as

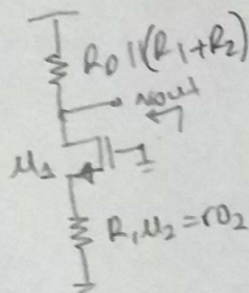

$$R_{out} = R_{o1} \parallel (R_1 + R_2) \parallel \left[(1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \right]$$

Let's calculate the feedback factor K

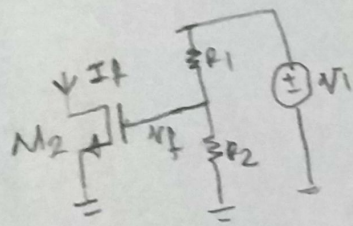

$$\Rightarrow K = \frac{I_f}{V_1} = \frac{V_f}{V_1} \cdot \frac{I_f}{V_f} = \frac{R_2}{R_1 + R_2} \cdot g_{m2}$$

Now, we can calculate the closed-loop parameters

$$R_{o, cl} = \frac{R_o}{1 + K R_o} = \frac{\frac{(R_{o1} \parallel (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_{o1} \parallel (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}{1 + \frac{g_{m2} R_2}{R_1 + R_2} \cdot \frac{(R_{o1} \parallel (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_{o1} \parallel (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}$$

\Rightarrow closed-loop gain of transimpedance amplifier

$$R_{in, cl} = \frac{R_{in}}{1 + K R_o} = \frac{\left[\frac{r_{o1} + (R_{o1} \parallel (R_1 + R_2))}{1 + g_{m1} r_{o1}} \right] \parallel r_{o2}}{1 + \frac{g_{m2} R_2}{R_1 + R_2} \cdot \frac{(R_{o1} \parallel (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_{o1} \parallel (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}$$

\Rightarrow closed-loop input impedance of transimpedance amplifier

$$R_{out, cl} = \frac{R_{out}}{1 + K R_o} = \frac{R_{o1} \parallel (R_1 + R_2) \parallel \left[(1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \right]}{1 + \frac{g_{m2} R_2}{R_1 + R_2} \cdot \frac{(R_{o1} \parallel (R_1 + R_2)) r_{o2}}{r_{o2} + \frac{r_{o2} + (R_{o1} \parallel (R_1 + R_2))}{1 + g_{m1} r_{o1}}}}$$

\Rightarrow closed-loop output impedance of transimpedance amplifier

\Rightarrow Negative feedback makes the amplifier close to the ideal by reducing R_{out} and R_{in} at the cost of reducing the gain.