

EE232-INTRODUCTION TO ELECTRONICS-FALL 2009
EXERCISE-BJT2

P1 In the amplifier circuit shown in Figure-1, $|V_{BE}| \cong 0.6V$, $V_T \cong 26mV$ and $\beta_F = 200$ are given for the transistors.

a) V_O is required "0V" in DC case when $V_i = 0V$.

Find R_{C3} . (10Points)

A-1a

$V_O = 0V$ has been given for $V_i = 0V$.

From the circuit topology;

$$I_{RC2} = I_{RC1} \cong \frac{I_K}{2} = 1mA \quad (I_{RK} \text{ can be neglected})$$

Then,

$$I_{RC2} \times R_{C2} = V_{RE3} + V_{EB} = I_{E3} \times R_{E3} + V_{EB}$$

$$1mA \times 2.2k = I_{E3} \times 1k + 0.6V \Rightarrow I_{E3} = 1.6mA \cong I_{C3}$$


$$V_{RC3} = I_{C3} \times R_{C3} = V_O - V_{ss} = 0 - (-12V) = 12V$$

$$R_{C3} = 7.5k\Omega$$

$R_{C3} = 7.5k$ is obtained.

b) Find ac gain (v_o/v_i) of the circuit. (10Points)

A-1b

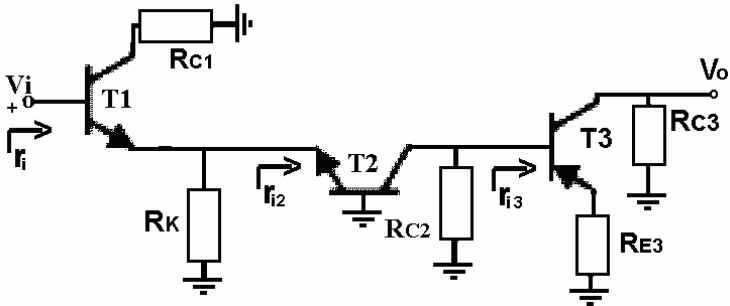

ac case of the circuit

T1: emitter-follower: $\frac{v_{e1}}{v_i} = \frac{g_{m1}R_{e1}}{1 + g_{m1}R_{e1}} = \frac{g_{m1}(R_K // r_{i2})}{1 + (R_K // r_{i2})}$

$$r_{i2} = \frac{1}{g_{m2}} + \frac{R_{b2}}{\beta_F} = \frac{1}{g_{m2}} + \frac{0}{\beta_F} = \frac{1}{g_{m2}}$$

T2: common-base: $\frac{v_{c2}}{v_{e2}} = \frac{g_{m2}R_{c2}}{1 + g_{m2}\frac{R_{b2}}{\beta_F}} = \frac{g_{m2}(R_{C2} // r_{i3})}{1 + g_{m2}\frac{0}{\beta_F}} = g_{m2}(R_{C2} // r_{i3})$

$$r_{i3} = \beta_F \left(\frac{1}{g_{m3}} + R_{e3} \right) = \beta_F \left(\frac{1}{g_{m3}} + R_{E3} \right)$$

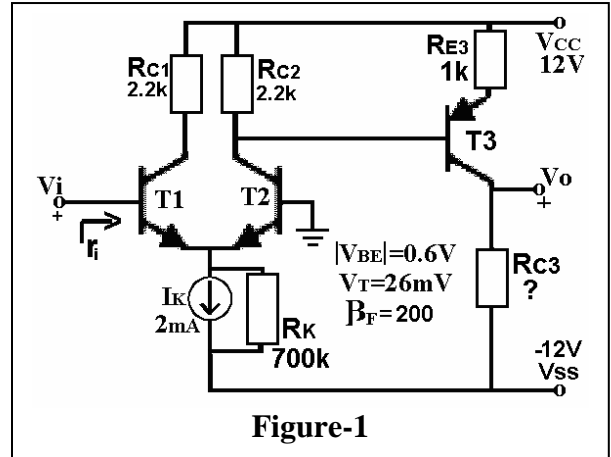


Figure-1

T3: common-emitter: $\frac{v_{c3}}{v_{b3}} = -\frac{g_{m3}R_{c3}}{1 + g_{m3}R_{e3}} = -\frac{g_{m3}R_{C3}}{1 + g_{m3}R_{E3}}$

$$g_{m1} = \frac{I_{C1}}{V_T} \quad g_{m2} = \frac{I_{C2}}{V_T} = g_{m1} \quad g_{m3} = \frac{I_{C3}}{V_T}$$

$$\frac{v_o}{v_i} = \frac{v_{e1}}{v_i} \times \frac{v_{c2}}{v_{e2}} \times \frac{v_{c3}}{v_{b3}} = \frac{1}{2} \times 88 \times (-7.38) = -325$$

~~c) Find CMRR of the circuit. (10Points)~~

A-1c

~~$$CMRR = \frac{1}{2} + g_{m1}R_{EE} = \frac{1}{2} + g_{m1}R_K = 0.5 + \frac{1}{25}700k \approx 28000$$~~