
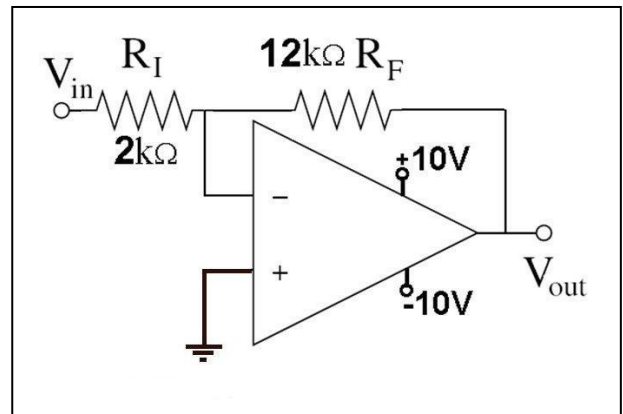


In the circuit employing an OPAMP

1) Find V_{out} for $V_{in}=1V$

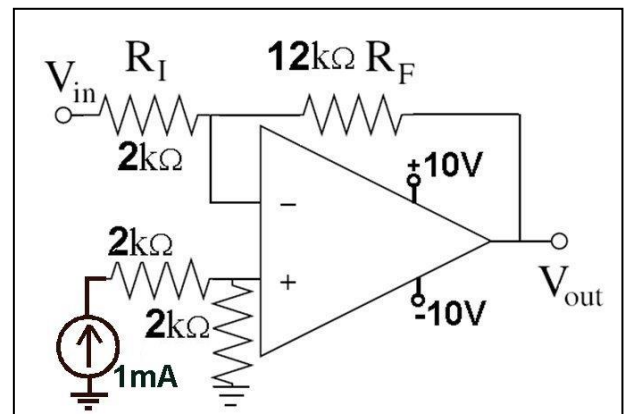

2) Find V_{out} for $V_{in}=-1V$



3) Draw V_{out} when V_{in} varies from -5V to +5V.

