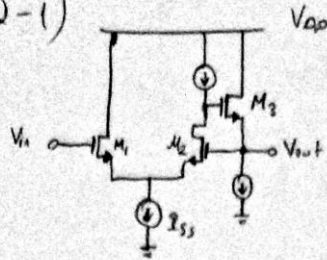


Q-1)



\Rightarrow Assume that $V_{in} \uparrow$. Since $I_{D_{M2}}$ and $I_{D_{M1}}$ can not change, to satisfy the increase of V_{in} ; V_{GS} should be increased.

\Rightarrow Since $V_{GS2} = V_{out} - V_{SS}$ as $V_{SS} \uparrow \Rightarrow V_{out} \uparrow$ ($I_{D_{M2}}$ is fixed)


\Rightarrow Since $V_{GS3} = V_{G3} - V_{out}$ as $V_{out} \uparrow \Rightarrow V_{G3} \uparrow$ ($I_{D_{M3}}$ is fixed)

\Rightarrow So, V_{G3} is increased when V_{in} is increased. As $V_{G3} \uparrow$, drain to source voltage of M_2 is increased, and $I_{D_{M2}}$ tends to increase, but we said that $I_{D_{M2}}$ is fixed. So, it can not increase, then this problem can be solved by decrease of V_{GS2} . Additionally, V_{out} has to decrease as V_{GS2} decrease. So, this circuit employs negative feedback.

As a summary


$V_{in} \uparrow \rightarrow V_{SS} \uparrow \rightarrow V_{out} \uparrow \rightarrow V_{G3} \uparrow \rightarrow V_{out} \downarrow$
 \uparrow Negative feedback \uparrow

Q-2)

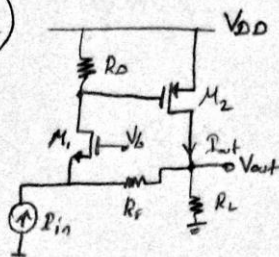

Desired: Current
 Returned: Current \sim Current-Current Amplifier (Shunt-Series)

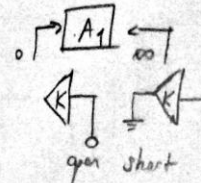\Rightarrow For breaking the loop \Rightarrow



Open-Loop Gain Calculations


$$\begin{aligned} * R_{in} &= \frac{1}{g_{m1}} \parallel (R_f + R_L) \\ * R_{out} &= R_f \parallel R_L \end{aligned}$$

With Current Divider

$$\frac{I_1}{I_{in}} = \frac{R_f + R_L}{R_f + R_L + \frac{1}{g_{m1}}}$$

* We can update the circuit as follows?

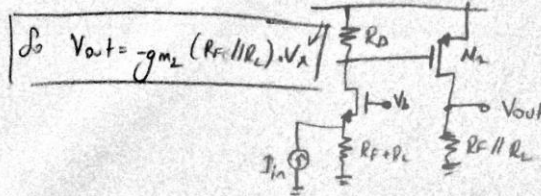
$$\Rightarrow V_x = R_D \cdot I_1 = \frac{R_D \cdot (R_f + R_L)}{R_f + R_L + \frac{1}{g_{m1}}} \cdot I_{in}$$



$$\text{So } V_{out} = -g_{m2} (R_f \parallel R_L) \cdot V_x$$

$$\Rightarrow I_{out} = \frac{V_{out}}{R_{out}} = -g_{m2} V_x = \frac{-g_{m2} \cdot R_D (R_f + R_L)}{\frac{1}{g_{m1}} + R_f + R_L} \cdot I_{in}, \quad A_E = \frac{I_{out}}{I_{in}} = - \frac{g_{m2} \cdot R_D (R_f + R_L)}{\frac{1}{g_{m1}} + R_f + R_L}$$

To determine feedback factor K

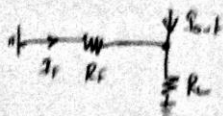

With Current Division: $I_F = \frac{-R_L}{R_F + R_L} \cdot I_{out}$

$$K = \frac{I_{out}}{I_F} = - \frac{R_L}{R_L + R_F}$$

Closed Loop Gain: $A_{v,CL} = \frac{A_v}{1 + K A_v} \rightarrow - \frac{g_{m2} R_o (R_L + R_F)}{\frac{1}{g_{m1}} + R_F + R_L}$

$$\text{So, } A_{v,CL} = - \frac{g_{m2} R_o (R_L + R_F)}{\left(\frac{1}{g_{m1}} + R_F + R_L\right) \cdot (1 + g_{m2} R_o R_L)}$$

$$1 + \left(\frac{-R_L}{R_L + R_F}\right) \left(\frac{-g_{m2} R_o (R_L + R_F)}{\frac{1}{g_{m1}} + R_F + R_L}\right)$$


Output Impedance?

$$R_{out,CL} = R_{out} (1 + K A_v) = (R_F \parallel R_L) \cdot \left[1 + \frac{g_{m2} R_o R_L}{\frac{1}{g_{m1}} + R_F + R_L} \right]$$

Input Impedance:

$$R_{in,CL} = \frac{R_{in}}{1 + K A_v} = \frac{\frac{1}{g_{m1}} \parallel (R_F + R_L)}{1 + \frac{g_{m2} R_o R_L}{\frac{1}{g_{m1}} + R_F + R_L}}$$


Q-3)

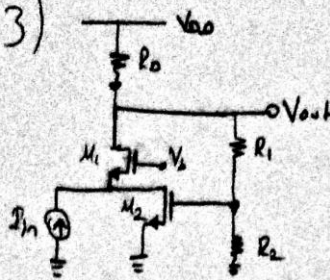



→ Sense of Voltage

Returned of Current

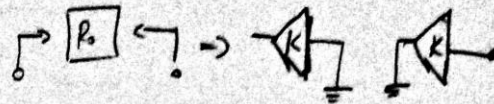→ Voltage - Current Amplifier (Shunt - Shunt)



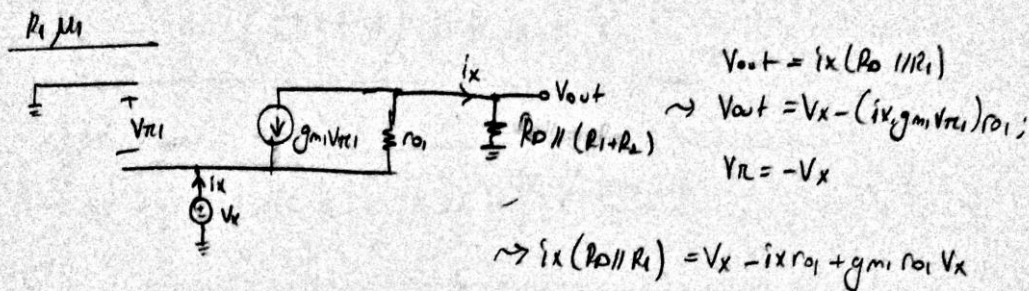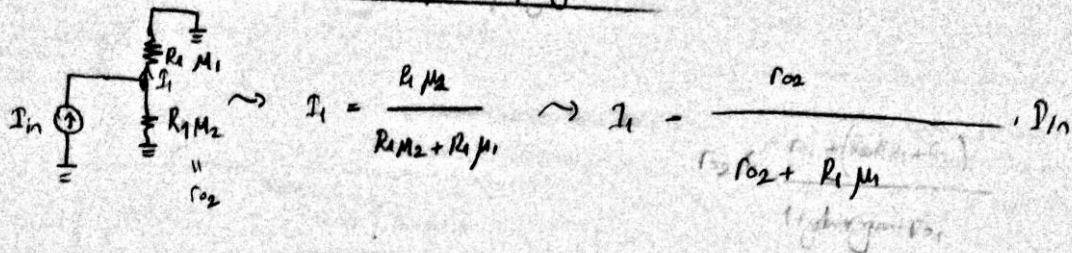⇒ Firstly let's determine the open loop gain




$$\text{So, } \frac{V_X}{i_x} = R_X = R_1 \mu_1 = \frac{r_{o1} + R_D \parallel (R_1 + R_2)}{1 + g_{m1} r_{o1}}$$

$$\text{So } \frac{I_1}{I_{in}} = \frac{r_{o2}}{r_{o2} + \frac{R_D \parallel (R_1 + R_2) + r_{o1}}{1 + g_{m1} r_{o1}}}, \text{ Since } V_{out} = (R_D \parallel R_1) \cdot I_1$$

$$\text{So, } \frac{V_{out}}{I_{in}} = (R_D \parallel R_1) \cdot \left[\frac{r_{o2}}{r_{o2} + \frac{R_D \parallel (R_1 + R_2) + r_{o1}}{1 + g_{m1} r_{o1}}} \right] = V_o$$

Q-4)

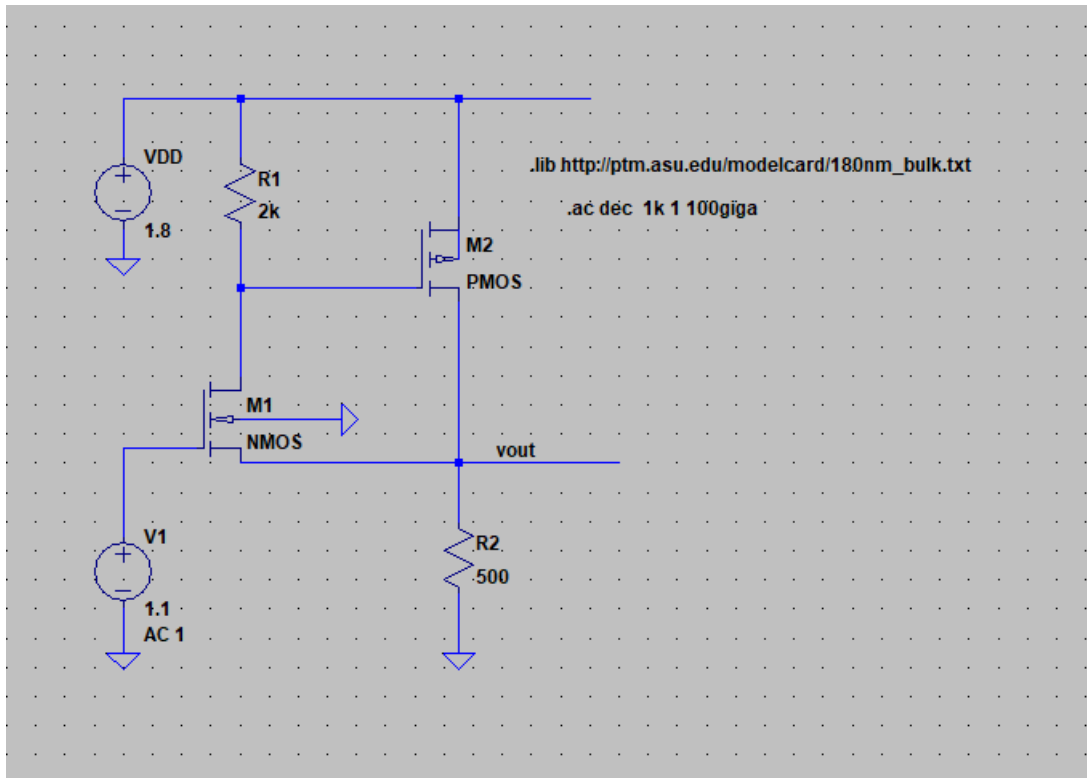→ The circuit generated via LTSpice can be seen below.




a-)

- The operation point analysis results of the circuit is as following.
- Vin value(Vn004) is as double as Vout value in DC çop point analysis.


```
--- Operating Point ---
V(n001):      1.8          voltage
V(n003):      1.22707     voltage
V(vout):      0.561053    voltage
V(n002):      1.65591     voltage
V(n004):      1.1          voltage
Id(M1):       0.000286464  device_current
Ig(M1):       0           device_current
Ib(M1):       -1.80813e-012 device_current
Is(M1):       -0.000286464 device_current
Id(M2):       0.000835643  device_current
Ig(M2):       -0          device_current
Ib(M2):       -1.65592e-012 device_current
Is(M2):       -0.000835643 device_current
I(R2):        0.00112211   device_current
I(R1):        0.000286464  device_current
I(V1):        0           device_current
I(Vdd):       -0.00112211  device_current
```


b-)

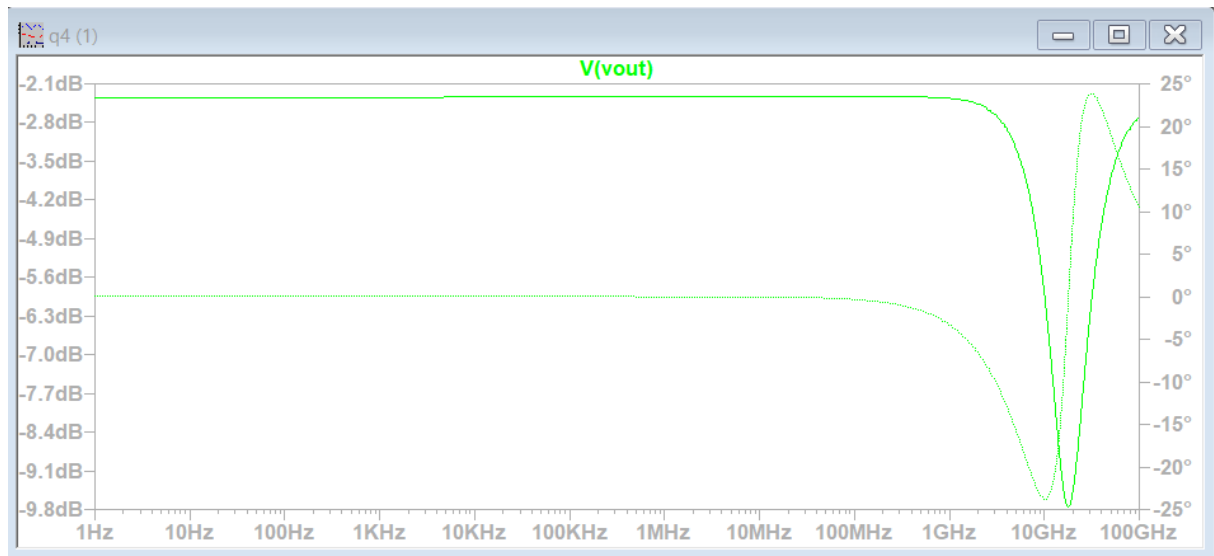→ The closed loop gain analysis with ac decade simulation can be seen below. We can say that the gain of circuit is about -2.3 dB



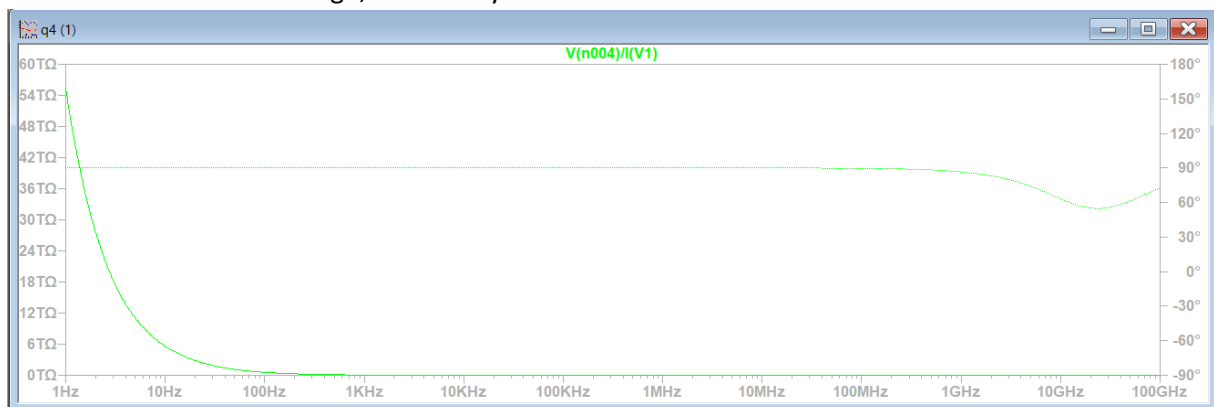→ For R_{in} , there is no change in the circuit. Ac analysis is done, then the result found as below. This value is too high, we can say that R_{in} is infinite.



→ Lastly, for R_{out} we connect an AC = 1V, DC = 0V voltage source to the Vout node. Then we do the AC simulation again.

→ It can be said that V_{out} is about 100 Ohms.

