

\*\*\*\*\*

Q3- Figure-1a shows an amplifier circuit employing a MOSFET.

For the MOSFET,  $\beta = 2\text{mA/V}^2$  and  $V_{TH} = 2\text{V}$  are given.

a)  $V_{DQ}$  is required to be 0V at the operating point. Find  $I_{DQ}$  and  $R_S$ .

(10Points)

b) Find the DC power dissipated on the MOSFET. (10Points)

c) Find ac input and output resistances of the circuit ( $r_i$  and  $r_o$ ).

(10Points)

d) Draw the ac output voltage  $v_o(t)$  for the ac input voltage  $v_i(t)$  given in Figure-1b. (10Points)

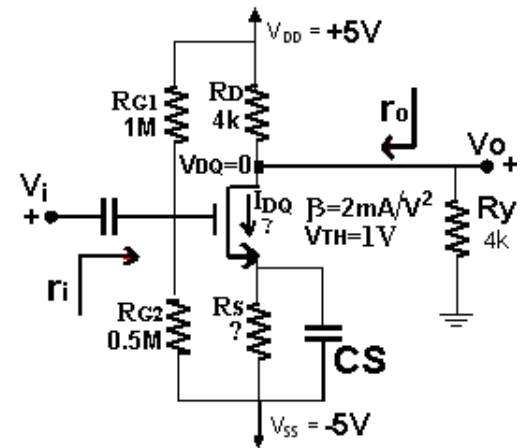


Figure-1a

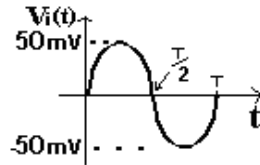


Figure-1b

\*\*\*\*\*

Q4- For the MOS transistors given in Figure-2a,

$\beta_1 = \beta_2 = \beta_3 = 1\text{mA/V}^2$ ,  $V_{TH1} = V_{TH2} = -1\text{V}$  and  $V_{TH3} = 1\text{V}$  are given.

a) Find drain currents of the transistors for  $V_i = 0\text{V}$ .

(10Points)

b) Find ac gain ( $v_o/v_i$ ) of the circuit.

(10Points)

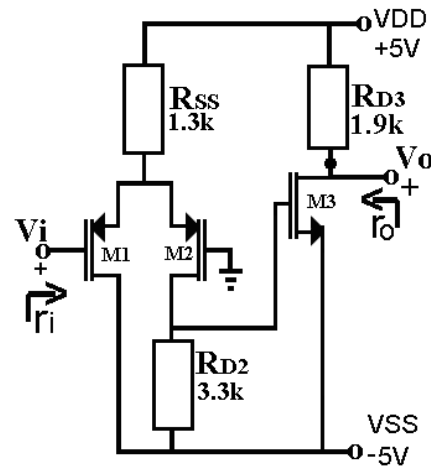


Figure-2a

c) A PMOS transistor will be used in place of  $R_{SS}$  (Figure-2b).

DC values of the circuit (the values found in a) are required not to change. Find the gate bias voltage ( $V_{GB}$ ) of

the transistor ( $\beta_4 = 2\text{mA/V}^2$ ,  $V_{TH4} = -1\text{V}$  and  $V_{A4} = 100\text{V}$ ).

(10Points)

d) Find the ac gain for the new case.

(10Points)

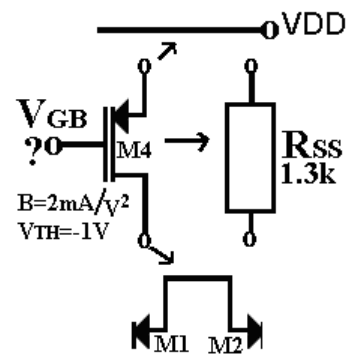


Figure-2b

C-3- a)  $V_{RD} = V_{DD} - V_{DQ} = 5 - 0 = 5V$

↓  
Voltage  
across  $R_D$

$$I_{RD} = \frac{V_{RD}}{R_D} = \frac{5V}{4k} = 1,25mA$$

$$I_D = I_{RD} = 1,25mA \text{ (from the circuit topology)}$$

Transistor is probably in the saturation mode.

Thus,  $I_D = \beta/2 \cdot (V_{GS} - V_{TH})^2 = 1,25mA$

$$\downarrow$$

$$V_{GS} = +\sqrt{\frac{2I_D}{\beta}} + V_{TH} \approx 3,12V$$

$$V_G = \frac{R_{G2}}{R_{G1} + R_{G2}} (V_{DD} - V_{SS}) + V_{SS} = \frac{0,5}{1,5} 10 - 5$$

$$V_G \approx -1,67V$$

$$V_S = V_G - V_{GS} = -1,67 - 3,12 \approx -4,8V$$

$$I_{RS} = I_D = 1,25mA \Rightarrow R_S = \frac{V_{RS}}{I_{RS}} = \frac{-4,8 + 5V}{1,25mA}$$

$$R_S \approx 160\Omega$$

b)  $V_{DQ} = 0V \quad V_{SQ} = -4,8V \rightarrow V_{DS} = 4,8V$

$$P_{Tr} = I_D \cdot V_{DS} = 1,25mA \cdot 4,8V \approx 6mW$$

c)  $r_i = R_{G1} // R_{G2} = 1M // 0,5M \approx 333k$


$$r_o \approx R_D = 4k$$

d)  $\frac{v_o}{v_i} = \frac{v_d}{v_f} = \frac{-\mu_m R_d}{1 + \mu_m R_S}$

$$R_d = R_D // R_L$$

$$R_S = 0$$

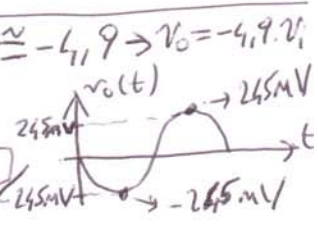
$$g_m = \sqrt{2\beta I_D} \approx 2,45mS$$



C-4-a) M1 is in the saturation mode, since its drain is at the lowest potential.

M2 is probably in the saturation mode.

Thus,  $I_{D1} = I_{D2}$  (probably)

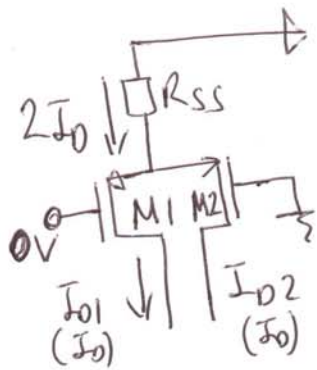

$$V_{GS1} = V_{G1} - V_{S1}$$

$$\downarrow$$

$$= 0 - (V_{DD} - 2I_D \cdot R_{SS})$$

$$I_D = \frac{\beta}{2} (V_{GS} - V_{Th})^2$$

$$\downarrow$$

$$= \frac{1 \text{ mA/V}^2}{2} \left( \underbrace{-5 + 2I_D \cdot R_{SS}}_{V_{GS}} - (-1) \right)^2$$

$$\downarrow$$

$$I_D = \frac{1 \text{ m}}{2} \left( 16 - 20,8 \text{ k} \cdot I_D + 6,76 \text{ M} \cdot I_D^2 \right)$$

$$\Delta = 21,84, \quad I_{D1,2} = \frac{-b \pm \sqrt{\Delta}}{2a} = \frac{-5 \pm \sqrt{21,84}}{2 \times 3,38 \text{ k}}$$

$$I_{D1} = I_{D2} = 1 \text{ mA}$$

1 mA  
M2 is in the  
saturation mode  
for  $I_D = 1 \text{ mA}$

~~2,38 mA~~  
 $V_{S1} < V_{G1}$   
 $V_{GS} > V_T$   
cut-off mode

M3 is probably in the saturation mode.

$$V_{G3} = V_{RD2} + V_{SS} = I_{D2} \cdot R_{D2} + V_{SS}$$

$$\downarrow$$

$$= 1\text{mA} \cdot 3,3\text{k} - 5 = -1,7\text{V}$$

$$V_{GS3} = V_{G3} - V_{S3} = -1,7 + 5 = 3,3\text{V}$$

$$\rightarrow I_{D3} = \frac{\mu}{2} (V_{GS3} - V_{TH3})^2$$

$$\downarrow$$

$$= \frac{1\text{m}}{2} (3,3 - 1)^2 \approx 2,65\text{mA}$$

$$\rightarrow V_{D3} = V_{DD} - V_{RD3} = V_{DD} - I_{D3} \cdot R_{D3} \approx 0$$

$$5\text{V} \quad 2,65\text{mA} \quad 1,9\text{k}$$

(check the condition)

$$V_{GD3} = V_{G3} - V_{D3} = -1,7 - 0 = -1,7$$

$$V_{GD3} < V_{TH3}$$


$$-1,7 < 1 \Rightarrow \text{M3 is in the saturation mode.}$$

$$I_{D3} = 2,65\text{mA}$$

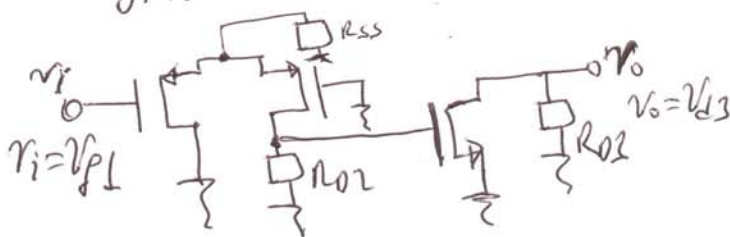b)  $g_{m1} = \sqrt{2\beta I_{D1}} \approx 1,41\text{mS}$

$$g_{m1} = g_{m2} = 1,41\text{mS}$$


$$g_{m3} = \sqrt{2\beta I_{D3}} \approx 2,3\text{mS}$$



$$\frac{v_o}{v_i} = \frac{v_{S1}}{v_{p1}} \cdot \frac{v_{D2}}{v_{S2}} \cdot \frac{v_{D3}}{v_{p3}}$$

$\downarrow$  Source Follower     $\downarrow$  Common-gate     $\downarrow$  Common-source
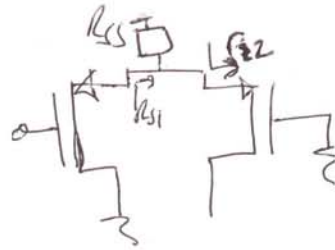
$$\frac{v_{s1}}{v_{p1}} = \frac{\mu_{m1} \cdot R_{s1}}{1 + \mu_{m1} R_{s1}}$$




$$R_{s1} = R_{ss} // r_{i2}$$

$$r_{i2} = \frac{1}{\mu_{m2}} \approx 710 \Omega$$


$$R_{s1} = 1,3k // 710 \Omega \approx 460 \Omega$$

$$\frac{v_{s1}}{v_{p1}} = \frac{1,41m \cdot 0,46k}{1 + 1,41m \cdot 0,46k} \approx 0,39$$
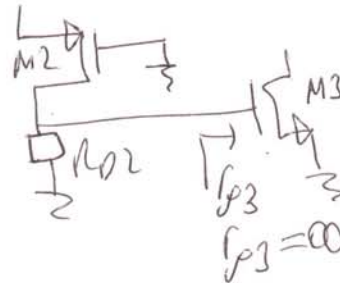
$$\begin{aligned} \frac{v_{d2}}{v_{s2}} &= \mu_{m2} \cdot R_{d2} \\ &\downarrow \\ &= \mu_{m2} \cdot R_{o2} \\ &\downarrow \\ &= 1,41m \cdot 3,2k = 4,65 \end{aligned}$$



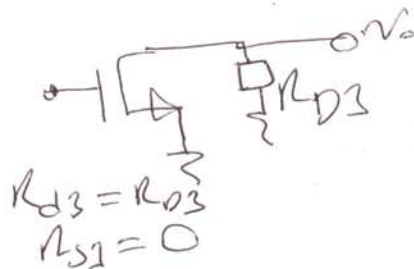
$$\frac{v_{d3}}{v_{p3}} = \frac{-\mu_{m3} \cdot R_{d3}}{1 + \mu_{m3} R_{s3}}$$



$$\begin{aligned} \frac{v_{d3}}{v_{p3}} &= \frac{-2,3m \cdot 1,9k}{1 + 0} \\ &\downarrow \\ &= -4,37 \end{aligned}$$

$$\begin{aligned} R_{d3} &= R_{o3} \\ R_{s3} &= 0 \end{aligned}$$
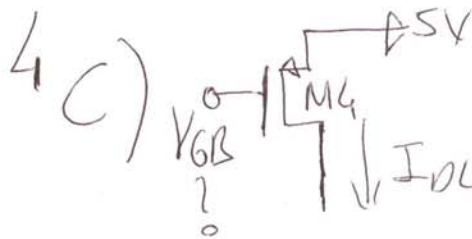
$$\frac{v_o}{v_i} = 0,39 \times 4,65 \times (-4,37) \approx -7,9$$



This transistor is not a amplification transistor.  
It is used as a DC current source the output  
resistance of which is not infinite. .

$$I_{D4} = I_{D1} + I_{D2} = 2 \text{ mA}$$

M4 should be in the saturation mode.

$$I_{D4} = \frac{\beta_4}{2} (V_{GS4} - V_{TH4})^2$$


$$V_{GS4} = -\sqrt{\frac{2I_{D4}}{\beta_4}} + V_{TH4} = -2,41 \text{ V}$$

$$V_{GS4} = V_{G4} - V_{S4} = V_{GB} - V_{DD} = -2,41 \text{ V}$$

$$V_{GB} = -2,41 + V_{DD}$$

$$V_{GB} = \underline{\underline{2,59 \text{ V}}}$$

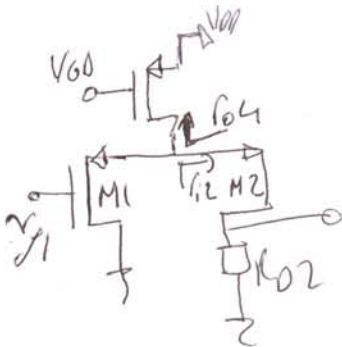↓) Only  $\frac{V_{S1}}{V_{P1}}$  changes, the others does  
not change.



$$\frac{V_{S1}}{V_{P1}} = \frac{\beta_{M1} R_{S1}}{1 + \beta_{M1} R_{S1}} \quad \left\{ \begin{array}{l} R_{S1} = r_{o4} \parallel r_{i2} \\ R_{S1} = r_{o4} \parallel r_{i2} \\ \downarrow 50k \parallel 710\Omega \approx 710\Omega \end{array} \right.$$

$$r_{o4} = \frac{V_{A4}}{I_{D4}} = \frac{100 \text{ V}}{2 \text{ mA}} = 50k$$

$$\frac{V_{S1}}{V_{P1}} = \frac{1,41 \text{ m} \cdot 0,71k}{1 + 1,41 \text{ m} \cdot 0,71k} \approx 0,5$$

$$\frac{V_o}{V_i} = 0,5 \times 4,65 \times (-4,77) \approx -10 //$$