


23/07/15 - w8

①

EWD 322E Digital Electronic Circuits



① Delays considering internal caps

Elmore delay model for RC ladder

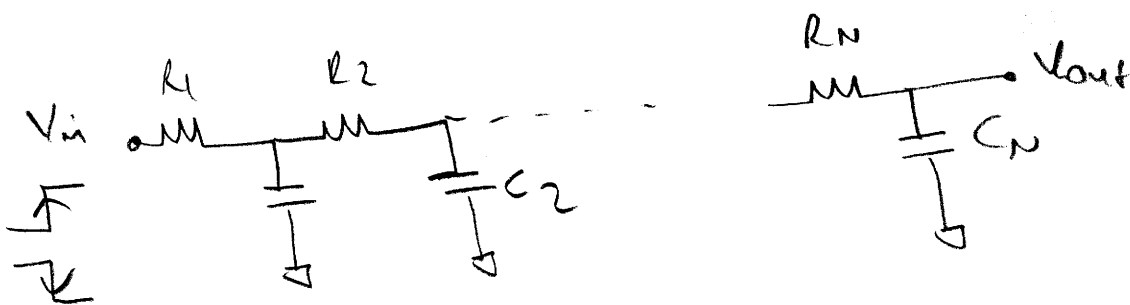


$$t_{PHL}/t_{PLH} = 0.69 \left[R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + \dots + R_N) C_N \right]$$
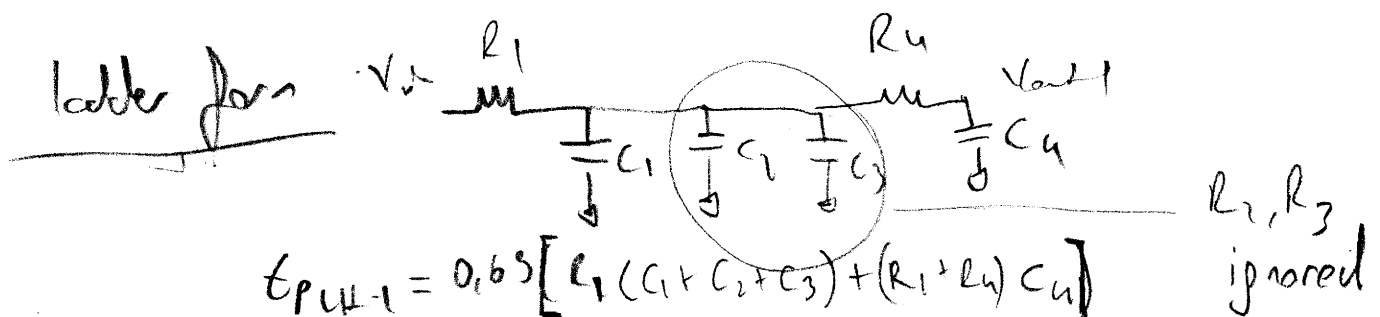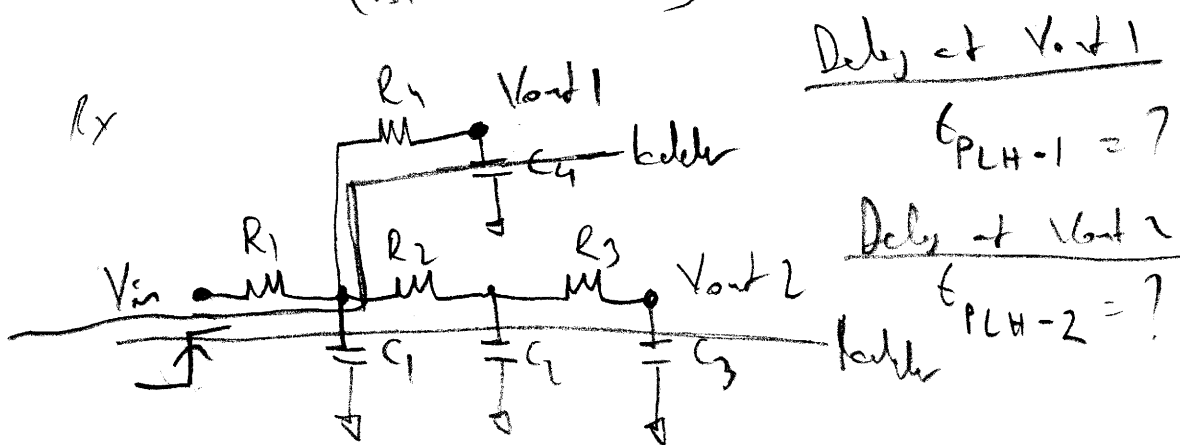
$$t_{PHL}/t_{PLH} = 0.69 \left(\sum_{i=1}^N \left(C_i \left(\sum_{j=1}^i R_j \right) \right) \right)$$




(2)

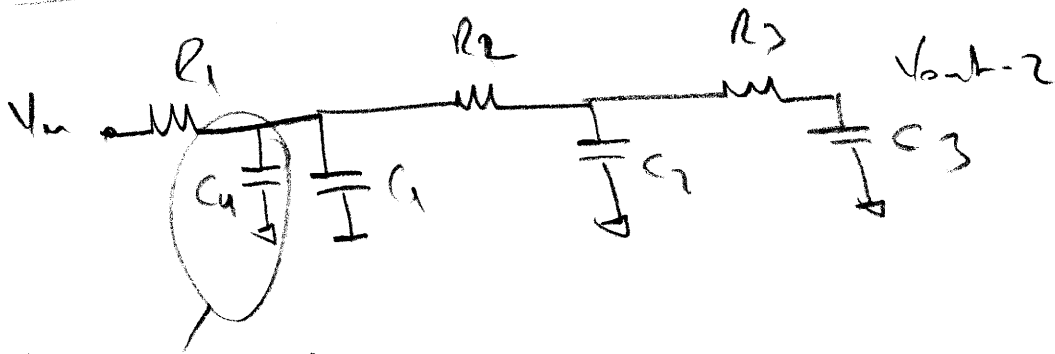Ladder form R_4 ignored

$$t_{PLH-2} = 0.69 \left\{ R_1 (C_1 + C_2) + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 \right\}$$

Elmore model for CMOS circuitsEx 2-input NAND gate

$$f = (x_1 \cdot x_2)$$

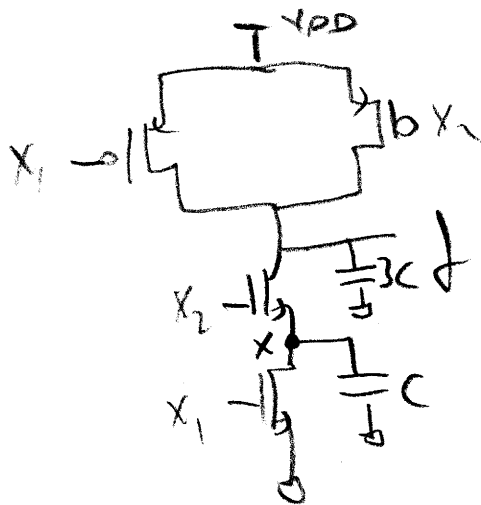

c) $x_1 = 1 \rightarrow 0$ \nearrow
 $x_2 = 1 \rightarrow 0$ \nearrow

Suppose that each tran. has an internal capacitor of C at its DRAIN.

note. Each ON tran. is modeled with a resistor of R .

Calculate the delays

a) $x_1 = 0 \rightarrow 1$ \nearrow

$x_2 = 0 \rightarrow 1$ \nearrow


$V_{x-init} = V_{DD}$

b) $x_1 = 1$ •

$x_2 = 0 \rightarrow 1$ \nearrow

3


a) t_{PHL}

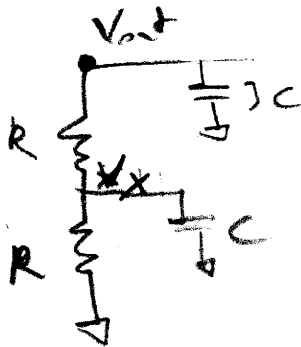

$$V_{out-initial} = V_{DD}$$


$$t_{PHL} = 0.69 \{ R C + 2R \cdot 3C \}$$

b) t_{PHL}

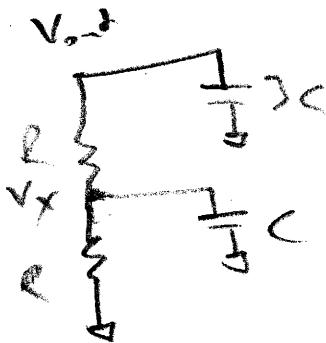


$$V_{out-initial} = V_{DD}$$

$$V_{X-initial} = 0 \rightarrow$$

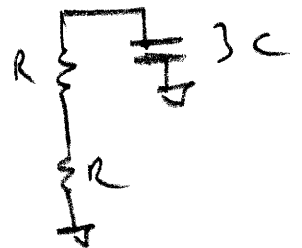

$$t_{PHL} = 0.69 \{ 2R \cdot 3C \}$$

c) t_{PLH}

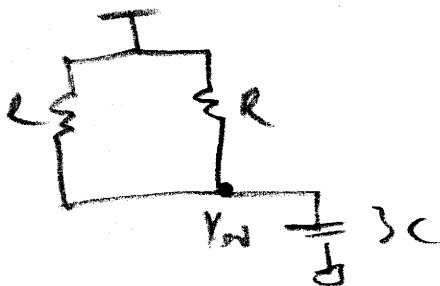


$$V_{out-initial} = 0$$

$$t_{PLH} = 0.69 \left\{ \frac{R}{2} \cdot 3C \right\}$$

(4)

Ex Consider a CMOS circuit shown below. Each NMOS transistor has an equivalent resistor R_N . Suppose that V_{TN} is very small compared to V_{DD} .

Calculate the delays.

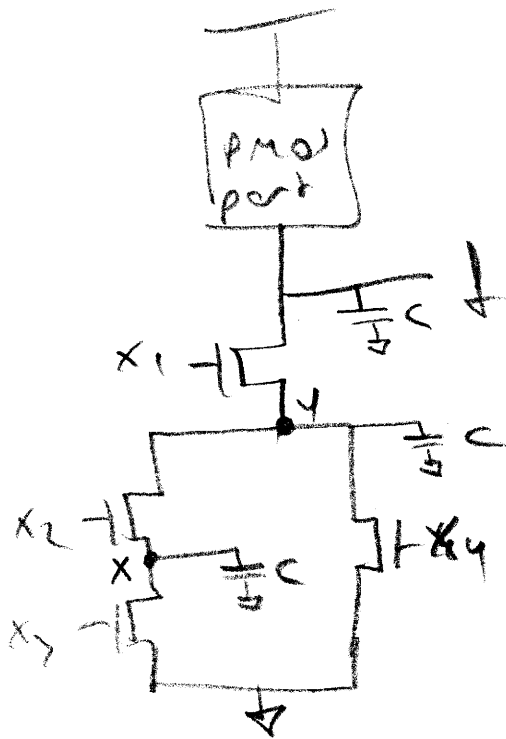

a) $x_1 = 1 \rightarrow 0$

$x_2 = 1 \rightarrow 0$

$x_3 = 0 \rightarrow 1$

$x_4 = 0 \rightarrow 1$

b) $x_1 = 0 \rightarrow 1$

$x_2 = 1$

$x_3 = 1$

$x_4 = 1$

a) $V_{out-init} = V_{DD}$
 $(V_{DD} - V_{TN}) \leq V_{x-init} \leq V_{DD} \approx V_{DD}$
 $V_{DD} - V_{TN} \leq V_{x-init} \leq V_{DD} \approx V_{DD}$

$t_{PHL} \approx 0.69 \left\{ (R + (R/1/2R))C + (R/1/2R)C \right\}$

ignored

b) $V_{out-init} = V_{DD}$

$V_{x-init} = 0$

$V_{y-init} = 0$

$t_{PHL} = 0.69 \left[(R + R/1/2R)C \right]$

ignored

