

① If  $V_{in} \uparrow$ , to provide same current value,  $V_{O1} \uparrow, V_{O2} \uparrow \Rightarrow V_{out} \uparrow$

By feedback circuit  $\Rightarrow V_{O1} \downarrow, V_{O2} \downarrow \Rightarrow V_{out} \downarrow \Rightarrow$  It is a negative feedback.

②  $\tan^{-1} \frac{f}{10^5} + \tan^{-1} \frac{f}{3,16 \cdot 10^5} + \tan^{-1} \frac{f}{10^6} = 135^\circ \quad f \approx 3,16 \cdot 10^5 \text{ Hz}$


$$A(j\omega) = \frac{10^4}{\left(\frac{j\omega}{10^5} + 1\right) \left(\frac{j\omega}{3,16 \cdot 10^5} + 1\right) \left(\frac{j\omega}{10^6} + 1\right)}, \quad \text{When } f = 3,16 \cdot 10^5 \text{ Hz}$$

$$\Rightarrow |A| \approx 66 \text{ dB}$$

So,  $20 \log\left(\frac{1}{\beta}\right) = 66 \text{ dB} \Rightarrow \beta = 5 \cdot 10^{-4}$

$$A_f = \frac{10^4}{1 + 5 \cdot 10^{-4} \cdot 10^4} = 1667 \text{ V/V or } 64,4 \text{ dB}$$

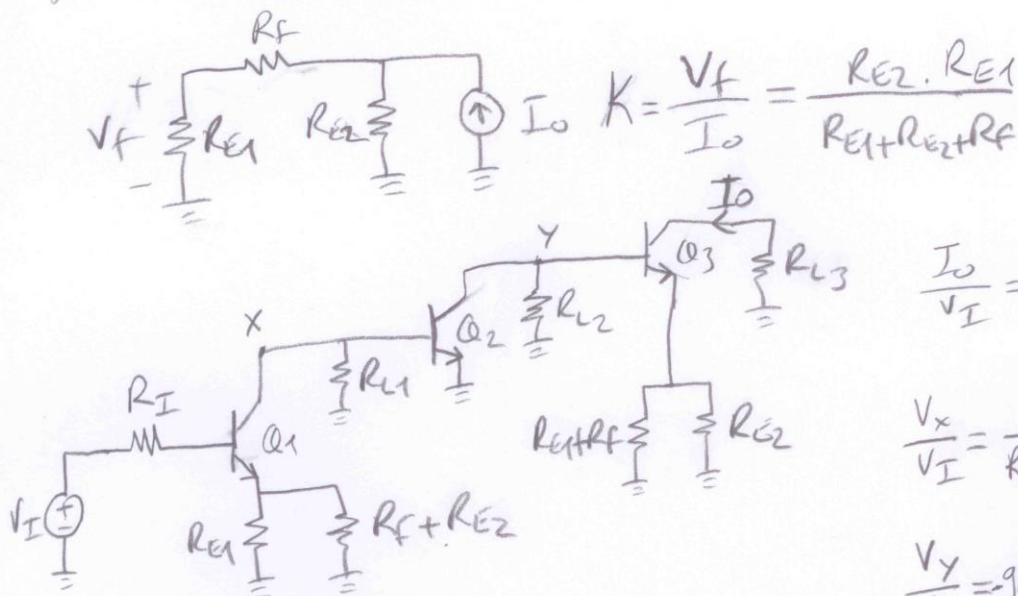③ The amplifier is a transconductance amplifier. So, the feedback topology should be series-series.



$$K = \frac{V_f}{I_o} = \frac{R_{E2} \cdot R_{E1}}{R_{E1} + R_{E2} + R_F}$$

$$\frac{I_o}{V_I} = A_o = \frac{V_x}{V_I} \cdot \frac{V_Y}{V_x} \cdot \frac{I_o}{V_Y}$$

$$\frac{V_x}{V_I} = \frac{-\beta(R_{L1} \parallel R_{L2})}{R_I + r_{\pi 1} + (\beta + 1)R_{E1} \parallel (R_F + R_{E2})}$$

$$\frac{V_Y}{V_x} = g_{m2} R_{L2} \parallel [r_{\pi 3} + (\beta + 1)R_{E2} \parallel (R_{E1} + R_F)]$$

$$\frac{I_o}{V_Y} = \frac{g_{m3}}{1 + g_{m3} \cdot (R_{E2} \parallel (R_{E1} + R_F))}$$

$$R_{in} = R_I + r_{\pi 1} + (\beta + 1)(R_{E1} \parallel (R_F + R_{E2}))$$


$$R_{out} = \infty$$

$$R_{if} = R_{in} (1 + K A_o)$$


$$R_{of} = R_{out} (1 + K A_o)$$

$$A_f = \frac{A_o}{1 + K A_o}$$

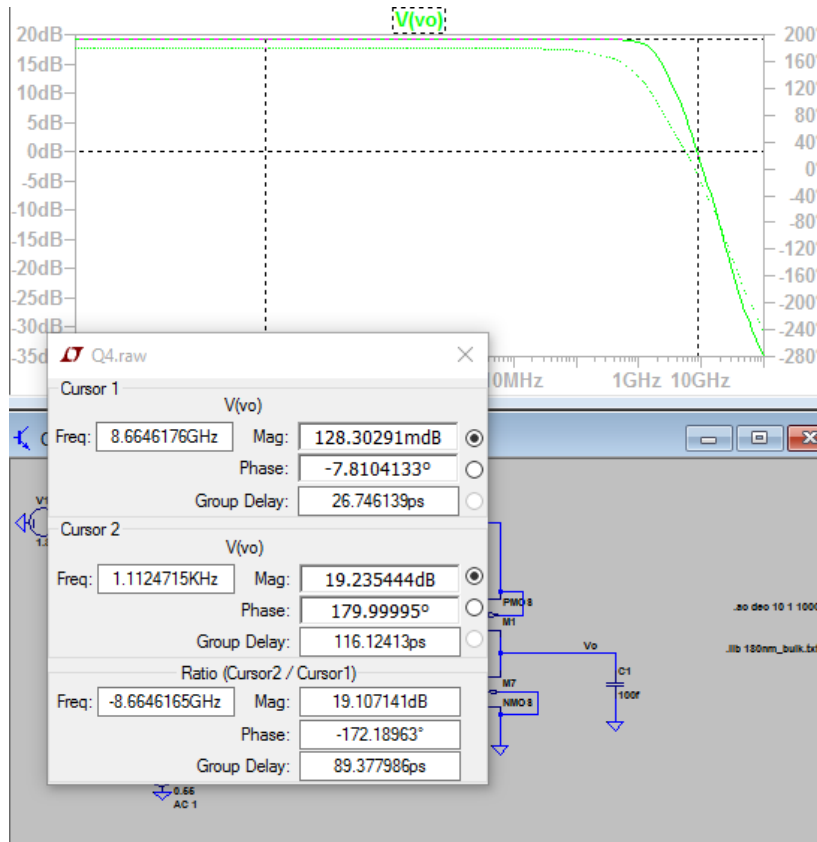4) With no compensation, the phase margin is about -8 degrees.



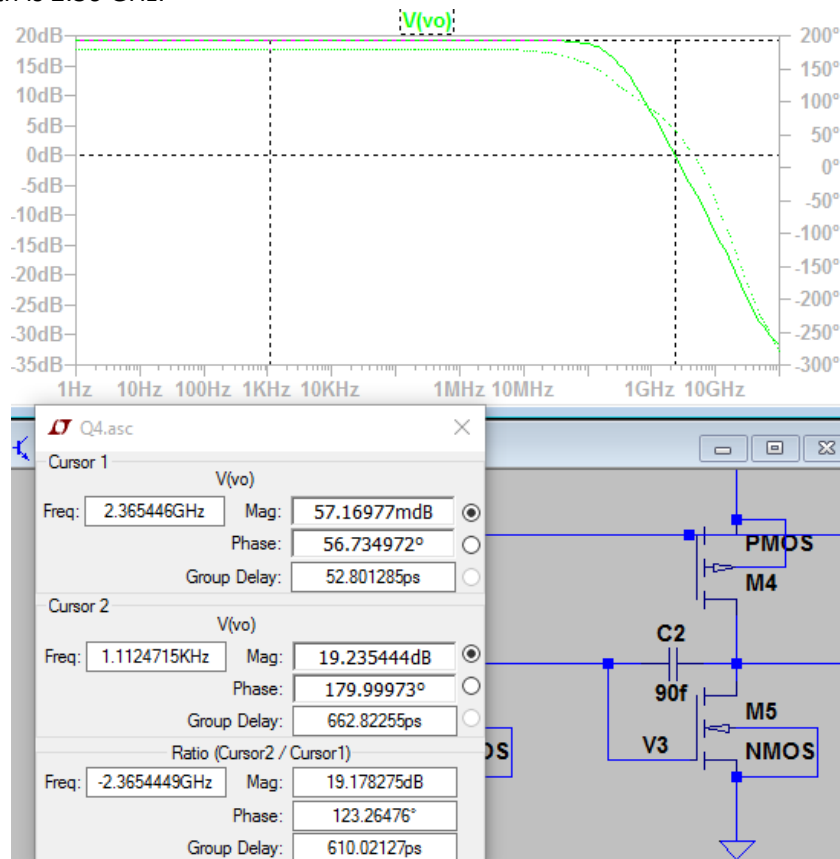If a capacitance of 90 fF is applied between X and Y, phase margin reaches 55 degrees. Under this condition, unity-gain bandwidth is 2.36 GHz.



If a capacitance of 0.9pF is applied between X and the ground, phase margin reaches again 55 degrees. Under this condition, unity-gain bandwidth is 2 GHz.

