


# Memory I: Overview of Semiconductor Memories

- Random Access Memories
- ROMs;
  - ROM
  - Decoders
  - PLA's
  - EEPROM

# Static Random Access

- **Memory Classification**
- **CMOS Static Memory**
  - Six transistor memory cell
  - Memory architecture
  - Decoders
  - Read/write circuitry
- **RMOS Static Memory**
  - Four transistor memory cell
  - Technology
  - Memory cell layout

# Memory Classification

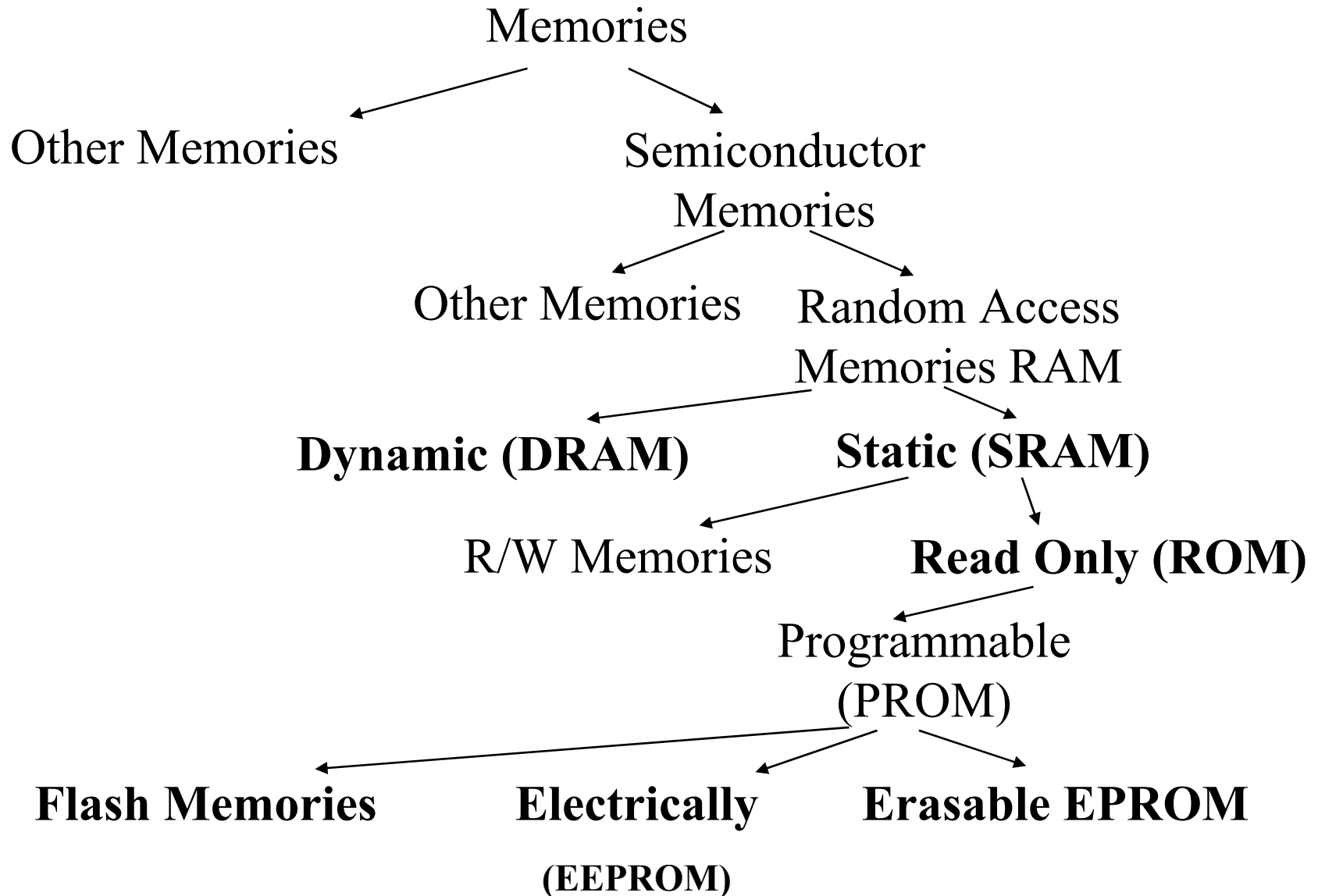

# Memory Classification


## Semiconductor Memories

**Read Only (ROM)    L 23**


**Static (SRAM)            L 23/24**

**Dynamic (DRAM)        L 24**


# Random Access Memories

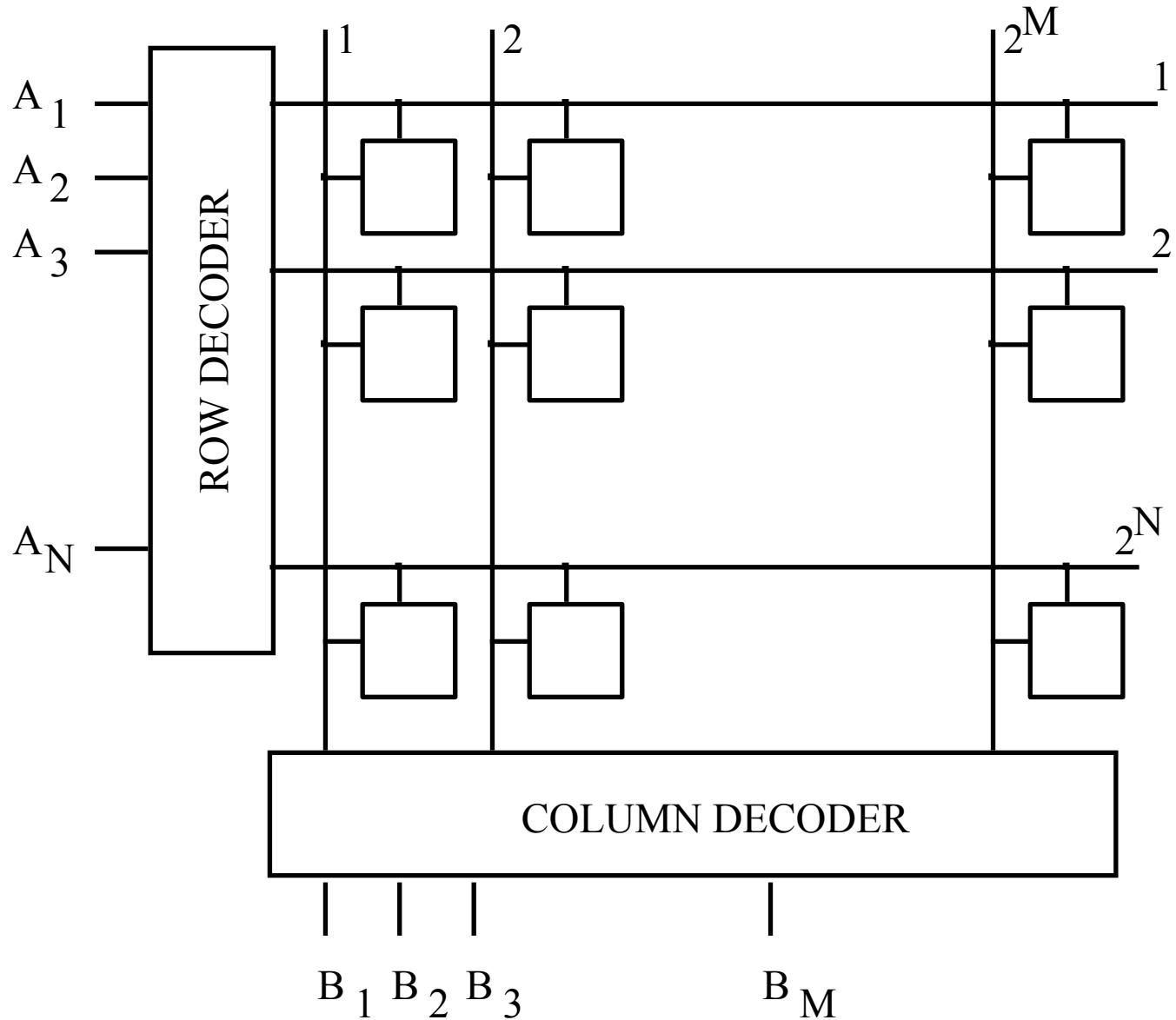


# Read Only Memory (ROM)

 

# Read Only Memory (ROM)

 


# Read Only Memory (ROM)

 




# Row Decoder

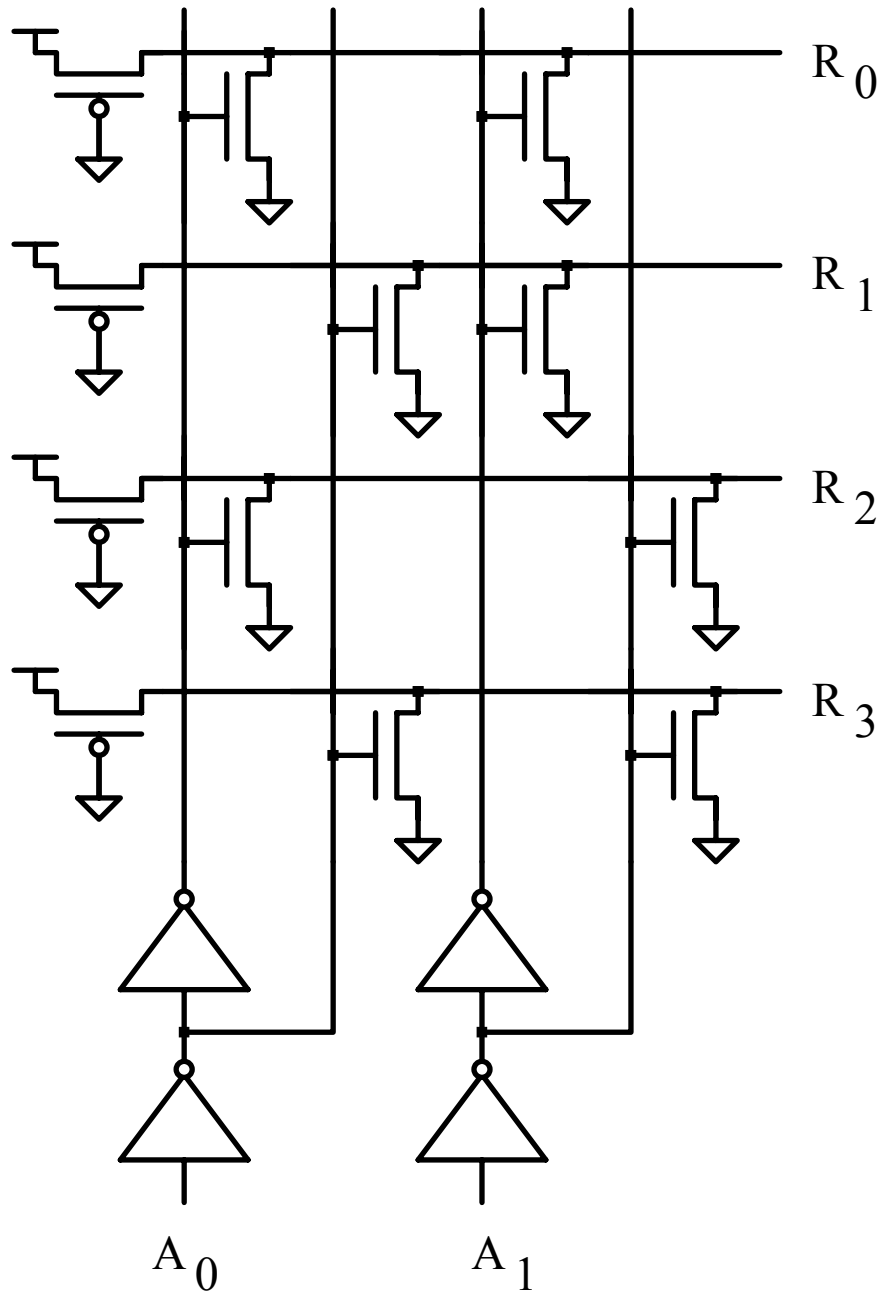


$A_0$   $A_1$   $R_0$   $R_1$   $R_2$   $R_3$



# Column Decoder

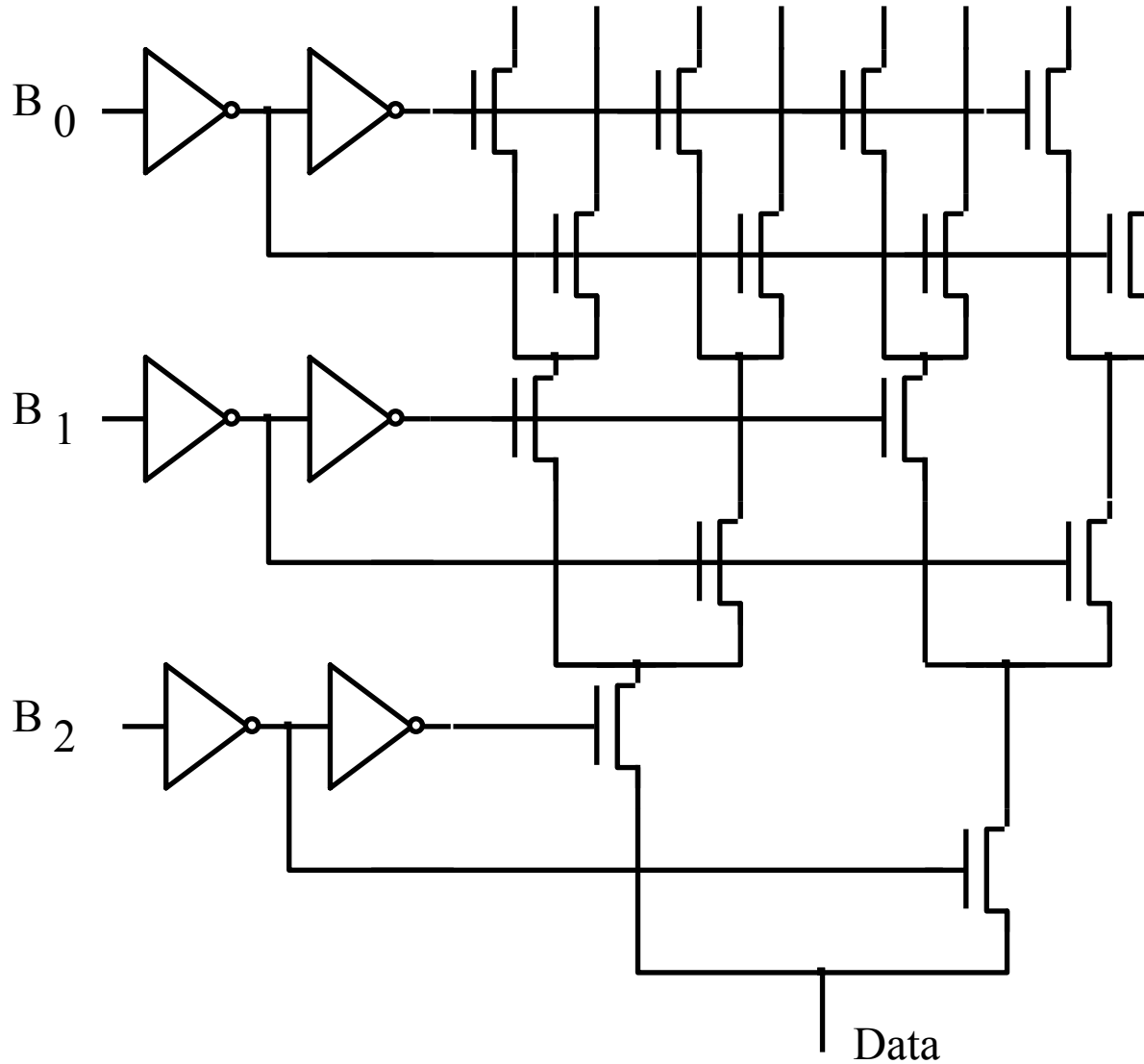

# Column Decoder

 


# Read Only Memory (ROM)

  


# Read Only Memory (ROM)

Active

 


# Read Only Memory (ROM)

Poly

 


# Read Only Memory (ROM)

Metal

 


# Read Only Memory (ROM)

 





# Read Only Memory (ROM)

 


# Read Only Memory (ROM)

 


# Read Only Memory (ROM)

 





# Read Only Memory (ROM)

 


# Read Only Memory (ROM)

 

# Programmable Logic Array (PLA)

    


# Programmable Logic Array (PLA)

 

# PLA

AND

 

B

$\bar{A}$

$$\overline{\overline{A + B}} = AB$$

$$\overline{A + B} = \bar{A} \bar{B}$$


A

B




OR

PLA

 


# PLA

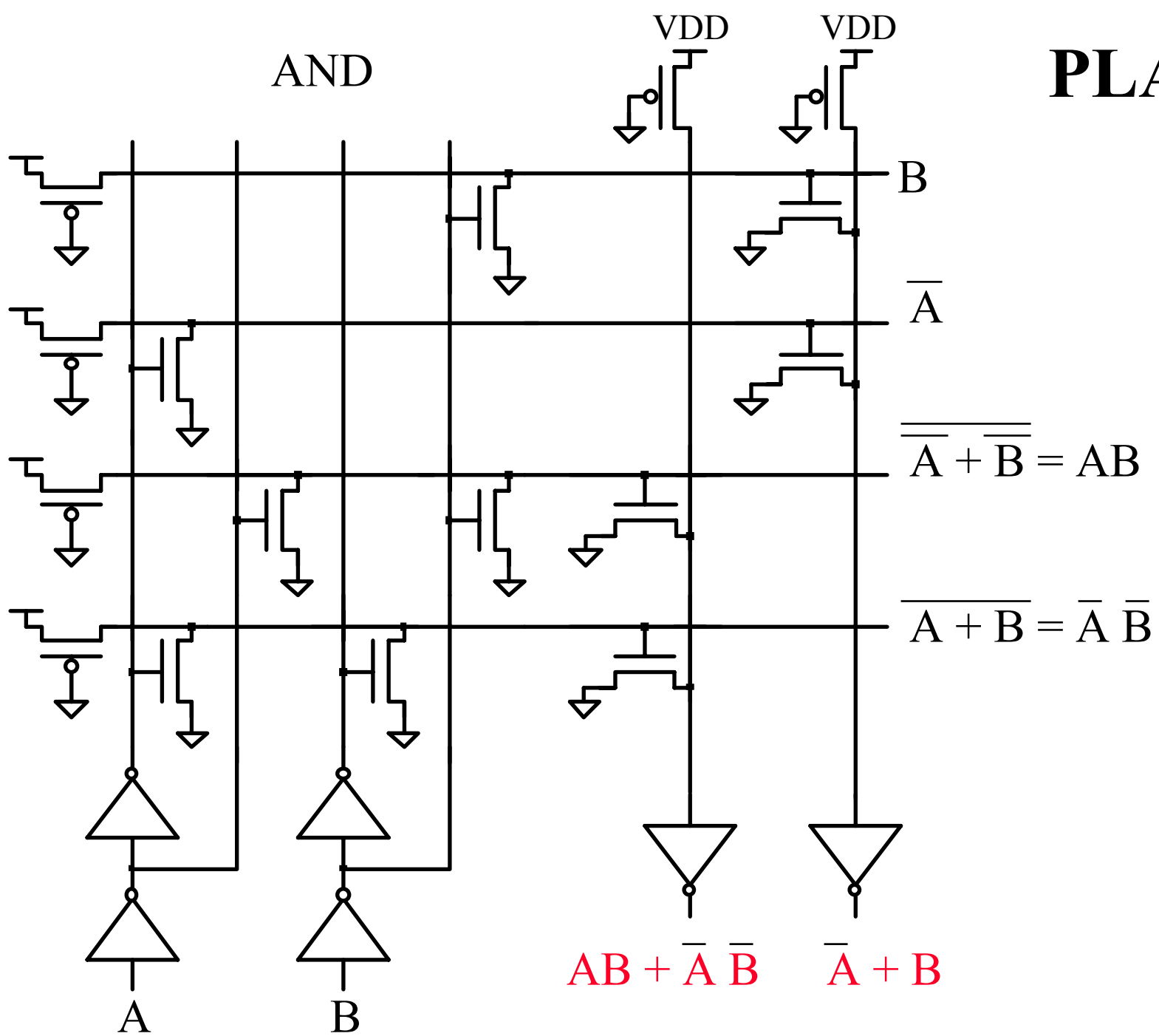


# PLA

Active

 


# PLA

Poly

 


# PLA


Metal

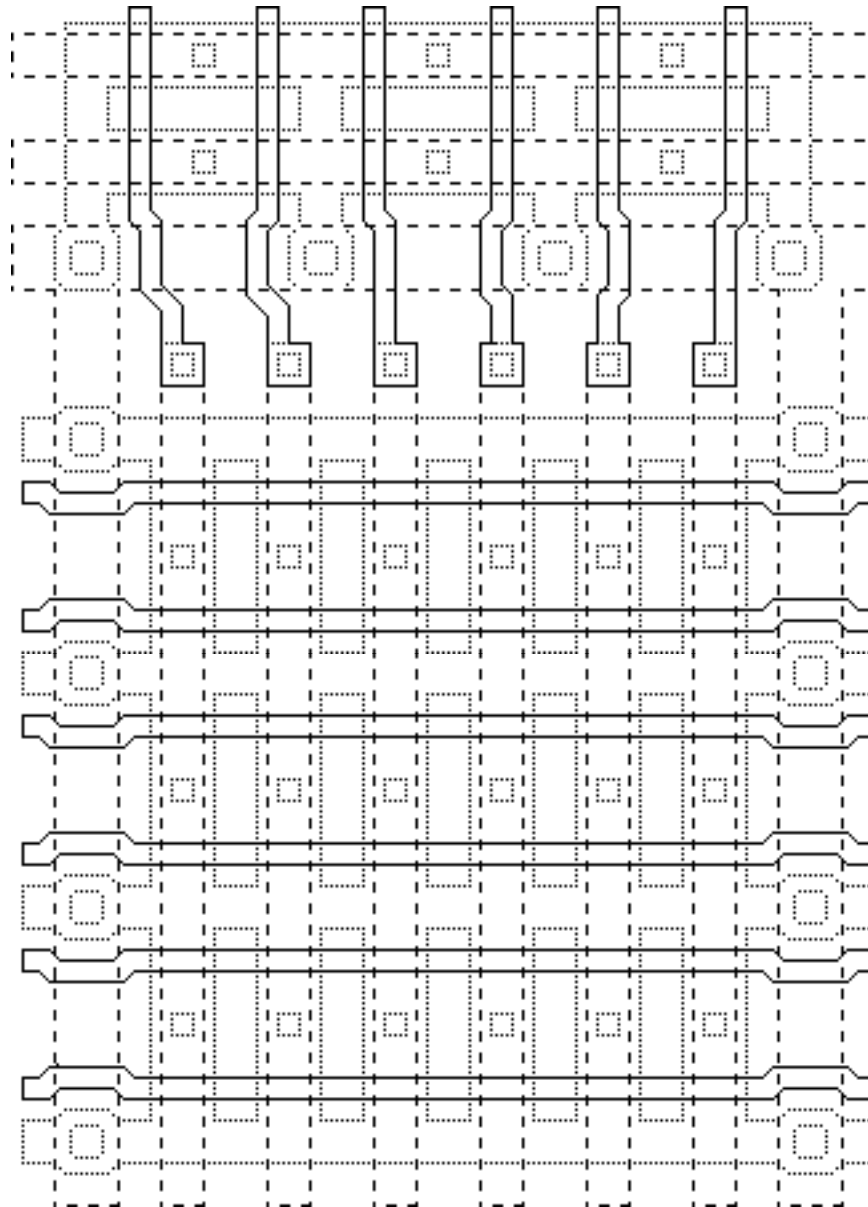


# PLA

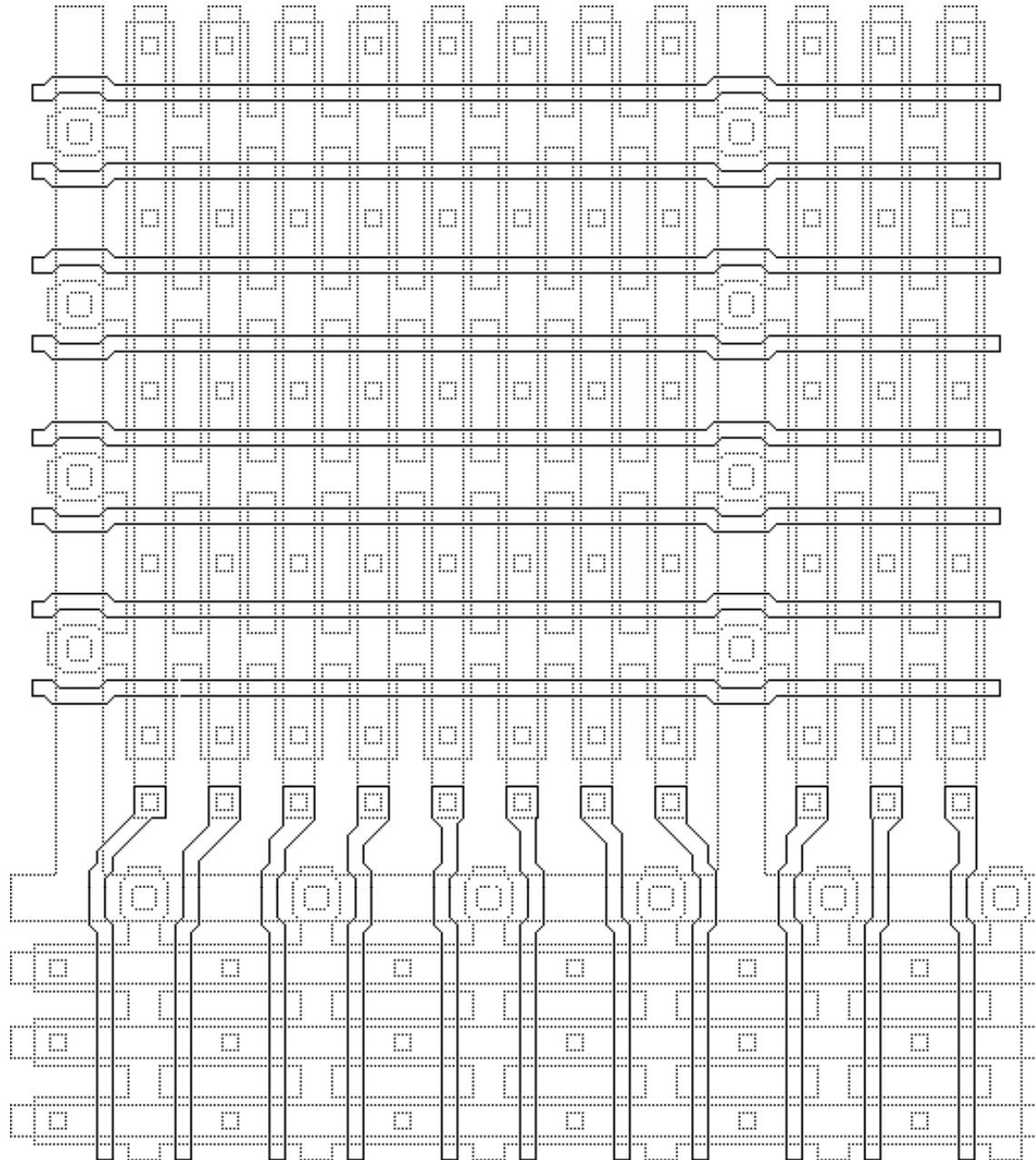

# PLA


 


# PLA

 



# Electrically Programmable

  


Erase --> Apply UV

--> Low  $V_t$  --> Transistor ON when Selected

Program --> CG = High, Drain = High, Source = Low

--> High  $V_t$  --> Transistor OFF when Selected


# Electrically Programmable

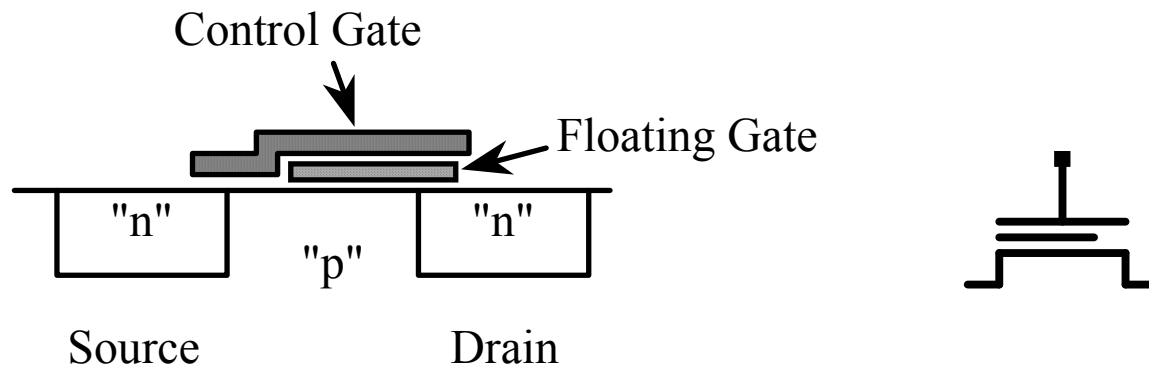

Erase --> CG = High, Drain = Low, Source = Low  
--> High  $V_t$  --> Transistor OFF when Selected

Program --> CG = Low, Drain = High, Source = Low  
--> Low  $V_t$  --> Transistor ON when Selected

# Electrically Programmable

 


# Flash EEPROM

- Same as EEPROMs
- Erased in Single Cycle
- Relatively low number of erase/program cycles

# Static Random Access Memories




- **Memory Classification**
- **CMOS static memory**
  - **Six transistor memory cell**
  - **Memory architecture**
  - **Decoders**
  - **Read/Write circuitry**

# Memory Classification

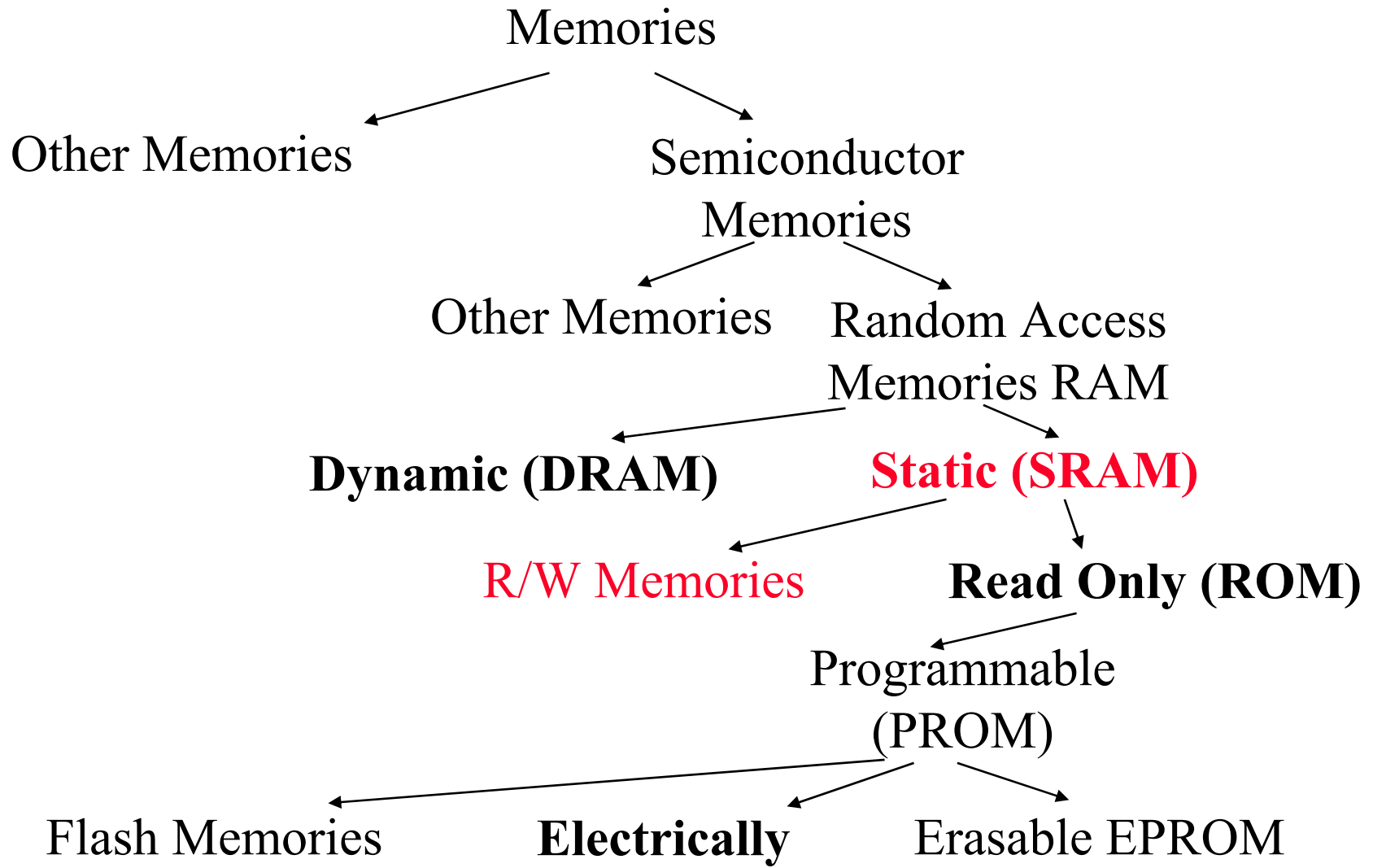





# CMOS static memory

## Six transistor memory cell

   

# CMOS static memory


## Six transistor memory cell

    





# CMOS static memory

## Memory architecture

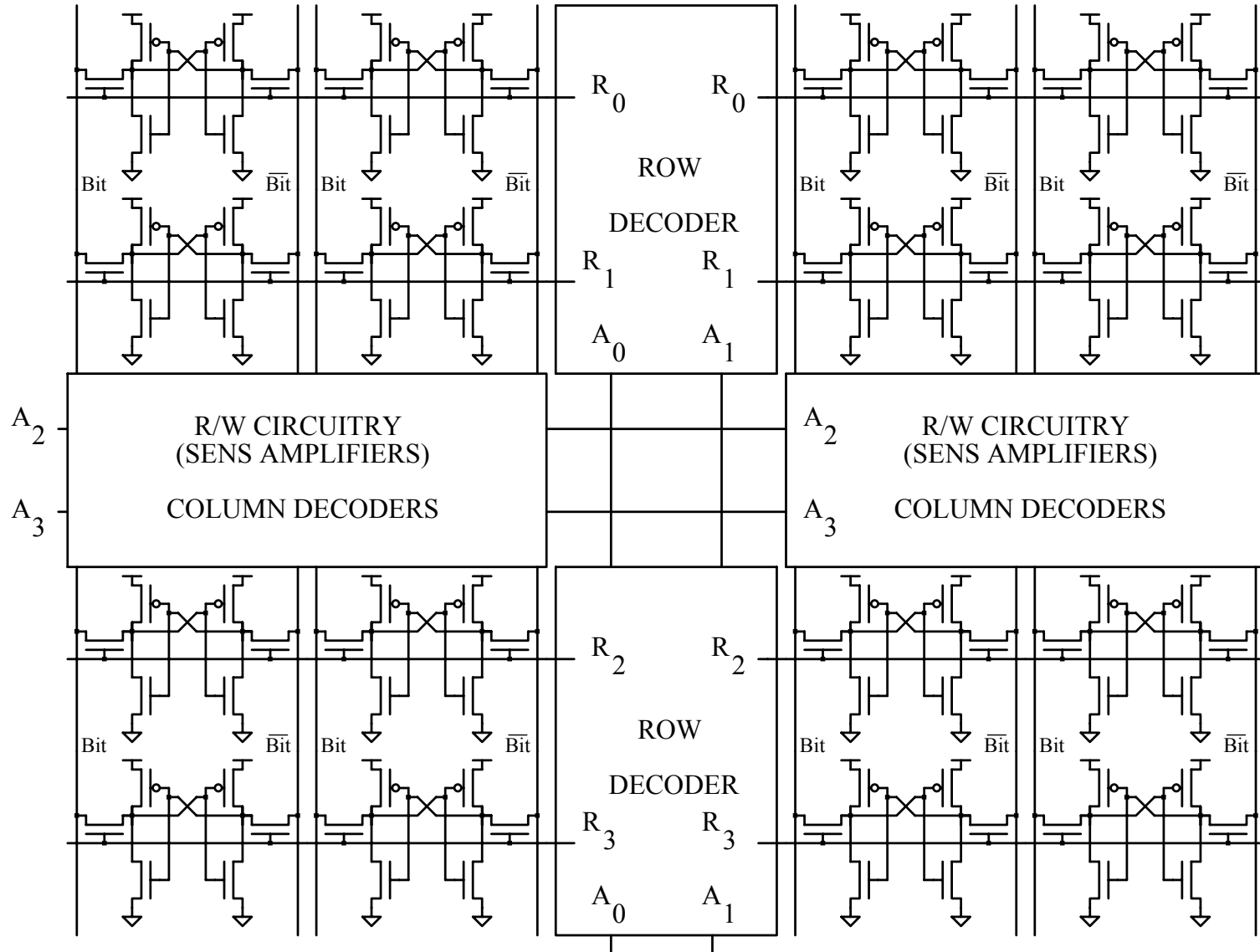


# CMOS static memory

## Decoders

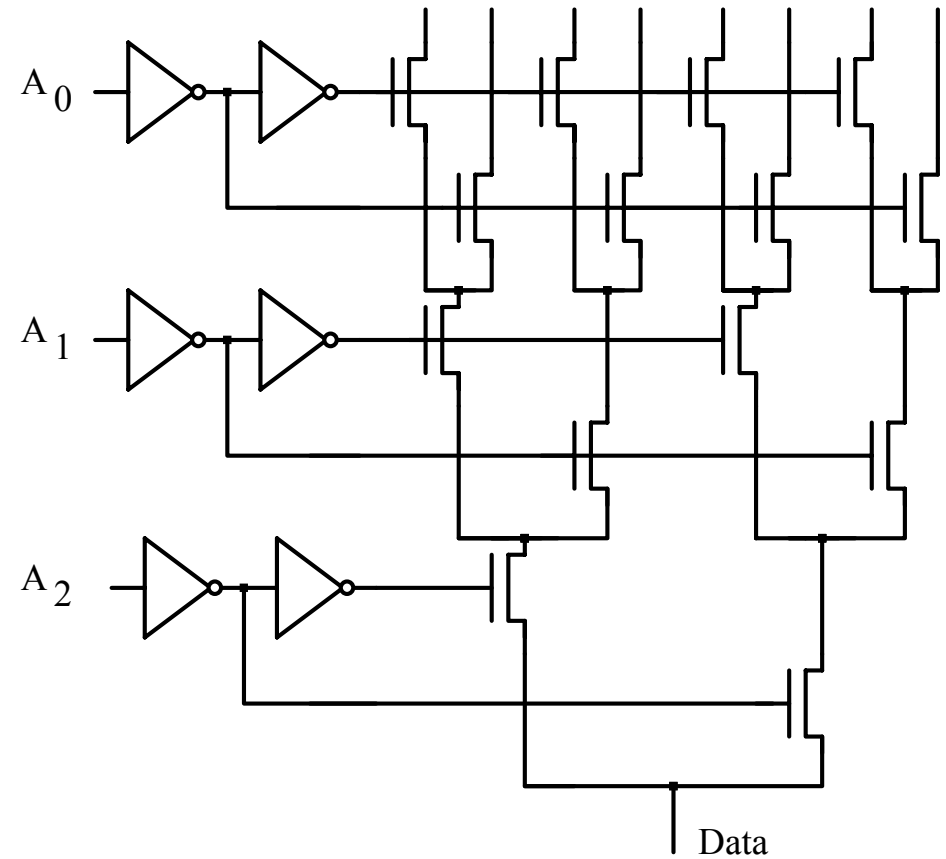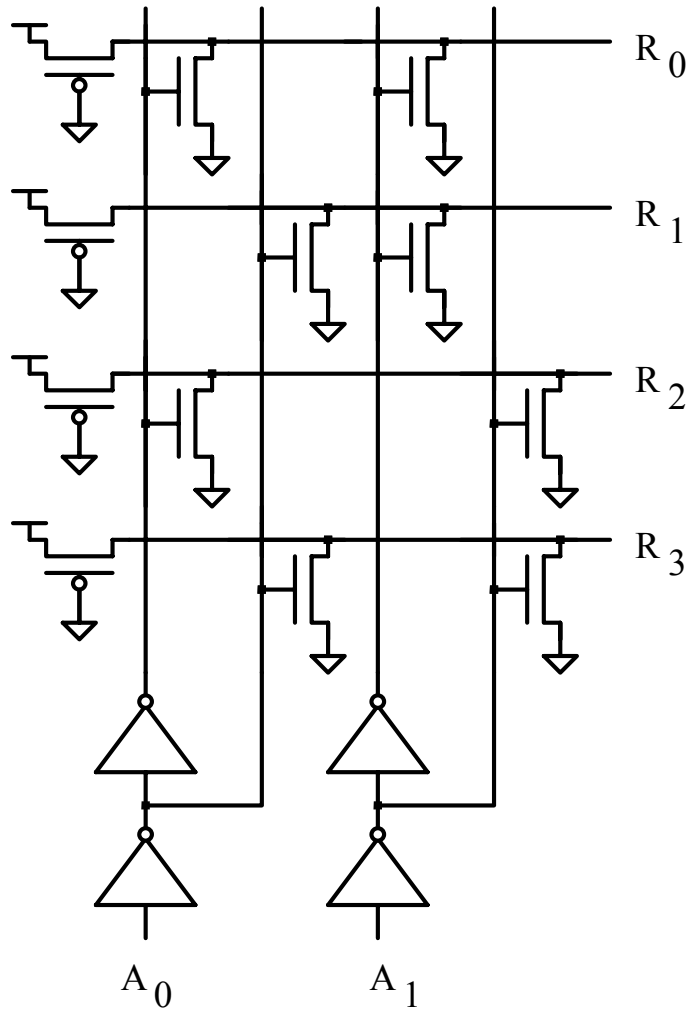


# CMOS static memory

## Read/Write circuitry

 

# CMOS static memory

## Read

 

# CMOS static memory

## Write

