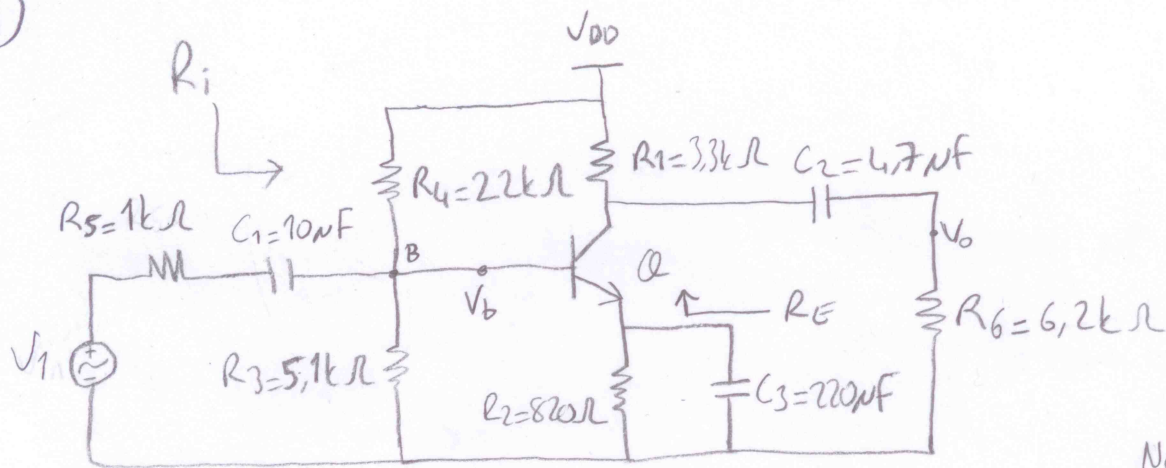


①



$$\begin{aligned} g_m &= 0.072 \text{ A/V} \\ r_\pi &= 2.47 \text{ k}\Omega \\ \beta &= 178 \\ C_\pi &= 66.5 \text{ pF} \\ C_\mu &= 4 \text{ pF} \\ \text{Neglect } C_{cs} \text{ and } r_o. \end{aligned}$$

Draw the frequency response of the circuit.

Solution:

Midband Gain,  $A_o$

$$A_o = \frac{V_b}{V_1} \cdot \frac{V_o}{V_b} = \frac{R_i}{R_i + R_s} \cdot -g_m \cdot R_{out} = -g_{m,55} \quad R_i = R_3 \parallel R_4 \parallel r_\pi = 1.55 \text{ k}\Omega$$

$$(39.5 \text{ dB}) \quad R_{out} = R_1 \parallel R_6 = 2.15 \text{ k}\Omega$$

Due to input coupling capacitor:

$$f_{p1} = \frac{1}{2\pi C_1 (R_5 + R_i)} = 6.25 \text{ Hz}$$

Also, it creates zero at DC.

Due to output coupling capacitor:

$$f_{p2} = \frac{1}{2\pi C_2 (R_1 + R_6)} = 3.56 \text{ Hz}$$

Also, it creates zero at DC.

Due to emitter bypass capacitor:


$$f_z = \frac{1}{2\pi C_3 R_2} = 0.88 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi C_3 R_k} = 40.3 \text{ Hz}$$

$$R_k = R_E \parallel R_2, \quad R_E = \frac{R_5 \parallel R_3 \parallel R_4}{\beta + 1} + r_e$$

$$= 17.9 \Omega \quad = 18.33 \Omega$$

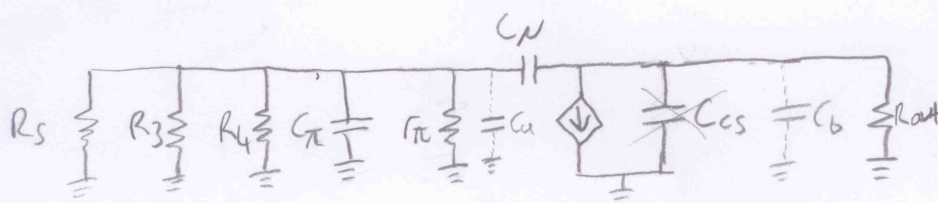High frequency small signal equivalent circuit:



Miller Approximation

$$A_1 = \frac{V_o}{V_b} = -g_m \cdot R_{out} = -155$$

$$C_a = C_\mu (1 - A_1) = 620 \text{ pF}$$

$$C_b = C_\mu \left(1 - \frac{1}{A_1}\right) = 4.02 \text{ pF}$$

①

① Continue

$$f_{Hi} = \frac{1}{2\pi(Ca + C\pi)R_a}$$


$$= 382 \text{ kHz}$$

$R_a$  is the resistance seen from node B:

$$R_a = R_3 // R_4 // R_5 // r_\pi = 607 \Omega$$

$$f_{Ho} = \frac{1}{2\pi \cdot C_b \cdot R_{at}} = 18,4 \text{ MHz}$$
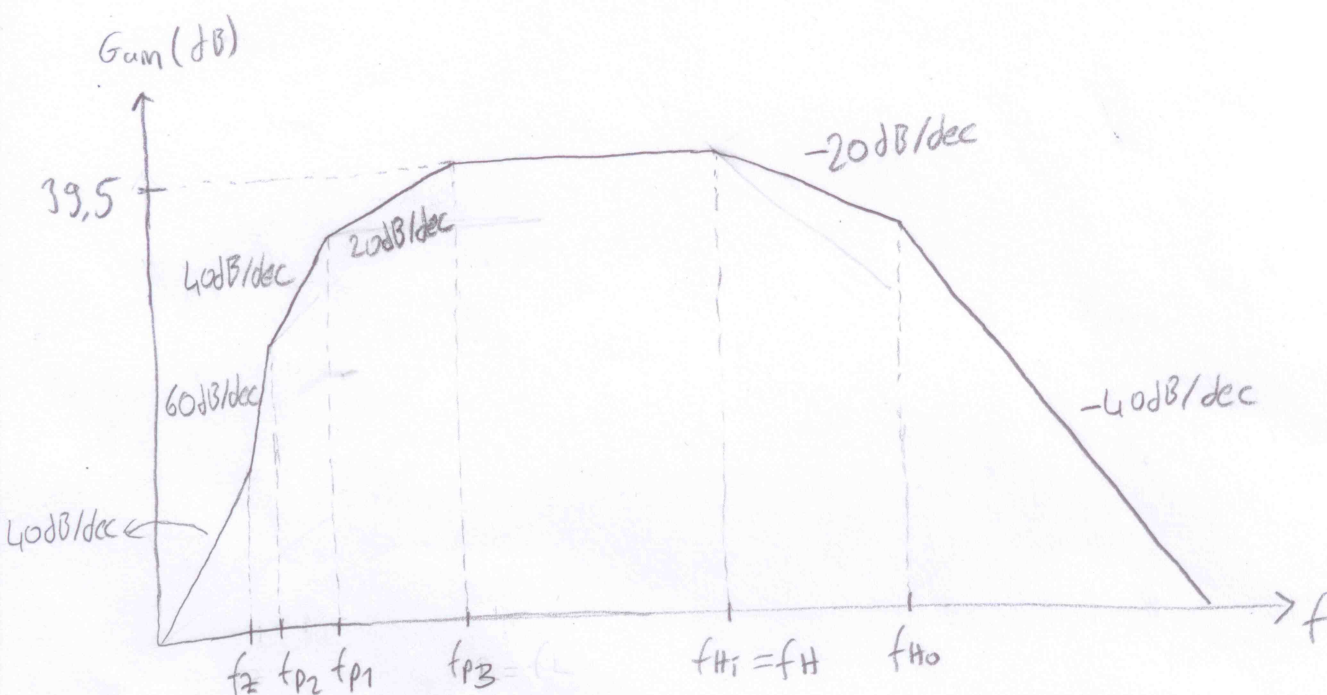
$$A_v = A_o \cdot \frac{s + \omega_z}{s + \omega_{p3}} \cdot \frac{s}{s + \omega_{p1}} \cdot \frac{s}{s + \omega_{p2}} \cdot \frac{\omega_{Hi}}{s + \omega_{Hi}} \cdot \frac{\omega_{Ho}}{s + \omega_{Ho}}$$




There is a dominant pole. So,  $f_{p1} \neq f_{p3}$ .

Therefore,  $f_L = \omega_{p1} + f_{p2} + f_{p3} - 2f_2 =$

$$\frac{1}{f_1} + \frac{1}{f_2}$$



2

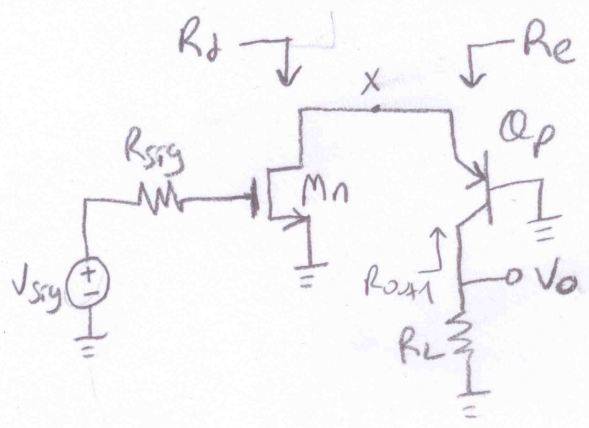

$R_{sig} = 10k\Omega$   
 $R_L = 100k\Omega$

For  $M_n$

$I_D = 0,25\text{ mA}$   
 $k = 1,28\text{ mA/V}^2$   
 $f_T = 400\text{ MHz}$   
 $\lambda = 1/(15\text{ V})$   
 $C_{gd} = C_{db} = 25\text{ fF}$

For  $Q_p$

$\beta = 200$   
 $V_A = 50\text{ V}$   
 $C_p = C_s = 0,25\text{ pF}$   
 $I_C = 0,25\text{ mA}$   
 $f_T = 400\text{ MHz}$

- a) Find the low-frequency gain.
- b) Estimate upper corner frequency for the folded-cascode circuit using open circuit time constant method.

Solution:

a)  $M_n$ :  $g_{mn} = \sqrt{2kI_D} = \sqrt{2 \cdot 1,28 \cdot 0,25} = 0,8\text{ mA/V}$       $r_{on} = \frac{1}{\lambda I_D} = \frac{15\text{ V}}{0,25\text{ mA}} = 60k\Omega$


$C_{gs} = \frac{g_{mn}}{2\pi f_T} - C_{gd} = \frac{0,8 \cdot 10^{-3}}{2\pi \cdot 4 \cdot 10^8} - 25 \cdot 10^{-15} = 293\text{ fF}$

$Q_p$ :  $g_{mp} = \frac{I_C}{V_{Tn}} = \frac{0,25\text{ mA}}{25\text{ mV}} = \frac{1}{104\Omega}$       $r_{\pi} = \frac{\beta}{g_{mp}} = 200 \cdot 104 = 20,8\text{ k}\Omega$

$r_{op} = \frac{V_A}{I_C} = \frac{50\text{ V}}{25\text{ mA}} = 200\text{ k}\Omega$       $r_{ep} = \frac{r_{\pi}}{\beta+1} = \frac{20,8k}{201} = 103,5\Omega$

$C_{\pi} = \frac{g_{mp}}{2\pi f_T} - C_p = \frac{1}{104 \cdot 2\pi \cdot 4 \cdot 10^8} - 0,25 \cdot 10^{-12} = 3,58\text{ pF}$

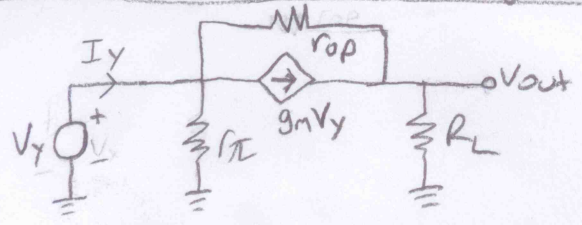Equivalent resistance seen looking down to emitter,  $R_e$



$(I_Y - g_m V_Y - \frac{V_Y}{r_{\pi}}) r_{op} + (I_Y - \frac{V_Y}{r_{\pi}}) R_L = V_Y$

$R_e = \frac{V_Y}{I_Y} = \frac{r_{op} + R_L}{1 + \frac{r_{op} + R_L}{r_{\pi}} + g_m r_{op}} \approx 155\Omega$


$R_d = r_{on} \Rightarrow R_x = R_d \parallel R_e \approx 155\Omega$

$\frac{V_x}{V_{sig}} = -g_{mn} \cdot R_x = -0,124$

3

② Continue

## Output Resistance, $R_{out}$

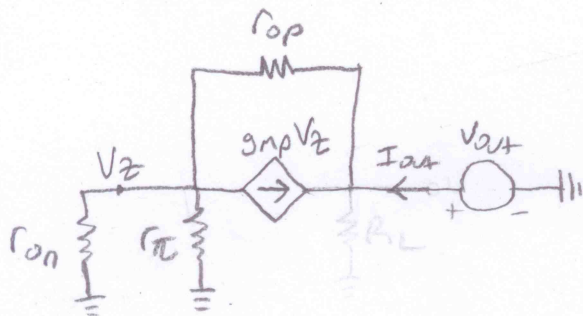

$$I_{out} \cdot r_{on} \parallel r_{\pi} + (I_{out} + g_m V_z) r_{op} = V_{out}$$


$$V_z = I_{out} \cdot r_{on} \parallel r_{\pi}$$

$$\frac{V_{out}}{I_{out}} = R_{out1} = r_{on} \parallel r_{\pi} + r_{op} + g_m \cdot r_{on} \parallel r_{\pi} \cdot r_{op}$$


$$R_{out} = R_L \parallel R_{out1} = \frac{V_{out}}{V_x} = \frac{R_{out}}{R_e} = 643$$

$$A_0 = \frac{V_x}{V_{sig}} \cdot \frac{V_{out}}{V_x} = -79,7$$

b)

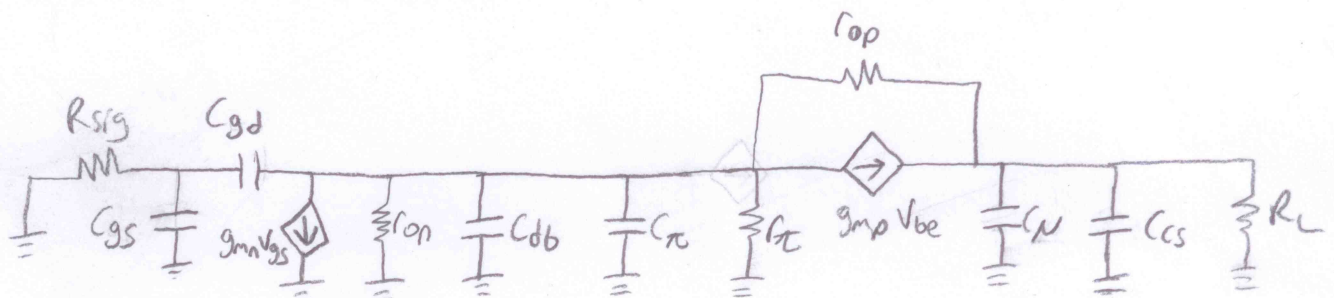


$\tau_{gs} \Rightarrow$

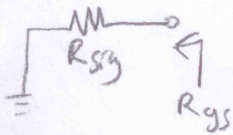

$$\tau_{gs} = R_{sig} \cdot C_{gs} = 2,93 \text{ ms}$$

$\tau_{gd} \Rightarrow$

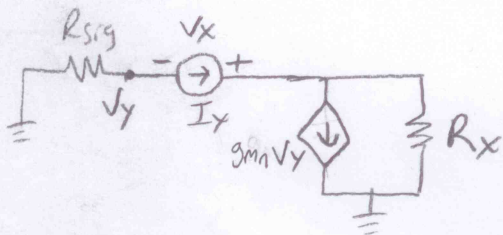


$$V_y = -R_{sig} \cdot I_x$$

$$(I_x - g_m V_y) R_x = V_x + V_y$$

$$\frac{V_x}{I_x} = R_{gd} = R_{sig} + R_x + g_m R_x R_{sig}$$


$$\tau_{gd} = R_{gd} \cdot C_{gd} = 0,285 \text{ ms}$$

$\tau_x \Rightarrow$

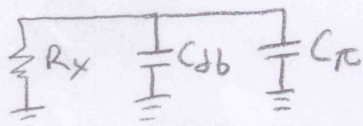

$$\tau_x = R_x \cdot (C_{db} + C_{\pi}) = 0,559 \text{ ms}$$

$\tau_o \Rightarrow$

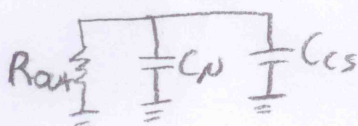


$$\tau_o = R_{out} (C_{\mu} + C_{cs}) = 49,8 \text{ ms}$$

$$f_{-3dB} = \frac{1}{2\pi \tau_{gs} + \tau_{gd} + \tau_x + \tau_o} = 3 \text{ MHz}$$



3

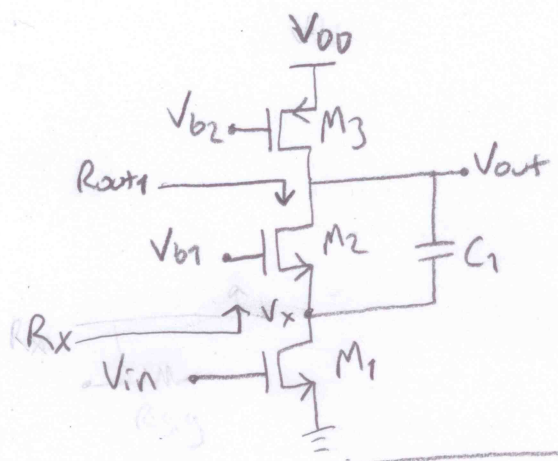


Assume internal capacitance of transistors are negligible compared to  $C_1$ .

$$\lambda > 0$$

Find poles of the circuit by Miller's approximation.

Solution:

Applying Miller's approximation

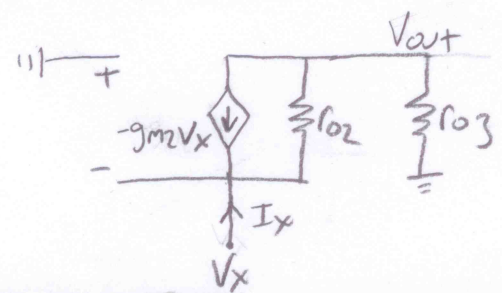

$$-(I_x - g_{m2}V_x)r_{o2} + V_x = V_{out}$$

$$I_x = \frac{V_{out}}{r_{o3}} \quad A_2 = \frac{V_{out}}{V_x} = \frac{g_{m2}r_{o2}r_{o3} + r_{o3}}{r_{o3} + r_{o2}}$$


$$C_x = C_1 \cdot (1 - A_2) \quad C_{out} = C_1 \cdot \left(1 - \frac{1}{A_2}\right)$$

Calculating  $R_x$

$$(I_x - g_{m2}V_x)r_{o2} + I_x r_{o3} = V_x \Rightarrow R_x = \frac{r_{o2} + r_{o3}}{1 + g_{m2}r_{o2}}$$

$$\omega_{p1} = \frac{1}{C_x(R_x \parallel r_{o1})}$$

Calculating  $R_{out1}$

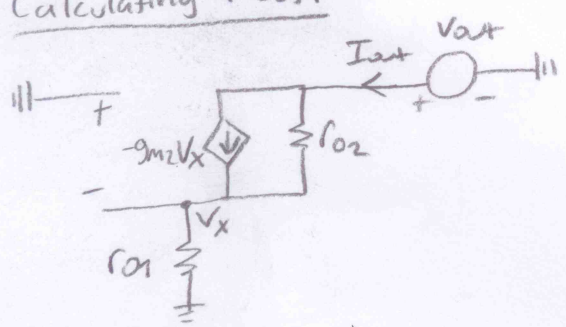


$$V_x = I_{xt} \cdot r_{o1}$$

$$r_{o2} \cdot I_{xt} + g_{m2}V_x \cdot r_{o2} + I_{xt} r_{o1} = V_{out}$$

$$R_{out1} = \frac{V_{out}}{I_{xt}} = g_{m2}r_{o1}r_{o2} + r_{o1} + r_{o2}$$
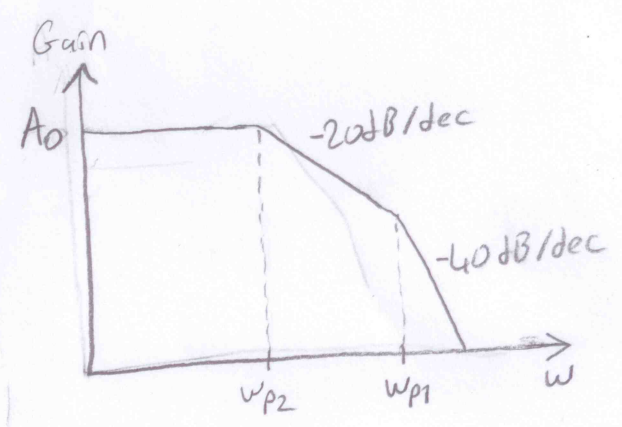
$$R_{out} = R_{out1} \parallel r_{o3} \Rightarrow \omega_{p2} = \frac{1}{C_{out} \cdot R_{out}}$$



5