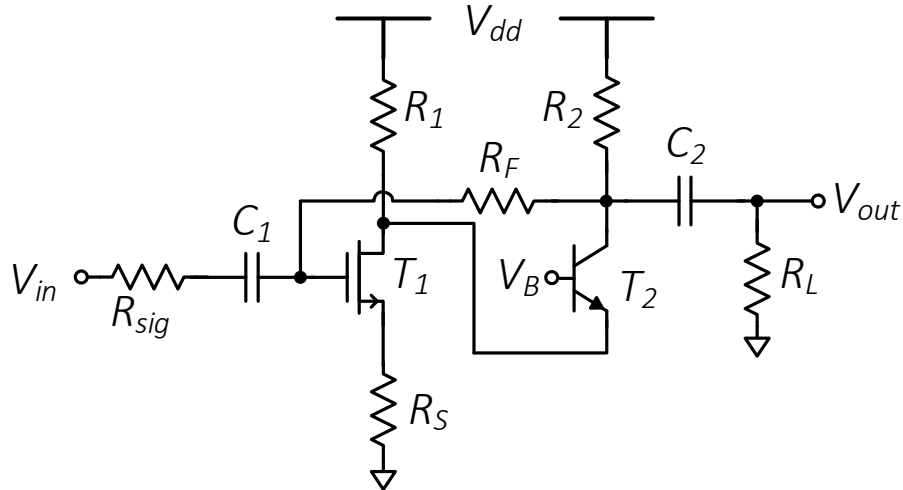


10 December 2020

2) In the amplifier below, $C_1 = 10 \mu F$ and $C_2 = 0.1 \mu F$ are coupling capacitors. Consider $g_{m1} = 10 mS$, $g_{m2} = 2 mS$, $R_F = 50 k\Omega$, $R_{sig} = 150 \Omega$, $R_S = 100 \Omega$, $R_1 = 1 k\Omega$, and $R_2 = R_L = 40 k\Omega$. Assume $V_A = \infty$ and $\lambda = 0$. You can write the voltage gain expressions by properly indicating to what they correspond.



- Find the lower corner frequency (-3 dB) expression of the cascaded amplifier by first applying the Miller Effect followed by the short-circuit time constants method.
- If an ideal (zero rise time) periodic pulse with an on-time of $T_D = 1 ms$ is applied at the input of the amplifier, find the tilt observed in the output signal.