

The circuit whose state diagram is shown in Figure 1 will be designed using D-type flip-flops and AND (VE), OR (VEYA), NOT (TÜMLEME). ($Q = D$)

- 1) What kind of state machine is the circuit? Why?
- 2) Draw the state transition table of the circuit using the codes shown above the states.
- 3) Find the reduced Boolean functions for flip-flop inputs and outputs.

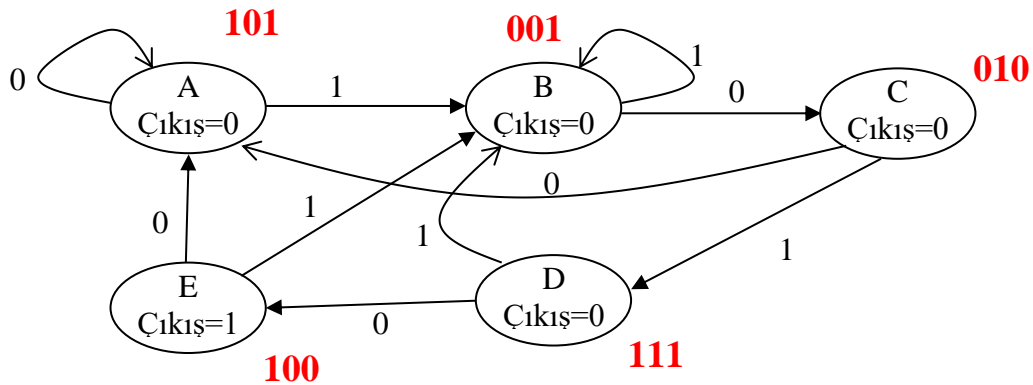


Figure 1