



ISTANBUL TECHNICAL UNIVERSITY

Digital System Design & Applications

If/else & case

RES. ASST. FIRAT KULA & RES. ASST. BILGI GÖRKEM YAZGAÇ

if-else Statement

```
if(<conditional_expression1>)
  begin
    ...
    <procedural_statement1>;
  end
else if(<conditional_expression2>)
  ...
  <single_statement2>;
...
else
  begin
    ...
    <procedural_statement3>;
  end
```

- Used to make a decision whether the statements within the block should be executed or not
- if conditional expression is true, execute all statements within particular block
- if false ('0','x','z'), particular block won't be executed
- If there is 'optional' **else** statement, it will be executed in case of false conditional expression
- If-else structure corresponds to MUX

Can only be used within a procedural statement (always or initial blocks)
For non-procedural coding styles, we use **? :** operator

```

always @ (*)
begin
    if(IN & ENABLE)
    begin
        OUT = 2'b01;
    end
    else
        OUT = 'b10; // If only one statement is written, |
                    // begin-end encapsulation might be discarded
    end
end


```

```

assign OUT = (ENABLE & IN) ? 2'b01 : 2'b10;
//      condition    if_true    if_false

```

Non-procedural equivalent

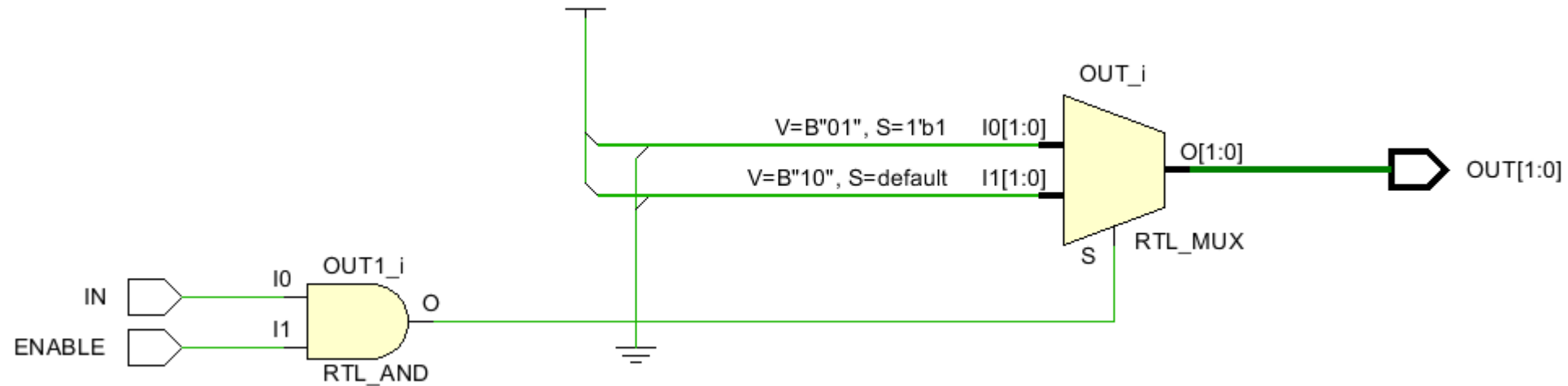

An if-else pair corresponds to a MUX structure

if-else Statement

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 exor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	

- For given truth table
 - Let inputs I3 and I2 be used as conditions:
 - When they are both zero, we see that the function works as **I0 and I1**
 - When I3=0 and I2=1, we see that the function works as **I0 or I1**
 - When I3=1 and I2=0, we see that the function works as **I0 xor I1**
 - Otherwise, F = 1.

if-else Statement

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 exor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	

```

module function_F(I,F);
    input [3:0] I;
    output reg F;

    always @ (I)
    begin
        if( {I[3],I[2]} == 2'd0 )
            F = I[1] & I[0];
        else if( {I[3],I[2]} == 2'd1 )
            F = I[1] | I[0];
        else if( I[3]==1 && I[2]==1'b0 ) // Alternative!
            F = I[1] ^ I[0];
        else
            F = 1'b1;
    end
endmodule

```

if-else Statement

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 exor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	

```

`timescale 1ns / 1ps
module conditional_test;
wire O;
reg [3:0] I;

                                # run 1000ns

initial
    $monitor($time, "I=%b: O=%b",I,O);

conditional_if c1(.I(I),.F(O));

initial
begin

    I=4'b0000; #20;
    I=4'b0001; #20;
    I=4'b0010; #20;
    I=4'b0011; #20;
    I=4'b0100; #20;
    I=4'b0101; #20;
    I=4'b0110; #20;
    I=4'b0111; #20;
    I=4'b1000; #20;
    I=4'b1001; #20;
    I=4'b1010; #20;
    I=4'b1011; #20;
    I=4'b1100; #20;
    I=4'b1101; #20;
    I=4'b1110; #20;
    I=4'b1111; #20;

end

endmodule

```

0I=0000: O=0
20I=0001: O=0
40I=0010: O=0
60I=0011: O=1
80I=0100: O=0
100I=0101: O=1
120I=0110: O=1
140I=0111: O=1
160I=1000: O=0
180I=1001: O=1
200I=1010: O=1
220I=1011: O=0
240I=1100: O=1
260I=1101: O=1
280I=1110: O=1
300I=1111: O=1


```

module function_F(I,F);
    input [3:0] I;
    output reg F;

    always @ (I)
    begin
        if( {I[3],I[2]} == 2'd0 )
            F = I[1] & I[0];
        else if( {I[3],I[2]} == 2'd1 )
            F = I[1] | I[0];
        else if( I[3]==1 && I[2]==1'b0 ) // Alternative!
            F = I[1] ^ I[0];
        else
            F = 1'b1;
    end
endmodule

```

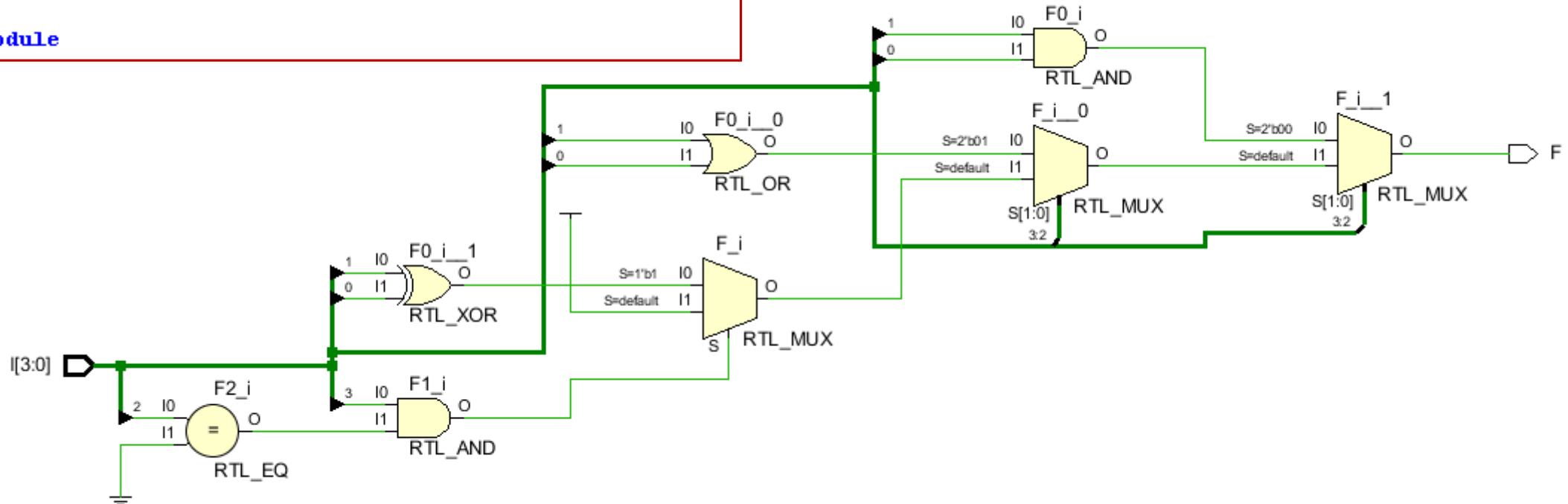if-else if-else chains correspond to **priority mux structure**




Nested if-else Example

```
module example1
(
    input [1:0] SEL,
    input [1:0] IN,
    input ENABLE,
    output reg [1:0] OUT
);

always @ (*)
begin
    if(SEL==2'b11)
    begin
        if(ENABLE) OUT = IN[0] + IN[1]; //Nested if-else
        else OUT = 0;
    end
    else if(SEL==2'b01)
    begin
        OUT[0]= IN[1] & IN[0];
        OUT[1]= IN[1] ^ IN[0];
    end
    else
        OUT = 0;
    end
endmodule
```


Nested if-else Example

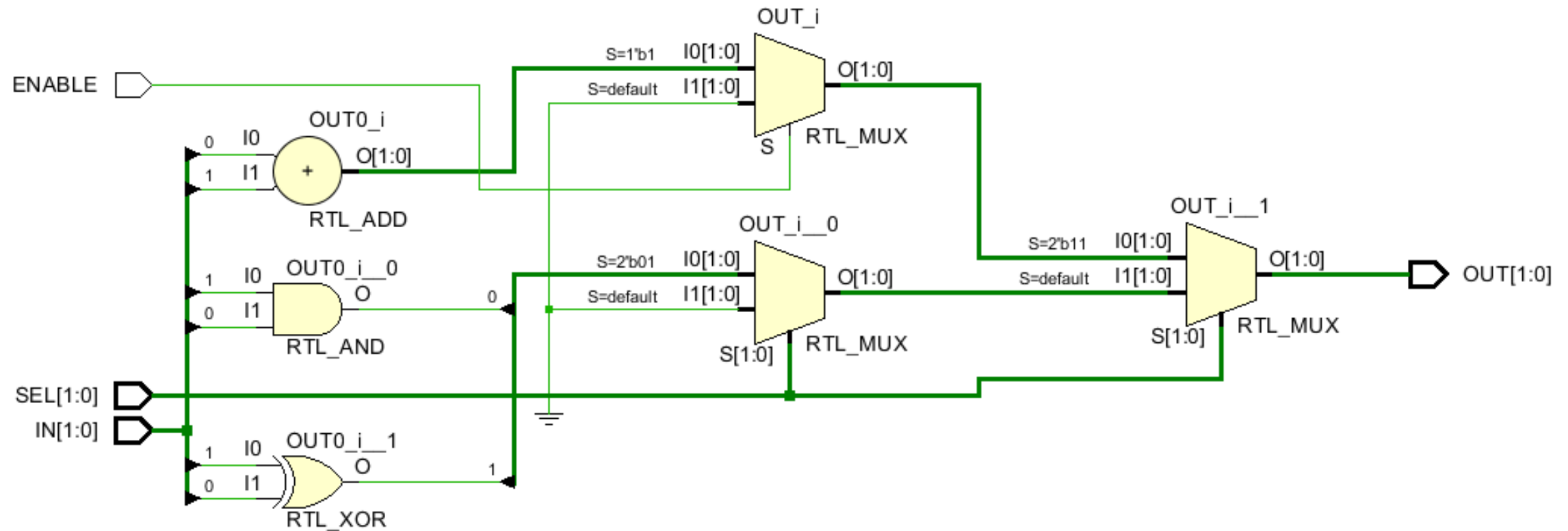

“if” without “else”

- ❑ While coding combinational logic, **if statements without elses** will produce **latches**. This should be avoided.
- ❑ Latches are mostly unintentional and caused by incomplete conditional assignments (forgetting to define outputs for certain possible input cases)
- ❑ Latches cause timing and routing complications in FPGAs. Design tools usually throw a warning if they detect an inferred latch.
- ❑ Note that latches only appear while coding combinational logic with procedural statements.

```
module example2
(
    input [1:0] SEL,
    input [1:0] IN,
    input ENABLE,
    output reg [1:0] OUT
);


always @ (*)
begin
    if(ENABLE)
    begin
        if(SEL==2'b11)
        begin
            OUT = IN[0] + IN[1];
        end

        else if(SEL==2'b01)
        begin
            OUT[0]= IN[1] & IN[0];
            OUT[1]= IN[1] ^ IN[0];
        end


        else
            OUT = 0;
    end
end

endmodule
```

“if” without “else”

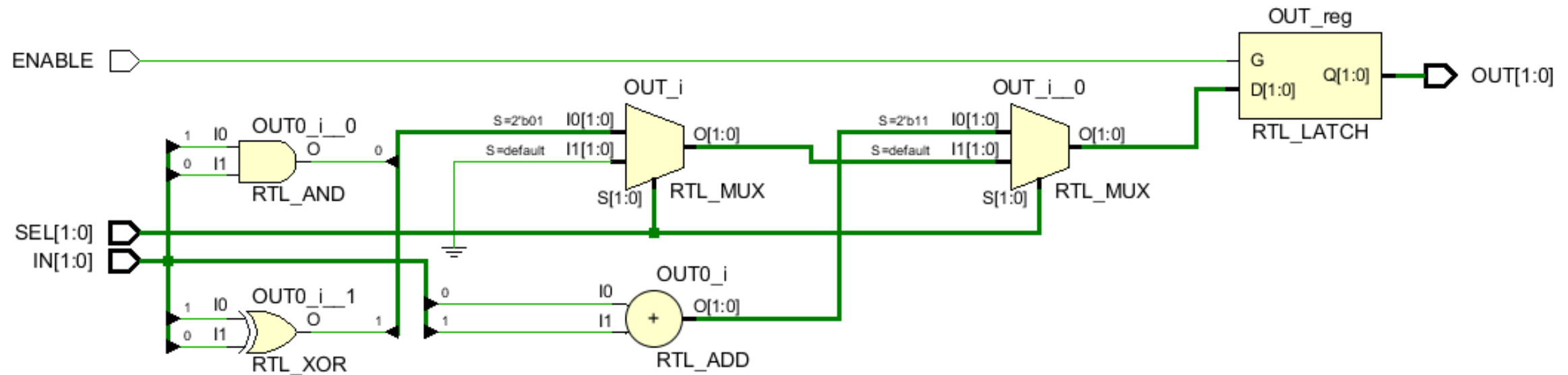

Resulting RTL schematic...

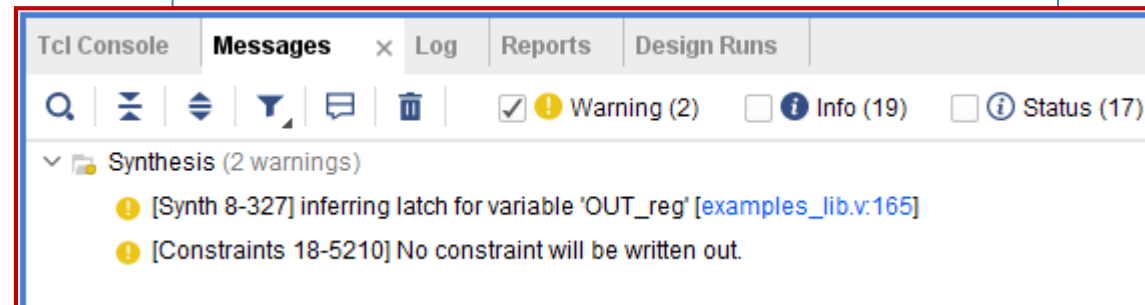

Tool throwing a warning...

case Statement

```
case(<expression>
    alternativel: <single_statement1>;
    alternative2:
        begin
            <procedural_statement2>;
        end
    ....
    default: <single_statement>
endcase
```

- When there are many possible alternatives case is more suitable for reading
- The value of the expression and each alternative are compared bit by bit
- When there are more possible variations than number of alternatives 'optional' **default** statement should be used.

case Statement

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 exor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	


```

module conditional_case(I,F);
input [3:0] I;
output reg F;

always @(I)
    case({I[3],I[2]})
        2'd0:F=I[1]&I[0];
        2'd1:F=I[1]|I[0];
        2'd2:F=I[1]^I[0];
        default:F=1'b1;
    endcase
endmodule

```

case Statement

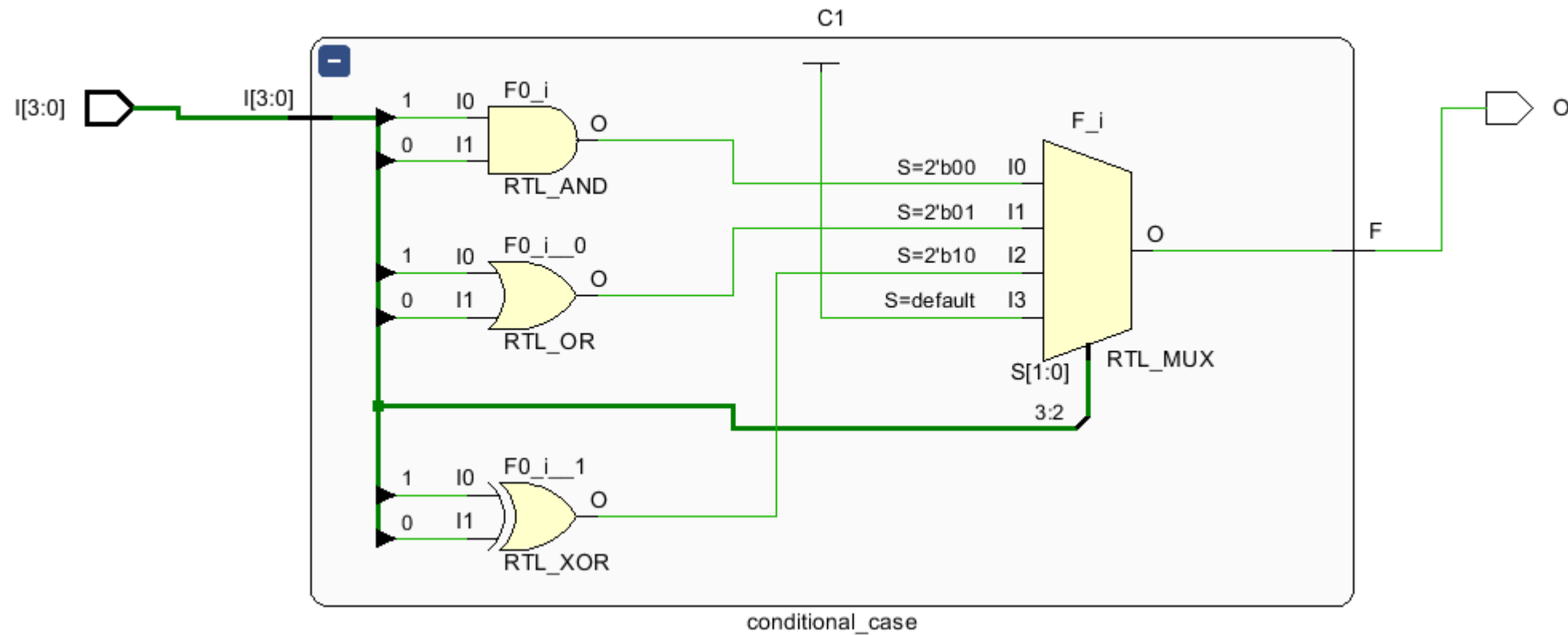

case Statement – Missing cases

```

module example5
(
    input [1:0] IN,
    output reg O1,O2


);

always @ (*)
begin
    case( IN)
        0:
            begin
                O1 = 1;
                O2 = 1;
            end
        1:
            begin
                O1 = 1; O2 = 0;
            end
        2:
            begin
                O1 = 0;
            end

        // Missing case 3:
        // Missing default

    endcase
end
endmodule

```

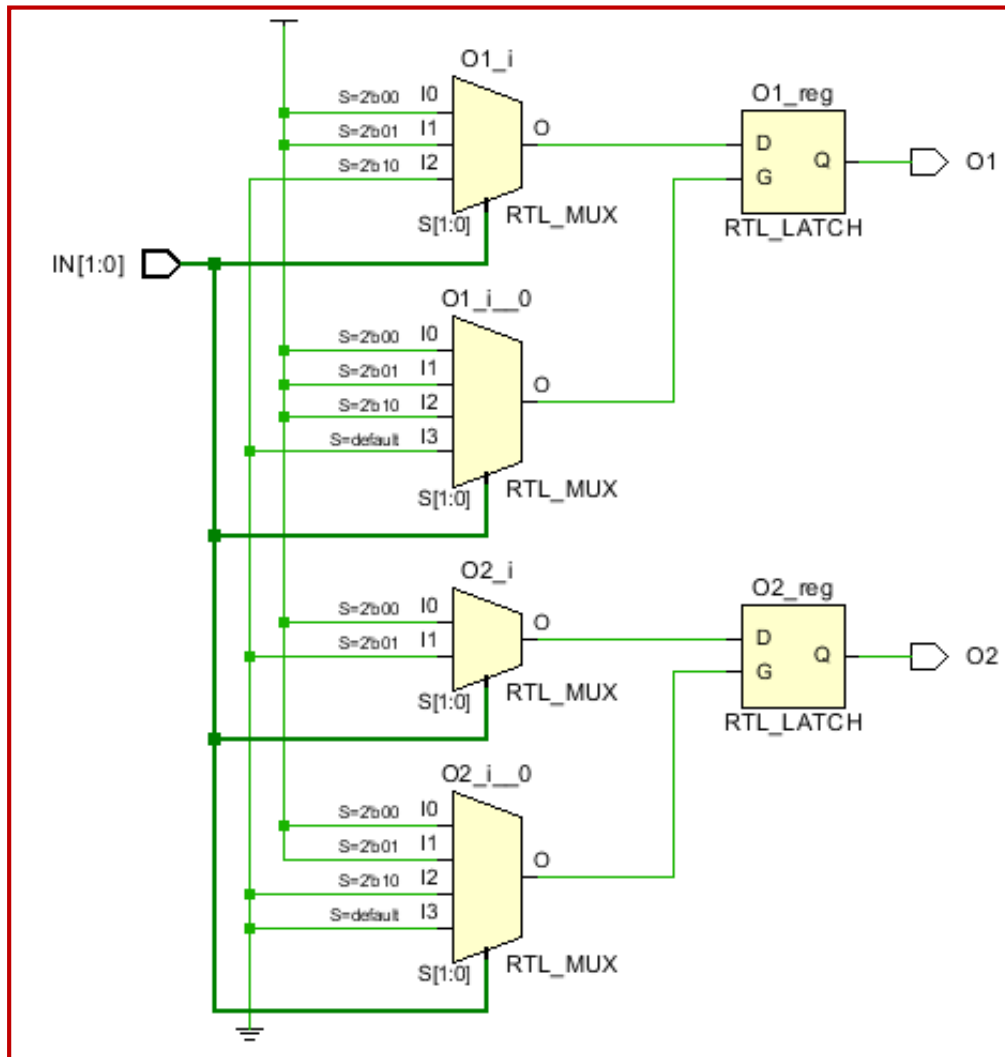

Missing/uncovered cases causes latching, and should be avoided while coding combinational circuits!


To avoid this condition, always cover all possible cases or use "default" keyword

case Statement – Combined cases

```
module conditional_case2(I,F);
input [3:0] I;
output reg F;

always @(I)
    case(I)
        4'b0000,4'b0001,4'b0010,4'b0011:F=I[1]&I[0];
        4'b0100,4'b0101,4'b0110,4'b0111:F=I[1]|I[0];
        4'b1000,4'b1001,4'b1010,4'b1011:F=I[1]^I[0];
        4'b1100,4'b1101,4'b1110,4'b1111:F=1'b1;
    endcase
endmodule
```

 If all possible input combinations are covered, default statement is not necessary



case Statement – case with full pre-defined values


- How would the schematic look like if the design is like below?

```

module conditional_case2(I,F);
input [3:0] I;
output reg F;

always @(I)
    case(I)
        4'b0000:F=I[1]&I[0];
        4'b0001:F=I[1]&I[0];
        4'b0010:F=I[1]&I[0];
        4'b0011:F=I[1]&I[0];
        4'b0100:F=I[1]|I[0];
        4'b0101:F=I[1]|I[0];
        4'b0110:F=I[1]|I[0];
        4'b0111:F=I[1]|I[0];
        4'b1000:F=I[1]^I[0];
        4'b1001:F=I[1]^I[0];
        4'b1010:F=I[1]^I[0];
        4'b1011:F=I[1]^I[0];
        4'b1100:F=1'b1;
        4'b1101:F=1'b1;
        4'b1110:F=1'b1;
        4'b1111:F=1'b1;
    endcase
endmodule

```

 

case Statement - case with full pre-defined values


- How would the schematic look like if the design is like below?

```

module conditional_case2(I,F);
input [3:0] I;
output reg F;

always @(I)
case(I)
4'b0000:F=I[1]&I[0];
4'b0001:F=I[1]&I[0];
4'b0010:F=I[1]&I[0];
4'b0011:F=I[1]&I[0];
4'b0100:F=I[1]|I[0];
4'b0101:F=I[1]|I[0];
4'b0110:F=I[1]|I[0];
4'b0111:F=I[1]|I[0];
4'b1000:F=I[1]^I[0];
4'b1001:F=I[1]^I[0];
4'b1010:F=I[1]^I[0];
4'b1011:F=I[1]^I[0];
4'b1100:F=1'b1;
4'b1101:F=1'b1;
4'b1110:F=1'b1;
4'b1111:F=1'b1;
endcase
endmodule

```

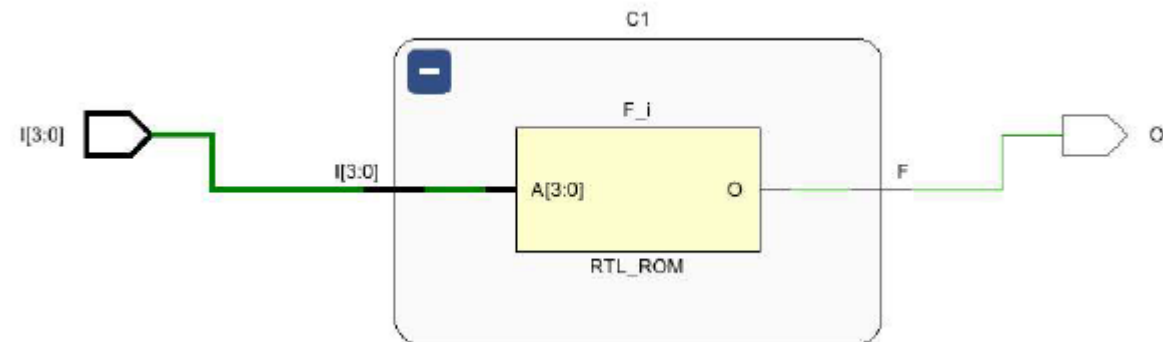

Case Statement – “casez” and “casex”

- casez:
 - Allows ‘z’ and ‘?’ in the alternatives of expression to be seen as don’t care values
- casex:
 - Allows ‘x’, ‘?’ and ‘z’ as don’t care characters
- If more than one match occurs, firstly listed one will be taken.
- They are “wildcard” styles of coding cases, but prone to bugs. For example if in[0] is left unconnected (value Z), then the first case branch will still be true

```
module example6
(
    input [2:0] in,
    output reg out1,out2,out0
);
    always @(in)
    begin
        {out2,out1,out0} = 3'b000;
        casez (in)
            3'b1?? : out2 = 1'b1;
            3'b?1? : out1 = 1'b1;
            3'b??1 : out0 = 1'b1;
            default: {out2,out1,out0} = 3'b000;
        endcase
    end
endmodule
```

Case Statement

- Example run

```
module conditional_case3(I,F);
input I;
output reg [1:0] F;

always @(I)
    case(I)
        1'b0:F=2'b00;
        1'b1:F=2'b01;
        1'bx:F=2'b10;
        1'bz:F=2'b11;
    endcase
endmodule

module conditional_casex(I,F);
input I;
output reg [1:0] F;

always @(I)
    casex(I)
        1'b0:F=2'b00;
        1'b1:F=2'b01;
        1'bx:F=2'b10;
        1'bz:F=2'b11;
    endcase
endmodule
```

```
`timescale 1ns / 1ps
module conditional_test2;
wire [1:0] O;
reg I;

initial
    $monitor($time, "I=%b: O=%b",I,O);

conditional_casex cl(.I(I),.F(O));

initial
begin
    I=1'b0; #20;
    I=1'b1; #20;
    I=1'bx; #20;
    I=1'bz; #20;

end

endmodule
```

```
# run 1000ns
```

```
0I=0: O=00
20I=1: O=01
40I=x: O=10
60I=z: O=11
```

“case” result

```
# run 1000ns
```

```
0I=0: O=00
20I=1: O=01
40I=x: O=00
60I=z: O=00
```

“casex” result

Thank you! Questions...



References



- Brown&Vrasenic, "Fundamentals of Digital Logic with Verilog Design", McGraw-Hill
- Use google 😊
 - <http://www.asic-world.com/verilog>
 - Etc.