

Due: 13 December 2019 @17 o'clock – No late homework will be accepted.

HW assignments will be brought to the TA @ VLSI Laboratory (upstairs) – not to Prof. Yelten.

- 1) An amplifier has a dc gain of 3×10^4 and poles at 2×10^5 Hz, 3×10^5 Hz, and 2×10^6 Hz. Find the value of β , and the corresponding closed-loop gain, for which a phase margin of 45° is obtained.
- 2) An amplifier having a low-frequency gain of 10^4 and poles at 10^4 Hz and 10^5 Hz is operated in a closed negative-feedback loop with a frequency-independent K .
 - a. For what value of K do the closed-loop poles become coincident? At what frequency?
 - b. What is the low frequency, closed-loop gain corresponding to the situation in (a)? What is the value of the closed-loop gain at the frequency of the coincident poles?
- 3) Assuming $V_A = \infty$, determine the closed-loop gain and I/O impedances of the amplifier in Fig. 1a.

 


Fig. 1a Figure of Question 3

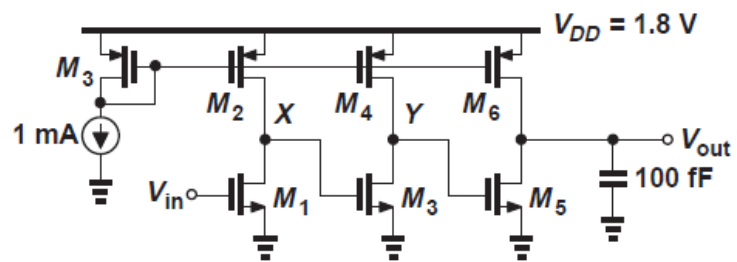


Fig. 1b Figure of Question 4

- 4) In the three-stage amplifier of Fig. 1b, all transistors except M_1 and M_5 have $W/L = 20 \mu\text{m} / 0.18 \mu\text{m}$. For M_1 use $W/L = 42 \mu\text{m} / 0.18 \mu\text{m}$ and for M_5 use $W/L = 10 \mu\text{m} / 0.18 \mu\text{m}$. Employ the transistor models provided in the last homework for Spice simulations. Assume a DC input level of 0.55 V.
 - a. Determine the phase margin.
 - b. Place a capacitor between nodes X and Y so as to obtain a phase margin of 50 degrees. What is the unity-gain bandwidth under this condition?
 - c. Repeat (b) if the compensation capacitor is tied between X and ground and compare the results.