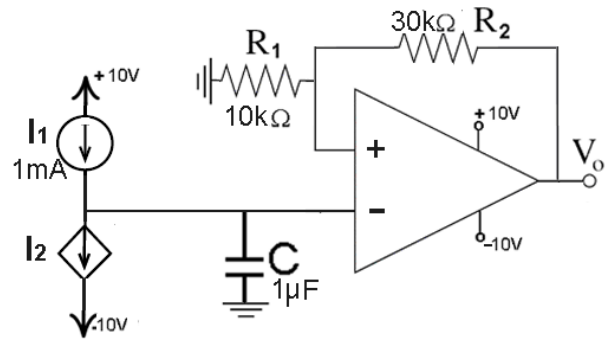


The controlled current source in the figure given as

$$V_o = +10V \rightarrow I_2 = 0$$

$$V_o = -10V \rightarrow I_2 = 2 \times I_1 = 2mA$$



- Find the hysteresis limits.
- Draw $V_o(t)$ for the hysteresis limit values of $-3V$ and $+3V$
- Design I_2
- For the same frequency, for the pulse-space ratio of $1/3$, find I_1/I_2 and I_1 .

$$2- a) \quad V_{E+} = \frac{10}{40k} \cdot 10k = 2.5V$$

$$V_{E-} = \frac{-10}{40k} \cdot 10k = -2.5V$$

$$b) \quad V_c > 3V \rightarrow V_o = -10V$$

$$V_c < -3V \rightarrow V_o = +10V$$

Lets take that $V_c(0) = 0V$ $V_o(0) = +10V$

$$V_p = V_{E+} = 3V \text{ olur.}$$

C charges and when $V_c = 3V$, the output becomes $V_o = -10V$

Then, C discharges and When $V_c = -3V$, the output becomes $V_o = +10V$


These cases repeat continuously.

$$\Delta V_c = 3 - (-3V) = 6V \text{ olur}$$

The current charging C; $I_1 - I_2 = 1mA - 0 = 1mA$
(When C charges, $V_o = 10V$ and $I_2 = 0$)

The current discharging C; $I_1 - I_2 = 1mA - 2mA = -1mA$
(When C discharges, $V_o = -10V$ and $I_2 = 2mA$)

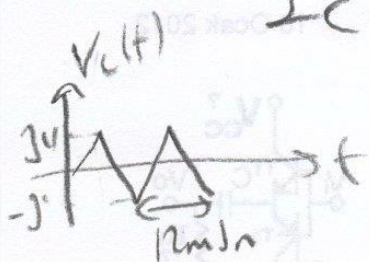
$$I_C = C \cdot \frac{\Delta V_C}{\Delta t} \rightarrow \Delta t_d = C \cdot \frac{\Delta V_C}{I_C} = 1 \mu F \cdot \frac{6V}{1mA}$$



$$\Delta t_d = 6ms = \Delta t_b$$

$$T = \Delta t_d + \Delta t_b = 12ms \approx 83Hz$$

c)

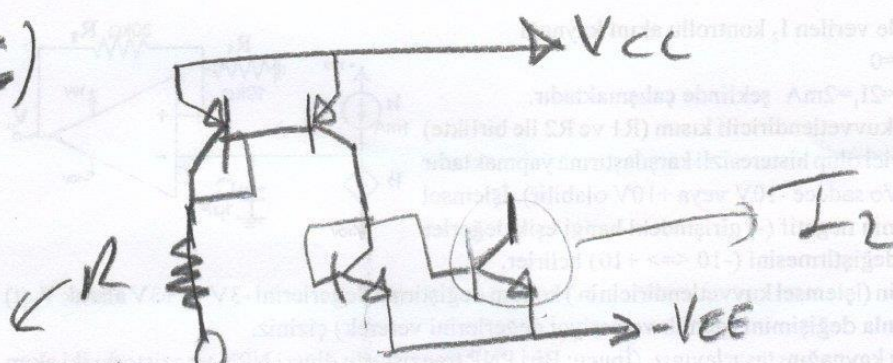

$$R = \frac{20 - 9.7}{2mA} V_0 \approx 9.7k\Omega$$

d) $V_0 = 10V$ pulse

$V_0 = 10V$ space

$$\frac{I_2 - I_1}{I_1} = \frac{1}{3} \text{ should be provided}$$

$$\left(\frac{\text{discharging}}{\text{charging}} = \frac{1}{2} \right)$$

$$\frac{I_2}{I_1} = \frac{4}{3}$$

$$T = 12ms \rightarrow t_d = 6ms = C \cdot \frac{\Delta V_C}{I_1}$$

$$I_1 = \frac{1\mu F \cdot 6}{1ms} = 2mA$$