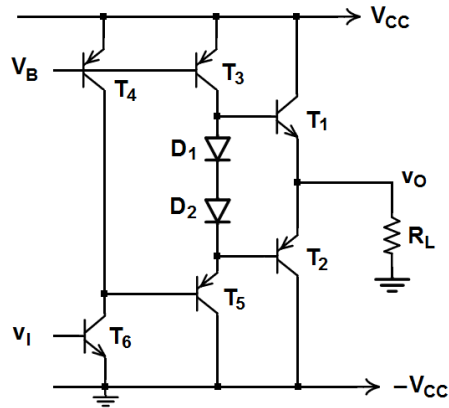


1. $V_{CC}=15\text{ V}$, $\beta_{Fn}=200$, $\beta_{Fp}=50$, $|V_{BEon}|=0.7\text{ V}$, $|V_{CEsat}|=0.2\text{ V}$ is given for the circuit in Figure below. Assume $I_{C3}=0.22\text{ mA}$ and sinusoidal signals.
- a) Calculate the positive and negative limits of the output voltage for $1\text{ k}\Omega$ and $200\ \Omega$ load resistance values when positive and negative voltages are applied at the input.
 - b) How should the current I_{C3} be chosen so that the output voltage swings equally on both sides for $R_L=200\ \Omega$?
 - c) Calculate the maximum power which can be delivered to the load before clipping occurs for $R_L=1\text{ k}\Omega$.
 - d) Calculate the efficiency for the output devices only, for conditions given in c).
 - e) Design a V_{BE} multiplier circuit which can replace the diodes D_1 and D_2 .



Solutions:

① a) For $R_L = 1k\Omega$

$$\begin{aligned} V_o^- &= -V_{CC} + V_{CEsat6} + V_{EB5} + V_{EB2} \\ &= -15 + 0,2 + 0,7 + 0,7 = -13,4V \end{aligned}$$

$$V_o^+ = V_{CC} - V_{CEsat3} - V_{BE1} = 14,1V$$

For $R_L = 200\Omega$

V_o^- is same.

V_o^+ is limited by the current of T_3 .

$$I_{omax} = \beta_{Fn} \cdot I_{C3} = 200 \cdot 0,22mA = 44mA$$

$$V_o^+ = I_{omax} \cdot R_L = 44mA \cdot 200 = 8,8V$$

b) $V_o^- = V_o^+$ should be satisfied.

$$13,4 = I_{omax} \cdot 200 \Rightarrow I_{omax} = 67mA$$


$$I_{C3} = \frac{I_{omax}}{\beta_{Fn}} = 0,335mA$$

$$c) P_{Lmax} = \frac{(V_o^-)^2}{2 \cdot R_L} = \frac{(13,4)^2}{2 \cdot 10^3} = 89,8mW$$

$$d) P_{DC} = 2 \cdot V_{oc} I_{DC} = 2 \cdot V_{oc} \cdot \frac{V_o^-}{\pi \cdot R_L} = \frac{2 \cdot 15 \cdot 13,4}{\pi \cdot 10^3} = 128mW$$

$$\eta = \frac{P_{Lmax}}{P_{DC}} = \frac{89,8mW}{128mW} = \%70$$

e)

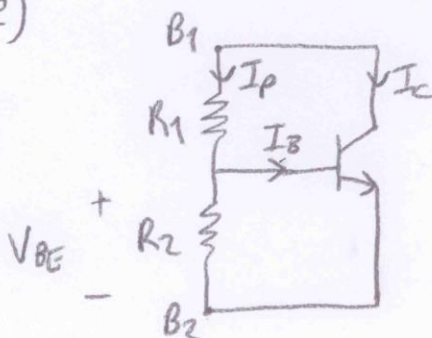

$$V_{B1,B2} = \frac{R_1 + R_2}{R_2} \cdot V_{BE}$$

$$I_P \gg I_B$$

$$I_C \gg I_P$$