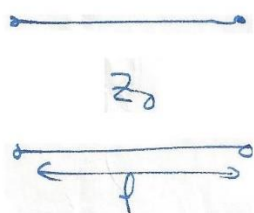



Examples of Scattering Coefficients

Length of transmission line:




Consider a length, l , of transmission line. From symmetry considerations there is no difference between port 1 and port 2. The reference planes are naturally the ends of the

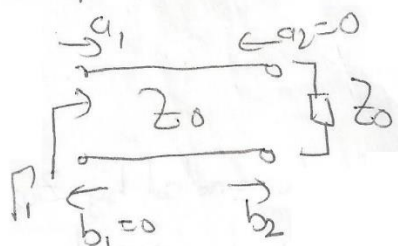line. Port 2 is terminated by a matched load and a normalised voltage wave a_1 is assumed to be incident at port 1. This voltage is not reflected because of the continuity of impedance:




$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \Gamma_1 = 0, \quad \Gamma_2 = S_{22} = 0$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \quad b_1 = e^{-\gamma l} a_2 \Rightarrow S_{12} = e^{-\gamma l}$$

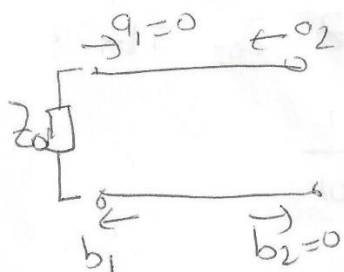

then $S = \begin{bmatrix} 0 & e^{-\gamma l} \\ e^{-\gamma l} & 0 \end{bmatrix}$
(from symmetry)

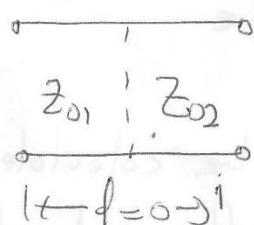Junction with different characteristic impedance



Port 2 is terminated by a matched load which is equal to Z_{02} , at the Z_0 of the line will be Z_{01} . Thus,


$$S_{11} = \Gamma_1 = \frac{b_1}{a_1} \Big|_{a_2=0} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}}$$

Similarly

$$S_{22} = \Gamma_2 = \frac{b_2}{a_2} \Big|_{a_1=0} = \frac{Z_{01} - Z_{02}}{Z_{01} + Z_{02}} = -S_{11}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}$$

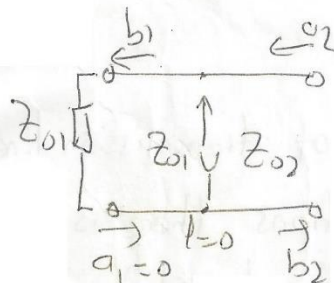we can use the voltage equation of the junction: $V_1 = V_2$



$$V_{a1} + V_{b1} = V_{a2} + V_{b2}$$


but because of the matched load at port 2, $a_2 = 0$ then

$$V_{b1} = V_{a2} + V_{b2} \Rightarrow \sqrt{Z_{01}} b_1 = \sqrt{Z_{02}} (a_2 + b_2)$$

$$\frac{b_1}{a_2} = S_{12} = \sqrt{\frac{Z_{02}}{Z_{01}}} \left(1 + \frac{b_2}{a_2} \right) = \sqrt{\frac{Z_{02}}{Z_{01}}} (1 + S_{22})$$

$$S_{12} = 2 \frac{\sqrt{Z_{01} Z_{02}}}{Z_{01} + Z_{02}}$$

A series impedance on the junction

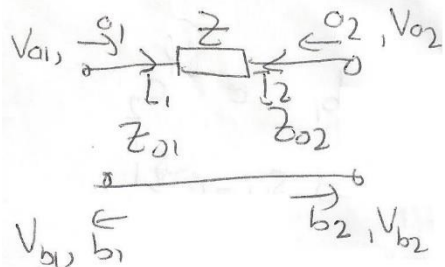

for S_{11} , port 2 is terminated by Z_{02} and the equivalent load impedance at port 2 is $Z + Z_{02}$. Then S_{11} will be,

$$S_{11} = \frac{(Z + Z_{02}) - Z_{01}}{(Z + Z_{02}) + Z_{01}}$$

similarly $S_{22} = \frac{(Z + Z_{01}) - Z_{02}}{(Z + Z_{01}) + Z_{02}}$

For the transfer parameters S_{12} and S_{21} we can use the currents to the impedance Z : $I_1 = -I_2$


$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \Rightarrow \frac{V_{a1} - V_{b1}}{Z_{01}} = \frac{V_{b2}}{Z_{02}} \quad (a_2=0 \Rightarrow V_{a2}=0)$$

$$\frac{a_1 \sqrt{Z_{01}} - b_1 \sqrt{Z_{01}}}{Z_{01}} = \frac{b_2 \sqrt{Z_{02}}}{Z_{02}}$$

$$b_2 \sqrt{\frac{Z_{01}}{Z_{02}}} = (a_1 - b_1)$$

$$S_{21} = \sqrt{\frac{Z_{02}}{Z_{01}}} (1 - S_{11}) = \frac{2 \sqrt{Z_{01} Z_{02}}}{Z + Z_{01} + Z_{02}} = S_{12}$$

A Shunt Admittance

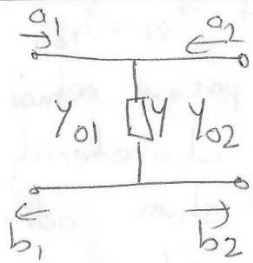


A commonly occurring waveguide network is formed by a shunt susceptance. To examine such a junction, for generality, the characteristic impedances of the transmission lines on either side of the admittance are different.

Consider a wave incident at port 1 when port 2 is terminated by its characteristic impedance. Then $a_2 = V_{02} = 0$. The scattering coefficient S_{11} is equal to the reflection coefficient Γ_1 at port 1.

Thus

$$\Gamma_1 = S_{11} = \left. \frac{b_1}{a_1} \right|_{b_2=0} = \frac{Y_{01} - (Y + Y_{02})}{Y_{01} + (Y + Y_{02})}$$

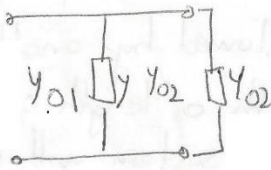

Similarly by terminating port 1 by the transmission line characteristic impedance, we obtain

$$S_{22} = \frac{Y_{02} - (Y + Y_{01})}{Y_{02} + (Y + Y_{01})}$$

The voltage on either side of the admittance Y must be the same, thus $V_1 = V_2$ or $V_{a1} + V_{b1} = V_{b2}$ (when $a_2 = 0 = V_{02}$)

$$\frac{1}{\sqrt{Y_{01}}} (a_1 + b_1) = \frac{1}{\sqrt{Y_{02}}} b_2$$

Dividing through by a_1 and rearranging yields

$$S_{21} = \frac{b_2}{a_1} = \sqrt{\frac{Y_{02}}{Y_{01}}} (1 + S_{11}) = \frac{2\sqrt{Y_{01}Y_{02}}}{Y_{01} + Y + Y_{02}}$$

Similarly, $S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$

$$V_1 = V_2 \Rightarrow V_{b1} = V_{a2} + V_{b2} \Rightarrow \frac{b_1}{\sqrt{Y_{01}}} = \frac{1}{\sqrt{Y_{02}}} (a_2 + b_2)$$

$$S_{12} = \sqrt{\frac{Y_{01}}{Y_{02}}} (1 + S_{22}) = \sqrt{\frac{Y_{01}}{Y_{02}}} \frac{2 Y_{02}}{Y + Y_{01} + Y_{02}} = \frac{2 \sqrt{Y_{01} Y_{02}}}{Y + Y_{01} + Y_{02}}$$

Comparing S_{12} and S_{21} , it will be seen that $S_{21} = S_{12}$, thus showing that $S_{ij} = S_{ji}$ for this linear passive network.

When the transmission lines have the same characteristic impedance $Y_0 = Y_{01} = Y_{02}$, then the normalised shunt admittance is y ($y = Y/Y_0$), and the scattering matrix becomes

$$S = \begin{bmatrix} -\frac{y}{y+2} & \frac{2}{y+2} \\ \frac{2}{y+2} & -\frac{y}{y+2} \end{bmatrix}$$

in this case $S_{11} = S_{22}$ and the system is symmetric.