

NAME:**Number:**


Final exam includes 5 problems.

Write your answers on A4-white papers and sign each page.

P1- For the MOSFETs in the figure, $k_p' = \mu_p C_{ox} = 40 \mu A/V^2$, $k_n' = \mu_n C_{ox} = 100 \mu A/V^2$, $V_{A_n} = V_{A_p} = 40V$, $V_{Th,p} = -0.5V$, $V_{Th,n} = 0.5V$ are given. $C_{gs} = 10pF$, $C_{dg} = 2pF$ for the transistors. The input of the next circuit has a parasitic capacitance of $20pF$ ($C_o = 20pF$).


$I_o = 1mA$, $(W/L)_N = 20$, $\beta_N = \beta_P$ are given.

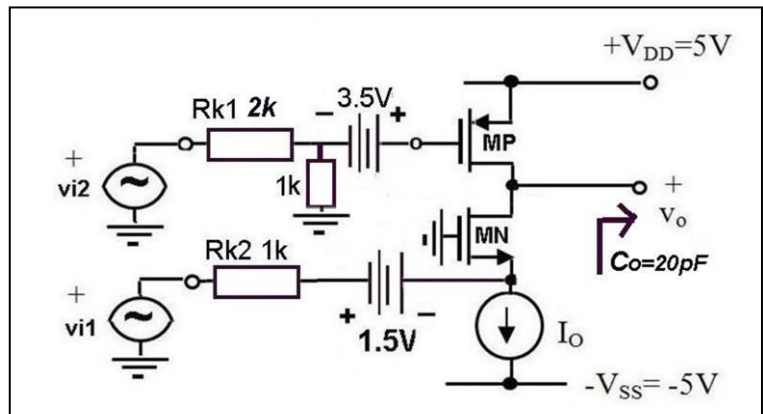Find the **cut-off frequency** of the ac differential gain of the circuit $v_o/(v_{i1}-v_{i2})$. (20P)



P2- For the MOSFET in the figure, $\beta = 100mA/V^2$ and $V_{Th} = 2V$ are given. The OPAMP is **ideal**. The bias point for the input is given as $V_{iDC} = 0V$. (L and C have very large values.)

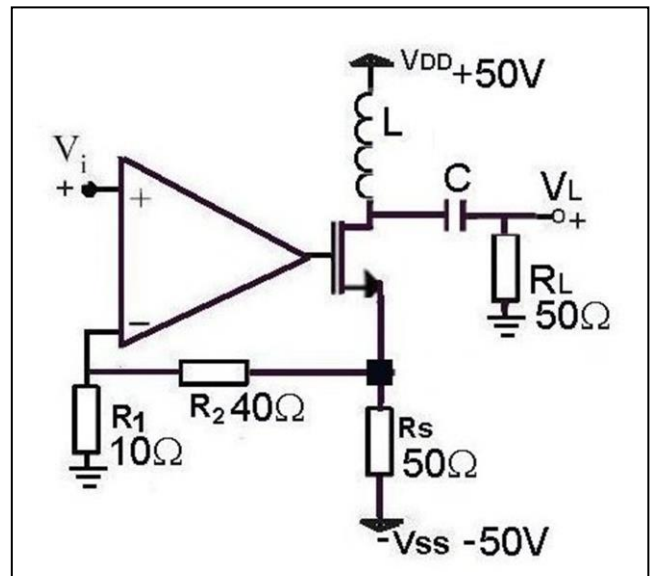Find ac **midband gain** of the circuit (V_L/V_i) **by using the feedback method**. (20P)



P3 The circuit in P2 will be used as a **class-A power amplifier** circuit (*in spite of that it is not a convenient circuit for power amplifier applications*);


- Find the optimum load value for the circuit. ($R_{L-OPT} = ?$) (7P)
- Find the maximum efficiency value for the sinusoidal case. (7P)
- Find the maximum power value dissipated on the MOS transistor. (7P)

P4- For the MOS transistors in the Figure,
 $\beta_1=\beta_2=\beta_3=0.4\text{mA/V}^2$, $\beta_4=\beta_5=\beta_6=0.8\text{mA/V}^2$,
 $V_{AP}=V_{AN}=50\text{V}$ and
 $|V_{TH1}|=|V_{TH2}|=|V_{TH6}|=V_{TH3}=V_{TH4}=V_{TH5}=0.5\text{V}$ are
 given. (**$V_{inDC}=0$ and $V_{outDC}=0$**)

($C_{gs6}=2C_{gs4}=2C_{gs5}=2C_{gs1}=2C_{gs2}=4C_{gs3}=40\text{pF}$)
 ($C_{ds}=C_{gs}/4$ for all the transistors)

a) Find the **loop-gain** of the circuit in the figure
 (**$V_{in}=0$ for the loop gain**). (10P)

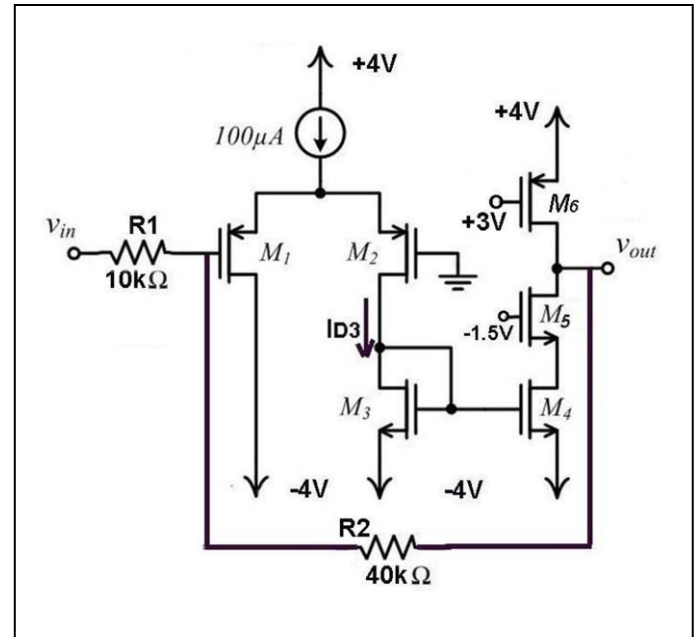b) Draw the magnitude and phase characteristics of
 the **loop-gain**. Find the Phase Margin (**PM**). (10P)



P5 The circuit given in the figure will be used
 as a relaxation oscillator after a modification.
 In order to obtain the oscillation behavior,
 a capacitor ($C=1\mu\text{F}$) will be used **in place of**
RA or RB (which resistor?). Put the **capacitor**
 in place of the **right resistor** for the oscillation.
 Then;

a) Find the **oscillation frequency** value. (10P)

b) Draw the signals at **Vout** and **Vo1**. (10P)

