
Logic and Computer Design Fundamentals

Chapter 10 – Computer Design Basics

Part 1 – Datapaths

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

Overview

- **Part 1 – Datapaths**
 - **Introduction**
 - **Datapath Example**
 - **Arithmetic Logic Unit (ALU)**
 - **Shifter**
 - **Datapath Representation**
 - **Control Word**
- **Part 2 – A Simple Computer**
 - **Instruction Set Architecture (ISA)**
 - **Single-Cycle Hardwired Control**
 - **Instruction Decoder**
 - **Sample Instructions**
 - **Single Cycle Computer Issues**
 - **Multiple Cycle Hardwired Control**
 - **Sequential Control Design**

Introduction

■ Computer Specification

- ***Instruction Set Architecture (ISA)*** - the specification of a computer's appearance to a programmer at its lowest level
- ***Computer Architecture*** - a high-level description of the hardware implementing the computer derived from the ISA
- **The architecture usually includes additional specifications such as speed, cost, and reliability.**

Introduction (continued)


- **Simple computer architecture decomposed into:**
 - **Datapath for performing operations**
 - **Control unit for controlling datapath operations**
- **A *datapath* is specified by:**
 - **A set of registers**
 - **The microoperations performed on the data stored in the registers**
 - **A control interface**

Datapaths

- **Guiding principles for basic datapaths:**
 - **The set of registers**
 - **Collection of individual registers**
 - **A set of registers with common access resources called a *register file***
 - **A combination of the above**
 - **Microoperation implementation**
 - **One or more shared resources for implementing microoperations**
 - **Buses - shared transfer paths**
 - ***Arithmetic-Logic Unit (ALU)* - shared resource for implementing arithmetic and logic microoperations**
 - **Shifter - shared resource for implementing shift microoperations**


Datapath Example

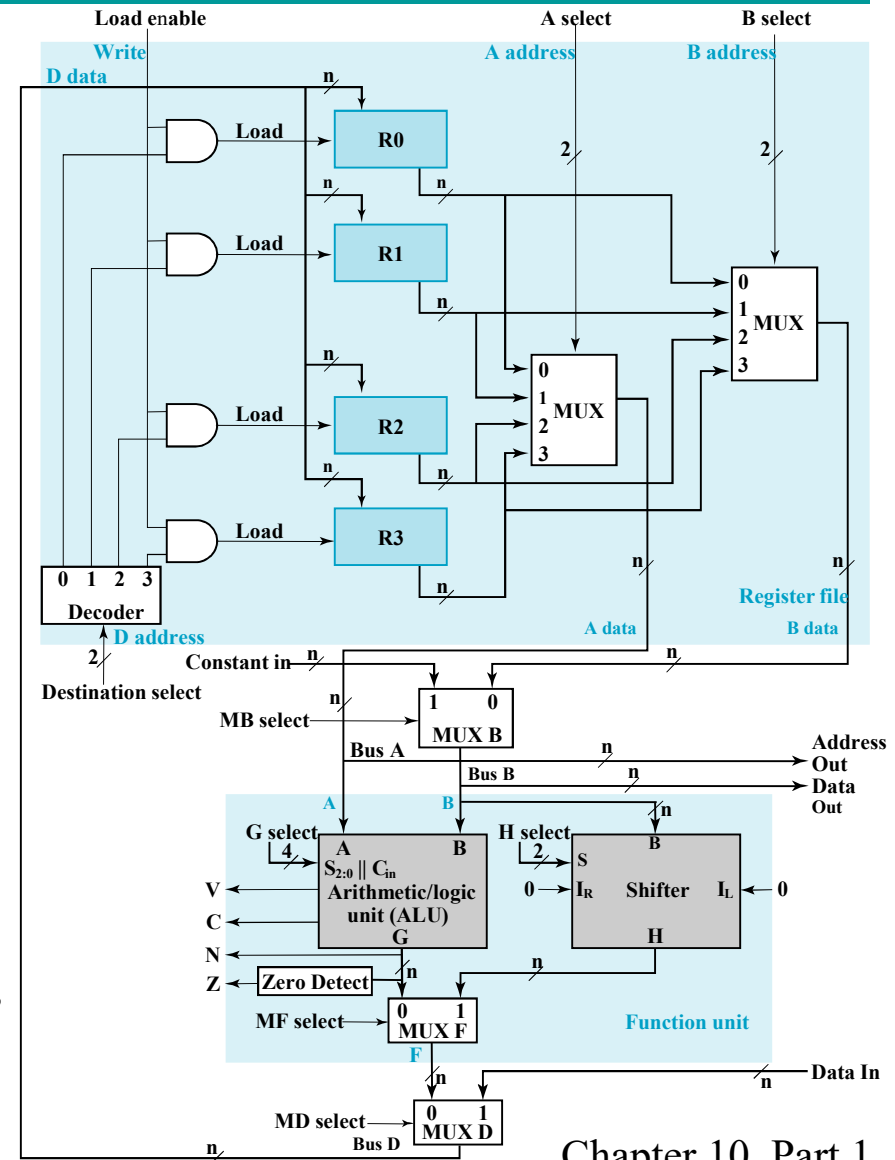- Four parallel-load registers
- Two mux-based register selectors
- Register destination decoder
- Mux B for external constant input
- Buses A and B with external address and data outputs
- ALU and Shifter with Mux F for output select
- Mux D for external data input
- Logic for generating status bits V, C, N, Z




Datapath Example: Performing a Microoperation

- **Microoperation: $R0 \leftarrow R1 + R2$**
- **Apply 01 to A select to place contents of R1 onto Bus A**
- **Apply 10 to B select to place contents of R2 onto B data and apply 0 to MB select to place B data on Bus B**
- **Apply 0010 to G select to perform addition $G = \text{Bus A} + \text{Bus B}$**
- **Apply 0 to MF select and 0 to MD select to place the value of G onto BUS D**
- **Apply 00 to Destination select to enable the Load input to R0**
- **Apply 1 to Load Enable to force the Load input to R0 to 1 so that R0 is loaded on the clock pulse (not shown)**
- **The overall microoperation requires 1 clock cycle**

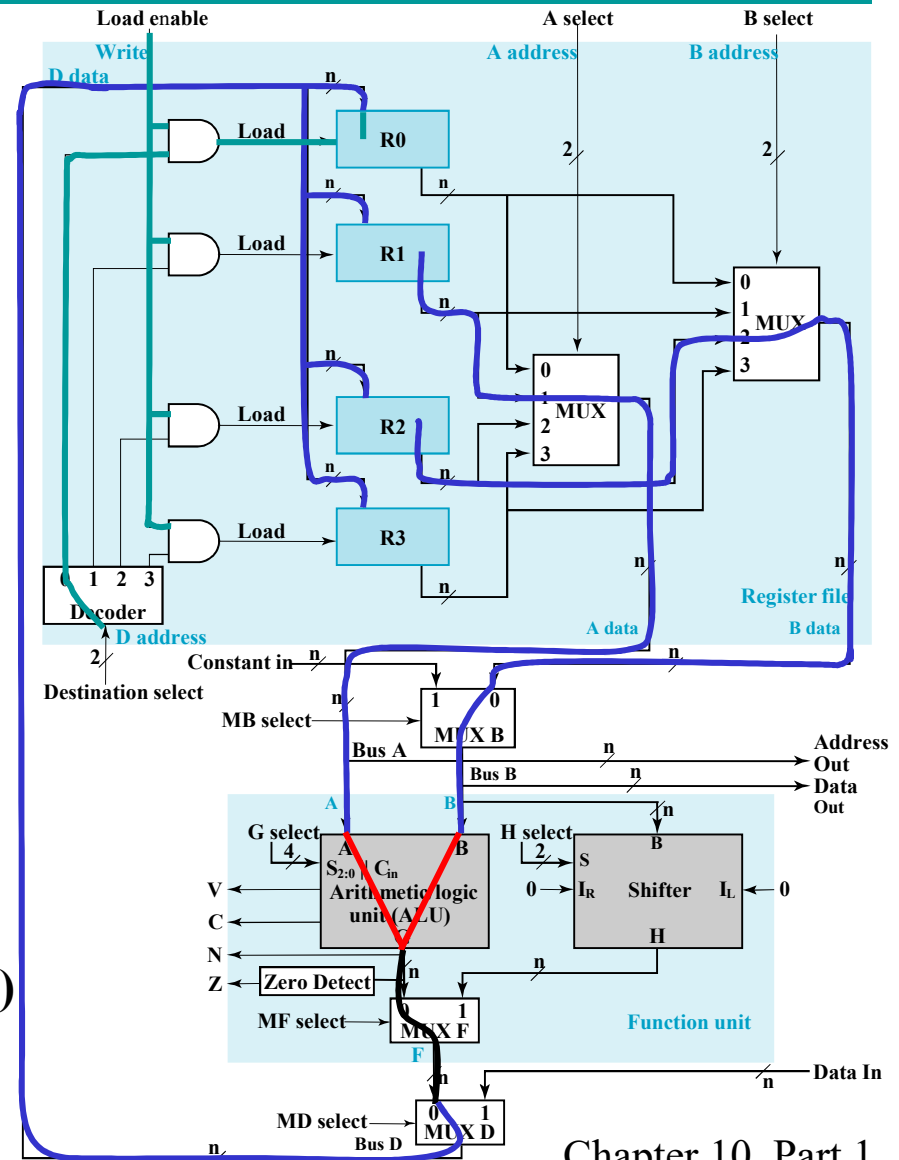

Datapath Example: Key Control Actions for Microoperation Alternatives

- Perform a shift microoperation – apply 1 to MF select
- Use a constant in a micro-operation using Bus B – apply 1 to MB select
- Provide an address and data for a memory or output write microoperation – apply 0 to Load enable to prevent register loading
- Provide an address and obtain data for a memory or output read microoperation – apply 1 to MD select
- For some of the above, other control signals become don't cares

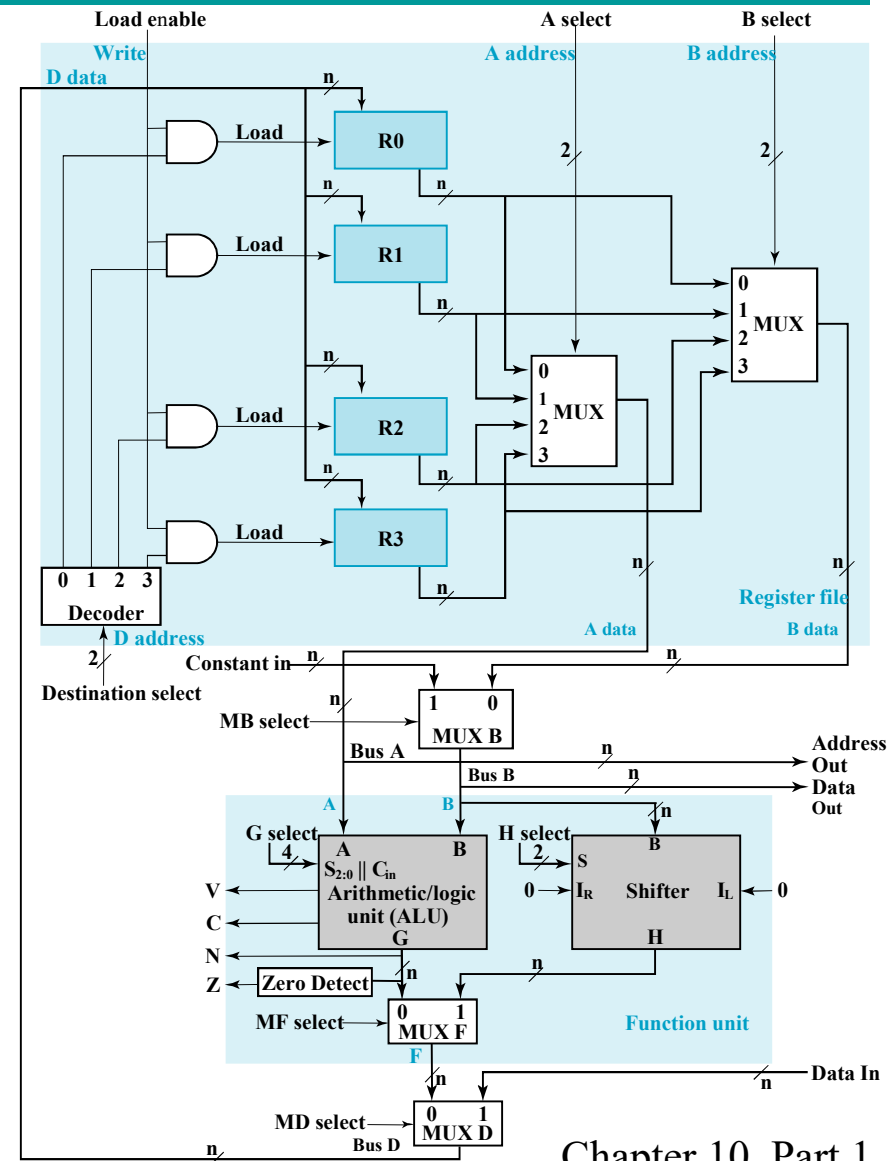

Arithmetic Logic Unit (ALU)


- In this and the next section, we deal with detailed design of typical ALUs and shifters
- Decompose the ALU into:
 - An arithmetic circuit
 - A logic circuit
 - A selector to pick between the two circuits
- Arithmetic circuit design
 - Decompose the arithmetic circuit into:
 - An n-bit parallel adder
 - A block of logic that selects four choices for the B input to the adder
 - See next slide for diagram

Arithmetic Circuit Design (continued)

- There are only four functions of B to select as Y in $G = A + Y$:


	$C_{in} = 0$	$C_{in} = 1$
• 0	$G = A$	$G = A + 1$
• B	$G = A + B$	$G = A + B + 1$
• \overline{B}	$G = A + \overline{B}$	$G = A + \overline{B} + 1$
• 1	$G = A - 1$	$G = A$

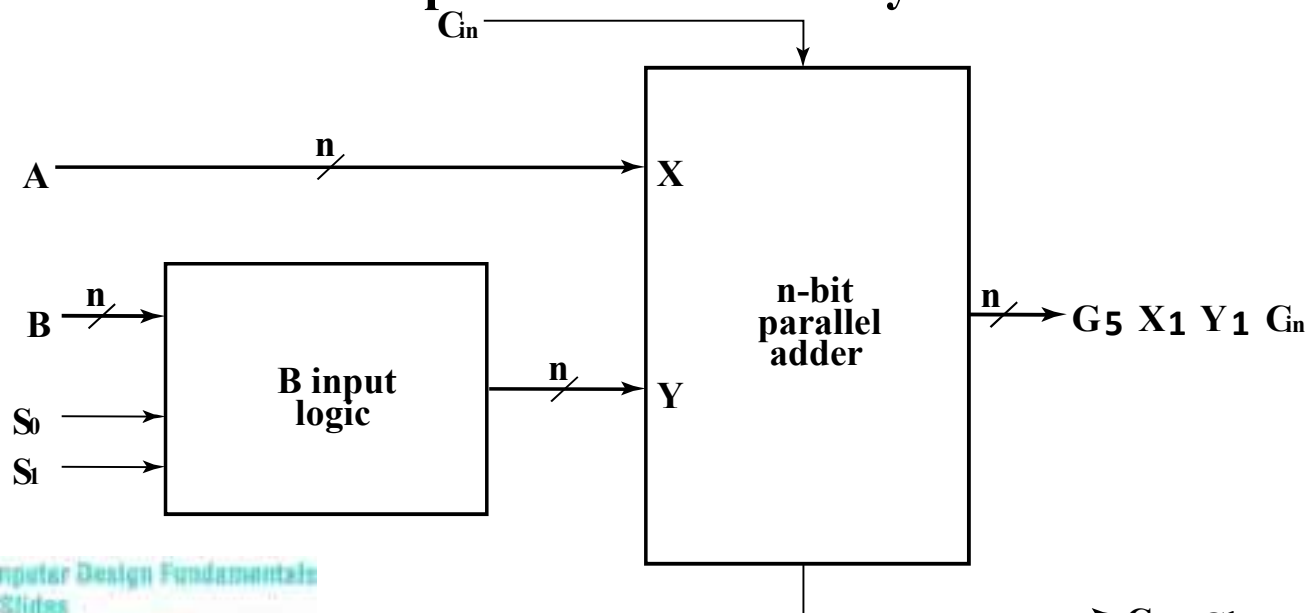- What functions are implemented with carry-in to the adder = 0?
=1?



Arithmetic Circuit Design (continued)

 - Adding selection codes to the functions of B:



- The useful arithmetic functions are labeled in the table
- Note that all four functions of B produce at least one useful function

Logic Circuit


- The text gives a circuit implemented using a multiplexer plus gates implementing: AND, OR, XOR and NOT
- Here we custom design a circuit for bit G_i by beginning with a truth table organized as a K-map and assigning (S_1, S_0) codes to AND, OR, etc.
- $G_i = S_0 \bar{A}_i B_i + \bar{S}_1 A_i \bar{B}_i + S_0 A_i \bar{B}_i + S_1 \bar{S}_0 \bar{A}_i$
- Gate input count for MUX solution > 29
- Gate input count for above circuit < 20
- Custom design better

$S_1 S_0$	AND	OR	XOR	NOT
$A_i B_i$	0 0	0 1	1 1	1 0
0 0	0	0	0	1
0 1	0	1	1	1
1 1	1	1	0	0
1 0	0	1	1	0

Arithmetic Logic Unit (ALU)

- The custom circuit has interchanged the (S_1, S_0) codes for XOR and NOT compared to the MUX circuit. To preserve compatibility with the text, we use the MUX solution.
- Next, use the arithmetic circuit, the logic circuit, and a 2-way multiplexer to form the ALU. See the next slide for the bit slice diagram.
- The input connections to the arithmetic circuit and logic circuit have been assigned to prepare for seamless addition of the shifter, keeping the selection codes for the combined ALU and the shifter at 4 bits:
 - Carry-in C_i and Carry-out C_{i+1} go between bits
 - A_i and B_i are connected to both units
 - A new signal S_2 performs the arithmetic/logic selection
 - The select signal entering the LSB of the arithmetic circuit, C_{in} , is connected to the least significant selection input for the logic circuit, S_0 .

Arithmetic Logic Unit (ALU) (continued)

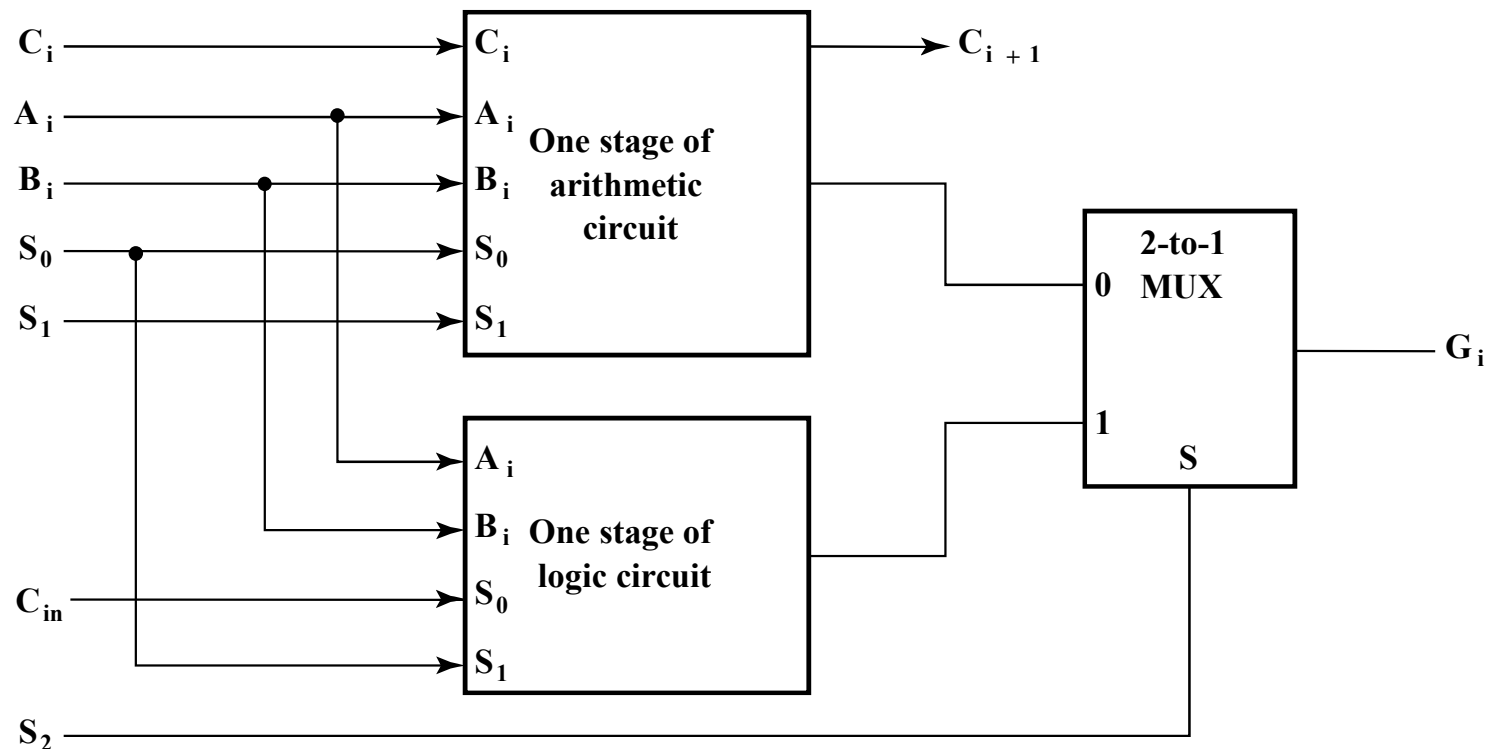


- The next most significant select signals, S_0 for the arithmetic circuit and S_1 for the logic circuit, are wired together, completing the two select signals for the logic circuit.
- The remaining S_1 completes the three select signals for the arithmetic circuit.

Combinational Shifter Parameters

- **Direction: Left, Right**
- **Number of positions with examples:**
 - **Single bit:**
 - 1 position
 - 0 and 1 positions
 - **Multiple bit:**
 - 1 to $n - 1$ positions
 - 0 to $n - 1$ positions
- **Filling of vacant positions**
 - Many options depending on instruction set
 - Here, will provide input lines or zero fill

4-Bit Basic Left/Right Shifter

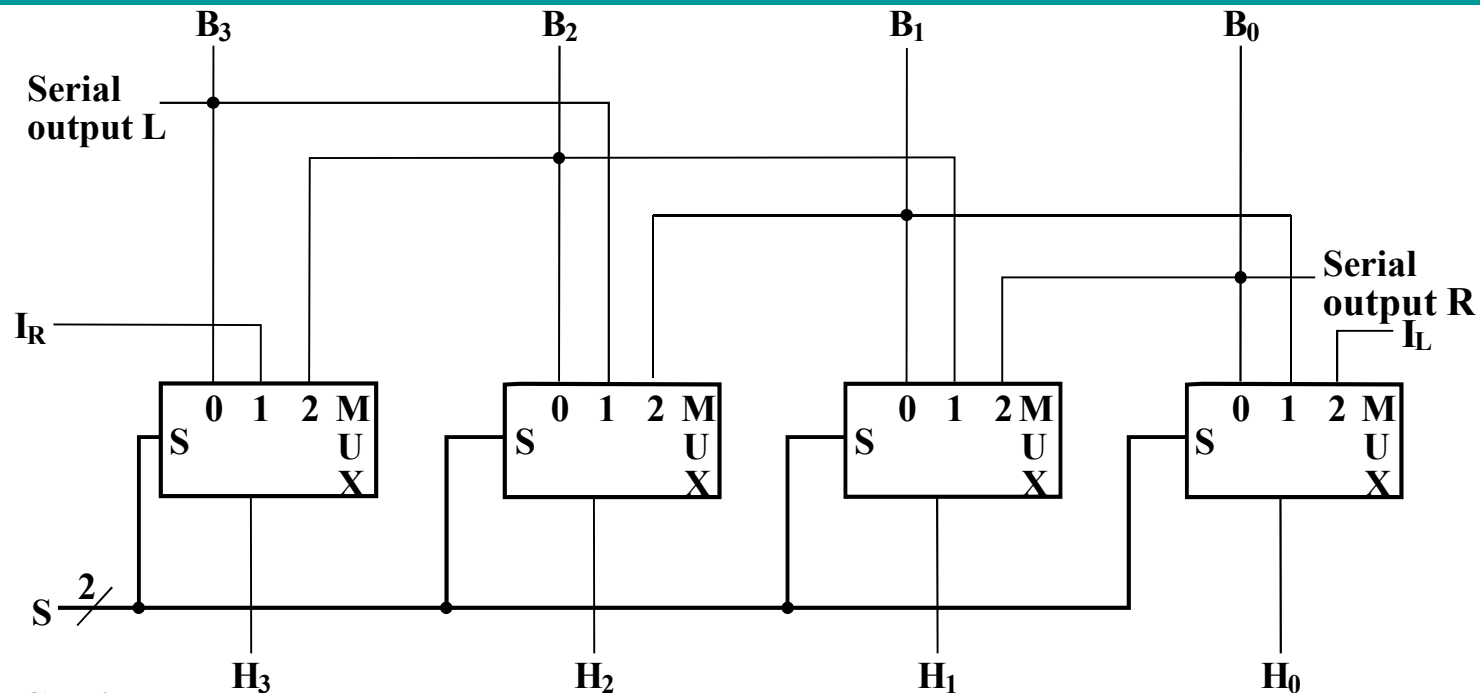

Serial Inputs:

- I_R for right shift
- I_L for left shift


Serial Outputs

- R for right shift (Same as MSB input)
- L for left shift (Same as LSB input)

Shift Functions:

- $(S_1, S_0) = 00$ Pass B unchanged
 01 Right shift
 10 Left shift
 11 Unused

Barrel Shifter

 


- A rotate is a shift in which the bits shifted out are inserted into the positions vacated
- The circuit rotates its contents left from 0 to 3 positions depending on S:
 S = 00 position unchanged S = 10 rotate left by 2 positions
 S = 01 rotate left by 1 positions S = 11 rotate left by 3 positions
- See Table 10-3 in text for details

Barrel Shifter (continued)

- **Large barrel shifters can be constructed by using:**
 - **Layers of multiplexers - Example 64-bit:**
 - Layer 1 shifts by 0, 16, 32, 48
 - Layer 2 shifts by 0, 4, 8, 12
 - Layer 3 shifts by 0, 1, 2, 3
 - See example in section 12-2 of the text
 - **2 - dimensional array circuits designed at the electronic level**


Datapath Representation

- Have looked at detailed design of ALU and shifter in the datapath in slide 8
- Here we move up one level in the hierarchy from that datapath
- The registers, and the multiplexer, decoder, and enable hardware for accessing them become a *register file*
- The ALU, shifter, Mux F and status hardware become a *function unit*
- The remaining muxes and buses which handle data transfers are at the new level of the hierarchy

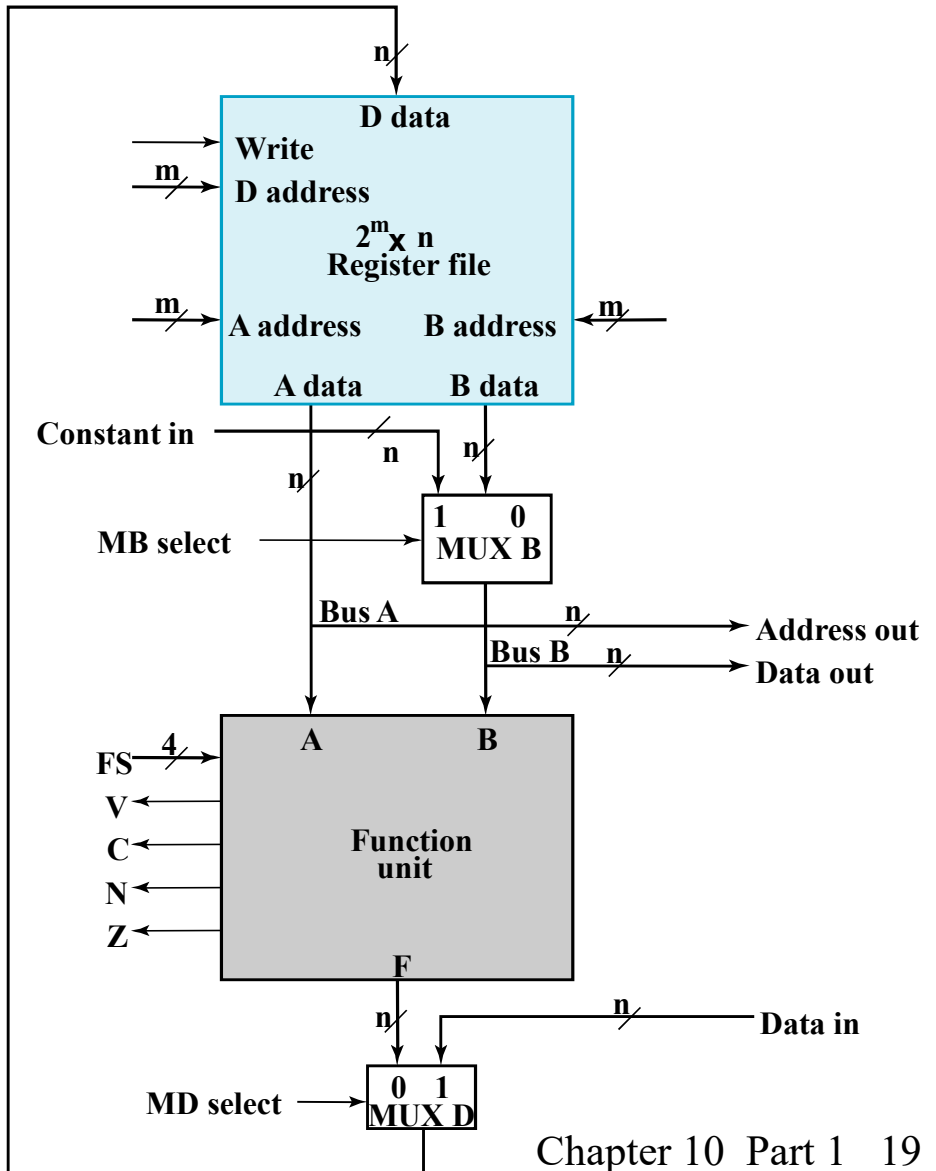

Datapath Representation (continued)

- In the register file:
 - Multiplexer select inputs become A address and B address
 - Decoder input becomes D address
 - Multiplexer outputs become A data and B data
 - Input data to the registers becomes D data
 - Load enable becomes write
- The register file now appears like a memory based on clocked flip-flops (the clock is not shown)
- The function unit labeling is quite straightforward except for FS

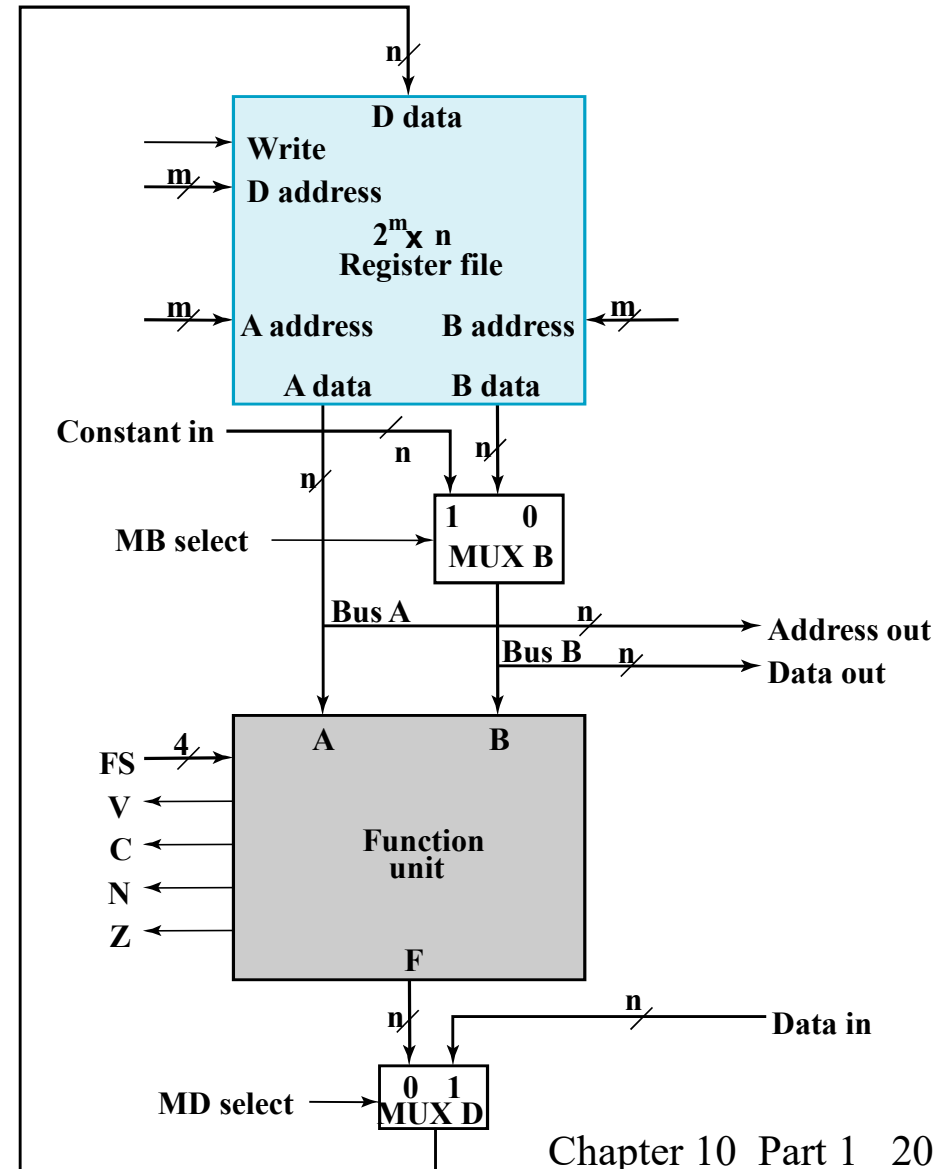

Definition of Function Unit Select (FS) Codes

FS(3:0)	MF Select	G Select(3:0)	H Select(3:0)	Microoperation	
0000	0	0000	XX	$F \leftarrow A$	Boolean Equations: $MFS = F_3 F_2$ $GS_i = F_i$ $HS_i = F_i$
0001	0	0001	XX	$F \leftarrow A + 1$	
0010	0	0010	XX	$F \leftarrow A + B$	
0011	0	0011	XX	$F \leftarrow A + B + 1$	
0100	0	0100	XX	$F \leftarrow A + \overline{B}$	
0101	0	0101	XX	$F \leftarrow A + \overline{B} + 1$	
0110	0	0110	XX	$F \leftarrow A - 1$	
0111	0	0111	XX	$F \leftarrow A$	
1000	0	1X00	XX	$F \leftarrow A \wedge B$	
1001	0	1X01	XX	$F \leftarrow A \vee B$	
1010	0	1X10	XX	$F \leftarrow A \oplus B$	
1011	0	1X11	XX	$F \leftarrow \overline{A}$	
1100	1	XXXX	00	$F \leftarrow B$	
1101	1	XXXX	01	$F \leftarrow sr B$	
1110	1	XXXX	10	$F \leftarrow sl B$	

The Control Word

- The datapath has many control inputs
- The signals driving these inputs can be defined and organized into a *control word*
- To execute a microinstruction, we apply control word values for a clock cycle. For most microoperations, the positive edge of the clock cycle is needed to perform the register load
- The datapath control word format and the field definitions are shown on the next slide

The Control Word Fields

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
DA				AA			BA		M B	FS				M D	R W


Control word

■ Fields

- DA – D Address
- AA – A Address
- BA – B Address
- MB – Mux B
- FS – Function Select
- MD – Mux D
- RW – Register Write

■ The connections to datapath are shown in the next slide

Control Word Block Diagram

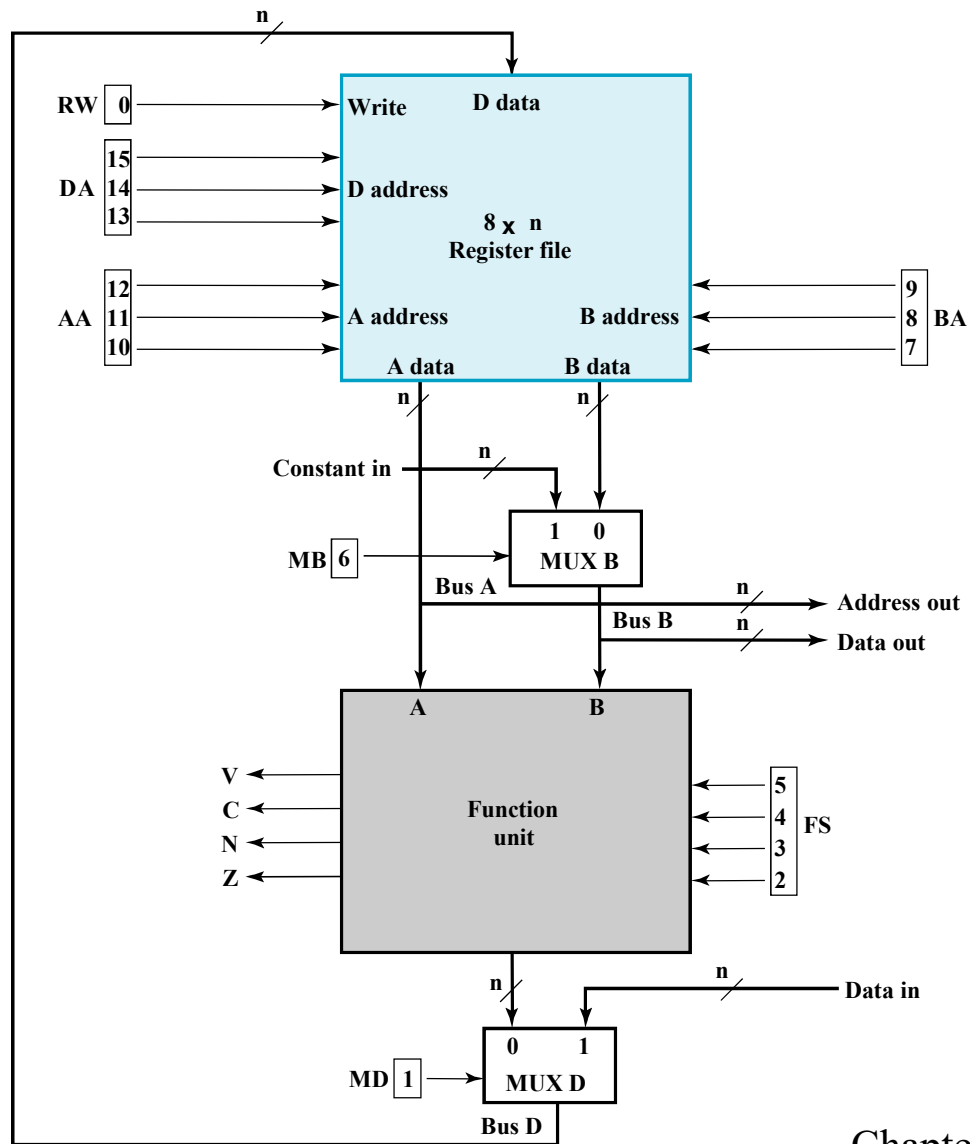

Control Word Encoding

DA, AA, BA		MB		FS		MD		RW	
Function	Code	Function	Code	Function	Code	Function	Code	Function	Code
$R0$	000	Register	0	$F \leftarrow A$	0000	Function	0	No write	0
$R1$	001	Constant	1	$F \leftarrow A + 1$	0001	Data In	1	Write	1
$R2$	010			$F \leftarrow A + B$	0010				
$R3$	011			$F \leftarrow A + \overline{B} + 1$	0011				
$R4$	100			$F \leftarrow A + \overline{B}$	0100				
$R5$	101			$F \leftarrow A + \overline{B} + 1$	0101				
$R6$	110			$F \leftarrow A - 1$	0110				
$R7$	111			$F \leftarrow A$	0111				
				$F \leftarrow A \wedge B$	1000				
				$F \leftarrow A \vee B$	1001				
				$F \leftarrow A \oplus B$	1010				
				$F \leftarrow \overline{A}$	1011				
				$F \leftarrow B$	1100				
				$F \leftarrow \text{sr } B$	1101				
				$F \leftarrow \text{sl } B$	1110				

Microoperations for the Datapath - Symbolic Representation


Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	$R1$	$R2$	$R3$	Register	$F = A + \overline{B} + 1$	Function	Write
$R4 \leftarrow \text{sl } R6$	$R4$	—	$R6$	Register	$F = \text{sl } B$	Function	Write
$R7 \leftarrow R7 + 1$	$R7$	$R7$	—	Register	$F = A + 1$	Function	Write
$R1 \leftarrow R0 + 2$	$R1$	$R0$	—	Constant	$F = A + B$	Function	Write
Data out $\leftarrow R3$	—		$R3$	Register	—	—	No Write
$R4 \leftarrow \text{Data in}$	$R4$	—		—	—	Data in	Write
$R5 \leftarrow 0$	$R5$	$R0$	$R0$	Register	$F = A \oplus B$	Function	Write

Microoperations for the Datapath - Binary Representation

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow s1 R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow R7 + 1$	111	111	XXX	0	0001	0	1
$R1 \leftarrow R0 + 2$	001	000	XXX	1	0010	0	1
Data out $\leftarrow R3$	XXX	XXX	011	0	XXXX	X	0
$R4 \leftarrow$ Data in	100	XXX	XXX	X	XXXX	1	1
$R5 \leftarrow 0$	101	000	000	0	1010	0	1

- Results of simulation of the above on the next slide

Datapath Simulation

 

Terms of Use

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)