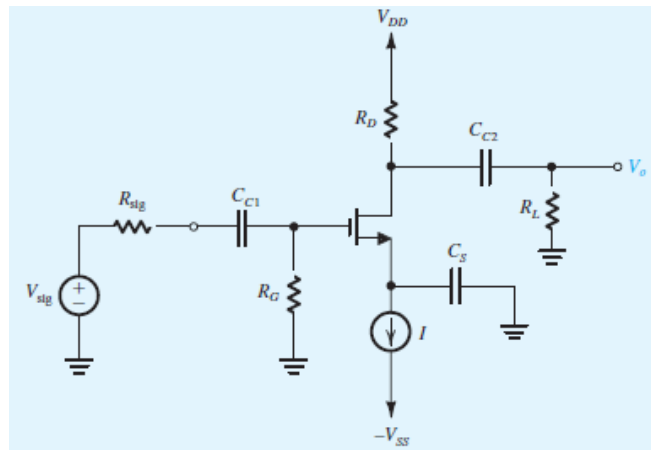


Due: 11 October 2017 @9:00 am – **No late homework will be accepted.**

- 1) Draw the magnitude and phase Bode diagrams of the following transfer function. Compare your results with MATLAB simulations.

$$H(s) = \frac{4(20 + s)(20000 + s)}{(200 + s)(2000 + s)}$$

- 2) By using the short-circuit time constant method, determine the lower corner frequency (–3 dB frequency) of the amplifier below. Assume that $\lambda \neq 0$.



- 3) Due to a manufacturing error, a parasitic resistance has appeared in series with the source of M_1 in Fig. 1a. Assuming $\lambda > 0$ and neglecting other capacitances, determine the input and output poles of the circuit.

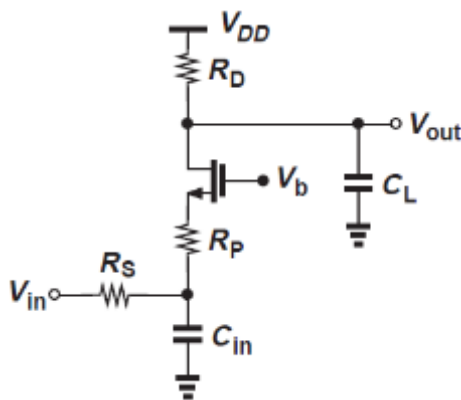


Fig 1a. Figure of Question 3

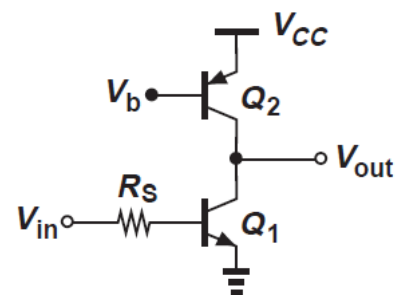


Fig 1b. Figure of Question 4

- 4) By using the open-circuit time constant method, determine the upper corner frequency (–3 dB frequency) of the amplifier in Fig 1b. Assume that $V_A < \infty$.
- 5) The amplifier below must drive a load capacitance of 100 fF. Use 2N2222 npn transistor in LTSpice.
 - a. Select the input DC level to obtain an output DC level of 1.2 V.
 - b. Plot the frequency response and find the low-frequency gain and the –3 dB bandwidth from the simulation results.

