


Isolator :

$$S = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$



we obtain $b_2 = a_1$ and
when a_2 wave applies the
port 2 there is no wave at port 1.

Circulator

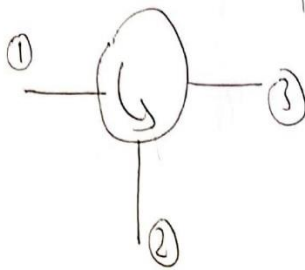


An interesting non-reciprocal 3-port is the circulator.
The S-matrix corresponding to the ideal form of a circulator
is,

$$S = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

$$S_{ii} = 0$$

The ideal circulator is lossless ($S^* S = I$)

Example:

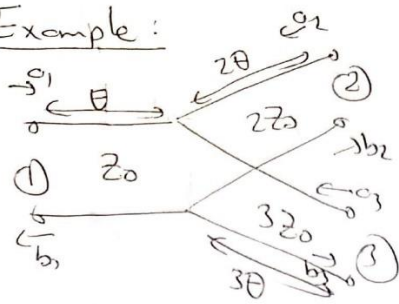

Find the S matrix of this three-port circuit when $\theta = \pi/2$

$$I_1 = I_2 = I_3 = 0$$

$$S_{11} = \Gamma_1 = \frac{b_1}{a_1} \Big|_{a_2=a_3=0}$$

$$S_{11} = \frac{(2Z_0 // 3Z_0) - Z_0}{(2Z_0 // 3Z_0) + Z_0} = \frac{1}{11} \quad , \quad S_{22} = \frac{(Z_0 // 3Z_0) - 2Z_0}{(Z_0 // 3Z_0) + 2Z_0} = -S_{11}$$

$$S_{33} = \Gamma_3 = \frac{(Z_0 // 2Z_0) - 3Z_0}{(Z_0 // 2Z_0) + 3Z_0} = -7/11$$

$$V_i = \sqrt{Z_{0i}} (a_i + b_i)$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=a_3=0}$$

$$V_{b1} = V_{a2} + V_{b2} \Rightarrow \sqrt{Z_0} b_1 = \sqrt{2Z_0} (a_2 + b_2)$$

$$S_{12} = \sqrt{2} (1 + S_{22}) = \frac{6\sqrt{2}}{11}$$

$$S_{13} = \frac{b_1}{a_3} \Big|_{a_1=a_2=0} = \sqrt{3} (1 + S_{33}) = \frac{4\sqrt{3}}{11}$$

$$S_{21} = \frac{1}{\sqrt{2}} (1 + S_{11}) = \frac{6\sqrt{2}}{11} = S_{12} \quad , \quad S_{23} = \sqrt{\frac{3}{2}} (1 + S_{33}) = \frac{2\sqrt{6}}{11}$$


$$S_{31} = \frac{1}{\sqrt{3}} (1 + S_{11}) = \frac{4\sqrt{3}}{11} = S_{13} \quad , \quad S_{32} = \sqrt{\frac{2}{3}} (1 + S_{22}) = \frac{2\sqrt{6}}{11} = S_{23}$$

$$[S] = \frac{1}{11} \begin{bmatrix} 1 & 6\sqrt{2} & 4\sqrt{3} \\ 6\sqrt{2} & -5 & 2\sqrt{6} \\ 4\sqrt{3} & 2\sqrt{6} & -7 \end{bmatrix} \Rightarrow |S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1$$

$$I_1 \neq 0, I_2 \neq 0, I_3 \neq 0 \quad , \quad \beta I_1 = \frac{\pi}{2} \quad , \quad \beta I_2 = \pi \quad , \quad \beta I_3 = \frac{3\pi}{2}$$

$$S'_{ij} = S_{ij} e^{-j\beta(I_i + I_j)}$$
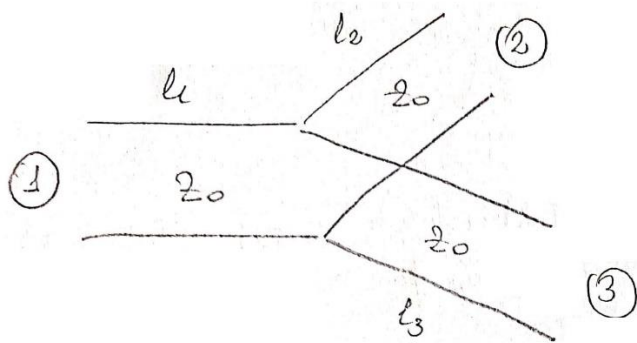
$$\Rightarrow S' = \frac{1}{11} \begin{bmatrix} -1 & j6\sqrt{2} & 4\sqrt{3} \\ j6\sqrt{2} & -5 & -j2\sqrt{6} \\ 4\sqrt{3} & -j2\sqrt{6} & 7 \end{bmatrix}$$



$$l_1 = \frac{\pi}{2}$$

$$l_2 = \frac{\lambda}{6}$$

$$l_3 = \frac{\pi}{4}$$

$$l_1 = l_2 = l_3 = 0 \quad \text{tam simetrik dur}$$

diğer iki port sonlandırılıyor

$$\begin{bmatrix} S_{11} & S_{12} & S_{12} \\ S_{12} & S_{11} & S_{12} \\ S_{12} & S_{12} & S_{11} \end{bmatrix}$$

$$S_{11} = \rho_1 = -\frac{1}{3} = 0.33 \angle \pi$$

$$2|S_{12}|^2 + |S_{11}|^2 = 1$$

$$|S_{12}| = \frac{2}{3}$$

$$\begin{aligned} & \frac{2 \cdot \frac{4}{9} + \frac{1}{9}}{1} = 1 \\ & \rightarrow 2 \cdot \frac{4}{9} + \frac{1}{9} = 1 \end{aligned}$$

$$S_{12}^* (S_{11} + S_{12}) = -S_{12} S_{11}^*$$

$$S_{12} = 0.66 \angle 0$$

$$S'_{ij} = S_{ij} e^{-j(\beta l_1 + \beta l_2)}$$

$$\beta l_1 = \pi$$

$$\beta l_2 = \frac{\pi}{3}$$


$$\beta l_3 = \frac{\pi}{2}$$

$$S'_{11} = 0.33 e^{-j(\pi + \pi + \pi)} = 0.33 e^{-j\pi}$$

$$S'_{12} = 0.66 e^{-j(0 + \pi + \pi/3)} = 0.66 e^{-j\frac{4\pi}{3}}$$

$$S'_{13} = 0.66 e^{-j(0 + \pi + \pi/2)} = 0.66 e^{-j\frac{3\pi}{2}}$$
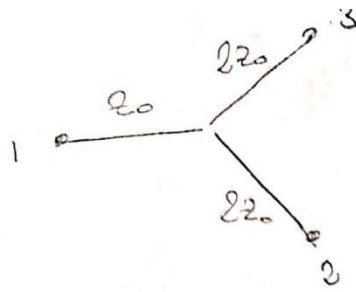
$$\frac{1}{3} \begin{bmatrix} (1 \angle -\pi) (2 \angle -4\pi/3) (2 \angle -3\pi/2) \\ (2 \angle -4\pi/3) (1 \angle -2\pi/3) (2 \angle -5\pi/6) \\ (2 \angle -3\pi/2) (2 \angle -5\pi/6) (1 \angle 0) \end{bmatrix}$$



$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{22} & S_{23} \\ S_{13} & S_{23} & S_{22} \end{bmatrix}$$

$$S_{11} = 0 \quad 2|S_{12}|^2 = 1 \quad |S_{12}| = \frac{1}{\sqrt{2}}$$

$$S_{22} \text{ in } Z_0 \parallel Z_0 \rightarrow \frac{2Z_0}{3}$$

$$\rho_2 = \rho_3 = \frac{\frac{2Z_0}{3} - 2Z_0}{\frac{2Z_0}{3} + 2Z_0} = -\frac{1}{2}$$

$$|S_{12}|^2 + |S_{23}|^2 + |S_{22}|^2 = 1$$

$$\frac{1}{2} + |S_{23}|^2 + \frac{1}{4} = 1 \quad |S_{23}| = \frac{1}{2}$$

$$[S^*]^T [S] = [I] \quad \text{ kayipaz }$$

$$S_{11} S_{21}^* + S_{12} S_{22}^* + S_{13} S_{23}^* = 0$$

$$S_{22}^* + S_{23}^* = 0 \quad S_{23} = \frac{1}{2} \quad S_{12} = \frac{1}{\sqrt{2}}$$

$$\begin{bmatrix} 0 & 1/\sqrt{2} & 1/\sqrt{2} \\ 1/\sqrt{2} & -1/2 & 1/2 \\ 1/\sqrt{2} & 1/2 & -1/2 \end{bmatrix}$$