



DIGITAL SYSTEM DESIGN APPLICATION – EHB 436E

Experiment V-Bonus Questions

Yiğit Bektaş GÜRSOY

040180063

Class Lecturer: Sıddıka Berna Örs Yalçın

Class Assistant:

Serdar Duran

Yasin Fırat Kula

Mehmet Onur Demirtürk

1. SLIDING LEDS

- Verilog Code

```
`timescale 1ns / 1ps

module sliding_leds#(
    parameter MAX_CNT_DEST = 500 // 100MHz / 10 = 10M
) (
    input rst,clk,
    input [1:0]SW,
    output reg [15:0]LED
);
    reg [$clog2(MAX_CNT_DEST-1)-1:0] divcounter = 0;
    reg divclk;
    always @(posedge clk or posedge rst)

        begin
            if(rst)
                LED<= 16'h0001;
            else
                begin
                    case(SW)
                        //stop
                        2'b00:
                            LED <= LED;

                        //10Hz
                        2'b01:
                            begin
                                if(LED == 16'h8000)
                                    begin
                                        if (divcounter % (MAX_CNT_DEST-1) == 0 && divcounter !=0)
                                            LED <= 16'h0001;
                                        end
                                    end
                                else
                                    begin
                                        if (divcounter % (MAX_CNT_DEST-1) == 0 && divcounter !=0)
                                            LED <= LED<<1'b1;
                                        end
                                    end
                                end
                            end


                        //20Hz
                        2'b10:
                            begin
                                if(LED == 16'h8000)
                                    begin
                                        if (divcounter % ((MAX_CNT_DEST-1)/2) == 0 && divcounter !=0)
                                            LED <= 16'h0001;
                                        end
                                    end
                                else
                                    begin
                                        if (divcounter % ((MAX_CNT_DEST-1)/2) == 0 && divcounter !=0)
                                            LED <= LED<<1'b1;
                                        end
                                    end
                                end
                            end

                        //50Hz
                        2'b11:
                            begin
                                if(LED == 16'h8000)
                                    begin
                                        if (divcounter % ((MAX_CNT_DEST-1)/5) == 0 && divcounter !=0)
                                            LED <= 16'h0001;
                                        end
                                    end
                                else
                                    begin
                                        if (divcounter % ((MAX_CNT_DEST-1)/5) == 0 && divcounter !=0)
                                            LED <= LED<<1'b1;
                                        end
                                    end
                                end
                            end
                        default : LED <= LED;
                    endcase
                end
            end
        end
```

```
always @(posedge clk or posedge rst)
begin
    if(rst)
        divcounter <=0;
    else
        begin
            if (divcounter == MAX_CNT_DEST)
                divcounter <= 0;
            else
                divcounter <= divcounter+1;
        end
    end
endmodule
```

- Behavioral Simulation

 - Our input named clk specifies the fpga clk. Our rst input initializes the system and lights the first led. Our SW inputs change the flashing speed of the leds (50Mhz, 20Mhz, 10Mhz), and in the 00 state, the leds keep their last state. As seen in the simulation, the frequencies of the LEDs increased and took up less space in the simulation. Frequency speeds can be controlled with switches.



- Realization

- Frequency adjustment was made with the switch case structure. An rst definition was made before these cases started, the rst state is set to 1 before the program starts. In addition to this structure, there is always block where the frequency rate is set.

- Utilization report and critical path slack

➤ Setup Time

Unconstrained Paths - NONE - NONE - Setup											
Name	Slack	Levels	Routes	High Fanout	From	To	Total ... 1	Logic Delay	Net Delay	Requi...	Source Clock
Path 1	∞	12	9	29	divcounter_reg[4]/C	LED_reg[1]/CE	9.027	3.372	5.655	∞	
Path 2	∞	12	9	29	divcounter_reg[4]/C	LED_reg[2]/CE	9.027	3.372	5.655	∞	
Path 3	∞	12	9	29	divcounter_reg[4]/C	LED_reg[4]/CE	8.888	3.372	5.516	∞	
Path 4	∞	12	9	29	divcounter_reg[4]/C	LED_reg[0]/CE	8.881	3.372	5.509	∞	
Path 5	∞	12	9	29	divcounter_reg[4]/C	LED_reg[3]/CE	8.881	3.372	5.509	∞	
Path 6	∞	12	9	29	divcounter_reg[4]/C	LED_reg[3]_lopt_replica/CE	8.881	3.372	5.509	∞	
Path 7	∞	12	9	29	divcounter_reg[4]/C	LED_reg[4]_lopt_replica/CE	8.881	3.372	5.509	∞	
Path 8	∞	12	9	29	divcounter_reg[4]/C	LED_reg[5]/CE	8.850	3.372	5.478	∞	
Path 9	∞	12	9	29	divcounter_reg[4]/C	LED_reg[5]_lopt_replica/CE	8.850	3.372	5.478	∞	
Path 10	∞	12	9	29	divcounter_reg[4]/C	LED_reg[6]/CE	8.850	3.372	5.478	∞	

➤ Hold Time


Unconstrained Paths - NONE - NONE - Hold

Name	Slack ^{^1}	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement
Path 11	∞	1	1	3	LED_reg[3]/C	LED_reg[4]_lopt_replica/D	0.262	0.128	0.134	-∞
Path 12	∞	1	1	3	LED_reg[14]/C	LED_reg[15]/D	0.268	0.141	0.127	-∞
Path 13	∞	1	1	3	LED_reg[8]/C	LED_reg[9]/D	0.274	0.141	0.133	-∞
Path 14	∞	1	1	3	LED_reg[5]/C	LED_reg[6]/D	0.275	0.141	0.134	-∞
Path 15	∞	1	1	3	LED_reg[8]/C	LED_reg[9]_lopt_replica/D	0.277	0.141	0.136	-∞
Path 16	∞	1	1	3	LED_reg[5]/C	LED_reg[6]_lopt_replica/D	0.277	0.141	0.136	-∞
Path 17	∞	1	1	3	LED_reg[10]/C	LED_reg[11]/D	0.278	0.141	0.137	-∞
Path 18	∞	2	1	3	LED_reg[3]/C	LED_reg[0]/D	0.303	0.227	0.076	-∞
Path 19	∞	1	1	3	LED_reg[3]/C	LED_reg[4]/D	0.322	0.128	0.194	-∞
Path 20	∞	1	1	3	LED_reg[11]/C	LED_reg[12]_lopt_replica/D	0.325	0.141	0.184	-∞

➤ Utilization Summary

Summary

Resource	Utilization	Available	Utilization %
LUT	50	32600	0.15
FF	38	65200	0.06
IO	20	210	9.52

 

- There are 50LUT , 38FF(flip-flop) and 20IO (input-out) in usage in our device.