
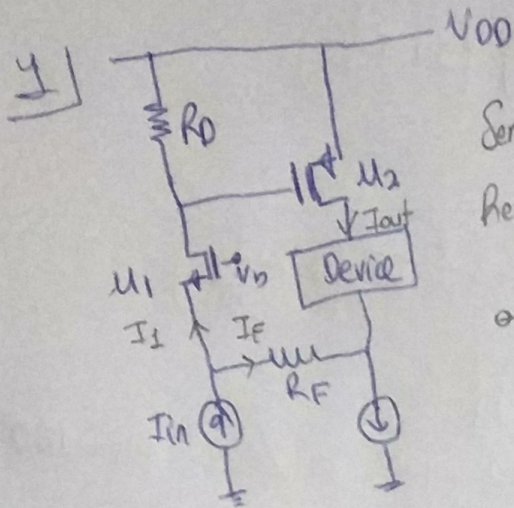


# 

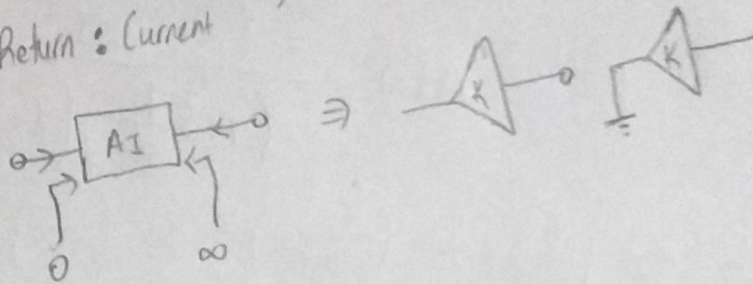


Sense : Current  
Return : Current


CL Amplifier  $\Rightarrow$  Shunt-Series Amplifier



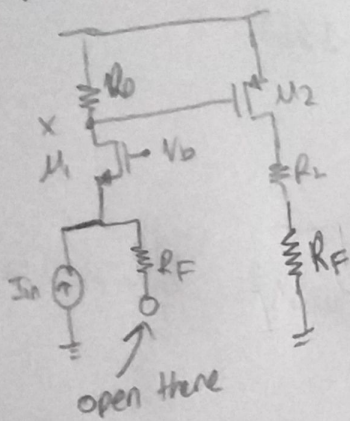When we break the loop, the new circuit is



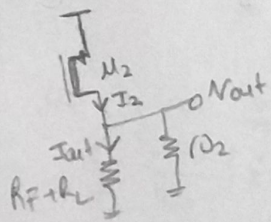Since  $\lambda_1 = 0$ , and DC current source is open in AC analysis  
 $V_x = I_{in} R_o$  (All current flows into the transistor)  
However  $\lambda_2 \neq 0$



$$V_{out} = -g_{m2} [(R_L + R_F) \parallel r_{o2}] V_x$$


$$I_2 = \frac{V_{out}}{[(R_L + R_F) \parallel r_{o2}]} = -g_{m2} V_x$$

$$I_{out} = \frac{r_{o2}}{R_F + R_L + r_{o2}} I_2 = -\frac{g_{m2} r_{o2}}{R_F + R_L + r_{o2}} V_x$$

Simple Current Division


$$\Rightarrow A_I = \frac{I_{out}}{I_{in}} = -\frac{g_{m2} r_{o2} R_o}{R_F + R_L + r_{o2}}$$
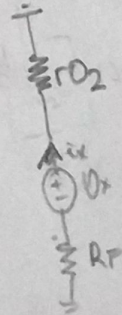
$$\Rightarrow R_{in} = \frac{1}{g_{m1}} ; R_{out} =$$



$$\Rightarrow \frac{V_x}{i_x} = R_{out} = r_{o2} + R_F$$

Let's determine K-factor

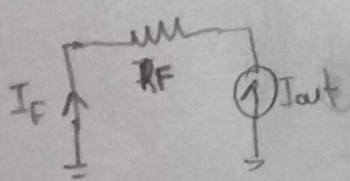

$$\Rightarrow K = \frac{I_F}{I_{out}} = -1$$

$$A_{I,CL} = \frac{A_I}{1 + K A_I} = \frac{-\frac{g_{m2} r_{o2} R_o}{R_F + R_L + r_{o2}}}{1 + (-1) \left( -\frac{g_{m2} r_{o2} R_o}{R_F + R_L + r_{o2}} \right)}$$

$$A_{I,CL} = -\frac{g_{m2} r_{o2} R_o}{R_F + R_L + r_{o2} + g_{m2} r_{o2} R_o}$$

$$R_{in,CL} = \frac{R_{in}}{1 + K A_I} = \frac{\frac{1}{g_{m1}}}{1 + \frac{g_{m2} r_{o2} R_o}{R_F + R_L + r_{o2}}}$$

$$R_{out,CL} = (1 + K A_I) R_{out} = \left( 1 + \frac{g_{m2} r_{o2} R_o}{R_F + R_L + r_{o2}} \right) [r_{o2} + R_F]$$



$$2) A_0 = 10^4 \left( \frac{V}{V} \right)$$

$$f_1 = 10^5 \text{ Hz}$$

$$f_2 = 3.16 \times 10^5 \text{ Hz}$$

$$f_3 = 10^6 \text{ Hz}$$

$$\Rightarrow A(s) = \frac{A_0}{\left(1 + \frac{s}{f_1}\right) \left(1 + \frac{s}{f_2}\right) \left(1 + \frac{s}{f_3}\right)}$$

$$A(s) = \frac{10^4}{\left(1 + \frac{s}{10^5}\right) \left(1 + \frac{s}{3.16 \times 10^5}\right) \left(1 + \frac{s}{10^6}\right)}$$

$$\angle A(s) = - \left[ \tan^{-1} \left( \frac{f}{10^5} \right) + \tan^{-1} \left( \frac{f}{3.16 \times 10^5} \right) + \tan^{-1} \left( \frac{f}{10^6} \right) \right]$$

We want a phase margin of  $45^\circ$ ,  $PM = \angle A(s) + 180^\circ \Rightarrow \angle A(s) = PM - 180^\circ$

$$\Rightarrow \angle A(s) = 45^\circ - 180^\circ = -135^\circ$$

$$\Rightarrow = \left[ \tan^{-1} \left( \frac{f_1}{10^5} \right) + \tan^{-1} \left( \frac{f_2}{3.16 \times 10^5} \right) + \tan^{-1} \left( \frac{f_3}{10^6} \right) \right] = 135^\circ$$

By using Wolfram Alpha we find  $f_1 \approx 3.16 \times 10^5 \text{ Hz}$

$$A(j\omega_1) = \frac{10^4}{\left(1 + \frac{j 3.16 \times 10^5}{10^5}\right) \left(1 + \frac{j 3.16 \times 10^5}{3.16 \times 10^5}\right) \left(1 + \frac{j 3.16 \times 10^5}{10^6}\right)} \Rightarrow |A(j\omega_1)| = 2034.25 \left( \frac{V}{V} \right)$$

$$|A(j\omega_1)| \text{ (dB)} = 20 \log_{10} (2034.25) \approx 66.17 \text{ dB (open-loop gain)}$$

Since at gain-crossover frequency loop gain is 0 dB. We can calculate  $\beta$  -

$$\beta \text{ (dB)} \approx -66.17 \text{ dB} \Rightarrow 20 \log_{10} \beta = -66.17 \Rightarrow \beta = 10^{-\frac{66.17}{20}} \approx 6.91 \times 10^{-4}$$


Then, we can calculate the closed-loop gain by the formula  $A_f = \frac{A_0}{1 + K A_0}$

$$\Rightarrow A_{f0} = \frac{10^4}{1 + (6.91 \times 10^{-4})(10^4)} = \frac{10^4}{5.91} = 1.69 \times 10^3 \left( \frac{V}{V} \right)$$


$$\Rightarrow A_{f0 \text{ (dB)}} = 20 \log (1.69 \times 10^3) = 64.56 \text{ dB}$$





3

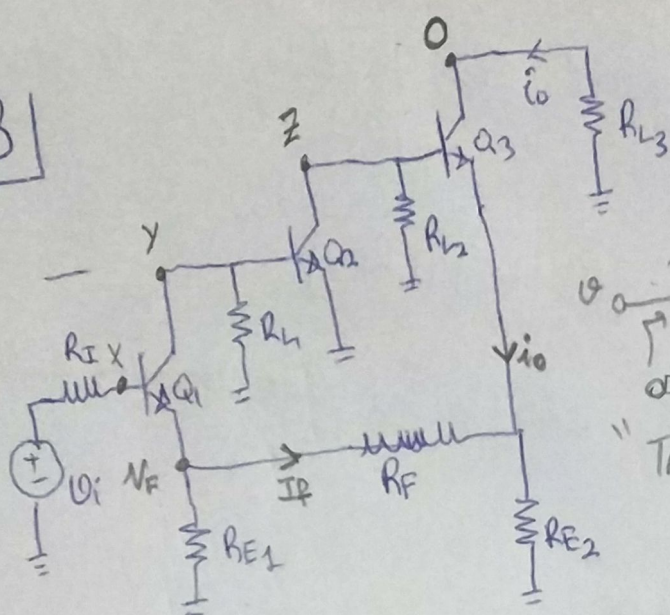

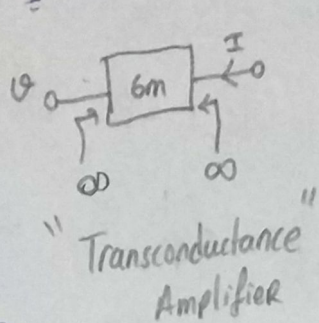→ we are sensing current  
→ and returning voltage (\$U\_{be}\$ subtractor)





"Transconductance Amplifier"

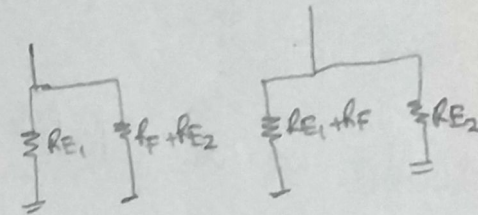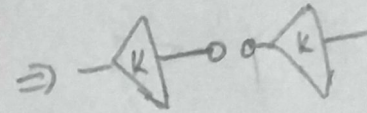

$$\frac{i_o}{v_i} = \frac{v_x}{v_i} \cdot \frac{v_y}{v_x} \cdot \frac{v_z}{v_y} \cdot \frac{i_o}{v_z} \Rightarrow \text{Let's calculate these gains separately}$$

$$\frac{v_x}{v_i} = \frac{(\beta+1)[R_{E1} \parallel (R_F + R_{E2})] + r_{\pi 1}}{(\beta+1)[R_{E1} \parallel (R_F + R_{E2})] + r_{\pi 1} + R_I}$$

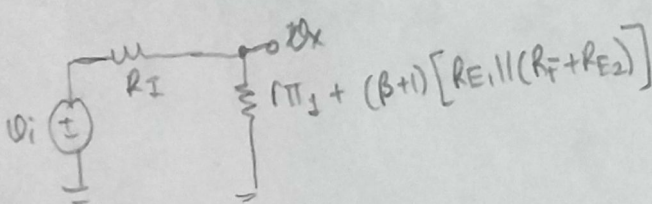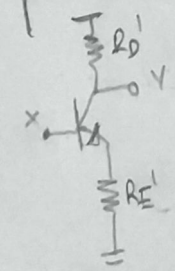
$$\frac{v_y}{v_x} = - \frac{g_{m2}[R_{L2} \parallel r_{\pi 2}]}{1 + g_{m2}[R_{E2} \parallel (R_F + R_{E2})]}$$



"Voltage Divider"

"Emitter Degenerated CE stage with \$g\_m' = \frac{g\_m}{1 + g\_m R\_{E1}}\$"
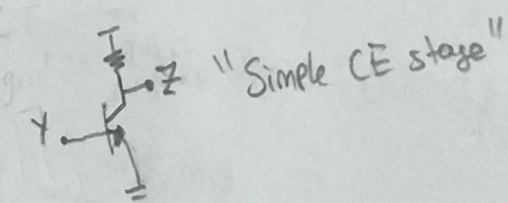
$$\frac{v_z}{v_y} = - g_{m2} \left\{ R_{L2} \parallel [r_{\pi 3} + (\beta+1)(R_{E1} + R_F) \parallel R_{E2}] \right\}$$



"Simple CE stage"

"emitter degenerated CE stage"

$$\frac{i_o}{v_z} = \frac{g_{m3}}{1 + g_{m3}[(R_{E1} + R_F) \parallel R_{E2}]}$$

Then, the open loop gain \$G\_{m,OL}\$ (We have assumed that collector and emitter currents are the same for \$Q\_3\$)


$$G_{m,OL} = \underbrace{\frac{(\beta+1)[R_{E1} \parallel (R_F + R_{E2})] + r_{\pi 1}}{(\beta+1)[R_{E1} \parallel (R_F + R_{E2})] + r_{\pi 1} + R_I}}_{\frac{v_x}{v_i}} \cdot \underbrace{\frac{g_{m1}[R_{L1} \parallel r_{\pi 2}]}{1 + g_{m1}[R_{E1} \parallel (R_F + R_{E2})]}}_{\frac{v_y}{v_x}} \cdot \underbrace{g_{m2} \left\{ R_{L2} \parallel [r_{\pi 3} + (\beta+1)(R_{E1} + R_F) \parallel R_{E2}] \right\}}_{\frac{v_z}{v_y}} \cdot \underbrace{\frac{g_{m3}}{1 + g_{m3}[(R_{E1} + R_F) \parallel R_{E2}]}}_{\frac{i_o}{v_z}}$$



→ We can calculate open-loop input resistance simply by looking into the base of the  $Q_1$ . That is,


$$R_{in, OL} = r_{\pi 1} + (\beta + 1) [(R_F + R_{E2}) \parallel R_{E1}]$$

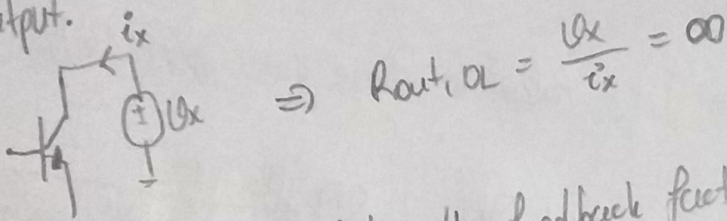→ Also, we can calculate the  $R_{out}$  by adding a test source in series to the output.



→ Now, we can calculate the feedback factor  $K$  in order to find closed-loop

Parameters

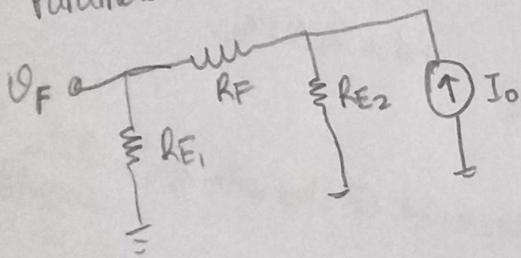

$$\Rightarrow K = \frac{V_t}{I_0} = \frac{R_{E2} \cdot R_{E1}}{R_{E1} + R_{E2} + R_F}$$

→ CLOSED-LOOP PARAMETERS

- $G_{m, CL} = \frac{G_{m, OL}}{1 + K G_{m, OL}}$
- $R_{in, CL} = R_{in, OL} (1 + K G_{m, OL})$
- $R_{out, CL} = R_{out, OL} (1 + K G_{m, OL})$