

10 December 2020

- 1) For the following circuit, $C_{GS} = 1 \text{ pF}$, $C_{SB} = 400 \text{ fF}$, $C_{\pi} = 100 \text{ fF}$, $g_{m1} = g_{m2} = 10 \text{ mS}$, $\beta = 50$, $R_{sig} = 100 \Omega$, and $R_L = 1 \text{ k}\Omega$. Assume $V_A = \infty$ and $\lambda = 0$. Considering just the given capacitors and using the open-circuit time constants method, find the upper corner frequency (-3 dB). Show all your work.

