
## Balun Transformer

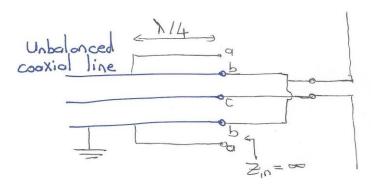

Balancel dipol antenna

> Motohing a cooxid coble to a dipole entenna using a balun transformer


Another type of quarter-wave transformer is called bolun transformer.

It is able to transform from a balanced (or agrounded) line (or load) line (or load) line (or load) without disturbing the equilibrium conditions on either line.

A bolun transformer can be used as an transition between on unbalanced coaxial line and a balanced antenna or two-wire line.

A two-wire line should be bollonced with respect to ground so that the conductors carry equal and opposite currents.

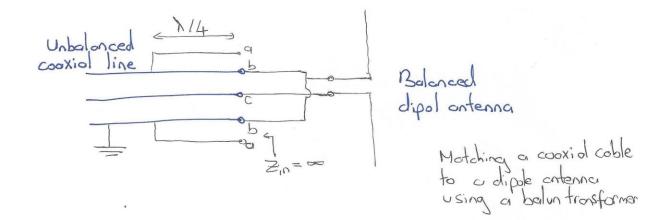If a cooxial line is connected to an unbolonced load, a current will be transmitted along the outside of the cooxial cable. This will result in high loss.



One type of bolun transformer is shown in the figure above.

It consists of a short-circuited quarter wavelength sleeve (arm) mounted concentrically around the end of a cooxial coble. The outer conductor of the cooxial line is grounded.

Since the bolun sleeve is a quarter-vove long and short-circuited, the input impedance at the open ends 'a-b' is infinite.

Hence, conductor b is isolated from ground, and the ends b-c of the coaxial cobe may be connected to a bolanced dipole antenna.