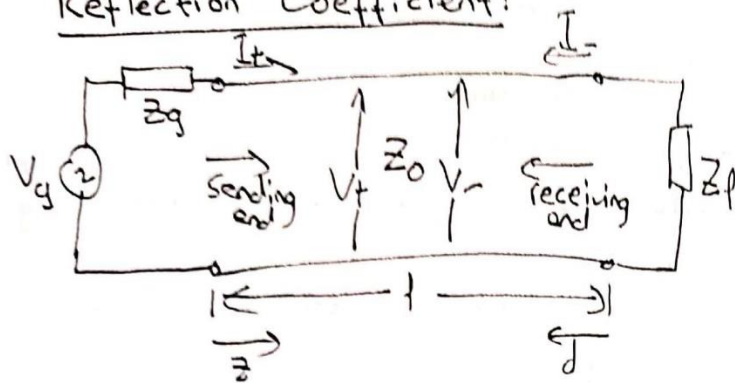


Reflection and Transmission Coefficients:

Reflection Coefficient:



If the load impedance equals the line characteristic impedance, there is no reflected traveling wave. ($V_- = \frac{I_+}{2} (Z_L - Z_0) e^{-\gamma l}$, $Z_L = Z_0 \Rightarrow V_- = 0$)

Because of the voltage-current relationship of the load point is fixed by the load impedance, we usually prefer to write down the expressions for the receiving end. Remember,

$$V = V_+ e^{-\gamma z} + V_- e^{\gamma z} \text{ and } I = I_+ e^{-\gamma z} + I_- e^{\gamma z} = Y_0 (V_+ e^{-\gamma z} - V_- e^{\gamma z})$$

If the line is of length l , the voltage and current at the receiving end become:

$$V = V_+ e^{-\gamma l} + V_- e^{\gamma l} \text{ and } I = Y_0 (V_+ e^{-\gamma l} - V_- e^{\gamma l})$$

and Z_L is,

$$Z_L = \frac{V_l}{I_l} = Z_0 \frac{V_+ e^{-\gamma l} + V_- e^{\gamma l}}{V_+ e^{-\gamma l} - V_- e^{\gamma l}}$$

We define the reflection coefficient, designated by Γ , as

Reflection coefficient = $\frac{\text{Reflected voltage or negative reflected current}}{\text{Incident voltage or current}}$

or $\Gamma \equiv \frac{V_{ref}}{V_{inc}} = \frac{-I_{ref}}{I_{inc}} = |\Gamma| e^{i\theta}$ (generally a complex quantity)

at any point on the line.

$|\Gamma|$ is never greater than 1 for a passive load.

The reflection coefficient at the receiving end is

$$\Gamma_f = \frac{V_- e^{\gamma l}}{V_+ e^{\gamma l}} = \frac{Z_l - Z_0}{Z_l + Z_0}$$

The generalized reflection coefficient is (at any z point on the line)

$$\Gamma = \frac{V_- e^{\gamma z}}{V_+ e^{-\gamma z}} = \frac{Z - Z_0}{Z + Z_0} \quad \text{where } Z \text{ is the line impedance at point } z.$$

If we let $z = l - d$, Γ at a point located distance d from the receiving end is,

$$\Gamma_d = \frac{V_- e^{\gamma(l-d)}}{V_+ e^{-\gamma(l-d)}} = \frac{V_- e^{\gamma l}}{V_+ e^{-\gamma l}} e^{-2\gamma d} = \underline{\underline{\Gamma_f e^{-2\gamma d}}}$$

$$\Gamma_d = \Gamma_f e^{-2\gamma d} = |\Gamma_f| e^{i\theta_f} e^{-2\alpha d} e^{-j2\beta d} = |\Gamma_f| e^{-2\alpha d} e^{j(\theta_f - 2\beta d)}$$

For a lossless line, $|\Gamma|$ remains constant, $\angle \Gamma$ changes with $-2\beta d$.

When $Z_f = Z_0$, there will be no reflection from the receiving end, then $\Gamma_f = 0$, so Γ_d also equals to zero. Thus, any $Z_f \neq Z_0$ impedance will create a reflected traveling wave towards to $-z$ direction. If $Z_s \neq Z_0$, this sending end impedance will also create a reflected wave towards to $+z$ direction.

Example:

A transmission line has a characteristic impedance of $50 - j0.012 \Omega$ and terminates in an impedance of $73 + j42.50 \Omega$. Determine Γ at the load.

$$\Gamma = \frac{Z_f - Z_0}{Z_f + Z_0} = 0.377 \angle 42.7^\circ = 0.2735 + j0.2525$$

Transmission Coefficient:

A reflection coefficient Γ exists at any point along an improperly terminated line.

The transmission coefficient T is defined as,

$$T \equiv \frac{\text{Transmitted voltage}}{\text{incident voltage}} = \frac{V_{tr}}{V_{inc}}$$

Let us define P_{inc} as incident power to the load, P_{ref} as reflected power from the load and P_{tr} as the transmitted power on the load.

Let the traveling waves at the receiving end be,

$$V_+ e^{-\gamma z} + V_- e^{\gamma z} = V_{tr} e^{-\gamma z} \quad \text{and} \quad Y_0 (V_+ e^{-\gamma z} - V_- e^{\gamma z}) = \frac{V_{tr}}{Z_L} e^{-\gamma z}$$

When we multiply the second eq. by Z_L and substitute the result into the first eq. we get

$$\Gamma = \frac{V_- e^{\gamma z}}{V_+ e^{-\gamma z}} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{and we use this result in the first eq. again}$$

$$T = \frac{V_{tr}}{V_+} = \frac{2Z_L}{Z_L + Z_0}$$

The net average power carried by the inc. and ref. waves is,

$$\langle P_{it} \rangle = \frac{|V_+ e^{-\alpha z}|^2}{2Z_0} - \frac{|V_- e^{\alpha z}|^2}{2Z_0}$$

and the average power carried to the load by the transmitted wave is,

$$\langle P_{tr} \rangle = \frac{|V_{tr} e^{-\alpha z}|^2}{2Z_L}$$

Setting $\langle P_{it} \rangle = \langle P_{tr} \rangle$ and using $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ and $T = \frac{2Z_L}{Z_L + Z_0}$, we obtain

$$T^2 = \frac{Z_L}{Z_0} (1 - \Gamma^2)$$

Example

A transmission line has $Z_0 = 75 + j0,01 \Omega$ and $Z_L = 70 + j50 \Omega$. a) $\Gamma = ?$ b) $T = ?$

c) verify the relationship between Γ and T d) verify that $T = 1 + \Gamma$

$$a) \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 0,33 \angle 76,68^\circ = 0,08 + j0,32$$

$$b) T = \frac{2Z_L}{Z_L + Z_0} = 1,12 \angle 16,51^\circ = 1,08 + j0,32$$

$$c) T^2 = 1,25 \angle 33,02^\circ, \quad \frac{Z_L}{Z_0} (1 - \Gamma^2) = 1,25 \angle 33^\circ$$

Thus we have verified the equation.

$$d) T = 1,08 + j0,32 = 1 + 0,08 + j0,32 = 1 + \Gamma$$

Thus we have verified that

$$\boxed{T = 1 + \Gamma}$$