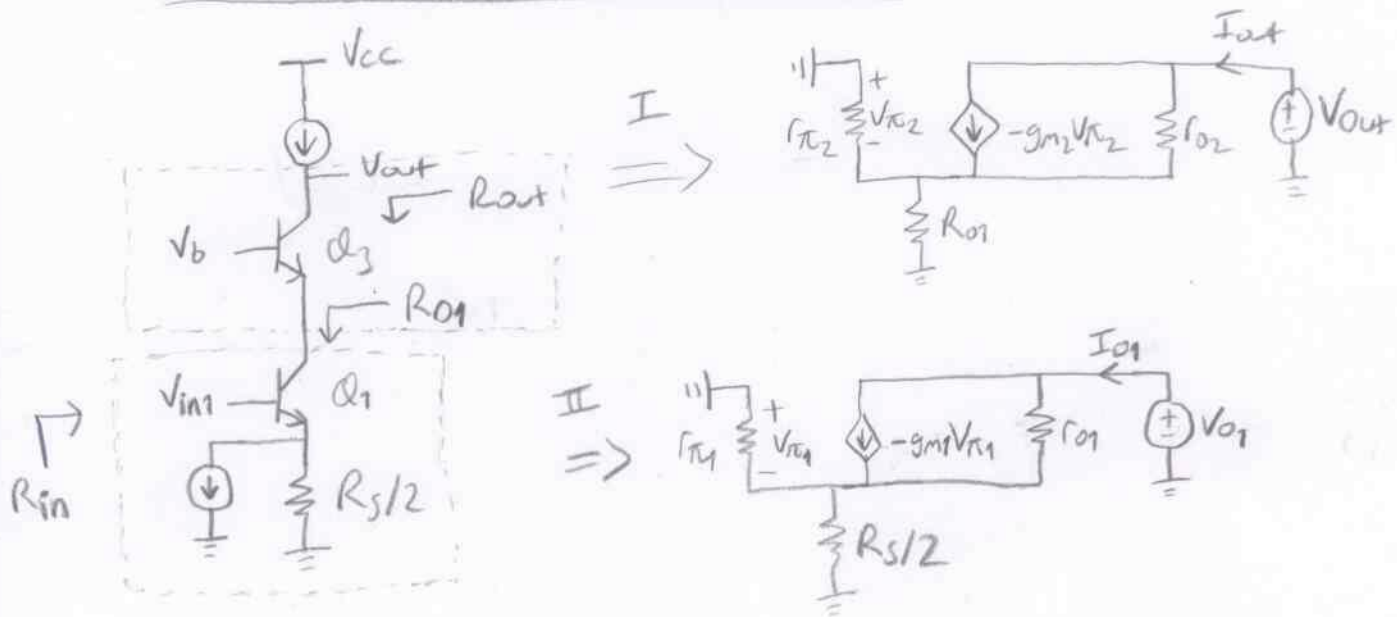


①

Half circuit of the differential amplifier



Calculating impedance seen looking into Q1's collector, Ro1:

$$V_{o1} = (I_{o1} + g_{m1}V_{\pi 1})r_{o1} + I_{o1}(r_{\pi 1} \parallel R_{s/2}) \quad V_{\pi 1} = I_{o1}(R_{s/2} \parallel r_{\pi 1})$$

$$\frac{V_{o1}}{I_{o1}} = R_{o1} = g_{m1}(R_{s/2} \parallel r_{\pi 1}) \cdot r_{o1} + r_{o1} + (r_{\pi 1} \parallel R_{s/2})$$

Calculating output impedance, Rout:

Small signal equivalent circuit I and II are identical, so their output impedance will be similar:

$$\frac{V_{out}}{I_{out}} = R_{out} = g_{m2}(R_{o1} \parallel r_{\pi 2}) \cdot r_{o2} + r_{o2} + (r_{\pi 2} \parallel R_{o1})$$

Transconductance of the amplifier, Gm:


$$G_m = \frac{I_{out}}{V_{in}} = \frac{i_c}{R_{in} \cdot i_B} = \frac{\beta}{R_{in}}$$

$$R_{in} = r_{\pi 1} + (\beta + 1)R_{s/2}$$


$$\approx \frac{g_{m1}}{1 + g_{m1}R_{s/2}}$$

$$\Rightarrow \boxed{A_v = G_m \cdot R_{out}}$$

② a)

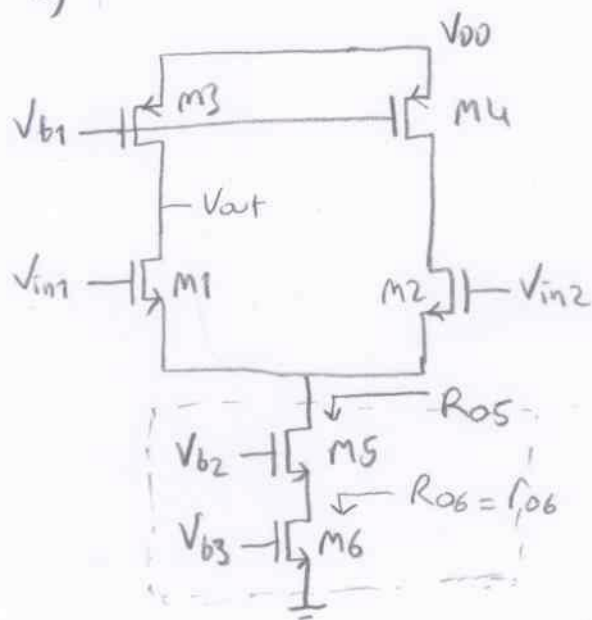


\Rightarrow

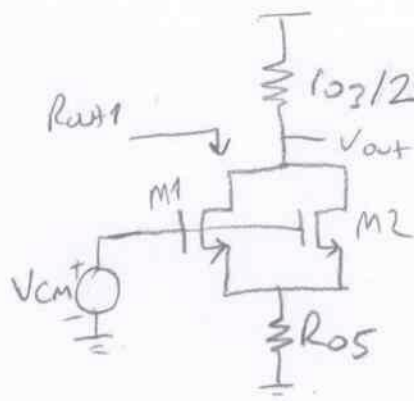

\Downarrow

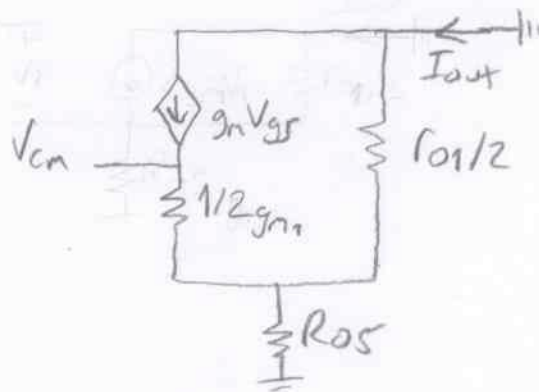
Because of two parallel transistor, transconductance will be $2g_{m1,2}$.



If we assume that $1/2g_{m1} \ll r_{01}/2$.

$$\Rightarrow G_m = \frac{I_{out}}{V_{cm}} = \frac{1}{1/2g_{m1} + R_{05}}$$

Calculation of R_{out1}

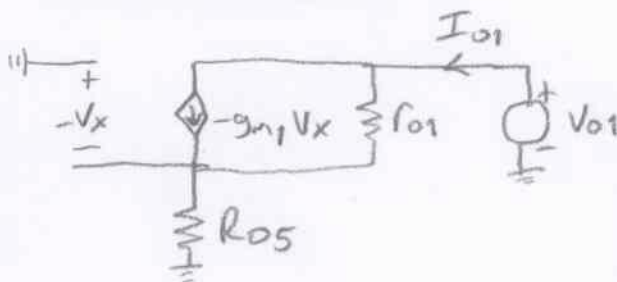

$$V_{01} = (I_{01} + g_{m1}V_x)/r_{01} + I_{01}R_{05}$$

$$V_x = I_{01} \cdot R_{05}$$



$$R_{out1} = g_{m1}r_{01} \cdot R_{05} + R_{05} + r_{01}$$

$$R_{out} = R_{out1} \parallel r_{03}/2$$

$$A_{cm} = -G_m \cdot R_{out}$$

\Leftarrow

② b)

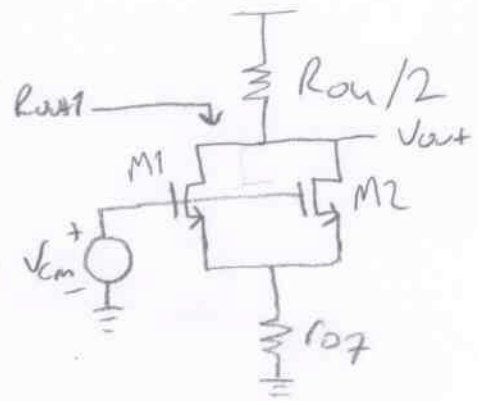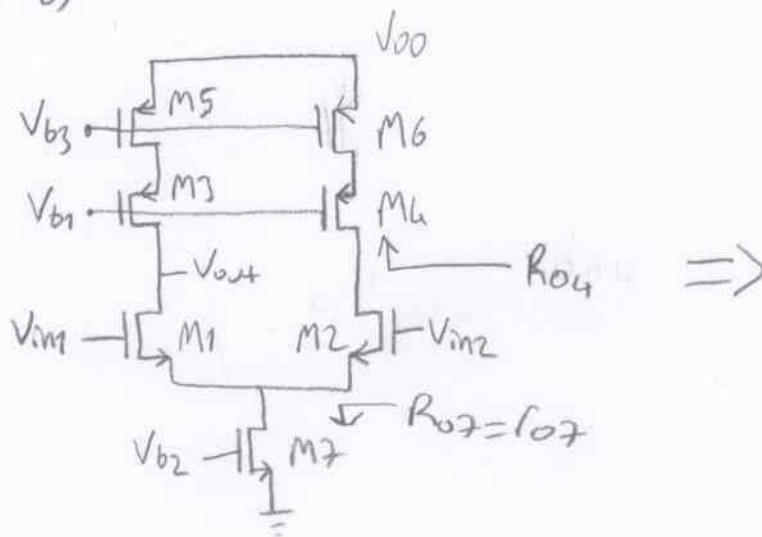

For R_{Ou} , we can use the expression of R_{O5} in Part a).

$$R_{Ou} = g_{m4} r_{Ou} r_{O6} + r_{Ou} + r_{O6}$$

This circuit has similar structure to the differential amplifier in Part a).


$$\text{So, } G_m = \frac{I_{out}}{V_{cm}} = \frac{1}{1/2g_{m1} + r_{O7}}$$

$$R_{out1} = g_{m1} r_{O1} r_{O7} + r_{O1} + r_{O7}$$

$$R_{out} = R_{out1} \parallel R_{Ou}/2$$

$$A_{cm} = -G_m \cdot R_{out} = \frac{-R_{out}}{1/2g_{m1} + r_{O7}}$$

③ a)

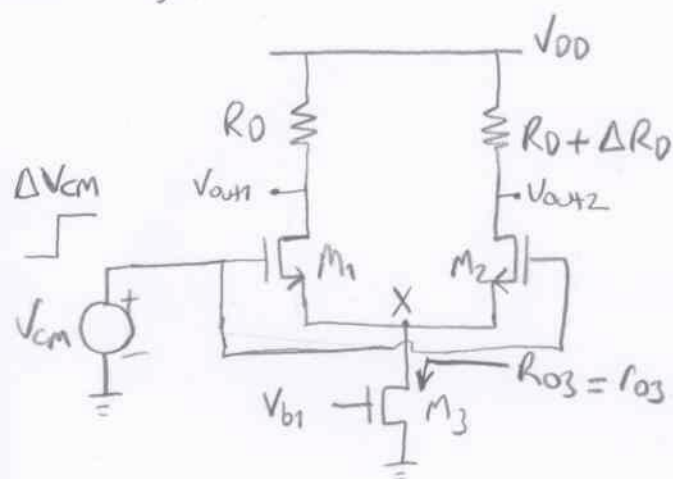

$$\Delta V_{GS} = \Delta V_{GS1} = \Delta V_{GS2}$$

$$\Delta I_D = \Delta I_{D1} = \Delta I_{D2}$$

$$\begin{aligned} \Delta V_{cm} &= \Delta V_{GS} + 2\Delta I_D \cdot R_{03} \\ &= \frac{\Delta I_D}{g_{m1}} + 2\Delta I_D \cdot r_{03} \end{aligned}$$


$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta R_D \cdot \Delta I_D$$

$$A_{vcm} = \left| \frac{\Delta V_{out}}{\Delta V_{cm}} \right| = \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{03}}$$

X node appears as virtual ground when differential input signals are applied.

So, $\Rightarrow A_{vdiff} = -g_{m1} R_D$

$$CMRR = \frac{|A_{vdiff}|}{|A_{vcm}|} = \frac{R_D}{\Delta R_D} \cdot (1 + 2g_{m1} \cdot r_{03})$$

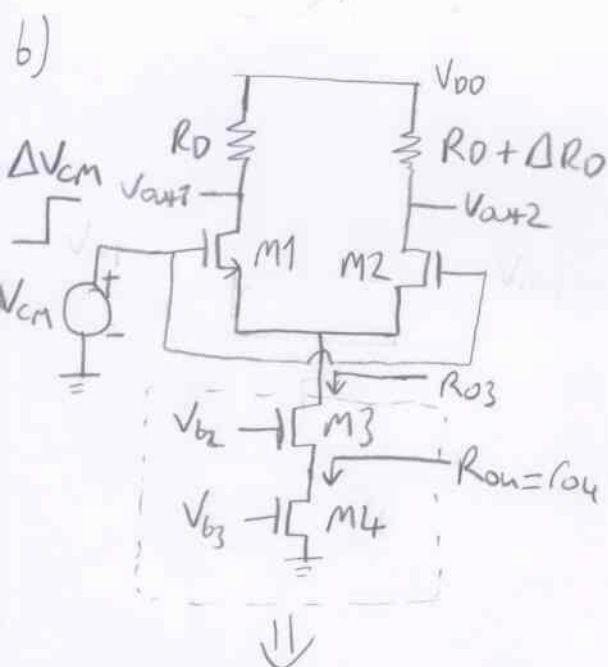


$$\Delta V_{cm} = \Delta V_{GS} + 2\Delta I_D R_{03} = \Delta I_D \left[\frac{1}{g_{m1}} + 2r_{03} \right]$$

$$\Delta V_{out} = -\Delta R_D \cdot \Delta I_D$$

$$A_{vcm} = \left| \frac{\Delta V_{out}}{\Delta V_{cm}} \right| = \frac{\Delta R_D}{1/g_{m1} + 2r_{03}}$$

$$A_{vdiff} = -g_{m1} \cdot R_D$$

$$\Rightarrow CMRR = \left| \frac{A_{vdiff}}{A_{vcm}} \right| = \frac{R_D}{\Delta R_D} \cdot (1 + 2g_{m1} g_{m3} r_{03} r_{04})$$

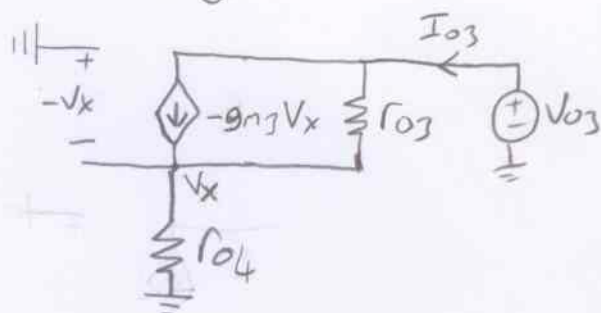


$$V_{03} = (I_{03} + g_{m3} V_x) r_{03} + I_{03} \cdot r_{04}$$

$$V_x = I_{03} \cdot r_{04}$$

$$\begin{aligned} R_{03} &= \frac{V_{03}}{I_{03}} = g_{m3} \cdot r_{03} \cdot r_{04} + r_{04} + r_{03} \\ &\approx g_{m3} \cdot r_{03} \cdot r_{04} \end{aligned}$$


(4)

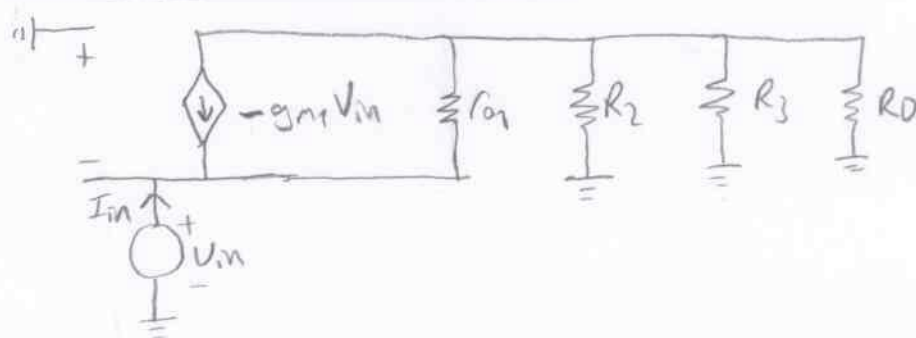Calculating input resistance R_{in} 

$$R_{eq} = R_2 // R_3 // R_O$$

$$V_{in} = (I_{in} - g_{m1}V_{in})r_{o1} + I_{in}R_{eq}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{r_{o1} + R_{eq}}{1 + g_{m1}r_{o1}}$$

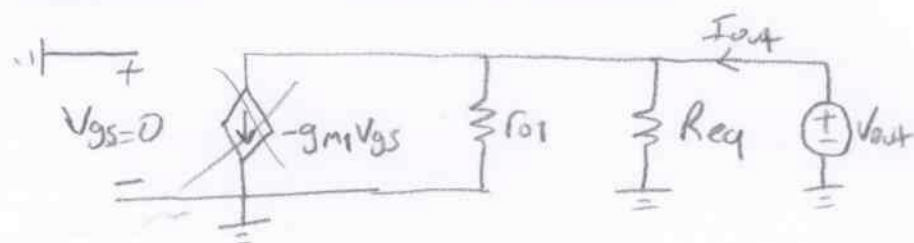Calculation of output resistance, R_{out} 


$$R_{out} = \frac{V_{out}}{I_{out}} = r_{o1} // R_{eq} \approx R_{eq}$$

Equal amount of current flows through input and output.

$$\text{So, } A_V = \frac{R_{out}}{R_{in}} = \frac{(1 + g_{m1}r_{o1})R_{eq}}{r_{o1} + R_{eq}}$$


⑤

Half of the amplifier

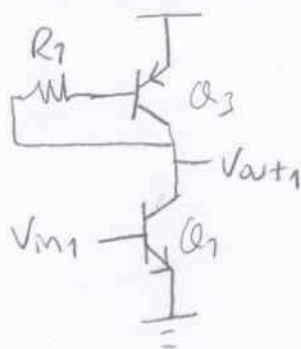


$$G_m = \frac{I_{out}}{V_{in}} = g_{m1}$$

Small signal equivalent circuit

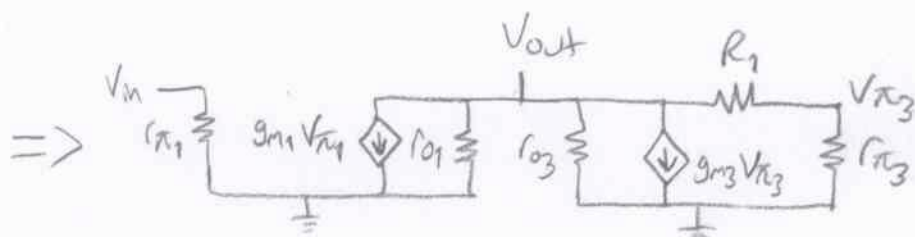

Calculation of Rout

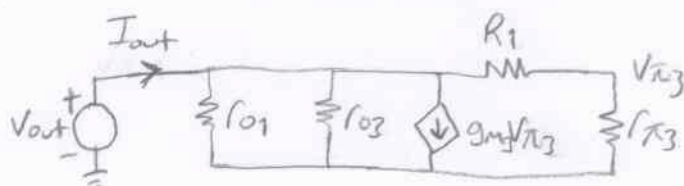

$$\frac{V_{out}}{V_{\pi 3}} = \frac{R_1 + r_{\pi 3}}{r_{\pi 3}} \Rightarrow V_{\pi 3} = \frac{V_{out} r_{\pi 3}}{R_1 + r_{\pi 3}}$$

$$(I_{out} - g_{m3} V_{\pi 3}) (r_{o1} \parallel r_{o3} \parallel (R_1 + r_{\pi 3})) = V_{out}$$


R_{eq}

$$\frac{V_{out}}{I_{out}} = R_{out} = \frac{R_{eq} (R_1 + r_{\pi 3})}{g_{m3} r_{\pi 3} R_{eq} + R_1 + r_{\pi 3}} \approx \frac{R_1 + r_{\pi 3}}{g_{m3} r_{\pi 3}}$$

$$A_v = \frac{V_{out}}{V_{in}} = -g_{m1} \cdot \frac{R_1 + r_{\pi 3}}{g_{m3} r_{\pi 3}}$$

Due to constant current, we can't change value of g_{m1} , g_{m3} and $r_{\pi 3}$.
However, we can increase R_1 to obtain higher gain. Note that after a certain R_1 value, input transistors will go into saturation region leading to gain drop.

AC simulation of the amplifier

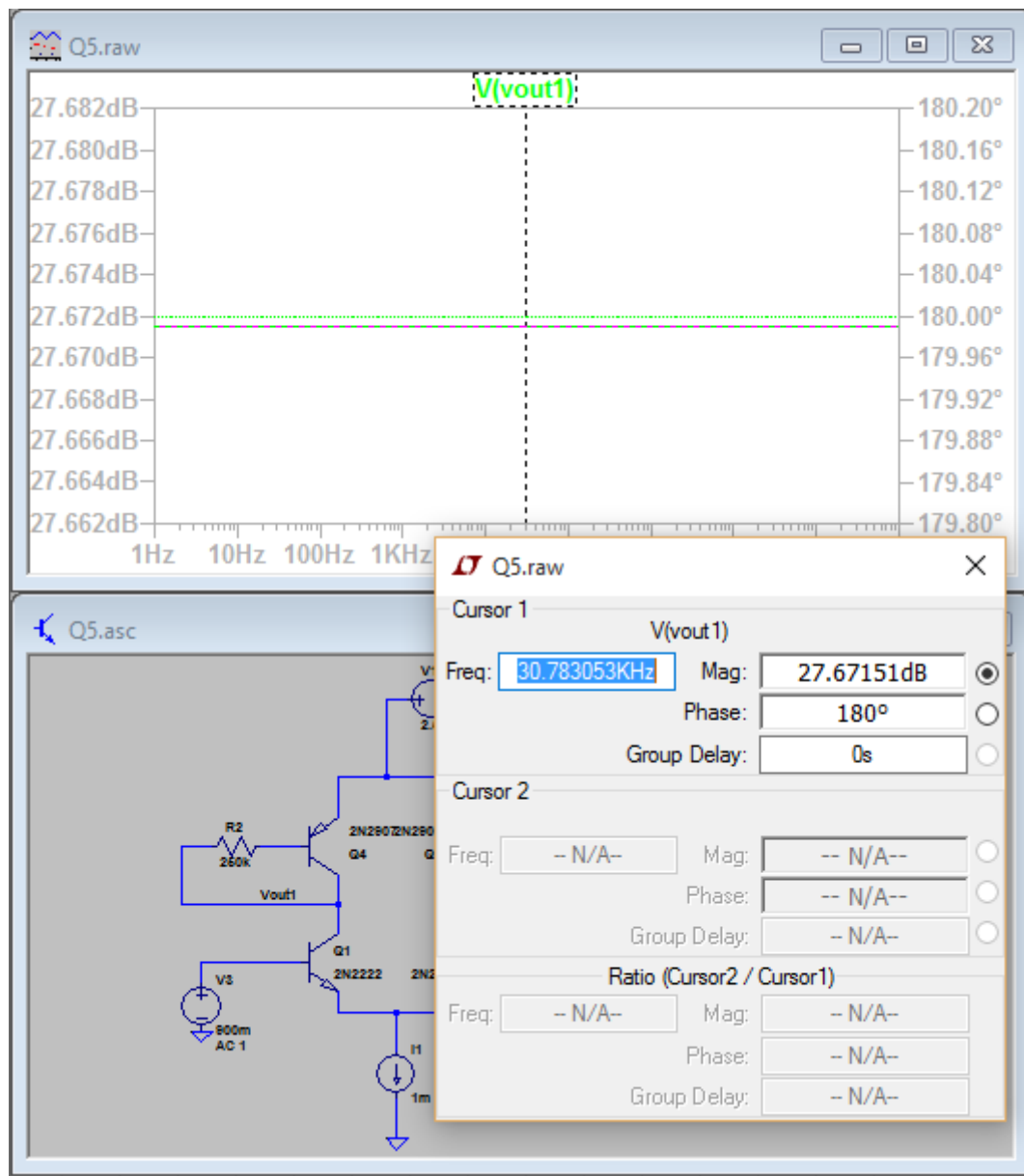

Transient response of the amplifier

