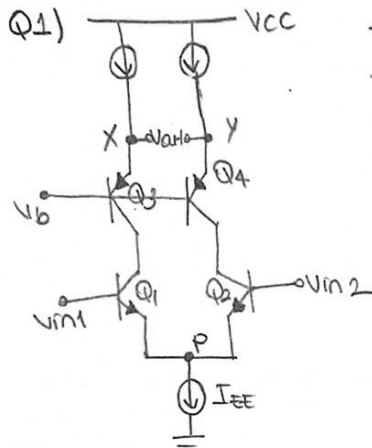



EHB 262 HW #6




Node P does not change with time in small signal analysis. Therefore it is AC Ground. So we get two half circuits which are symmetric. Gain is equal to the half-circuits' gains.

$$A_v = -G_m R_{out}$$

(current source becomes opened)

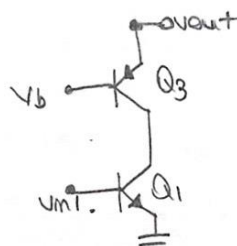

to calculate R_{out} ;

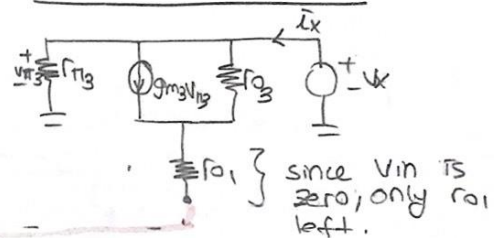


$$V_x = \left(i_x - g_{m3} V_x - \frac{V_x}{r_{D3}} \right) r_{O3} + \left(i_x - \frac{V_x}{r_{D3}} \right) r_{O1}$$

$$\rightarrow \frac{V_x}{i_x} = \frac{r_{O1} + r_{O3}}{1 + g_{m3} r_{O3} + \frac{g_{m3} r_{O3}}{\beta_3} + \frac{g_{m3} r_{O1}}{\beta_3}} = R_{out} \quad \left[\text{since } \beta \text{ is too big denominator is equal to } 1 + g_{m3} r_{O3} \text{ approximately} \right]$$


$$R_{out} \approx \frac{r_{O1} + r_{O3}}{1 + g_{m3} r_{O3}}$$
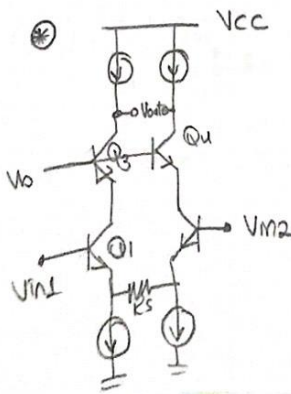
$$G_m = \frac{i_o}{V_{in}} \approx g_{m1} \rightarrow A_v = -g_{m1} \cdot \frac{r_{O1} + r_{O3}}{1 + g_{m3} r_{O3}} = \frac{V_y - V_x}{V_{in1} - V_{in2}}$$




Same logic exists for this diff also.

Half circuit;

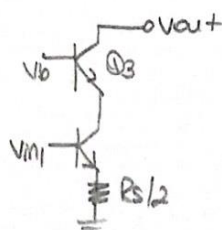

$$\frac{V_x}{R_S} = \frac{V_x}{R_S/2} \times \frac{V_x}{R_S/2}$$

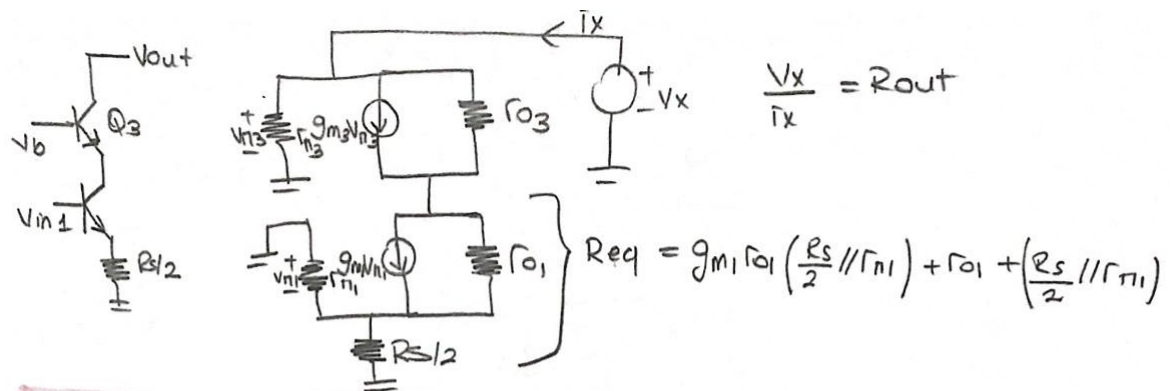can be written in series. X point does not change with time. So it is also AC GND. The point is in symmetry line.



$$\frac{V_x}{i_x} = g_{m3} r_{o3} (R_{eq} \parallel r_{\pi 3}) + r_{o3} + (R_{eq} \parallel r_{\pi 3}) = R_{out}$$


Gm calculation;

$$V_{\pi 1} \approx \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{R_s}{2}} \cdot V_{in} = \frac{1}{1 + g_{m1} \frac{R_s}{2}} \cdot V_{in}$$

we neglect
early effect
in Gm calculations
for ease

$$G_m = \frac{i_o}{V_{in}} = \frac{g_{m1} \cdot V_{\pi 1}}{V_{in}} = \frac{g_{m1}}{1 + g_{m1} \frac{R_s}{2}}$$
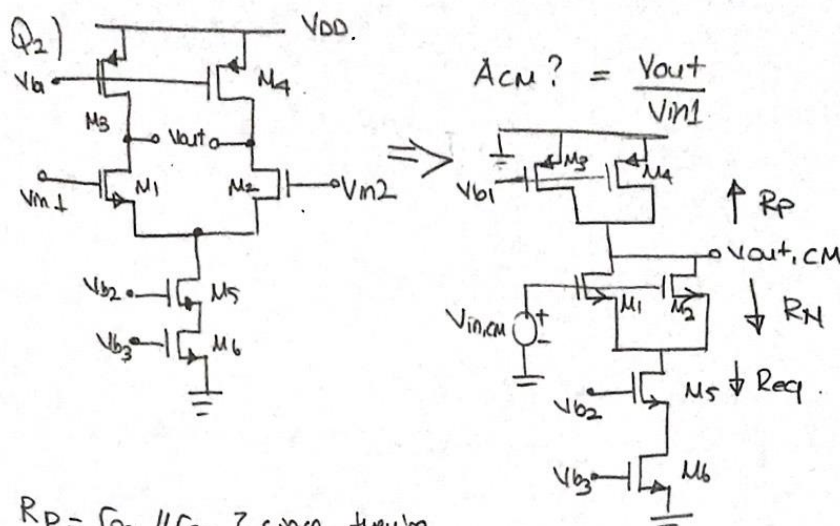
$$A_v = \frac{-g_{m1}}{1 + g_{m1} \frac{R_s}{2}} \left[g_{m3} r_{o3} (R_{eq} \parallel r_{\pi 3}) + r_{o3} + (R_{eq} \parallel r_{\pi 3}) \right]$$



$$R_P = r_{o3} \parallel r_{o4} \quad \left\{ \begin{array}{l} \text{since they're} \\ \text{identical} \end{array} \right. \Rightarrow \frac{r_{o3}}{2}$$


$$R_N = \frac{r_{o1}}{2} + R_{eq} + 2g_{m1} \frac{r_{o1}}{2} R_{eq} \approx g_{m1} r_{o1} R_{eq} \approx g_{m1} r_{o1} g_{m5} r_{o5} r_{o6}$$

$$R_{out} = R_P \parallel R_N = \frac{r_{o3}}{2} \parallel g_{m1} r_{o1} g_{m5} r_{o5} r_{o6} \quad \left\{ \begin{array}{l} \text{since second term is way too} \\ \text{bigger than the first} \end{array} \right.$$

Gm calculation

$$G_m = \frac{i_o}{V_{in,CM}} = \frac{2g_{m1} V_{gs1}}{V_{in,CM}} = \frac{2g_{m1}}{V_{in,CM}} \cdot \frac{1}{\frac{1}{2g_{m1}} + R_{eq}} \cdot V_{in,CM} \approx \frac{1}{R_{eq}}$$
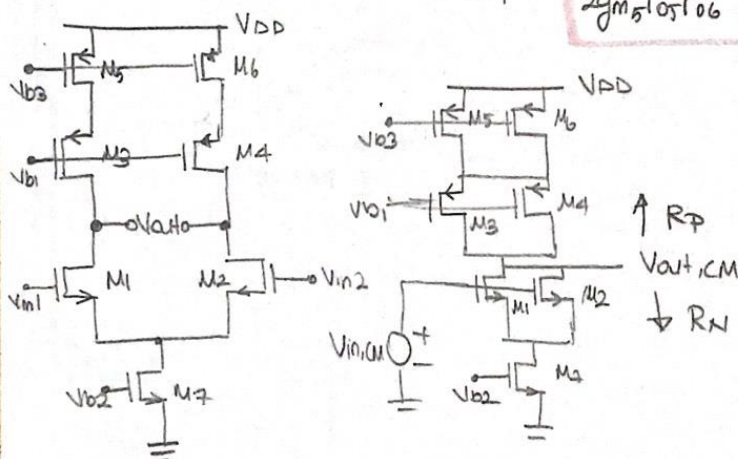
$$A_{CM} = -G_m R_{out} = \frac{-r_{o3}}{2R_{eq}} = \frac{-r_{o3}}{2g_{m5} r_{o5} r_{o6}}$$



$$R_P = 2g_{m3} \frac{r_{o3}}{2} \frac{r_{o5}}{2} + \frac{r_{o3}}{2} + \frac{r_{o5}}{2} \approx \frac{g_{m3} r_{o3} r_{o5}}{2} \quad \left. \vphantom{R_P} \right\} R_{out} = R_N \parallel R_P$$


$$R_N = 2g_{m1} \frac{r_{o1}}{2} r_{o7} + \frac{r_{o1}}{2} + r_{o7} \approx g_{m1} r_{o1} r_{o7}$$

Gm calculation

$$G_m = \frac{I_o}{V_{in,cm}} = \frac{2g_m V_{gs1}}{V_{in,cm}} = \frac{2g_m}{V_{in,cm}} \cdot \frac{1}{\frac{1}{2g_m} + r_{o2}} \cdot V_{in,cm} \approx \frac{1}{r_{o2}}$$


$$\Rightarrow A_{cm} = -\frac{1}{r_{o2}} \cdot \left(\frac{g_{m3} r_{o3} r_{o5}}{2} \parallel g_{m1} r_{o1} r_{o2} \right)$$

Q3)

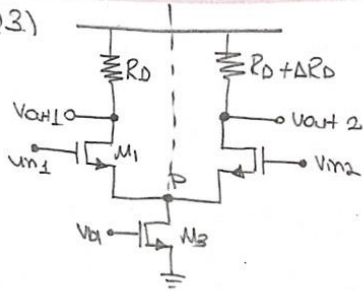


we can use half-circuit to calculate

\$A_{DM}\$

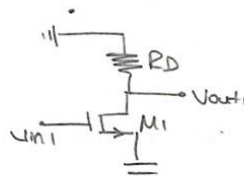

$$A_{DM} = \frac{v_{out1}}{v_{in1}} = -g_{m1} R_D$$

To calculate, \$A_{CM-DM}\$ we have;

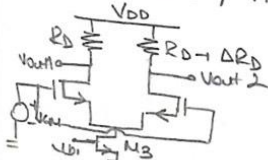


$$A_{CM-DM} = \frac{\Delta v_{out}}{\Delta v_{cm}}$$

$$\Delta v_{cm} = \Delta v_{gs} + 2\Delta I_D r_{o3} \Rightarrow$$


$$\Delta v_{out} = \Delta v_{out1} - \Delta v_{out2} = -\Delta R_D \Delta I_D \Rightarrow$$

$$A_{CM-DM} = \frac{-\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}}$$
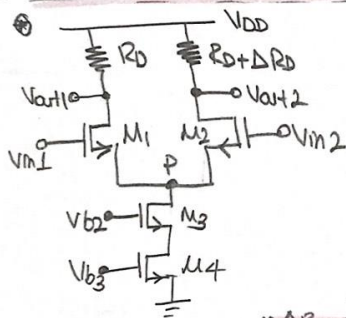
$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = \frac{g_{m1} R_D}{\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}$$


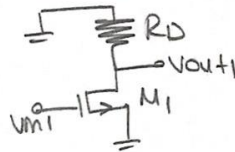
$$A_{DM} = \frac{v_{out1}}{v_{in1}} \Rightarrow$$




$$A_{DM} = -g_{m1} R_D$$


$$A_{CM-DM} = -\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2[g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]}$$

* \$\Delta R_D \ll R_D\$ so we could use half circuit since \$g_{m3}\$ are nearly equal.
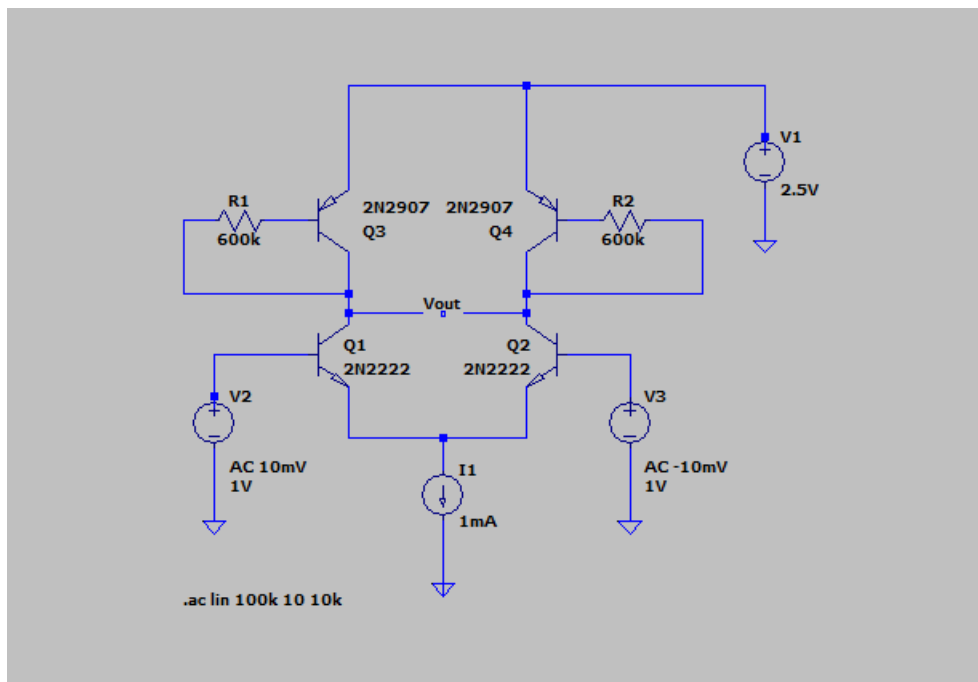
$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = (1 + 2g_{m1} [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]) \frac{R_D}{\Delta R_D}$$



Gain:

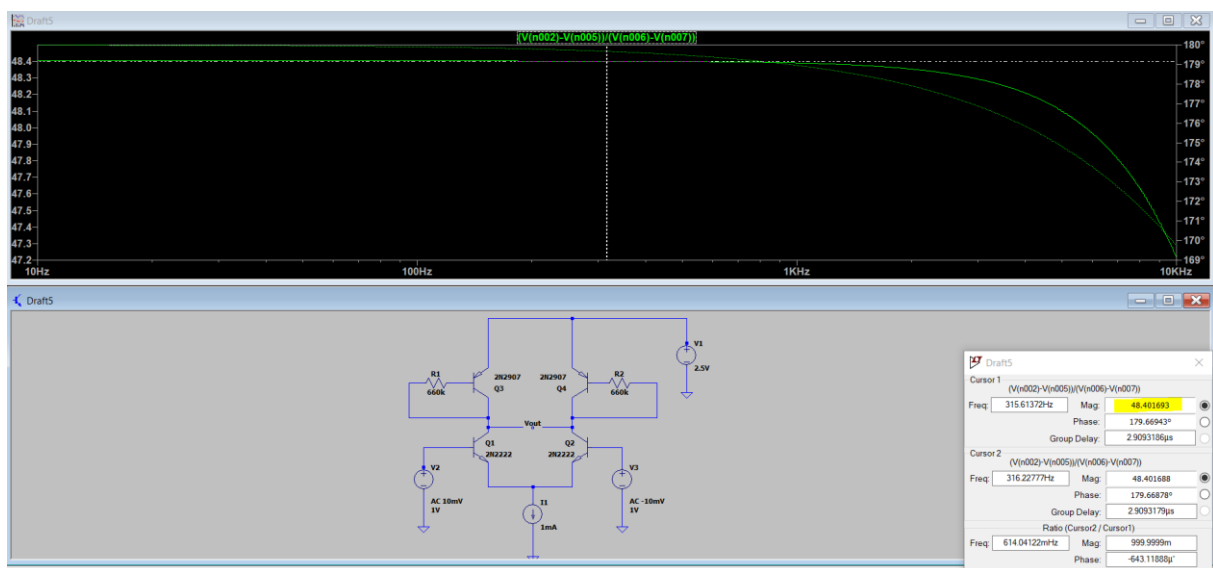

Transient Response:

V(n002)=Vout1

$V(n005)=V_{out2}$

