

EHB322E Digital Electronic Circuits

MIDTERM I

Duration: 120 Minutes

Grading: 1) 30%, 2) 30%, 3) 40%

Exam is in closed-notes and closed-books format; calculators are allowed

For your answers please use the space provided in the exam sheet


GOOD LUCK!

- 1) Consider a pseudo NMOS inverter shown below. Use the following equations for your calculations.

Saturation region current-voltage equation: $I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} (V_{GS} - V_{T0p,n})^2$

Linear region current-voltage equation: $I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} [2(V_{GS} - V_{T0p,n})V_{DS} - V_{DS}^2]$

 Transistor parameters: $k_p' = \mu_p c_{ox} = 55 \mu\text{A/V}^2$, $k_n' = \mu_n c_{ox} = 100 \mu\text{A/V}^2$, $V_{TN} = 1\text{V}$, $V_{TP} = -1\text{V}$, $W_N = 12\mu$, $L_P = 1\mu$, $L_N = 1\mu$.




Pseudo NMOS Inverter

- Find the value of W_P if $V_{in} = 5\text{V}$ results in $V_{out} = 0.25\text{V}$.
- Find the value of V_{out} if V_{in} switches from 5V to 0V .
- Find the value of the switching threshold voltage V_M ($V_{in} = V_{out}$).
- Derive an expression of the **output capacitor** in terms of C_{GS} and C_{GD} capacitors of the transistors.

 - 2) Consider a circuit with three CMOS inverters and three outputs shown below. A capacitor of $8fF$ is connected to the output-2; A capacitor of $4fF$ is connected to the output-3. A signal switching from high to low is applied to the input.

Transistor parameters: $c_{ox}=1 \text{ fF}/\mu\text{m}^2$, $\tau_n = \tau_p=1\text{ps}$, $W_{N1}=5\mu$, $W_{P2}=6\mu$, $W_{P3}=4\mu$, $L_{N1}=L_{P1}=L_{N2}=L_{P2}=L_{N3}=L_{P3}=1\mu$.



Digital circuit with three CMOS inverters

Propagation delays of an inverter are formulized as follows. C_L represents the load capacitor of the inverter.

$$t_{PHL} = (C_L/C_N) \tau_n \quad C_N = c_{ox} W_N L_N$$

$$t_{PLH} = (C_L/C_P) \tau_p \quad C_P = c_{ox} W_P L_P$$

Suppose that $C_{GS-N} = C_N$ and $C_{GS-P} = C_P$; neglect C_{GD} capacitors.

If **the total propagation delay** is 2ps at output-1, 4ps at output-2, and 4ps at output-3,

a) Find the value of W_{N2} and W_{N3} .

b) Find the value of W_{P1} .

- 3) For a specific technology and a specific supply voltage, a CMOS inverter with parameters $W_P=1\mu$, $W_N=1\mu$, $L_P=1\mu$, $L_N=1\mu$, and a load capacitor of 1 fF has $t_{PHL}=1\text{ ns}$ and $t_{PLH}=2\text{ ns}$.

By considering the same technology and the supply voltage,

- a) Implement $f = x_1x_2\overline{x_3} + x_1\overline{x_2}x_3 + \overline{x_1}x_2x_3 + \overline{x_1}\overline{x_2}\overline{x_3}$ with a **CMOS circuit** using **minimum** number of transistors. Draw the circuit. How many PMOS and NMOS transistors do you use?
- b) Select $W_P=4\mu$ for all PMOS transistors and $W_N=2\mu$ for all NMOS transistors of your CMOS circuit. Find the **worst case (largest)** and the **best case (smallest)** t_{PHL} and t_{PLH} values if a load capacitor of 2 fF is connected to the output. Neglect internal NMOS/PMOS capacitors (you should have 4 delay values).