

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 07/06/2021

EHB322E Digital Electronic Circuits QUIZ III


Duration: 100 Minutes

Grading: 1) 50%, 2) 50%

For your answers please use the space provided in the exam sheet

GOOD LUCK!

 1) Consider a CMOS D-flip-flop shown below.



A D-Flip-Flop

Use the following parameter values.

Equivalent resistor for an NMOS transistor: $R_N = 1\text{k}\Omega$

Equivalent resistor for a PMOS transistor: $R_P = 1,5\text{k}\Omega$

Suppose that each node in the flip-flop has an internal capacitance of 1pF .

When $\text{CLK}=1$ which condition (initial value of Q and change in D) gives the **worst case high-to-low propagation delay**. Find this delay value.

- 2) Implement $f = x_1 x_2 x_3 + \overline{x_1} \overline{x_2} \overline{x_3} + x_1 \overline{x_3}$ with a pseudo NMOS NOR based PLA circuit. **Sketch the circuit.** For pseudo NMOS, use PMOS as a load.