
 
 


09/03/2015-W6

①




EHB 322E: Digital Electronic Circuits Spring 2015

 
Implementing any Boolean function with NMOS, PMOS, and CMOS circuits



Ex Implement $x_1 + x_1$ with a CMOS circuit



x_1	x_2	f	S_1 is ON S_2 is OFF
0	0	0	→ Pull down is active - closed path between OUT and GND
0	1	1	S_1 is OFF S_2 is ON
1	0	1	→ Pull up is active - closed path between OUT and VDD
1	1	1	

 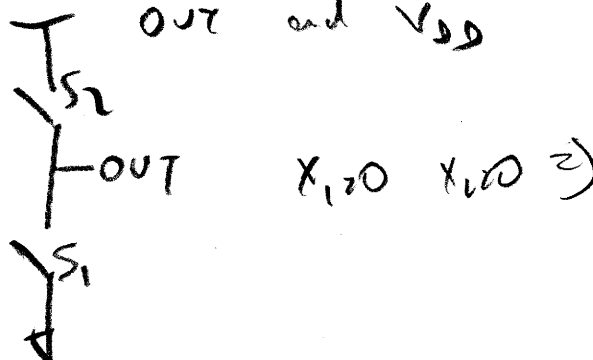 

 

- ②
- Use dual circuits for NMOS and PMOS parts
 - Use negated inputs
 - Use same inputs for NMOS and PMOS parts

  Rx Implement $f = x_1 + x_2$ with NMOS and PMOS transistors




(Universal)
Implementing NAND and NOR gates ③
with CMOS circuits

NAND




$$f = \overline{x_1 \cdot x_2}$$

 

NOR



$$f = \overline{x_1 + x_2}$$

 

Implementing complex gates for
any Boolean function with CMOS circuits

Given a Boolean function f


- 1.) Express f in minimal factored form such that the expression has minimal number of literals
 - # of literals = # of NMOS transistors (literal count)
 - = # of PMOS transistors

COST FUNCTION

- 2.) Assign negated form of each literal ④
 to an NMOS (PMOS) transistor such
 that AND operations in the expression
 correspond to parallel NMOS and
 (series PMOS)
 OR operations in the expression
 correspond to series NMOS transistors,
 (parallel PMOS).

Ex Implement $f = x_1 x_2 + x_1 x_3 + \bar{x}_1 x_4$
 a CMOS gate.

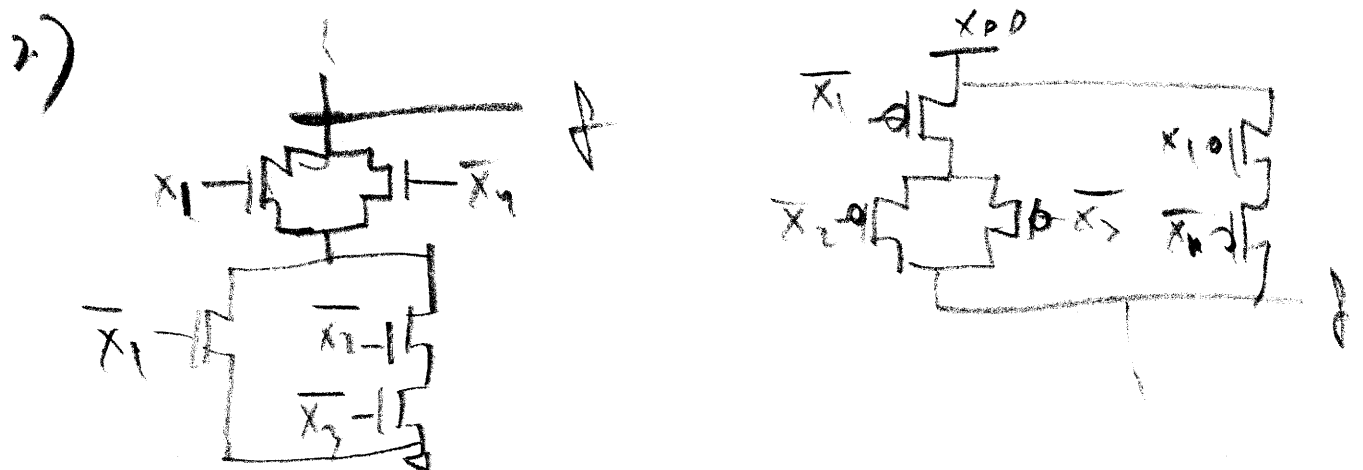
- 1.) $f = x_1 (x_2 + x_3) + \bar{x}_1 x_4$ 5 literals
 5 NMOS transistors 5 PMOS transistors



(5)


Propagation delay for static CMOS circuits or gates

t_{PLH}

 

$$t_{PLH} = 0.69 R_P C_L$$

t_{PHL}

 

$$t_{PHL} = 0.69 R_N C_L$$

→ How to obtain R & C values?

1.) Model each closed NMOS (PMOS) transistor with its equivalent resistor

- NMOS is closed if gate voltage is V_{DD}
- PMOS is closed if gate voltage is 0

2.) Model each open NMOS (PMOS) transistor as an open switch.

3.) For each node calculate the equivalent capacitor

- ⑥
- ① Neglecting internal capacitors
(only consider the output capacitor)
How to calculate w.c. & c delays?


Ex

$$f = x_1(x_2 + x_3) + \bar{x}_1 x_4$$

for each NMOS $R_N = 10k\Omega$
for each PMOS $R_P = 20k\Omega$

$$C_L = 10pF$$

Calculate the delays

 

a) $x_1 = 0$

$x_2 = 0$

$x_3 = 0$

$x_4 = 0 \rightarrow 1$

b) $x_1 = 1$

$x_2 = 0 \rightarrow 1$

$x_3 = 0 \rightarrow 1$

$x_4 = 1$

c) $x_1 = 1 \rightarrow 0$

$x_2 = 1 \rightarrow 0$

$x_3 = 1 \rightarrow 0$


$x_4 = 1 \rightarrow 0$

d) w.c. t_{PLH} t_{PHL}

e) \uparrow t_{PLH} t_{PHL}

7


c) t_{PLH}

 

$$t_{PLH} = 0,69(2R_P)C_L$$

$$= \underline{\underline{276\text{ ns}}}$$


b) t_{PLH}

 

$$t_{PLH} = 0,69\left(\frac{3}{2}R_P\right)C_L$$

$$= \underline{\underline{207\text{ ns}}}$$

c) t_{PHL}

 

$$t_{PHL} = 0,69\left(\frac{5}{3}R_N\right)C_L$$

$$= \underline{\underline{115\text{ ns}}}$$

d.) W.C. t_{PLH}

$$0,69 (2 RP) C_L = 276 ns$$

$$(x_1=0 \quad x_4=1, \quad x_2=x_3) \\ \text{W.C. } t_{PHL} \quad \text{do not care}$$

$$0,69 (2,5 RN) C_L = 172,5$$

$$(x_1=1 \quad x_2=0 \quad x_3=0 \quad x_4=0)$$

e.) B.C. t_{PLH}

$$0,69 (1,5 RP) C_L = 207 ns$$

$$(x_1=1 \quad x_2=1 \quad x_3=1 \quad x_4=) \quad \text{do not care}$$

B.C. t_{PHL}

$$0,69 (\frac{5}{2} RN) C_L = 115 ns$$

$$(x_1=0 \quad x_2=0 \quad x_3=0 \quad x_4=0)$$

$$207 ns \leq t_{PLH} \leq 276 ns$$

$$115 ns \leq t_{PHL} \leq 172,5 ns$$

$$\text{Note } R \propto \frac{1}{W}$$