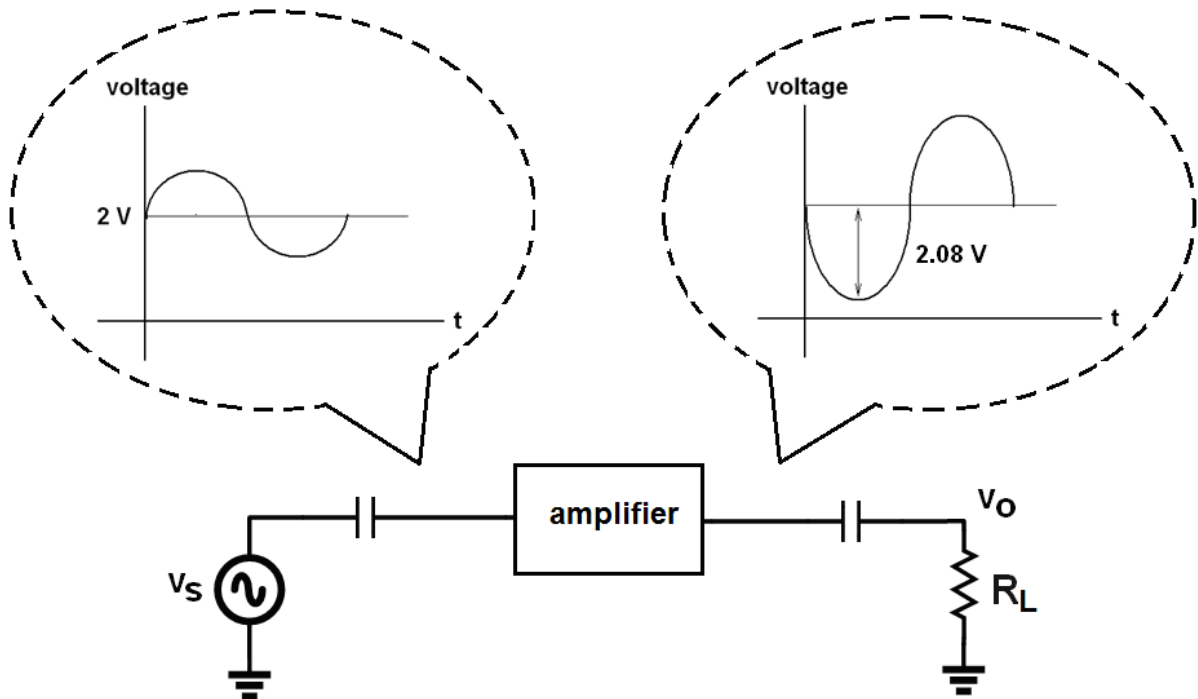


**EHB 262E Final Exam Problem-3 (30minutes)      UPLOAD till 19.35!**  
**Group 1 (Student last number: 0,1,2,3)** (G2 and G3 problems are in the next pages)

A one-stage amplifier represented as a box in the figure below will be designed so that symmetrical clipping is provided at the output. The maximum amplitude before the output signal clips and the corresponding input signal is shown below.

Assume  $R_L=10\text{ k}\Omega$ ,  $V_{CC}=9\text{ V}$ ,  $V_{BE}=0.7\text{ V}$ ,  $V_{CEsat}=0$ ,  $V_T=26\text{ mV}$ .


- Specify the type of amplifier inside the box. Explain your reasoning. Sketch the full amplifier circuit using an npn type BJT and passive components only (ignore the input bias circuitry but give the bias value).
- Find your bias point ( $I_C$  and  $V_{CE}$ ) and the resistor values. Explain in detail your design steps.



A one-stage amplifier represented as a box in the figure below will be designed so that symmetrical clipping is provided at the output. The maximum amplitude before the output signal clips and the corresponding input signal is shown below.

Assume  $R_L=12\text{ k}\Omega$ ,  $V_{CC}=10\text{ V}$ ,  $V_{BE}=0.7\text{ V}$ ,  $V_{CEsat}=0$ ,  $V_T=26\text{ mV}$ .

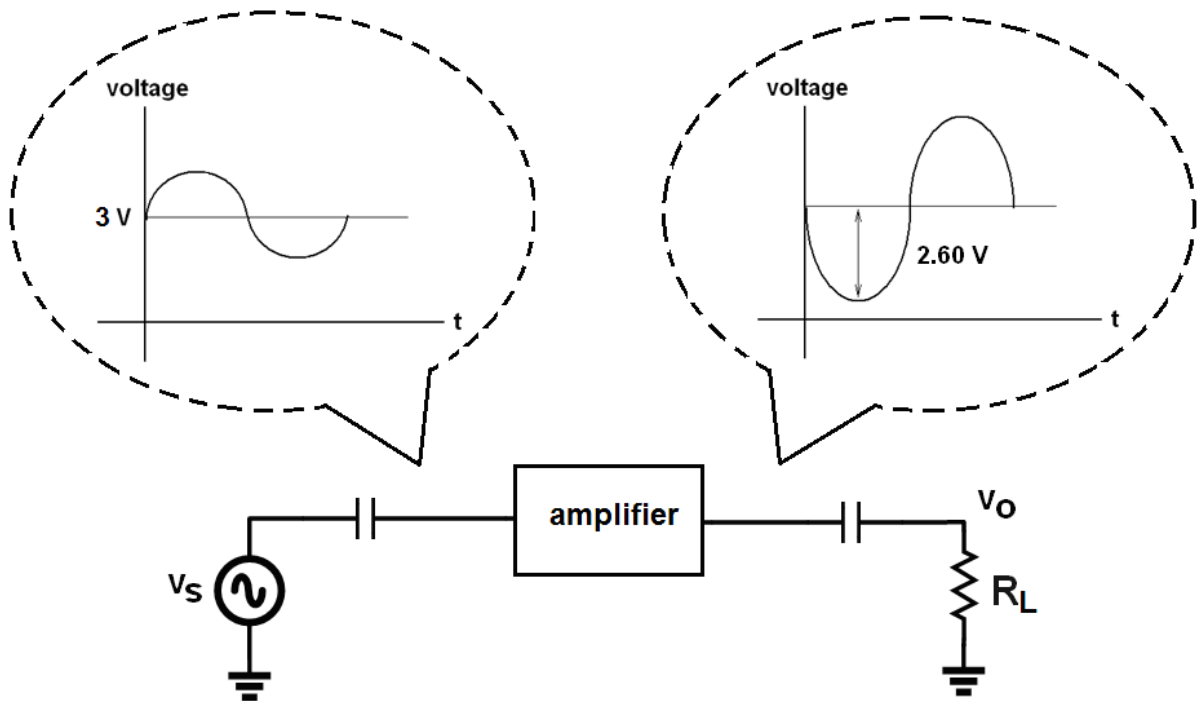- Specify the type of amplifier inside the box. Explain your reasoning. Sketch the full amplifier circuit using an npn type BJT and passive components only (ignore the input bias circuitry but give the bias value).
- Find your bias point ( $I_C$  and  $V_{CE}$ ) and the resistor values. Explain in detail your design steps.



EHB 262E Final Exam **Problem-3 (30minutes)** **UPLOAD till 19.35!**  
**Group 3 (Student last number: 7,8,9)**

A one-stage amplifier represented as a box in the figure below will be designed so that symmetrical clipping is provided at the output. The maximum amplitude before the output signal clips and the corresponding input signal is shown below.

Assume  $R_L=5\text{ k}\Omega$ ,  $V_{CC}=5\text{ V}$ ,  $V_{BE}=0.7\text{ V}$ ,  $V_{CEsat}=0$ ,  $V_T=26\text{ mV}$ .

- Specify the type of amplifier inside the box. Explain your reasoning. Sketch the full amplifier circuit using an npn type BJT and passive components only (ignore the input bias circuitry but give the bias value).
- Find your bias point ( $I_C$  and  $V_{CE}$ ) and the resistor values. Explain in detail your design steps.

