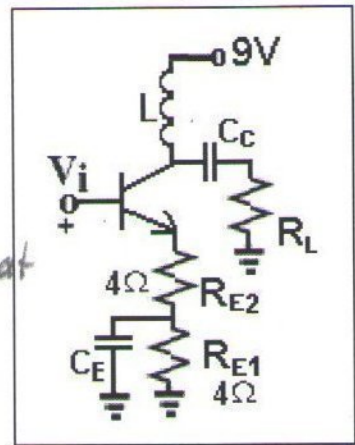


For the transistor, $V_{CEsat}=0.3V$ and $I_{Cmax}=200mA$ are given.
Find R_{Lopt} .



$$I_{CQ} = \frac{I_{Cmax}}{2} = 100mA //$$

$$V_{CEQ} = 9V \quad V_{CEmin} = I_{CQ} \cdot R_{E1} + 2I_{CQ} R_{Lopt} + V_{CEsat}$$

$$\downarrow$$

$$= 0,4 + 0,8 + 0,3$$

$$\downarrow$$

$$= 1,5V //$$

$$V_{RLmax} = V_{CEQ} - V_{CEmin}$$

$$\downarrow$$

$$= 9 - 1,5 = 7,5$$

$$I_{RLmax} = I_{CQ} = 100mA$$

$$\rightarrow R_{Lopt} = \frac{7,5V}{100mA} = 75\Omega //$$

Find V_{CEmax} .

9V

$I_{RLmax} \times R_{Lopt}$

$$V_{CEmax} = V_{CEQ} + V_{RLmax} = 16,5V$$

$$I_C \downarrow 0 \rightarrow V_C = V_{CEmax} \rightarrow V_E = I_{CQ} R_{E1} = 0,4V //$$

$$V_{CEmax} = 16,5V - 0,4V = 16,1V //$$

Find maximum efficiency.

$$P_{DC} = V_{CC} \cdot I_{CQ} = 9 \times 0,1A = 0,9W$$

$$P_{RLmax} = I_{RLmax} \times V_{RLmax} = 100mA \times 7,5V \times \frac{1}{2} = 0,375W$$

$$\eta_{max} = 0,375 / 0,9 \approx \% 42$$

Find the maximum power dissipated on the transistor

$$P_{Tmax} \approx P_{DC} = 0,9W \quad (V_i=0, V_L=0)$$

Detailed calculation; $V_{CEQ} = 9V - I_{CQ} \cdot R_E = 8,2V \quad I_{CQ} = 100mA$

$$P_{Tmax} = 8,2V \times 0,1A = 0,82W //$$

For the transistor, the maximum junction temperature is given as $180^\circ C$
The maximum air temperature is $50^\circ C$.

What should "the thermal resistance from the junction to air" be?

$$R_{ThTotal} \leq \frac{T_J - T_A}{P_{Tmax}} = \frac{180 - 50}{0,82W} \approx 158^\circ C/W //$$