

- 1) Obtain the flip-flop output Boolean functions equations on circuit shown in Fig. 1.
($Q=D$, $Q(t+1)=D$)
- 2) Fill in the timing diagram shown in Fig. 2 using the Boolean functions that you obtained.
- 3) State the task performed by this circuit by using your finding.

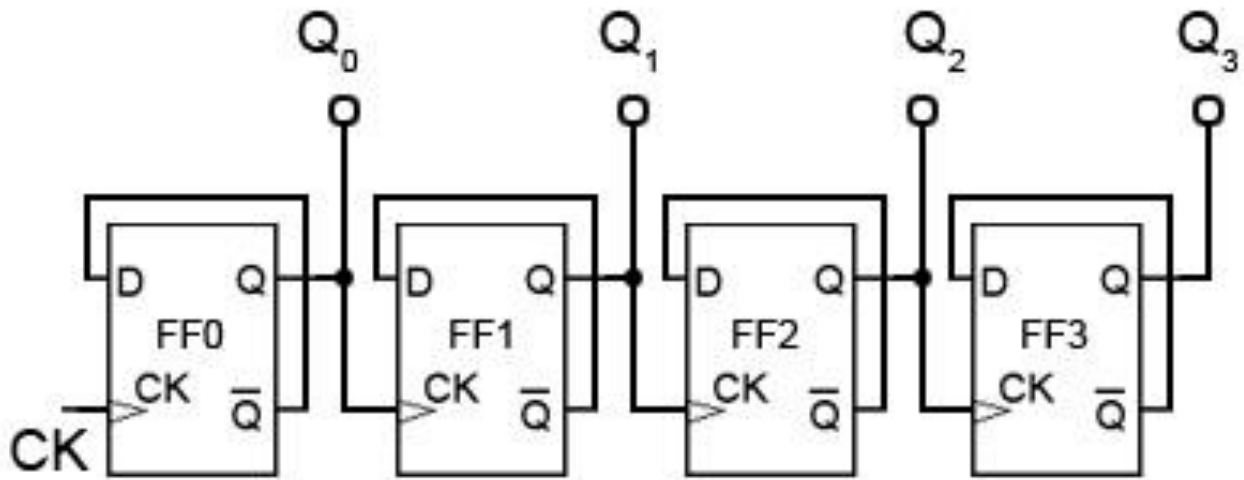


Figure 1

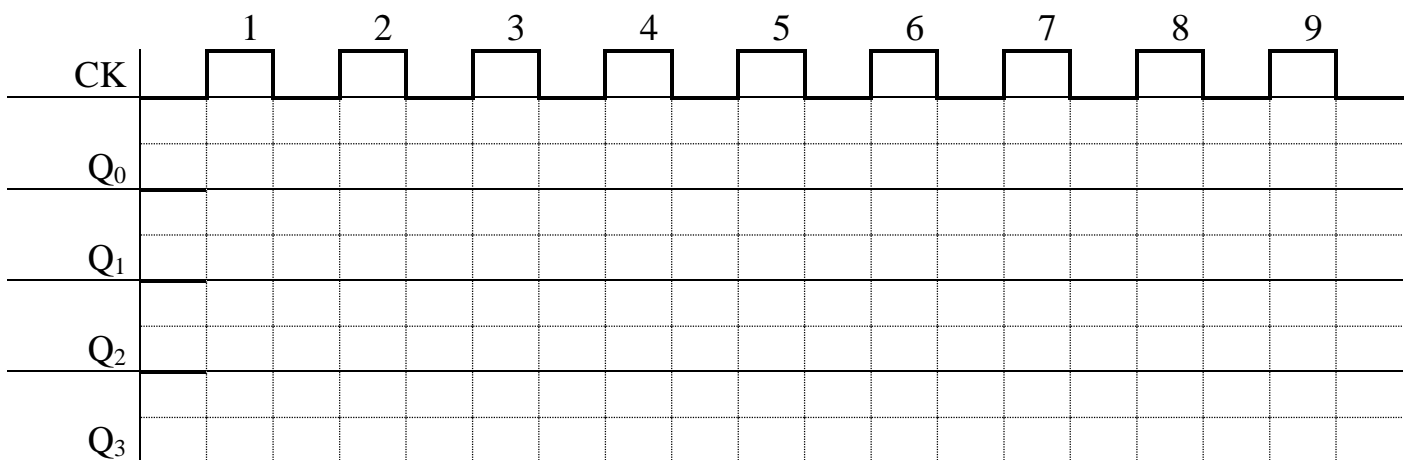


Figure 2