
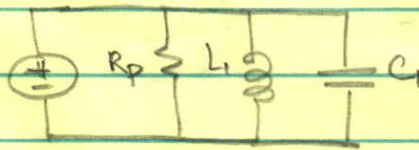


HWG Solutions

①

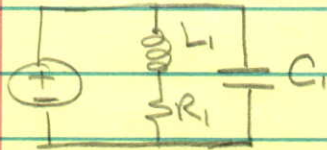

$$Z_1 = \frac{(R_1 + j\omega L_1) \cdot \frac{1}{j\omega C_1}}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}}$$

$$Z_p = \frac{\frac{jR_p\omega L_1}{R_p + j\omega L_1} \cdot \frac{1}{j\omega C_1}}{\frac{jR_p\omega L_1}{R_p + j\omega L_1} + \frac{1}{j\omega C_1}}$$

$$Z_1 = \frac{R_1 + j\omega L_1}{(1 - \omega^2 L_1 C_1) + j\omega C_1 R_1}$$

$$Z_p = \frac{jR_p\omega L_1}{R_p(1 - \omega^2 L_1 C_1) + j\omega L_1}$$

$$Z_1 = \frac{(R_1 + j\omega L_1)[(1 - \omega^2 L_1 C_1) - j\omega R_1 C_1]}{(1 - \omega^2 L_1 C_1)^2 + \omega^2 R_1^2 C_1^2}$$

$$Z_p = \frac{\omega^2 L_1^2 R_p + jR_p^2 \omega L_1 (1 - \omega^2 L_1 C_1)}{R_p^2 (1 - \omega^2 L_1 C_1)^2 + \omega^2 L_1^2}$$

$$\operatorname{Re}\{Z_1\} = \frac{R(1 - \omega^2 L_1 C_1) + \omega^2 R_1 C_1 L_1}{(1 - \omega^2 L_1 C_1)^2 + \omega^2 R_1^2 C_1^2}$$

$$\operatorname{Re}\{Z_p\} = \frac{\omega^2 L_1^2 R_p}{R_p^2 (1 - \omega^2 L_1 C_1)^2 + \omega^2 L_1^2}$$

$$\operatorname{Im}\{Z_1\} = j \frac{\omega L_1 (1 - \omega^2 L_1 C_1) - \omega R_1^2 C_1}{(1 - \omega^2 L_1 C_1)^2 + \omega^2 R_1^2 C_1^2}$$

$$\operatorname{Im}\{Z_p\} = j \frac{R_p^2 \omega L_1 (1 - \omega^2 L_1 C_1)}{R_p^2 (1 - \omega^2 L_1 C_1)^2 + \omega^2 L_1^2}$$

$$\operatorname{Re}\{Z_1\} = \operatorname{Re}\{Z_p\}$$

Assume $1 - \omega^2 L_1 C_1 \approx 0$


$$\cancel{\omega^2 R_1 C_1 L_1} = \cancel{\omega^2 L_1^2 R_p}$$

$$\Rightarrow \frac{L_1}{C_1} = R_p R_1 \quad \text{but} \quad \omega^2 = \frac{1}{L_1 C_1} \Rightarrow C_1 = \frac{1}{\omega^2 L_1}$$

$$\Rightarrow R_p R_1 = \omega^2 L_1^2$$

$$\Rightarrow \boxed{R_p = \frac{\omega^2 L_1^2}{R_1}}$$

(2)

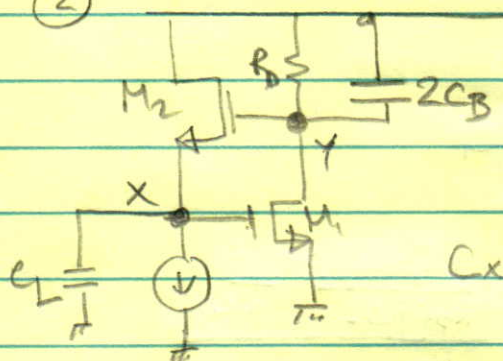

(due to virtual ground concept)


There are two poles associated with the nodes X & Y

$$C_x = C_L + C_{gs1} + C_{gd1x} - C_{gs2x} + C_{sb2} \Rightarrow \tau_x = \left(\frac{1}{g_{m2}} \parallel r_{o2} \right) C_x$$

$$C_y = 2C_B + C_{gd1y} + C_{gd2} + C_{db1} + C_{gs2y} = \tau_y = R_o C_y$$

Having 2 poles, the circuit would have oscillated at $\omega = \infty$ but there is zero gain at $\omega = \infty$. So, this circuit would not oscillate.

(3)

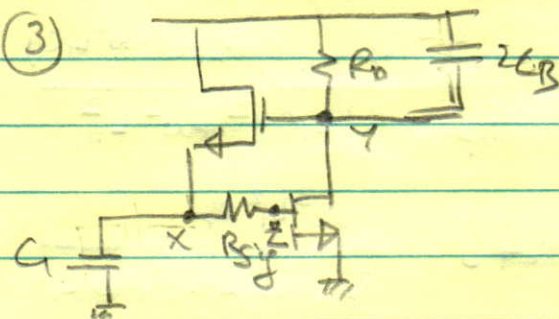

$$C_x = C_L + C_{gs2x} + C_{sb2} \Rightarrow \tau_x = \left(\frac{1}{g_{m2}} \parallel r_{o2} \right) C_x$$


$$C_y = 2C_B + C_{gd1y} + C_{gd2} + C_{db1} + C_{gs2y}$$

$$C_z = C_{gs1} + C_{gd1x}$$

$$\tau_x = \left(\frac{1}{g_{m2}} \parallel r_{o2} \right) C_x \quad \tau_y = R_o C_y \quad \tau_z = \left[R_{sig} + \left(\frac{1}{g_{m2}} \parallel r_{o2} \right) \right] C_z$$

This time, we have three poles, bringing the total phase shift to 180° , thus this circuit can oscillate.

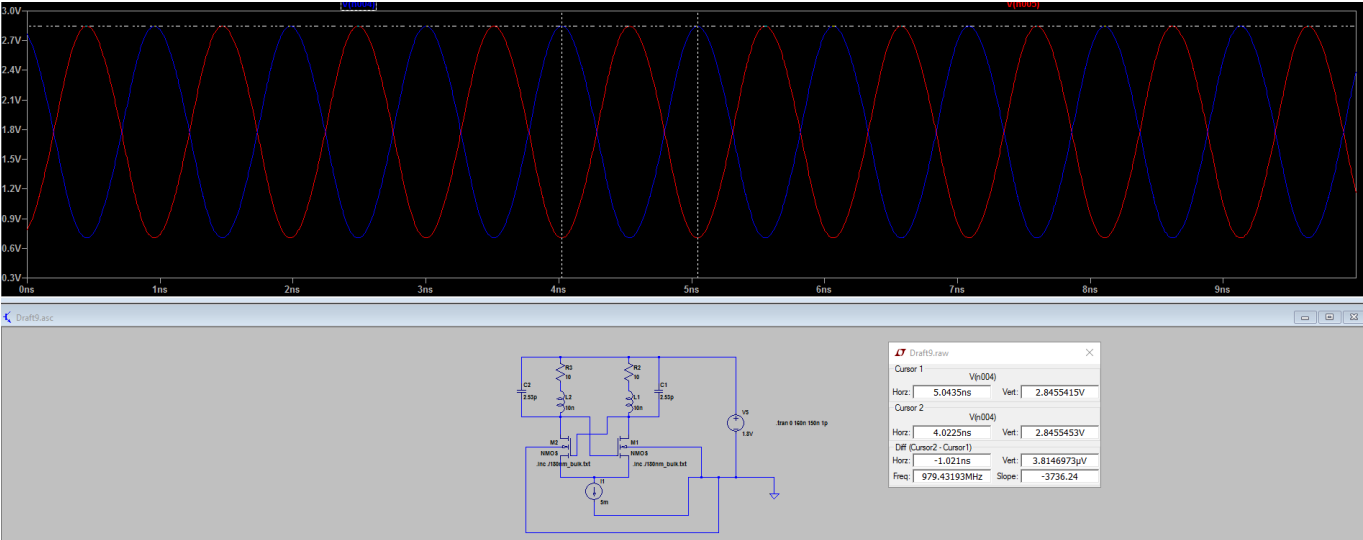Solution of 4) C value can be computed from $C = 1/(\omega^2 L) = 2.53 \text{ pF}$.



At $I_{SS} = 2.12 \text{ mA}$, the oscillation ceases.

